


ROBOTICS • MICROCONTROLLERS • COMPUTER CONTROL • LASERS

# Nuts & Volts

EVERYTHING FOR ELECTRONICS!

September 2001

Vol. 22 No.9

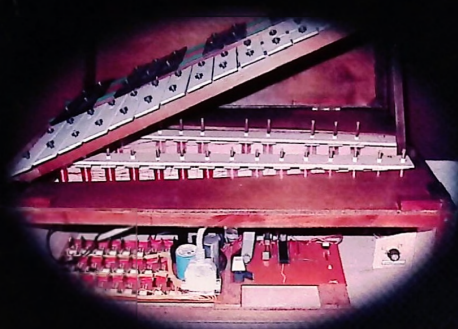

Update the original XYLOTRON project with the ability to "hear" a MIDI tune one time and play it back on command without being connected to a computer.

## Build These Projects

The X-Lock for X-10 Home Automation

Universal LCD Interface

MIDI-MAN Interface

The PhoneTester



## Getting Started in Electronics on a Shoestring

U.S. \$4.50 CANADA \$6.50




[www.nutsvolts.com](http://www.nutsvolts.com)


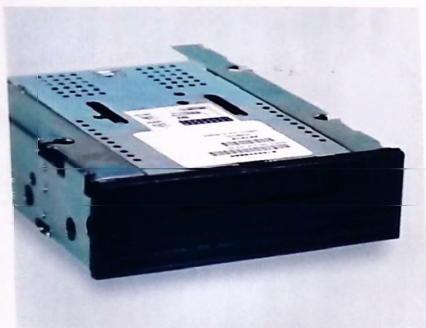
# AUCTION BLOWOUT!

Over 2,000 Items on Ebay! Many from Distressed or Bankrupt Dot-Coms!



**24GB Ultra SCSI DAT Tape Drives**  
**No Minimum Bids!**



**Cisco Routers and Hubs**  
**Bids Start at \$50**



**Sun Workstations and File Servers**  
**No Minimum Bids!**



**15,000 RPM Ultra 160 Hard Drives**  
**\$10 Minimum Bid**

Disk drives cost too much. Take advantage of dot-com closeouts and bankruptcies. We're liquidating thousands of PCs, hard drives, and accessories. Visit [www.scsidrives.com](http://www.scsidrives.com) and name your own price! Join our mailing list for advance notice when special sale items arrive!



**CORPORATE SYSTEMS CENTER**

3310 Woodward Avenue, Santa Clara, CA 95054 (408) 588-1110



## Disk Drive Deals!

Seagate ST19171WC, Ultra SCSI Wide ASA2  
3.5" sz. half-height (1.5" tall) 9.1GB  
Spindle speed: 7200 RPM

Average access time: 9.7-10.7 ms

Special: buy this drive & get a 50-pin (HSCA23700) or 68-pin (HSCA23720) Adapter for \$16.00 - normally a \$20-30 value!

**HSC#18753 \$59.00**

Seagate Full-Height 5.25" SCSI Disk Drives  
Model ST 41800N Elite 9" - 10 GB Capacity  
5400 rpm, Seek time: 11 ms  
Used, tested good

Standard 50-pin connector  
30-day HSC warranty  
**HSC# 18636 \$29.95**

Seagate ST15150N 4.3 GB "Barrocuda" SCSI  
7200 RPM, 8.0/9.0 ms avg. seek time  
21 Hds, 11 Disks, 3.711 Cyl.  
Standard 50-pin SCSI  
3.5" sz. half-height (1.5" tall)  
RmtB25, 90-day warranty

**HSC# 18412 \$32.50**

IBM Model No. DCA-22160  
2.5" Laptop Hard Drive, IDE  
Formfactor: 2160 MB  
3 Disks, 11 Hds, 7200 Cyl.  
Seek time: 11 ms, 8.0/9.0 RPM  
CFM package, 90-day warranty

**HSC# 18413 \$49.95**

IBM Model No. DCA-22160  
2.5" Laptop Hard Drive, IDE  
Formfactor: 2160 MB  
3 Disks, 11 Hds, 7200 Cyl.  
Seek time: 11 ms, 8.0/9.0 RPM  
CFM package, 90-day warranty

**HSC# 18414 \$65.00**

## Socket-7 Motherboard



Socket7 for Pentium I - 75 to 200 MHz CPU  
Four 72-pin SIMM, two 168-pin DIMM sockets  
Write-back Cache & Direct Mapped Organization  
On-board 64-bit 256K L2 SYNC. COAST module suit  
Two IDE, 80, USB, 1 P10, HOST/HUB support  
1 P252 mouse port, three PCI, four ISA slots  
OEM package, 90-day warranty

**HSC#18964 \$39.95**

## Satellite Dish for Tinkering!

Sony SAN-1802 DSS dish, at an

unbelievable price!

Perfect for add-on, backup or

storm damage repair

Dish measures 18.5" x 21"

Note: tuner not included!

HAMS! put on your own

LNB and get on 10GHz!

Great for club link project!

LNB: Input: 12-12.7GHz,

Output: 950-1450MHz (two F-connectors)

Power req. +11.5-14VDC for RHCP, +16-19VDC

for LHCP, 3-5W max. (Power supply not incl.)

Comes with LNB, installation manual, cable

guides, mounting hardware, cable boots

New units in original boxes! 90-day warranty

**HSC#18822 \$29.50**

If you're in Northern California,  
Get Ready for

**HSC's**  
**Giant Anniversary Sale!**  
Equipment sold by the pound!  
Selling the Warehouse!  
One Day Only! All 3 Stores!  
Sat., September 15  
9AM to 5PM  
Don't Miss It!  
Free Refreshments!  
Discounts & Closeouts!

## ATX Mid-Tower Case!

ATX-style mid-tower cabinet

Power supply included

Four 5.25" and two 3.5" front bays

16.5" H x 8.25" W x 16.5" D

Brand new, 90-day warranty

**HSC#80459 \$39.95**

## Mini-ATX Supply!

ATX-style fits popular "E" machine

and Future Power! computers

Model No. ISP120S, 120W, 110VAC

Case measures 2.5" H x 4" W x 5.83" L

Brand new! Bargain Priced! 90-day warranty

**HSC#18989 \$19.95**

## LAN NETWORK!

Multi-PC Web Access...

Save Money!

Up to 4 PC's on one phone line!

Perfect for homes/small business

Share printers, send faxes, backup-files

Proxy server for multi-PC internet access!

Only one phone line needed for ISP connection

Includes 4-port hub/56K modem & 1 network card

If you want more than two PC's networked, you will need more

network cards (HSC# 18493 \$4.95)

50 ft network cable, driver/installation manual CD

OEM package, new, 90-day warranty

**HSC#80599**

**\$29.95**

## Tablet PC!



Fujitsu "Stylus 1000" tablet PC, keyboard

and Microsoft mouse package!

Mono VGA display, 260MB hard drive

Super-slim keyboard for easy handling!

Purified from service, some scratches

No documents/manual/software or drivers! Note: Not for

30-day warranty!

**HSC#80604 \$99.00**

## Tiny Color Camera!

Camera On A Board, measures 1.87" x 1.3" x 1"

Glass micro-lens element, not prohibit!

Std. NTSC composite video output

350 lines horiz. res., 7 lines sensitivity

4 - 5 VDC, only 150 mA!

New, in GEM pkg (no box), 90-day warranty

**HSC#18209 \$45.00**

## Laugh at Blackouts!

Yuasa NPX-150R sealed lead acid battery

Great for UPS back-up or solar systems

Nominal capacity: 10 hr rate of 40A to 10.5V

(12 VDC @ 40 AOh)

Weights (approx): 34.2 pounds (15.5 kgs.)

Excellent condition pulls, 90-day HSC warranty

**HSC#18917 \$29.50**

**HSC Electronic Supply**

Toll Free (Orders Only) 1-800-4 HALTED (1-800-442-5833)

World Wide Web: <http://www.halted.com>

3500 Ryder St.

Santa Clara, CA 95051

408-732-1573

4837 Amber Ln.

Sacramento, CA 95841

916-338-2545

5681 Redwood Dr.

Rohnort Park, CA 94928

707-585-7344



For over 35 years, HSC has been your best source for high-tech goodies from Silicon Valley! Haven't visited us yet? You owe it to yourself to come see our constantly-changing, mind-boggling array of electronic parts, equipment, computers, and scientific gear! Find out why knowledgeable engineers, technicians and hobbyists make HSC their first stop for all their techno-shopping needs!


Terms: Some quantities limited; all items are subject to prior sale. Minimum order: \$10.00 plus shipping. Orders under \$20.00 subject to \$2.00 handling fee, in addition to shipping. All orders shipped FOB Santa Clara, CA (this means you pay freight) by UPS Surface (no P.O. Boxes) unless otherwise specified, in which case prevailing carrier rate plus \$5.00 handling fee may apply. Prepaid orders that don't include shipping charges will be shipped freight COD. There is a \$6.00 UPS charge added to shipping charges for COD shipments. If you have questions about your order, please call Customer Service at (408) 732-1851 M-F 9AM to 5PM PST.



NOW AVAILABLE!!

# Presenting ...

## The Nuts & Volts OF BASIC Stamps

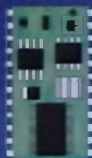


Applications from  
temperature and  
time to telephones  
and networking.

Volume 1. Applications #1-45

CD-ROM INCLUDED

**\$29.95**

## The Nuts & Volts OF BASIC Stamps

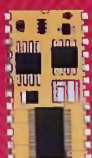

Applications from  
talking parrots and  
motor control to  
LCDs and the BS2

Volume 2. Applications #46-75

FEATURING THE BS2P

**\$29.95**

Order Both  
Volumes For  
**\$49.95!**

In 1995, Scott Edwards began authoring a column on BASIC Stamp projects in *Nuts & Volts Magazine*. The column quickly became a favorite of *Nuts & Volts* readers and was eventually turned over to Scott's handpicked replacement, Jon Williams. Lon Glazner took over the duties for about a year. Then Jon came back on the scene and is continuing to write to date. Between these three talented individuals, there's a tremendous set of

applications, tips and hardware solutions with the BASIC Stamp that now spans over 75 issues. Every project from talking parrot pet trainers and measuring water level to distributed factory control has been detailed with BASIC Stamp programming tips sprinkled throughout.

The Nuts and Volts of BASIC Stamps is the collection of these columns.

Order through the Nuts & Volts Book Store today!  
Call our order only line at 1-800-783-4624 or  
check out the On-Line Book Store at [www.nutsvolts.com](http://www.nutsvolts.com)  
for all the details!



# Contents

Call our subscription order only line at  
1-800-783-4624  
or our office at 909-371-8497.

## Columns

**AMATEUR ROBOTICS** 82 Robert Nansel  
Heavy on Heavy Iron, philosophy, and beer.

**ELECTRONICS Q & A** 18 TJ Byers  
What's Up: Audio, synthesizers, music, and sounds. Lights, lamps, and dimmers.  
How to make your own optical RS-232 link. Making an A/V and solar connection.  
Finally, a reader shares a discovery.

**LASER INSIGHT** 56 Stanley York  
Construct your own light show to use with a HeNe laser or a diode laser pointer.

**STAMP APPLICATIONS** 30 Jon Williams  
Tool Time.  
Check out a couple of freebie tools from Parallax.

**TECHKNOWLEDGEY 2001** 6 Jeff Eckert  
MEMS Coming of Age; Windows XP Coming in October; Free Access to IEEE 802 Networking Documents; The Dawn of the Digital Radio; Worldwide Computer Sales Fall; Avanti Executive Fined; Sentenced to Prison; and A Dim Ray of Hope for Internet Companies.



## Departments

Advertiser's Index . . . 64	New Product News . . . 93
Classified Ads . . . 60-64	NV Bookstore . . . . . 92
Classified Ad Info . . . 64	NV Showcase . . . 48-50
Dealer Directory . . . 69	Prize Drawing . . . . . 91
Events Calendar . . . 26	Reader Feedback . . . 12
News Bytes . . . . . 13	Tech Forum . . . . . 40

## Articles

### XYLOTRON II — THANKS FOR THE MEMORY

8 Bob Lang

Update your original project with these modifications that give the XYLOTRON the ability to "hear" a MIDI tune one time and remember it, and play it on command without being connected to a computer.



### BOARDING THE UNIVERSAL SERIAL BUS: PICK THE SOLUTION THAT FITS YOUR PROJECT

14 Jan Axelsson

Discover three ways to add USB to a project. Each is best suited for a particular situation, so you can select the one that works for you.

### MIDI-MAN

23 Terence Thomas

Looking to expand the capabilities of your home studio? Then look no farther ... it's MIDI-MAN to the rescue.

### GRAVITY, INERTIA, AND THE ELECTROMAGNETIC SPECTRUM — PART I

36 Richard Panosh

Revisit the study of physics and what it holds for the future magic of technology.



### LITTLE AUTO TUNERS FOR LITTLE RADIOS

44 Gordon West

In special applications like maritime mobile, aeronautic mobile, or when you have a single wire with multiple bands of necessary operation, automatic antenna couplers that tune well beyond the capabilities of built-in automatic antenna tuners are a logical choice.

### BUILD YOUR OWN UNIVERSAL LCD INTERFACE

51 Dennis Shepard

Spice up your projects with an LCD display that offers a simple serial interface and includes the most often desired features.

### GETTING STARTED ON A SHOESTRING

65 TJ Byers

Just getting started in electronics, but don't have access to a lot of equipment or money? If you have \$50.00 and a desire to learn, then you have the beginnings of a new hobby.

### OP-AMP COOKBOOK — PART 3: OSCILLATORS AND SWITCHING CIRCUITS

70 Ray Marston

Take a look at some practical op-amp oscillators and switching circuits.

### THE PHONETESTER

76 Bill Stiles

Test your own telephones, lines, and accessories with this handy device and "save a buck or two."

### BUILD THE X-LOCK

87 Jeff Mazur

Build this security module for your X-10 home automation system and never worry about someone inadvertently controlling your appliances, etc., again.





# TechKnowledge

## Events, Advances, and News 2001

by Jeff Eckert

### Advanced Technologies

#### MEMS Coming of Age

Miniaturization is not a new concept in electronics. The trend became apparent in the 1950s, when the first transistor radios hit the market. But more recently, engineers have started to think in terms of combining micro-scale electronic and mechanical devices to create a new technological class. This has come to be known as the science of "microelectromechanical systems" (MEMS), and it promises to provide reductions in size, weight, and power consumption ranging from 1/10 to 1/1,000.

Implementation involves existing microelectronics technologies, as well as emerging processes such as microphotolithography, thin film deposition and patterning, precision etching and electroplating, and other techniques that are usually applied to IC manufacture. The definition also includes microfluidic tools such as microvalves, micro-propulsion nozzles, and fully fluid transport systems.


An important application is in small satellites, which tend to be classified by weight. Picosats weigh <1 kg, nanosats (see figure) range from 1 to 10 kg, and microsats weigh 10 to 100 kg. Still in the planning stages are femosats, which would weigh <0.1 kg.

As an example of a MEMS device for satellite applications, a micro-


thruster array measuring one-quarter of the size of a penny has been developed by TRW ([www.trw.com](http://www.trw.com)) for use on micro-, nano-, and pico-satellites, and it has already passed a functionality test aboard a Scorpion sub-orbital sounding rocket. Individual micro-electromechanical system (MEMS) thrusters — each a poppy seed-sized coil fueled with lead styphnate propellant — fired more than 20 times at one-second intervals during a test staged earlier this year at the White Sands Missile Range. Each thruster delivered 10<sup>-4</sup> Newton seconds of impulse.

The MEMS design, based on silicon chip fabrication technology, has no moving parts; utilizes a variety of propellants; is scalable; eliminates the need for tanks, fuel lines, and valves; and fully integrates the structure of the satellite with the propulsion to power it. The micro-thruster was developed by TRW along with teammates Caltech and the Aerospace Corp., under a contract from the Defense Advanced Research Projects Agency.

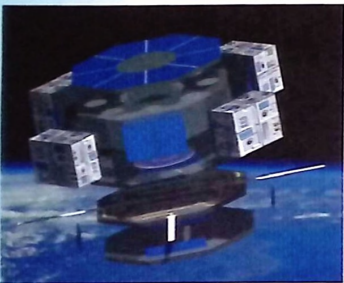
Another interesting MEMS application, developed at the Georgia Institute of Technology ([www.gatech.edu](http://www.gatech.edu)), is aimed at medical applications.



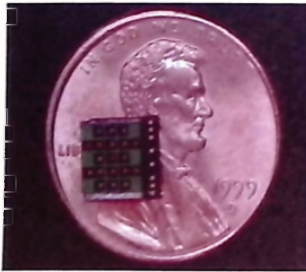Artist's conception of an orbiting nanosatellite, courtesy of The Aerospace Corp.



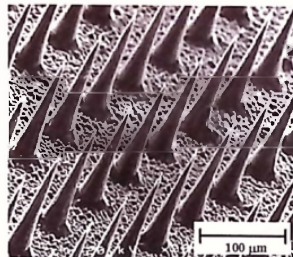The TRW Digital Micro-Thruster chip is designed to provide "digital propulsion" to small satellites. Courtesy of TRW, Inc., Space and Electronics division.



This array of needles is designed for painless transdermal drug delivery. Courtesy of Georgia Institute of Technology.


avoid stimulating nerves that lie in deeper tissue. According to the developers, they are mechanically strong, able to increase transdermal transport by more than four orders of magnitude, in vitro, and do not cause pain in human subjects.

Finally, in the area of non-inertial micro-mechanical devices, Draper Labs ([www.draper.com](http://www.draper.com)) has developed silicon micromachined condenser microphones that are implemented on a single chip with integral buffer amplification. Draper has conducted fundamental research and development of units that detect low frequencies (20 Hz to 5 kHz), as well as highly sensitive arrays of sensors for high frequencies (0.5 to 2.0 MHz).

Micro-level chemical sensors and optical devices are also under development.

Transdermal drug delivery is limited by the extraordinary barrier properties of the outer 10 to 15 mm of skin (stratum corneum). Conventional needles inserted across this barrier and into deeper tissue effectively deliver drugs, but can cause infection and pain. To create painless needles, Georgia Tech researchers Devin McAllister, Sudhasinee Smriti, S. Henry, and Mark G. Allen have microfabricated arrays of very short microneedles that are long enough to penetrate through the stratum corneum, but short enough to

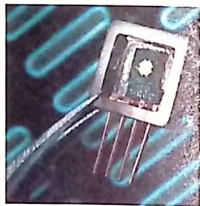avoid stimulating nerves that lie in deeper tissue. According to the developers, they are mechanically strong, able to increase transdermal transport by more than four orders of magnitude, in vitro, and do not cause pain in human subjects.



A micromechanical condenser microphone. Courtesy of Draper Labs.

### Computers and Networking

#### Windows® XP Coming in October

As of the last report from Microsoft ([www.microsoft.com](http://www.microsoft.com)), the new Windows XP operating system is still on track for release in October, despite reservations expressed by the US Congress, many privacy groups, and some of the half million users who tested a preliminary version. The system initially included a "Smart Tags" feature designed to recognize keywords in accessed documents and steer you toward related Web sites. Many beta test participants found the feature annoying, particularly because it mostly suggested web sites operated by Microsoft and its business partners. As a result, the Smart Tags will be removed from systems bought directly from Microsoft.

In addition, a complaint has been filed with the Federal Trade Commission, by Junkbusters Corp. ([www.junkbusters.com](http://www.junkbusters.com)), the Privacy Foundation ([www.privacyfoundation.org](http://www.privacyfoundation.org)), and a dozen other organizations about Windows XP features that collect ("Passport" and "Wallet") and distribute ("HailStorm") personal information about users. (You can download a PDF version of the 20-page document from [www.epic.org/privacy/consumer/ms\\_complaint.pdf](http://www.epic.org/privacy/consumer/ms_complaint.pdf).)

According to the complaint, "Microsoft has engaged in and is engaging in unfair and deceptive trade practices: Intended to profile, track, and monitor millions of Internet users." Existing web browsers use "cookies" to accomplish such things in a modest way, but the data is stored on your machine and can be readily deleted (Hetscape users, for example, can just trash the MagicCookie file). The Passport system, however, stores personal information — including passwords — on Microsoft servers where they cannot be deleted by users. But don't worry. Microsoft representatives have promised not to use the information without your approval. And you do trust Microsoft. Don't you!



## Free Access to IEEE 802 Networking Documents


The Institute of Electrical and Electronics Engineers Standards Association (IEEE-SA) has launched what it calls the "Get IEEE 802™" pilot program, which grants public access to view and download individual electronic versions of IEEE Local and Metropolitan Area Network (802) standards. This is said to be the first time the IEEE-SA has made a series of standards widely available at no charge.

IEEE 802 connectivity is a fairly low-cost concept, and the price of the printed standards alone could exceed the cost of implementation in hardware and software for some users. Therefore, in an apparent desire to make the specifications as widely available as possible, the IEEE-SA is offering free Acrobat PDF versions, which will be available six months after a particular standard's initial publication date. New IEEE 802 standards will be added to the program with this time delay.

There are approximately 50 IEEE 802 LAN/MAN standards at present. To view and download the files, you just need to visit <http://standards.ieee.org/getieee802/>.
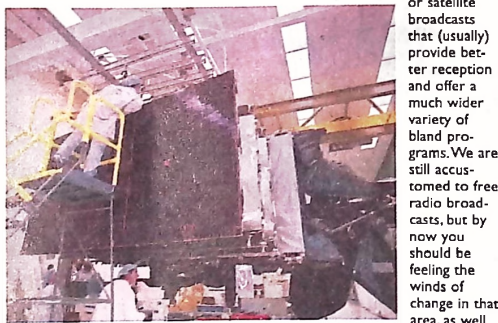
## Circuits and Devices The Dawn of Digital Radio

In the good old days, television was bland and limited to three networks, but at least it was free. Now most of us pay substantial monthly fees for cable



One of two telescoping solar wings aboard "Roll," a Boeing 702 satellite built for XM Satellite Radio. The 9,800-pound, 18 kW spacecraft generates 3,000 W of RF power. Courtesy of Boeing Satellite Systems, Inc.

On the transmission end, two satellite radio service providers are almost ready to get started. XM Satellite Radio, Inc. ([www.xmradio.com/](http://www.xmradio.com/)) and Sirius Satellite Radio, Inc. ([www.siriusradio.com/](http://www.siriusradio.com/)) will bring you 100 channels of music, news, weather, sports, etc., for, respectively, \$9.95 and \$12.95 per month. Broadcasts will be offered in English plus Spanish, Mandarin, Cantonese, Hindi, and Japanese, and perhaps others in the future. Both systems use geosynchronous satellites and terrestrial repeaters to beam the signals to you.

On the receiver end, you will need a digital radio that picks up signals in the 2,320 to 2,345 MHz range. The receivers use short external antennas and resemble existing

AM-FM car and table radios, but include some circuits that authenticate you as a paid subscriber. They also will cost a bit more.

For example, Pioneer will offer two add-on tuners that can be fitted to your existing radio for \$199.00 and \$249.00, depending on whether you want a digital display and remote control. A complete receiver/tuner package will run \$399.00. Other units will cost up to \$1,200.00, depending on the options selected (tape deck, CD player, etc.). Digital transmissions are scheduled to begin this fall, and receivers (which will also be available from Alpine, Jensen, Kenwood, Panasonic, and Sony, among others) should be on sale in time for Christmas.

## Industry and the Profession Worldwide Computer Sales Fall

According to market analysis company IDC ([www.idc.com](http://www.idc.com)), the worldwide PC market was stagnant in the second quarter of 2001, and sales for the year may decline for the first time in the history of the personal computer. Shipments totaled 29,783,000 units, as compared with 30,383,000 during the same period in 2000, for an overall decline of two percent. The picture was even worse in the US, where Q2 shipments in 2000 and 2001 were, respectively, 11,426,000 and 10,501,000, for a drop of 8.1 percent. The only major computer company showing a gain was Dell, with worldwide unit sales increasing from 3,459,000 to 3,979,000, for a 15 percent increase. (Earlier this year, Dell became the number one PC manufacturer, taking the title away from Compaq.) Major losers included Compaq (down 10.5 percent), IBM (down 5.6 percent), and Hewlett-Packard (down 8.6 percent). IDC predicts that the PC market will be flat to negative for at least the rest of the year.

With computer prices dropping faster than unit sales, profits also have been widely dismal so far this year. In July, Compaq reported a \$279 million quarterly loss on \$8.5 billion in revenues, including a \$493 million restructuring cost. This compares unfavorably with the company's \$388 million profit on \$10.1 billion in revenues during the same quarter of 2000. Compaq is predicting a further decline in the third quarter.

Similarly, Hewlett-Packard's revenues have dropped, and it is now predicting third-quarter revenues of about \$10 billion, which is off about 15 percent from last year's \$11.8 billion level. HP laid off 1,700 workers in January, another 3,000 in April, and has announced plans to let another 6,000 go by the end of the year. In addition some 80,000 employees have accepted pay cuts and unpaid vacations.

Apple Computer managed to stay in the black, with a net profit of \$61 million for the quarter that ended June 30, on revenues of \$1.5 billion. However, this represents a decline from \$200 million from revenues of 1.8 billion. The company shipped 827,000 Macintosh® computers during the quarter.

Continued on page 42

## Test Equipment From \$99.00



ATC modules provide for affordable pc based testing DSO, DVM, Spectrum Analyzer, Data Logging O-Scope Ip and O-Scope II Single and dual channels Serial a protocol analyzer software package DFA 5 low cost differential amplifier

Standalone digital oscilloscopes from HiRel and TPI

Pico Technology LTD leads in low cost pc based modules for test and data logging. Units to 100MSPS. 8 to 16 bits, 1 to 22 channels. Environmental monitoring. Science education with DRDAQ. Pricing from \$99

### Allison Technology Corporation

2006 Finney Valley Rd. Rosenberg, TX 77471

PH: 800-980-9806 or 281-239-8500, FAX 281-239-8006

<http://www.atcweb.com> atc@atcweb.com

## Tools for the Imagination



With dozens of embedded controllers and countless configurations, we can help you turn your imagination into reality. For a complete look at our product line, visit our website at [www.micromint.com](http://www.micromint.com).

## Micromint

[www.micromint.com](http://www.micromint.com)

(800) 635-3355




# XYLOTRON II

## Thanks for the Memory

by Robert Lang



Figure 1. Original XYLOTRON Design

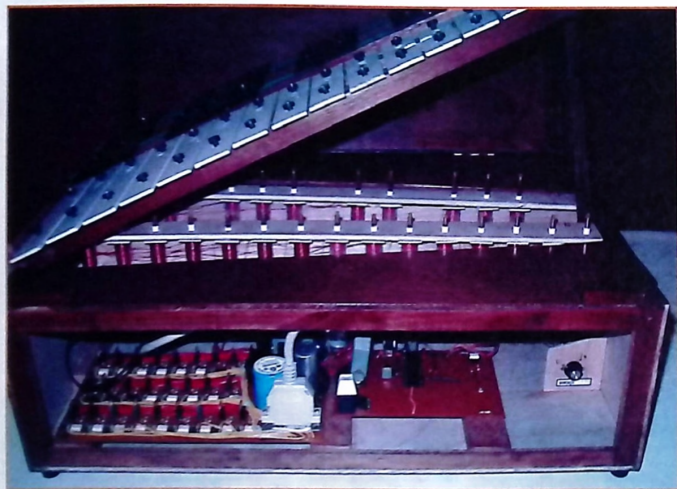

### INTRODUCTION

Since publishing the XYLOTRON article in the Oct. 2000 issue of *Nuts & Volts*, the XYLOTRON circuitry has been used to MIDI enable and automate a number of musical instruments including a harpsichord, a calliope, and a pipe organ. Several people have asked me whether the XYLOTRON circuitry from Reference 1 can play music if not connected to a computer.

The original XYLOTRON design shown in Figure 1 did not have the ability to play music unless it was connected to a computer and MIDI data was being downloaded in real time. After lugging a computer around to several demonstrations, I came to the conclusion that the XYLOTRON should have a computer-independent mode of operation.

This article will discuss the circuit and software modifications necessary to give the XYLOTRON the ability to "hear" a MIDI tune one

time and remember it, and play it on command without being connected to a computer. This article also provides some useful information on interfacing large external memory chips to a microcontroller.

### HARDWARE CHANGES

There were no changes to the solenoids or solenoid driver board as described in Reference 1. All the changes were made on the microcontroller circuit board. The hardware changes to the XYLOTRON consisted of some rewiring, the addition of a serial EEPROM, and two input switches to control the mode of operation as shown in Table 1. The total cost was less than \$5.00. The modified schematic for the XYLOTRON II is shown in Figure 2.

The EEPROM is electrically erasable memory that does not lose its information when the power is turned off. The EEPROM chosen

was the 24LC256 from Microchip. It stores 32K bytes of information. It uses the two wire inter-integrated circuit (I<sup>2</sup>C) serial interface with a maximum clock frequency of 400 kHz. It has a 5ms maximum write cycle time for up to 64 byte pages.

The 24LC256 data retention is greater than 200 years and it is guaranteed for 100,000 erase/write cycles. It is all conveniently packaged in an eight-pin PDIP package.

The addition of the EEPROM was done using the I<sup>2</sup>C pins on the Microchip 16F877 microcontroller. Unfortunately, in the original design these pins (18 and 23) were being used as note output pins. The new software redirected these outputs to pins 2 and 3 on the 16F877. The previously unused I/O pins 5 and 6 on the 16F877 were used as inputs on the new design. I/O pin A2 (pin 4) was used to control an LED that indicated when the real time clock was running. The RTC only runs when the XYLOTRON is reading or writing to the EEPROM.

Figure 3 shows the prototype of the XYLOTRON II on a breadboard. Figure 4 shows the modified XYLOTRON board with the hardware changes necessary to make it a XYLOTRON II. The hardware modifications allowed the XYLOTRON II to remember about 65,635/96-683 seconds of music or 32726/8-4090 notes, whichever comes first, using a 32K byte serial EEPROM chip. Each note required eight bytes of storage: four bytes for the NOTEON and four bytes for the NOTEOFF. The format is given in Table 2. The only MIDI information stored in the EEPROM is NOTEON and NOTEOFF. Table 3 is a list of the parts needed to create the XYLOTRON II.

### SOFTWARE CHANGES

The major changes in the XYLOTRON software were the changing from a polling system to an interrupt driven system and the adding of the software to service the external memory. The source coding for the XYLOTRON II is written in Microchip assembly language and the commented source is available for free download from Reference 3. If you don't want to do the chip programming yourself, pre-programmed 16F877 chips are also available at Reference 3.

During the busiest time — MODE=1 — the XYLOTRON may be running three critical processes. The first process is the update of

### REFERENCES/SOURCES

Reference 1. October 2000 issue of *Nuts & Volts* for the original XYLOTRON article.

Reference 2. Microchip Application Note #735 by Richard Fischer for information on interfacing memory chips to Microchip microprocessors using I<sup>2</sup>C.

Reference 3. XYLOTRON web page <http://www2.netdoor.com/~rlanq/xylotron/xylotron.htm> for

software and preprogrammed 16F877 microprocessors.

Reference 4. Microchip Web Page [www.microchip.com](http://www.microchip.com)

Reference 5. Peter Anderson at [www.phanderson.com](http://www.phanderson.com) for microprocessors and memory.

Reference 6. Electronics Express at [www.elexp.com](http://www.elexp.com) for electronic parts.

Reference 7. Jameco, Inc., at <http://www.jameco.com> for electronic parts.



the real time clock (RTC). The tick counter is incremented once every 1/96 second. This is accomplished by using the TIMERO of the 16F877. The input to the TIMERO is FOSC/4/PRESCALER. With a FOSC of 20 MHz and PRESCALER=256, the update frequency is 19531/sec. By initializing TIMERO to a value of 53, there will be a rollover interrupt 96 times per second.

The second critical process is the receiving of the serial MIDI data. This data is sent from the computer at the proper time to produce a note in a song. The data must be received and processed in real time. This process is also interrupt driven.

The third process is the storage of the MIDI data along with the time it is received. This allows the XYLOTRON II to remember a song and later play it back without being connected to a computer. Each of these time-critical processes will be described in some detail below.

## REAL TIME CLOCK

The real time clock is enabled in MODES 1 and 2 when MIDI data is being recorded to the EEPROM or MIDI data is being played from the EEPROM. The real time clock is reset and started when the first MIDI event is received in record MODE1 or the PLAY\_SONG routine is called to play the recorded song. The 16 bit real time clock counter is incremented 96 times per second via the TIMERO interrupt. The real time clock is automatically disabled when the count reaches 65,635 or about 683 seconds.

## MIDI DATA PROCESSING

A byte of MIDI data received in MODES 0-1 will cause an interrupt. The interrupt routine receives the byte. If the byte is a MIDI status byte, the mode is stored (91 is NOTEON and 81 is NOTEOFF). If the byte is a MIDI data byte and the current mode is NOTEON or NOTEOFF, then the data byte will be stored as NOTE and the next byte will be read and stored as VELOCITY. The proper 16F877 note output line will then be activated or deactivated.

## MIDI DATA STORAGE/RETRIEVAL

In MODE 1 when the first byte of MIDI information is received, the real time clock is started. Next, the real time clock 16 bit value, the MIDI status byte, and the MIDI note are saved in the format shown in Table 2 in a temporary four-byte buffer area starting at address 20H. When the buffer is filled, it is written to the EEPROM. The data is transmitted serially to the EEPROM at a 400k bits/second and, upon receipt, it takes a maximum of five

MODE	S3	S2	OPTION	Real Time Clock Interrupt	MIDI Interrupt	EEPROM
0	0	0	Don't remember MIDI, Normal power on/reset test	Disabled	Enabled	Unused
1	0	1	Do remember MIDI, Normal power on/reset test	Enabled	Enabled	Write
2	1	0	Don't remember MIDI, Play MIDI on power on/reset test	Enabled during reset test	Disabled	Read
3	1	1	Dump EEPROM contents at 9600 BAUD. If S2 is now turned off the EEPROM is erased.	Disabled	Disabled	Read then Write

Table 1. Input Switch Setting

MIDI COMMAND	BYTE 1	BYTE2	BYTE3	BYTE4
NOTE ON	MSB of time of MIDI event. The time is units of ticks from the start of the music. 1 tick = 1/96 second	LSB of time of MIDI event	91	The MIDI note to be played, 0-FF)
NOTE OFF	MSB of time of MIDI event	LSB of time of MIDI event	81	The MIDI note to be played, 0-FF)

Table 2. EEPROM MIDI Data Storage Format

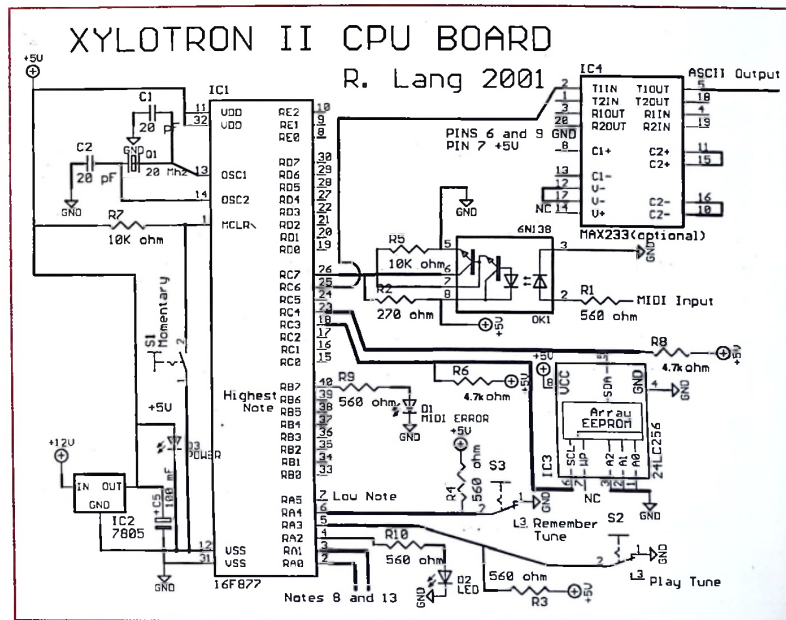


Figure 2. XYLOTRON II Schematic

milliseconds to write the data.

In MODE2, data is accessed sequentially four bytes at a time starting at location 0000 in the EEPROM. The first two bytes are checked against the RTC. When they match, the next two bytes are used as the MIDI mode and note and are played. Then another four bytes are read.

## A BUMPY START

The first task in the program development was to develop software to write and read from the

PART	DESCRIPTION	SOURCE
R10,R3,R4	1/4 watt 560 ohm resistor	Reference 6
R6,R8	1/4 watt 4.7k ohm resistor	Reference 6
IC3	24LC256 EEPROM	Reference 5
S2,S3	SPST switches	Reference 6
D2	LED	Reference 6
IC4	MAX232 RS-232 Interface Chip (optional for testing)	Reference 7

Table 3. XYLOTRON II Parts List

external 24LC256 EEPROM. There are only two wires connecting the 24LC256 to the 16F877, so I

thought this would be straightforward.

There are some application



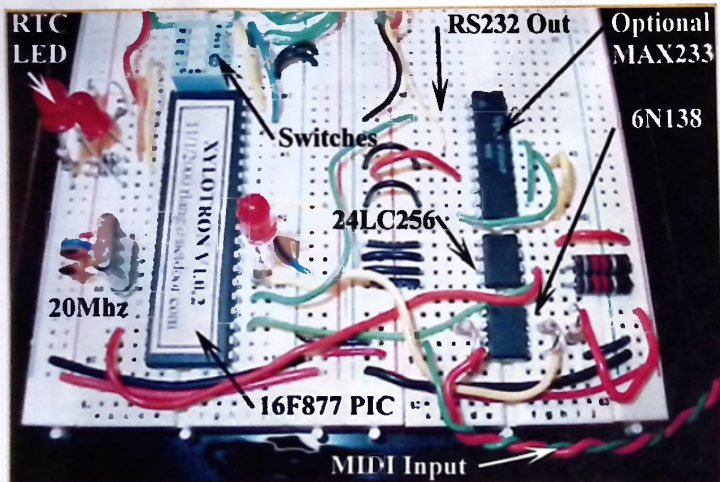


Figure 3. Prototype of the XYLOTRON II Hardware

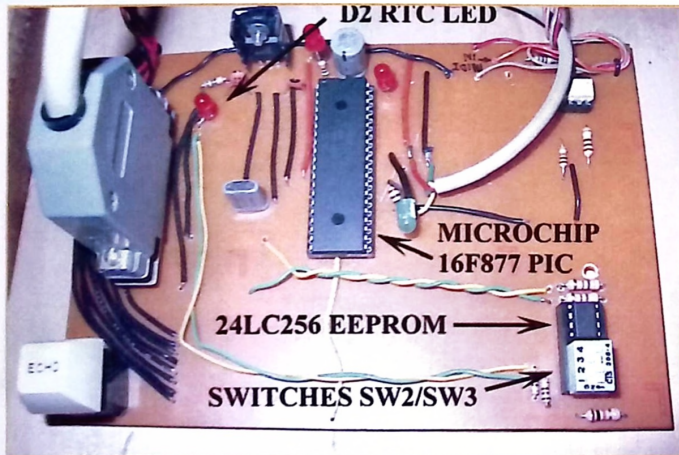


Figure 4. Completed XYLOTRON II Microcontroller Board (Modified XYLOTRON board)

```

(S2 and S3 are turned on to begin ASCII dump of EEPROM)
00 00 -00 77 91 37 00 82 81 37 00 86 91 3E 00 91 81 3E 00 95 91 37
00 95 91 38 00 A0 81 38 00 A0 81 37 00 A4 91 3E 00 AF 81 3E
00 B3 91 3E 00 B3 91 37 00 BE 81 37 00 BE 81 3E 00 C2 91 3E
00 CD 81 3E

00 40 -00 91 91 37 00 DC 81 37 00 DF 91 3E 00 EB 81 3E 00 EE 91 39
00 EE 91 42 00 F9 81 42 00 FA 81 39 00 FD 91 3E 01 08 81 3E
01 0C 91 39 01 17 81 39 01 1B 91 3E 01 26 81 3E 01 2A 91 3E
01 24 91 39

```

```

(S2 is turned off to begin EEPROM
00 00 -
00 40 -
00 80 -
00 C0 -
01 00 -
01 40 -

```

Table 4. Example of  
MODE3 Dump of  
EEPROM MIDI Data

done this by adding an additional address byte when transmitting the address to the EEPROM. There is also confusion in how to send data to the EEPROM by using or not using interrupts.

One of the best i2C application notes is Reference 2. I followed the examples as best I could because there was no example for doing exactly what I wanted to do, which was use the MSSP hardware module on the 16F877 microcontroller to read and write data blocks to a 24LC256 EEPROM using polling. The Microchip documentation describes many ways that might work: testing the buffer full (BF) bit, testing the acknowledge received (ACKSTAT) bit, testing the receive enabled (RCEN) bit, testing the SSP interrupt flag (SSPIF), etc. For over a month, I tried all possible combinations that I could think of and got absolutely nowhere. The EEPROM would not respond.

I reviewed all the available material on the internet, contacted Microchip by email a couple of times, and posted several messages to the Microchip online discussion groups. There were many appeals for help with this same type of problem. Finally, I was beginning to think I had a faulty memory chip when I made one more email to Microchip tech support. I sent my circuit diagrams and assembly source code. I received a quick reply from Ken Dietz that included some snippets of assembly language.

Comparing his source to mine, I was able to get single byte reads and writes working and then got the block reads and writes working. It seems the key to getting the source to work was clearing and checking the SSPIF bit in the PIR1 register after each write or read even when not using interrupts. My working assembly language source is available at Reference 3 free of charge.

## SETBACK #2

Once the memory problem was overcome, I had a working system. It would record and play songs with one problem. If the song was very fast, data would be lost in the record phase. The reason for this was that the EEPROM takes five milliseconds to write the data internally once it is received from the microcontroller. If an attempt is made to send more data while the internal write is in progress, it is ignored. It is important to note that it takes five milliseconds to write one byte or 64 bytes.

The solution was to implement a dual buffering system with 64 bytes in each buffer rather than the initial single four-byte buffer. One buffer is marked ACTIVE and the other is marked INACTIVE. When a MIDI input interrupt occurs, the MIDI data is written four bytes at a time to the ACTIVE buffer. When

notes available for free from Microchip (Reference 4) that explain how the i2C synchronous interface to the EEPROM memory works. Unfortunately, there are so many, that it is possible to get very confused. One source of confusion is that Microchip provides technical application notes on how to implement i2C protocol in software on microcontroller chips that do not have an i2C interface module (MSSP) built in.

Another source of confusion is that the addressing scheme differs depending on the memory chip. Microchip has expanded the i2C interface specifications to allow addressing up to 2Mb. They have



the active buffer is filled it is marked as the FULL INACTIVE buffer and the other buffer is marked ACTIVE.


New MIDI data will now be written to the new active buffer. A background task is always checking to see if the inactive buffer is full. If the inactive buffer is full, then it is dumped to the EEPROM and then marked as EMPTY. The alternating of the active and inactive buffers continues while MIDI data is received and stored.

Since the buffer is only dumped to the EEPROM when it is filled, it may be necessary to send a few extra notes along at the end of the song to flush the contents of the buffer to the EEPROM. These extra notes will be silent as long as they are not in the active note range of the XYLOTRON. The active note range is the chromatic range from C4 through C6 or MIDI notes 48-72.

## PROGRAM FLOW

When the program starts or the RESET button is pressed, the program first reads the data switches, S2 and S3, and sets the mode as shown in Table 1. In MODE0, the power on/test note sequence is played and then the MIDI interrupt is enabled. In MODE1, the power on/test note sequence is played and then the MIDI interrupt is enabled

**Figure 5.**  
**Musical**  
**Representation**  
**of Data in**  
**Table 4**

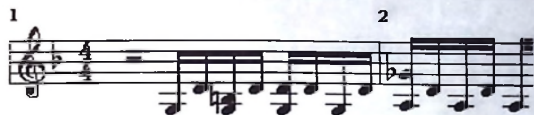

and the RTC interrupt is enabled on the receipt of the first MIDI byte. MIDI data is written to the EEPROM until it is filled or the RTC count overflows.

In MODE2, the RTC interrupt is enabled and the MIDI data is read from EEPROM and the recorded song is played. In MODE3, the MIDI data stored in EEPROM is dumped out at 9600 baud on pin 25 in the format shown in Table 4. The MIDI data shown in Table 4 corresponds to the music shown in Figure 5.

When two notes have the same start time, then they are part of a chord. The data can be viewed on any computer with a serial port and a communications program if the optional MAX233 chip has been installed.

Viewing the contents of the EEPROM is sometimes useful in debugging. If, during the dump process, the S2 switch is turned off, the program will begin to zero the external EEPROM memory 64 bytes at a time starting at location 0000.

## HOW TO USE THE NEW FUNCTIONS

In order to use the new functions, first the XYLOTRON II must be started in MODE 1 by setting switches S2 and S3 with the MIDI input connected to a source of MIDI data like a computer or MIDI keyboard. When the first note is played on the computer or MIDI keyboard, the XYLOTRON II will begin remembering all NOTEON and NOTEOFF data on MIDI channel 1. The recording will continue for 683 seconds or 4,090 notes, whichever comes first. The LED on pin 4 (D2) of the 16F877 will be lit during recording and playback indicating that the real time clock is running.

To play the recorded tune, turn the power off. Change the switch settings to MODE 2. Turn on the power and the recorded song will play. Hitting the reset switch (S1) will cause the song to restart at the

beginning. Setting the switch settings to MODE 0 is equivalent to the old XYLOTRON function. Setting the switches to MODE 3 will display or erase the entire EEPROM.

## CONCLUSION

With a minimum of hardware and some major software changes, the original XYLOTRON design has been improved by adding the ability to hear a MIDI tune one time, remember it, and play it on command without being connected to a computer. NV

*Robert Lang is a professional electrical engineer interested in robots, MIDI, and music. He has written several articles for computer, electronics, and synthesizer magazines. He welcomes your comments and can be reached at [rlang@netdoor.com](mailto:rlang@netdoor.com).*

**POLARIS - YOUR COMPLETE SOURCE FOR ALL YOUR VIDEO MONITORING NEEDS...**

CALL OR GO ON-LINE TO ORDER YOUR FREE VIDEO CATALOG - 100'S OF PRODUCTS - MICRO CAMERAS - WIRELESS VIDEO - LIPSTICK CAMERAS - DIGITAL VCR'S - 25" COLOR TFT PLAY SCREEN MODULE

**OUR NEW COLOR 25" TFT MODULE** can be used for a variety of purposes such as: custom automatic cash installations, hotel installations, covert surveillance, surveillance packages and more.

**UNIT IS ONLY 5.8mm THICK!**  
TFT-M25 - \$149.95  
Download (VHS/D) 0.5" x 0.5" x 2.5" x 2.5"

**INTERNET WEB CAMERA WITH BUILT-IN PAN/TILT/ZOOM CAPABILITY**

Featuring built-in Web browser, powerful 16x zoom, pan/tilt and alarm module, and alarm module, all in an ultra-compact unit. These Web cameras can be installed virtually anywhere and deliver high-quality images to the Internet for real-time monitoring or broadcast. Better yet, these cameras can be controlled and monitored via a standard Web browser making it ideal for a wide variety of applications. Size 120mm x 120mm x 120mm.

**SONY AUTO TRACKING VIDEO CAMERA**

**12X Zoom Built-In Pan/Tilt Auto Tracking Camera** from SONY

**EVI-D30** \$149.95

Download with remote software. Visit our website for a demonstration: [www.polarisusa.com](http://www.polarisusa.com)

High speed wide range pan tilt head, integrated 12X high speed auto focus zoom lens, auto tracking and motion detection, remote control, via RS-232C/VISCA, IR remote commander supplied.

**THE FLEXWATCH acts as an internal camera sensor. No software is needed to view your video, only your web browser such as Internet Explorer or Netscape. FlexWatch includes many special functions including video quality control, pan/tilt/zoom interface, and network configuration. Each function is remotely controlled by the web browser while using your personal computer. FlexWatch features 4 video inputs: 1 Internal - 3 external.**

**LIVE VIDEO!**

Fully adjustable focus from 0.5 inches to infinity. Contains a true color CCD chip rather than a CMOS type sensor for an excellent resolution of 330 TVL. Comes complete with a 12" video / power cable.

**VIDEO HEAD IS ONLY 7MM IN DIAMETER!**

**COVERT COLOR CCTV CAMERA**

Its small, sleek, adjustable dome and pinhole lens allow for various applications and simple installation. Comes equipped with a RCA JACK for easy connection to TV monitor or VCR. Great for covert use in any place imaginable.

**CMV-500P** - \$79.95 - 25mm (1" x 16mm)

**DAY/NIGHT LIPSTICK CAM**

Our new weatherproof daylight color camera can view in total darkness at a distance up to 10 meters. Comes enclosed in a weather-tight aluminum housing and equipped with a 3mm lens for a viewing angle of 60 degrees.

**ILC-300** \$239.95

**WORLD'S SMALLEST TRANSMITTING WIRELESS CAMERA**

Camera is so small it can be mounted in wall clocks, exit signs, briefcases, picture frames or even a baseball cap! Connects to a GV battery and will operate up to 6 hours.

**2.4GHz Wireless Receiver** GFR-5002 - \$119.95

**NAT-9 Color Camera** - \$289.95  
**NAT-5 B/W Camera** - \$249.95

**OPERATING RANGE IS APPROXIMATELY 400 FT.**

**RECEIVER**

**CAMERA TRANSMITTER**

**ADD UP TO 3 ADDITIONAL CAMERAS!**

Now you can enjoy peace of mind with our new wireless observation system. Comes with a 5" wireless color monitor and a wireless color camera. Just Plug-&Play for perfect wireless video any time! Great for around the house surveillance.

**WIRELESS SYSTEM**

**W-2400S** - \$379.95

**MINI-THEATRE CAMERAS - MANY MODELS TO CHOOSE FROM**

MD-1200012V7 Color Varifocal 4.3mm Lens 1.26" x 1.26" x 1.26"	MD-1200012V2 Hi-Res Color Pinhole 4.3mm Lens 1.26" x 1.26" x 1.26"	MD-430U B/W Audio 4.3mm Lens 1.18" x 1.18" x 1.18"	MD-1250P Color Pinhole 3.0mm Lens 1.27" x 1.27" x 1.27"	MD-610B Infrared B/W 3.6mm Lens 1.27" x 1.27" x 1.27"
\$109.95	\$149.95	\$69.95	\$99.95	\$119.95

**470 Armour Drive NE - Atlanta GA 30324-3843**  
Tech 404-872-0722 - Fax 404-872-1638

**WWW.POLARISUSA.COM**



# reader *FeedBack*

## Dear Nuts & Volts:

I bought your magazine for the first time and enjoyed reading your articles. It so happens that I recently have been interested in getting more information about Op-Amps and I saw the article "Part 1 Op-Amp Basics" by Ray Marston.

In reading the article, I noticed on page 17 in Figure 10(b) that the Out-Vin $\times(R1+R2)/R2$ . But in the diagram, only resistors R3 (twice) and R1 are shown.

Would you please correct this so that I can know what is the true value of Vout. As I said, I am very much interested in knowing the right answer.

Thank you and I'm looking forward to your response.

L.Y.  
Grafton, MA

## Response:

This is the corrected version of the original Figure 10(b), which contained two errors.

I generated the old artwork at 3am on a cold November day last year, when I was apparently rather tired.

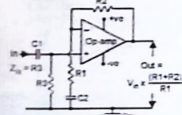


Figure 10(b). Basic non-inverting AC amplifier circuit.

Please accept my apology for the errors.

Ray Marston

## Dear Nuts & Volts:

In Ron Russ' June '01 article "Building a Flash Programmer for PIC Microcontrollers," the schematic calls for a switching transistor, Q1.

What is the part number for Q1? Is this just a garden variety switching transistor?

Dave Gianna  
via Internet

## Response:

The transistor I use is a 2N4401A or equivalent.

Ron Russ

## Dear Nuts & Volts:

Thank you for sending me a complimentary copy of your magazine.

I am one of the authors of a senior high school program called: Electricity and Electronics Technology, by Buban, Schmitt, and Carter. The program is published by Glencoe McGraw-Hill. This is the 7th edition.

The program consists of a Text, Teacher's Resource Guide, and Student Workbook.

The web site that lists our program is: [www.glencoe.com](http://www.glencoe.com). We have cited your magazine as one of several links for teachers.

I feel that teachers and their students can learn a lot from the products, articles, and other resources that your magazine provides.

Marshall L. Schmitt  
Springfield, VA

## Dear Nuts & Volts:

I was surprised at the answer you printed in the July '01 issue for question #6016. Not because you did not print my answer, but the text of those that you did print.

Question 6016 was "How can I convert a three-phase motor to single phase?" Answer #1 "The short answer is you can't..." Answer #2 "Rewind it" is impractical. Depending on the horsepower, this is so simple, it surprises me that no one describes how. You simply need to connect an AC capacitor between either line to the third line to create the third phase.

The capacitor must be able to withstand the voltages involved and AC current. This method works for low HP motors, but you must experiment with the values of the capacitor so that the voltages are the same across all three lines. If the voltage is too low, then more capacity must be added. If too high, then some must be removed. Capacitors can be connected in parallel to increase capacity, or in series to increase voltage rating.

For higher HP motors, the means must be provided to switch extra capacitors into the circuit until the motor starts. This can be done with a hand-operated relay or a current relay such as those found in ordinary household refrigerators. These are called static converters because they contain no moving parts. Building a rotary converter is another story, but is very simple to do.

I have used those methods to power my machine shop since 1952 without any trouble.

The US Department of Agriculture prints a booklet describing those methods, so that should be proof that it works.

I can write many pages describing those methods and also using ordinary induction

Published Monthly By  
T & L Publications, Inc.  
430 Prindle Court  
Corona, CA 92879-1300  
(909) 371-8497  
FAX (909) 371-3052

E-Mail — [editor@nutsvolts.com](mailto:editor@nutsvolts.com)  
URL — <http://www.nutsvolts.com>

Subscription  
Order ONLY Line  
1-800-783-4624

PUBLISHER  
Jack Lemieux N6ZTD

EDITOR  
Larry Lemieux KD6UWV  
MANAGING EDITOR  
Robin Lemieux KD6UWS

CONTRIBUTORS  
Robert Nansel  
Jon Williams  
Jeff Eckert  
TJ Byers  
Stanley York  
Gordon West  
Ray Marston  
Bob Lang  
Jan Axelsson  
Terence Thomas  
Richard Panosh  
Dennis Shepard  
Bill Stiles  
Jeff Mazur

ON-THE-ROAD EXHIBIT  
COORDINATOR  
Audrey Lemieux N6VXW

SUBSCRIPTIONS  
Robin Lemieux

CLASSIFIED ADS  
Natalie Sigafus

DISPLAY ADS  
Mary Gamara

Copyright 2001 by  
T & L Publications, Inc.  
All Rights Reserved

All advertising is subject to publisher's approval. We are not responsible for mistakes, misprints, or typographical errors. Nuts & Volts Magazine assumes no responsibility for the availability or condition of advertised items or for the honesty of the advertiser. The publisher makes no claims for the legality of any item advertised in Nuts & Volts. This is the sole responsibility of the advertiser. Advertisers and their agencies agree to indemnify and protect the publisher from any and all claims, action, or expense arising from advertising placed in Nuts & Volts. Please send all subscription orders, correspondence, UPS, overnight mail, and artwork to: 430 Prindle Court, Corona, CA 92879.

### Professional

**FREE**

## 10 HOUR RECORDER

"BUILT LIKE A BATTLESHIP"

- Heavy duty commercial recorder — NOT improvised from consumer models
- 12, 14, and 16 hour models also available
- BUILT-IN voice activation (add \$30)
- Applications information included
- Dimensions: 11.5 x 7.0 x 2.75"

**SPECIAL Microcassette Price...**

# \$159

FREE! OK. Sorry no mail order. Free shipping USA only other countries \$5. Price includes UPS to all States or Pre-Paid Orders

**Viking Systems International** 100 North Hill Drive #42, Brisbane, CA 94005  
Phone (415) 467-1220 • Fax: (415) 467-1221 • Web: [www.vikingint.com](http://www.vikingint.com)



# News Bytes

## New program automatically catalogs your CD music collection without typing a thing

**C**D Trustee is a new Windows program that catalogs your music collection, just by inserting and removing CDs in your computer. It accesses an Internet database to gather the artist name, album title, song titles, music genre — and more — automatically. None of this information exists on a music CD. The CD Trustee program compares a unique code on the CD with an Internet database containing information on over 880,000 CDs. This database is constantly kept up-to-date, with new albums added every day.

Simply press a button that says "Add CD's Automatically." You then insert a CD in the drive and wait a few seconds while the program reads the unique code and automatically ejects that CD. You continue to insert your CDs this way. When done, simply press another button to access the Internet, and sit back while your database is built for you. Additional data can be added manually, such as the location of the disc, your ratings, or whether you loaned it to a friend.

The entire process happens very quickly, taking only seconds per CD. You can catalog a large collection in a few hours, instead of the weeks it would take manually. You can then print reports, quickly find an artist, album, or song, or print jewel case inserts containing the list of songs. You can print cover images for insertion into a jewel case, or play a CD and have the artist, album, and song title displayed automatically.

CD Trustee is \$29.95 (US), but a \$10.00 discount is currently available. The program runs on computers that use Microsoft Windows. See <http://www.base40.com> for screen shots, to order, or to download a free trial copy.

## PLCs that are programmable over the Internet

**T**he new T100MD888+ programmable logic controller (PLC) is fully programmable over the Internet using any Java-enabled web browser. The programming software: Internet TRILOGI is a client/server software suite. The client portion is a Java applet that runs off any web-browser, giving users the ability to remotely program, monitor, or control the PLC via the Internet. The server portion is any PC running the T100MD888+ software and connects to the PLC via serial link.

Features of the T100MD888+ include eight digital inputs, eight digital outputs, and eight analog I/Os. It also has two MODBUS compatible serial ports and two 10A PWM outputs. The built-in 14-in LCD port is compatible with most LCD modules up to 4 lines x 20 characters.

The PLC is programmed using a unique LADDER + BASIC language which combines the relay-ladder logic language common in most industrial PLCs with a BASIC language interpreter to handle math with ease.

Unit selling price of the T100MD888 is \$199.00. The Starter Kit that includes the Internet PLC, the TRILOGI software, and the program-

# Go Wireless With Our Modules

## SILRX/TXM

The TXM and SILRX modules are a transmitter and receiver pair which can achieve a one-way radio data link up to a distance of 200m over open ground.

Both units are supplied in space-saving single in-line packages and offer SAW controlled, wide band FM transmission/reception.

The modules are particularly suited to battery-powered, portable applications where low power and small size are critical design criteria.

## TX2/RX2

The TX2 and RX2 radio transmitters and receivers give enable the simple implementation of a data link at up to 100m at distances up to 72m in building and 300m open ground. Both modules combine full immunity with automatic internal filtering to ensure EMC compliance by transmitting internal data and successions.

The TX2 as a RX2 modules will suit low-cost and multi-rate wireless links in applications including car and building security, EPOS and inventory tracking, remote industrial process monitoring, and computer networking.

## We now also offer long range SPREAD SPECTRUM, FREQUENCY HOPPING RF MODULES IN 900 MHz and 2.4 GHz

## RPC

The RPC module is an intelligent transceiver which enables a radio network link to be simply implemented between a number of digital devices. The module combines an RF circuit with processor intensive low-level packet formatting and recovery functionality.

requiring only a simple antenna and 5V supply to operate with a microcontroller or a PC.

## BiM

The BiM module integrates a low-power UHF FM transmitter and matching superhet receiver together with data recovery and TX/RX change over circuits to provide a low-cost solution to implementing a bi-directional short-range radio data link.

## Lemos International Co., Inc.

65 Southbridge Street, Auburn, MA 01501

Phone (508) 798-5004 • Fax (508) 798-4782

[www.lemosint.com](http://www.lemosint.com) • [sales@lemosint.com](mailto:sales@lemosint.com)

All products available in either 418 or 433 MHz

Circle #82 on the Reader Service Card.

ming cable sells for around \$259.00  
Contact Triangle Research  
International, Inc. for more detail at:  
1101 S. Winchester Blvd., J215  
San Jose CA 95128.

Tel: (877) 689-3245  
Fax: (530) 327-6609  
Email: [sales@tri-plc.com](mailto:sales@tri-plc.com)  
[www.tri-plc.com](http://www.tri-plc.com)

NV

## READER FEEDBACK CONTINUED ...

motors like found in a washing machine into 110V AC generators.

Francis Hillibush  
Ringtown, PA

### Dear Nuts & Volts:

I really liked Ed Driscoll, Jr.'s "Raiders of the Lost Mainframes." It's not easy to be bright and funny in an electronics article. He was.

It was fun. Hold on to him!

Travis Hardin  
via Internet

### Dear Nuts & Volts:

I was delighted by the very informative article "Raiders of the Lost Mainframes, Silicon Valley's Computer History Center" in your July '01 issue.

Please inform your readers that whereas The Computer History Center is probably the largest and best-funded computer museum, there are several other computer museums run by knowledgeable and dedicated volunteers that collect, preserve, and refurbish old computers for public display and historical research.

In New England, for example, there are the Rhode Island Computer Museum in North Kingston, RI (see [www.osfn.org/ricm](http://www.osfn.org/ricm)), and the RetroComputing Society of Rhode Island in Providence, RI (see [www.osfn.org/rcs](http://www.osfn.org/rcs)). Please stop by their websites and, when in New England, stop by for a visit.

Geoffrey Rochat  
via Internet

# Microprocessor Hands-On Training

The PRIMER Trainer is a flexible instructional tool featured in a Prentice Hall textbook and used by colleges and universities around the world. Ruggedly designed to resist wear, the PRIMER supports several different programming languages including Assembly, Machine Language, C, BASIC, and FORTRAN. A comprehensive instruction Manual contains over 25 lessons with several examples of program design and hardware control. The Applications Manual provides theory and sample code for a number of hands-on lab projects.



## Application Projects Include:

- Scan Keypad Input & Write to a Display
- Detect Light Levels with a PhotoCell
- Control Motor Speed using Back EMF
- Design a Waveform Generator
- Measure Temperature
- Program EPROMs
- Bus Interface to 8255 PPI
- Construct a Capacitance Meter
- Interface and Control Stepper Motors
- Design a DTMF Autodialer / Remote Controller

The PRIMER can be purchased as an unassemble kit (I2121) or as an assembled kit (I2122). Used in conjunction with the Prentice Hall book, it provides a hands-on approach to microprocessor connectivity via an RS232C serial port (shown in picture). Additional options include a heavy-duty keypad (shown in picture) and a 5V power supply — see our website. Quantity discounts are available. Satisfaction guaranteed.

Since 1985  
OVER  
16  
YEARS OF  
SINGLE BOARD  
SOLUTIONS

**EMAC, Inc.**  
Phone 618-529-4525 Fax 618-457-0110  
2390 EMAC Way, Carbondale, Illinois 62901  
World Wide Web: <http://www.emacinc.com>



# Boarding the Universal Serial Bus: Pick the Solution that Fits Your Project

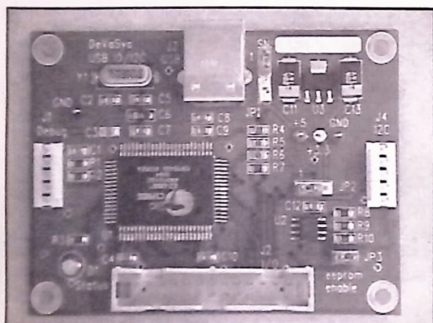


Figure 1. The USB12C10 board from DeVasys has everything you need to monitor and control 20 input/output bits via a USB port.

If you're designing something that will connect to a PC, chances are you'll consider using the Universal Serial Bus (USB). USB ports have been standard on new PCs for several years now, and the "legacy" serial and parallel ports that you could always count on in the past are beginning to disappear.

There are many ways to get a USB device up and running. In this article, I'll show three ways to add USB to a project. Each is best suited for a particular situation, so you can select the one that best fits your needs, skills, and budget.

## I Just Want to Do a Little I/O

If your needs are basic, the USB12C10 board from DeVasys

(Figure 1) is a ready-made solution that gives you 20 bits that you can use as inputs or outputs in any combination. The bits are standard 5V digital logic that can interface to switches, relay controls, LEDs, or other circuits. Windows applications can read and write to the bits. There's also an I2C serial interface that connects to an on-board serial EEPROM.

For the PC side of the link, DeVasys provides several files, including a Windows device driver that is the link between the applications you write and the low-level drivers that control communications on the bus.

To read and write to the ports, the device driver supports the functions ReadIOPorts and WriteIOPorts. In my tests of the board in a compiled Visual Basic 6 application, each read or write of the 20 I/O bits took about four milliseconds, which works out to 250 reads or writes per second. This is plenty fast for many projects.

You can add other chips to the board's I2C bus. For example, Philips Semiconductor's PCF8574 remote eight-bit I/O expander has an I2C interface and eight bits of parallel I/O. You can control this and other I2C chips with the driver's ReadI2C and WriteI2C functions.

DeVasys' website has example applications in Visual Basic and Visual C++ and a schematic of the board. The USB controller on the board is a Cypress AN2131 EZ-USB. The EZ-USB is an enhanced, 8051-compatible microcontroller with a full-speed USB interface. The board's 16-kilo-byte I2C EEPROM (a 24LC128) can store program code or data. The 3.3V regulator can receive power from the bus or an external 5V supply.

As shipped, the board contains no program code. Instead, the provided device driver uses the EZ-USB's ability to receive program code from the PC when the board attaches to the PC or the PC boots. This makes updates very easy because there are no EPROMs to program.

The board isn't limited to using the driver and device code that come with it. You can write your own program code and use other device drivers, including drivers provided with Windows. The EZ-USB chips are fast, flexible, and very capa-

NEW!

decadebox.com

ohmSOURCE® Resistance Decade Boxes

- Calculator-style keypad or rotary switch interface
- 100% mechanical isolation from circuit
- Current limiting feature to prevent device damage
- Quick Value keys for convenient one-touch store/recall
- Residual Resistance automatically included in output
- Dual Banana Plugs provide easy output connection

### PRODUCT SPECIFICATIONS

	ohmSOURCE	ohmSOURCE+
Range:	0 - 24 MΩ	0 - 24 MΩ
Resolution:	1Ω	0.1Ω
Accuracy:	± 1Ω up to 1 kΩ ± 1% 1 kΩ - 24 MΩ	± 0.5Ω up to 1 kΩ ± 1% 1 kΩ - 24 MΩ

labMetric  
The Source of Innovation®  
Scottsdale, Arizona  
PH: 480.566.7677  
FX: 480.566.7674





Order Online for  
FREE Shipping!

PATENT PENDING



**Figure 2. Microchip has two USB-capable PIC microcontrollers. Both have 19 I/O bits, and the '65 also has an external data bus. The USB data lines are D+ and D-. The VUSB pin provides power for the required pull-up resistor on D-.**

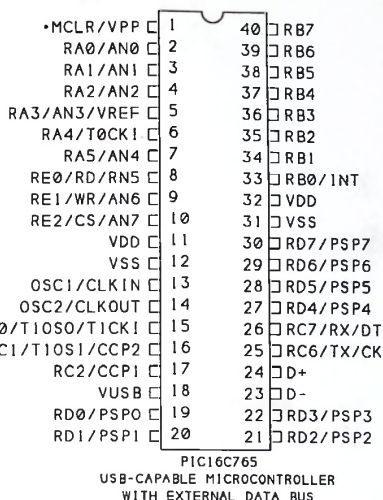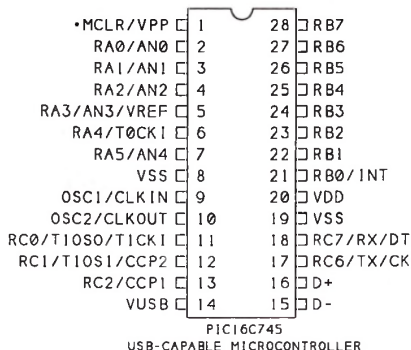

ble. They even have two UARTs for RS-232 or similar links. Because of the support built into the chips, the amount of code you need to add for USB communications is less than what other chips require. A free assembler and a trial version of a C compiler are available from Cypress, along with complete documentation and sample code.

## I Like PICs!


Microchip's PIC controllers are popular for good reason. They're inexpensive, easily available, and Microchip offers a variant for just about any purpose. Now there are two PICs that support USB: the PIC16C745 and PIC16C765 (Figure 2).

Both chips support USB's low speed. In the world of USB, low speed means a bus rate of 1.5 megabits per second, rather than full speed's 12 megabits per second or USB 2.0's new high speed of 480 megabits per second. To keep a single device from clogging the bus, the USB specification also limits the amount of bus time a low-speed device can reserve. At most, you can count on transferring 800 bytes per second in each direction.

The most popular use for low speed is devices in the human interface device (HID) class. HID's include mice, keyboards, and joysticks, but you can also use the HID class for devices that don't fit into one of these categories. Windows includes drivers for HID communications, so if the code in your device meets the requirements of the HID spec, you don't have to provide a driver.

The PICs are enhanced members of Microchip's 16C5x series. Code written for the 16C5x is portable to the 16C7x5. Besides the USB interface, the chips have 19 I/O pins, plus the '65 has an eight-bit parallel slave port for connecting to a microcontroller with an external data bus. Up to eight of the I/O pins can function as inputs to an on-chip analog-to-digital converter.

An on-chip USART supports two other kinds of serial links. With Maxim Semiconductor's MAX232 or a similar chip, you can use the USART for RS-232 communications. The USART also supports synchronous communications, where the interface includes a clock line. Either the PIC or an external source can provide the clock.

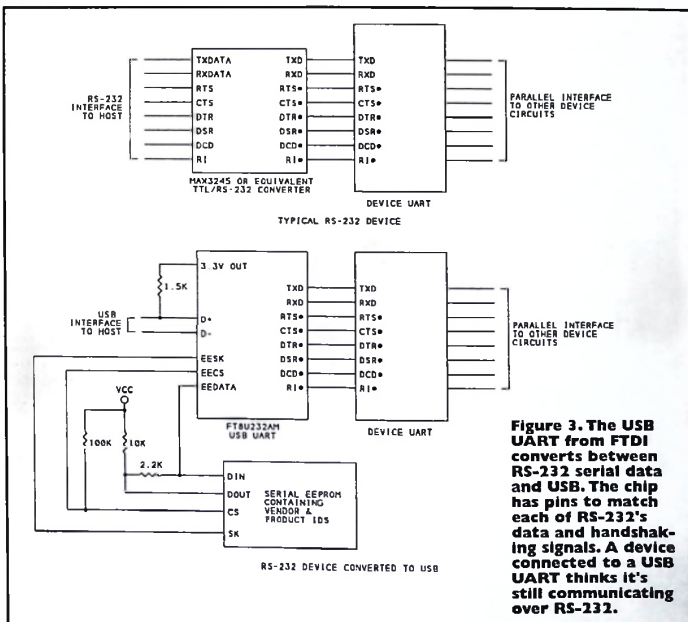

**Figure 3. The USB UART from FTDI converts between RS-232 serial data and USB. The chip has pins to match each of RS-232's data and handshaking signals. A device connected to a USB UART thinks it's still communicating over RS-232.**


You can use a crystal or an inexpensive ceramic resonator to clock the CPU. Program memory is EPROM or one-time-programmable (OTP) PROM. The chips are available in through-hole and surface-mount packages. Microchip's MPLAB In-Circuit Emulator (ICE) 2000 development system supports the chips.

The PICs require a fair amount of code to support USB communications, including the code that responds to the standard requests the PC

sends when the device attaches to the bus. Much of this code is the same for all applications, so adapting it for a specific project requires few changes. Microchip provides code for a HID-class device that sends and receives generic data.

Other microcontroller families also have USB-capable variants. If you have experience with a microcontroller, it makes sense to stick with it when you have a project with a USB interface. Fans of the 8051 can use Cypress' EZ-USB or Infineon's



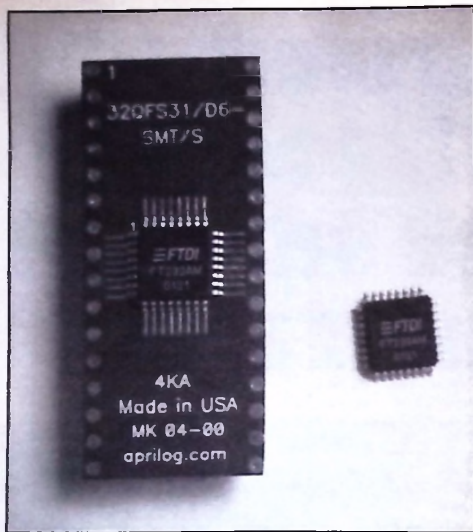

**Figure 4.** With an adapter, you can use the USB UART on a breadboard or a protoboard designed for through-hole components.

C541U. Atmel's AVR family includes the USB-capable AT76C711. For an eight-bit Motorola microcontroller, check out the 68HC05J83/4 and 68HC08J88.

### I Want the Option to Use Either RS-232 or USB

The RS-232 serial port is a good, general-purpose

interface that has been with the PC since its beginning. There are thousands of different RS-232 peripherals in use. But RS-232 ports are beginning to disappear from PCs. Fortunately, just about any RS-232 device can be designed to use USB, and it's easier than you might think to make a device that supports both interfaces. This way, you can use the device with everything from an old DOS PC that doesn't support USB to the latest "legacy-free" Windows PC that lacks an RS-232 port (though DOS will require different software on the PC).

An easy way to add USB capability to an RS-232 device is to buy a converter that translates between the two interfaces. A device driver included with the converter causes Windows to treat the USB device the same as if it were using a straight RS-232 connection.

With the converter option, you can use the same software on the PC to communicate with the

device, no matter which interface it's using. The only limitation to using a converter is that the PC's application software must use standard Windows functions for accessing COM ports (ReadFile, WriteFile) or a custom control such as Visual Basic's MSComm, which uses these functions internally. Inp and Out functions that write directly to a port address won't work. Converters are available from many sources, including B & B

## What About USB 2.0's New High Speed?

One of the biggest news items relating to USB is its new high speed of 480 megabits per second. High speed became a possibility with the release of version 2.0 of the USB specification in 2000. Making high speed a reality requires three things: a USB 2.0 host controller in the PC, support for USB 2.0 under Windows, and a device that contains a high-speed-capable controller.

USB 2.0 host controllers will soon be standard on new motherboards, or you can add a controller to an existing system on a card that fits in a PCI slot. Microsoft has promised that support for USB 2.0 will either be included in the latest Windows edition, called Windows XP, or it will be available as an update soon afterwards. Updates for Windows 2000 and Windows Me are likely to follow. High-speed controllers for peripherals are available now from a few vendors, and the selection will increase in time.

What about all of the older, slower USB 1.x hardware? Just about all of the high-speed peripherals will also function at full speed, so they'll be usable with older hardware. And the 2.0 controllers are backwards-compatible, so all of your full- and low-speed peripherals will still work fine with the new controllers.

Electronics, which has a large selection of USB-related items.

For a more elegant way to do the same thing, the USB UART from FTDI makes it easy to build a converter into a project.

A typical UART converts between the serial data used by RS-232 and a CPU's parallel data. Besides data lines, a UART may also support RS-232's handshaking signals such as RTS and CTS. Just about all UARTs use 5V (or 3V) logic, so converting to RS-232's positive and negative voltages

requires added components, such as a MAX232 chip.

The USB UART works in a similar way to other UARTs, except instead of converting to and from parallel data, it converts to and from USB (Figure 3). To adapt an RS-232 design for USB, you move the CPU's connections from the MAX232 or other RS-232 voltage converter to the matching pins on the USB UART. The device's internal code requires no changes because the device still thinks it's talking over an RS-232 link as usual.

The USB UART supports all of RS-232's handshaking signals, and FTDI provides a free device driver.

To support both interfaces, you can include a switch that routes the signals to the RS-232 converter or the USB UART. A circuit that detects

## Use your PC as a scope and datalogger!

**Parallel Port Scope**  
spectrum analyzer, and digital multimeter

\$99 - \$799



**ADC Virtual Instruments** turn your PC or laptop into a sophisticated storage scope AND spectrum analyzer AND multimeter. Display simultaneously on large screen! 100MS/s 8-bit or 12MS/s 12-bit or 330KS/s versions. Great for schools, test desks, etc. Input to Excel! LabView/NT drivers included.

**Environmental Logging**  
record temperature, humidity, etc.

\$129 - \$645



**ENVIROMON** - temperature (thermistors), humidity & light sensors, door position, etc. Record for 96524 without a PC even if power fails. Monitor 30 sensors 400 yds away. With cables and easy software. Remote audio alarm. Use TC-08 for most thermocouples.

**DRDAQ for PCs**  
science logger with sensors

\$99+



**DRDAQ** - is a PC adapter with sensors for light, pH, volts and temp. Great for science fairs! Supplied with ready-to-run software and lots of physics/chem exp'ts.

PC-based Instruments!

Download FREE demo software. Sales only: 1-888-7SAELIG

www.saelig.com 716-425-3753 - 3835 (fax) saelig@aol.com

**pico**  
Technology Limited

Stocked in NY by Saelig Company: Virtual Instruments, I2C and embedded controllers, BITLink 2-wire networks, RS232/422/485, CANbus, etc. See [www.saelig.com](http://www.saelig.com) for Product of the Month!

Jan Axelsson is the author of the just-released Second Edition of *USB Complete: Everything You Need to Develop Custom USB Peripherals*. Visit Jan's USB Central web page at [www.Lvr.com/usb.htm](http://www.Lvr.com/usb.htm).



## Web Links ...

Atmel USB-capable AVR controller  
(AT76C711) [www.atmel.com](http://www.atmel.com)

B & B Electronics  
USB/RS-232 converters  
[www.bb-elec.com](http://www.bb-elec.com)

Cypress Semiconductor EZ-USB  
[www.cypress.com](http://www.cypress.com)

DeVaSys USB2CIO board  
[www.devasy.com](http://www.devasy.com)

DIP adapter board for FTDI USB UART  
Part #32qfs31/D6-SMT/S  
[www.smt-adapter.com](http://www.smt-adapter.com)

FTDI USB UART  
[www.ftdichip.com/](http://www.ftdichip.com/)

Infineon 8051-compatible, USB-capable  
microcontroller (C541U)  
[www.infineon.com](http://www.infineon.com)

Microchip PIC16C745 and PIC16C765  
USB microcontrollers  
[www.microchip.com](http://www.microchip.com)

Motorola 68HC05JB3/4 and 68HC08JB8  
USB microcontrollers  
[www.motorola.com](http://www.motorola.com)

Philips Semiconductor's PCF8574 Remote  
8-bit I/O expander  
[www.philips.com](http://www.philips.com)

Saelig Company  
U.S. distributor of the USB UART  
[www.saelig.com](http://www.saelig.com)

Jan Axelson's USB Central  
Tutorials, example code, and other info  
for USB developers  
<http://www.lvr.com/usb.htm>

a voltage on the USB's power line could switch the signals automatically, using the USB UART when the USB voltage is present and RS-232 otherwise.

One cost of USB developing is that any product you sell must contain a Vendor ID and Product ID. When a device attaches to a PC, Windows reads this information from the chip and uses it in locating the correct device driver. Vendor IDs are assigned by the USB Implementers Forum, which is the non-profit corporation that publishes the USB specification and, in general, supports USB develop-

ment. A Vendor ID costs \$1,500.00 and includes the right to assign Product IDs associated with the Vendor ID.

The USB UART contains FTDI's Vendor ID and a Product ID. Because you don't change the programming in the chip, your product can use these values. You also have the option to store your own IDs in an external serial EEPROM. If you'd like a unique Product ID to use with FTDI's Vendor ID, you can request one free from FTDI.

The USB UART is a 32-lead surface-mount

chip (a quad flatpack, or QFP). The chips are available in the U.S. from Saelig Company.

For experimenting on a through-hole proto board, use a DIP (dual in-line package) adapter (Figure 4), though you'll need to do some fine soldering of the chip to the adapter. One source for adapters is [www.smt-adapter.com](http://www.smt-adapter.com).

For another approach to USB using a different FTDI chip, see "Add a Universal Serial Bus Interface to your Next Project" by Don L. Powrie in the May 2001 issue of *Nuts & Volts*. **NV**

# www.gatewayelec.com

(Electronically Speaking, Gateway's Got It!)



MAIL ORDERS CALL TOLL-FREE 1-800-669-5810



# ELECTRONICS Q & A

With TJ Byers

In this column, I answer questions about all aspects of electronics, including computer hardware, software, circuits, electronic theory, troubleshooting, and anything else of interest to the hobbyist.

Feel free to participate with your questions, as well as comments and suggestions.

You can reach me at:  
**TJBYERS@aol.com**  
or by snail mail at  
Nuts & Volts Magazine,  
430 Princland Ct.,  
Corona, CA 92879.

## What's Up:

Audio, synthesizers, music, and sounds. Lights, lamps, and dimmers. How to make your own optical RS-232 link. Making an A/V and solar connection.

Finally, a reader shares a discovery.

### Solar Fun Site

I'm looking for a book about using solar cells as a power source for recharging batteries. I've looked high and low, finding all sorts of information on powering your home, but nothing at the hobby level. Do you know of anything?


Patrick Robertson, Sr.  
via Internet

As for books, all I know about are out of print, including the one I wrote 15 years ago (20 Selected Solar Projects). However, there is a web site managed by G. Forrest Cook ([www.solarorb.com/elect/solarcirc/index.html](http://www.solarorb.com/elect/solarcirc/index.html)) that will satisfy your appetite for hobby solar projects. Here's a sample of his work.

### AA battery solar charger



Optional 8th cell and diode

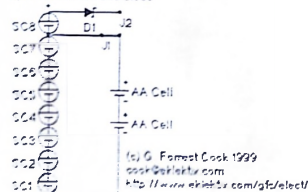

### Dawn To Dusk Dimmer

I am in need of information for a timer/dimmer combination. Specifically, I'm looking for a device that will control aquarium lighting: turn the light on at a very low level and increase to full brightness over a programmable period of time. Same for shutting off in the evening. This is useful for simulating the natural day-night cycle for the fish. If you know where I can obtain one in kit form, it would be most helpful. If not, schematics will do.


John A. Wass  
via Internet

AquaDirect by AquaLink (800-827-0117; [www.aquadirect.com/lighting/dimmers.html](http://www.aquadirect.com/lighting/dimmers.html)) makes exactly what you're looking for. They also make a lunar timer that's designed to promote coral growth by simulating the lunar cycle.
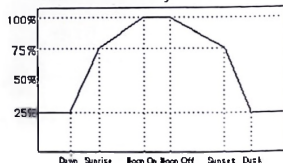
## Solar 1000



Dim lamps throughout the day for a natural intensity curve



### Finger Pickin' Good

I am interested in audio electronics techniques for musical special effects—microphones and electric guitars, in particular. I have scanned back issues and found a few related articles, but I could use some more knowledge about things like reverb and wawa effects. Can you recommend any resources that would help me get started?

William Frederick, MD  
via Internet

I'd start with a couple of books on the subject, such as *Do-It-Yourself Projects for Guitarists: 35 Useful, Inexpensive Projects That Help You Unlock Your Instrument's Potential*, by Craig Anderton, \$19.95.

The *Stompbox Cookbook: Build Advanced Effects for Electric Guitar & Bass* by Nicholas Boscarelli, \$29.95. The book by Craig Anderton is written for the beginner, while Nicholas Boscarelli's book is for the intermediate hobbyist. However, neither book has the circuits you are asking for, so I went to the Internet and discovered these web sites for understanding and building a reverb unit.

### Theory

Spring reverb explained  
<http://members.tripod.com/~royml/>

Reverb explained  
[www.harmony-central.com/Effects/Articles/Reverb/](http://www.harmony-central.com/Effects/Articles/Reverb/)

### Schematics

Spring reverb schematic  
<http://sound.westhost.com/project34.htm>

Orban 111B spring reverb schematic  
[www.walzingbear.com/~audio/Schematics/Orban111B.htm](http://www.walzingbear.com/~audio/Schematics/Orban111B.htm)

Audio equipment schematics  
[www.walzingbear.com/~audio/Schematics/Schematics.html](http://www.walzingbear.com/~audio/Schematics/Schematics.html)

### Construction Projects

Guitar reverb pedal  
[www.solarorb.com/elect/reverb/](http://www.solarorb.com/elect/reverb/)

Slinky Spring Reverb  
[www.angelfire.com/electronic/ceasants/projects/springs/springs.html](http://www.angelfire.com/electronic/ceasants/projects/springs/springs.html)

### Kits

Craig Anderton's Hot Springs Reverb (with schematic)  
[www.paia.com/hotsprgs.htm](http://www.paia.com/hotsprgs.htm)

Reverb kit from Rainbow Kits  
[www.gatewayclex.com/kits5.htm](http://www.gatewayclex.com/kits5.htm)

### Parts

Reverb springs  
[www.vibroworld.com/parts/tech18.html](http://www.vibroworld.com/parts/tech18.html)  
[www.torresengineering.com/acrevin.html](http://www.torresengineering.com/acrevin.html)  
[www.cyclonemusic.com/reverb.htm](http://www.cyclonemusic.com/reverb.htm)



Unfortunately, I can't find any information or construction projects for the wawa sound. Seems they fell out of favor after the keyboard replaced the guitar wawa pedal. I'd start by checking around for an old Crybaby wawa pedal — try second-hand music stores.

## Music Of The Spheres

I would like to do some experimental music synthesizer work and need your help in finding information and components to match my needs. Specifically, I want to go back in time and look at music created in the diatonic scale again (back in the days of the lap harp) using today's synthesizers or DSP chips. I know the background of this musical scale, and it doesn't match up with the chromatic scale we use today. What I need to know is how can I play with this ancient tuning method using modern-day tools.

Ennis Joseph  
via Internet

Let me lay a little background for our readers here. Before the days of Bach, most music was written for instruments like the harpsichord and flute in the diatonic scale — also known as Pythagorean tuning because of its rigid 2:1 and 3:2 music of the spheres. Check out the following web sites for background material.

**Physics of Music**  
[www.upscale.utoronto.ca/1YearLab/musicexp.pdf](http://www.upscale.utoronto.ca/1YearLab/musicexp.pdf)  
**The Development of Musical Tuning Systems**  
[www.midicode.com/tunings/index.shtml](http://www.midicode.com/tunings/index.shtml)

Unfortunately, this scale often meant frequent retuning of an instrument, so Bach (and others) ushered in a more tempered scale with a linear change between the notes, and some say a mellower sound. This changed the sound of music forever. But now the diatonic notes didn't match up with the new chromatic notes. The problem is that the subtle differences between true diatonic notes and the new chromatic notes are often infinite fractions, like the value of pi. So, therein lies the challenge.

If a piano made today was built around the diatonic scale, the keyboard would be about 40 keys longer — more than 100 keys. Fortunately, there are a handful of keyboards that are programmable enough to accommodate this old scale pattern. Here's a database of synthesizers, samplers, digital pianos, electronic instruments, portable keyboards, sound cards, and software synthesizers with user programmable microtonal scales or tunings.

**Microtonal Synthesis**  
<http://home.att.net/~microtonal/>

But before you dip into your purse for expensive microtonal programmable, there are still a few tricks up the old sleeve (literally). The notes aren't so different that you can't trick a keyboard synthesizer into doing your bidding.

Most synthesizers and sample playback units have a way to set the tuning of each physical key on the keyboard, or of each of the 12 keys per octave, in terms of cents. (There are 100 cents per semi-tone, 1,200 cents per octave). Sometimes it's cents (a penny or two change from the dollar) from the 12-tone per octave equal temperament. With a little interpolation, this fudge factor can be entered fairly easily into almost any modern, digital synth's tuning table — resulting in a whole new musical vocabulary. If you're lucky enough to have a real folk harp or lyre, you can use a synth as a tuning reference to put the strings in some subset of one of these tunings. Here are the details.

**Tunings for the Music of Middle-earth**  
[www.cineternet.net/users/jfinamore/d/tuningsme.html](http://www.cineternet.net/users/jfinamore/d/tuningsme.html)

Well, the ball is now in your court. Here are two other good references that may help you become the new Bach — or Beades — of the 21st century or the 5th.

**Tuning for Beginners**  
[www.cix.co.uk/~gbreed/start.htm](http://www.cix.co.uk/~gbreed/start.htm)

**Illusion of Circular Pitch**  
[www.illusionworks.com/html/auditory.html](http://www.illusionworks.com/html/auditory.html)

## Moog To MIDI

Do you know of a moderate audio sampling synthesizer circuit? Would you publish the schematic or steer me to a reference document? Do you know of any special interest groups that are doing work in this area?

Joseph Ennis  
Valparaiso, FL

This is a very broad question with many answers, depending on what path you take. That's because synthesizers take on many forms — there is no such thing as a generic audio sampling synthesizer. They can be audio, like the original Moog synthesizer (<http://arts.ucsc.edu/ems/music/equipment/synthesizers/analog/moog/Moog.htm#901>); digital, like modern keyboards (SynthZone: [www.synthzone.com](http://www.synthzone.com)); PC-based, like SoundBlaster ([www.soundblaster.com](http://www.soundblaster.com)); or MIDI. As you can see, there is no simple answer or circuit. It depends on what technology you select, and before you can make that decision you need more facts. Here's a good place to start.

**Beginner's synthesizer FAQ**  
<http://citilargo.fl.us/faq/synthfull.html>

Now here are some areas to do further research on the road you take. If you want to build a modern-day Moog, you can find the circuits for a DIY synthesizer at <http://machines.hyperreal.org/categories/do-it-yourself/schematics/>. For answers on MIDI, check out the following.

**Computer Music**  
[www.computer-music.com/articles/art001.htm](http://www.computer-music.com/articles/art001.htm)  
**DownLink**  
[www.downlink.com/proghtml/86/8695.htm](http://www.downlink.com/proghtml/86/8695.htm)

## Superior S-Video

I recently purchased a new A/V receiver with S-Video inputs. This finally allows me to switch all my S-Video sources to my monitor. The only component in my system without an S-Video output is my VCR, which uses composite video. While the receiver handles both S-Video and composite inputs, the receiver switches them separately, which would require two cables to my monitor for seamless operation. The problem is that the monitor can only have one active input — either S-Video or composite. I figure that what I need for the VCR is a composite-to-S-Video converter so the receiver can handle everything, but these units cost over \$100.00. I know the circuitry can't be that complex or expensive. Do you have a circuit available for this task?

Phil Combs  
via Internet

Let me give you a little background on this before I answer, so that you can better understand my answer. All video signals are made up of four components: red video, green video, blue video, and audio. The video has two components: luminance (brightness) and chroma (color). This is generally abbreviated Y/C, where Y stands for brightness and C represents color. To broadcast this much information over a single channel, the luminance and chroma signals are encoded alongside the audio signal. This is a composite video signal, which now goes over the airways.

At the receiving end, these signals are decoded and sorted out. In a TV receiver there's a filter that separates the chroma from the brightness, and places it on an S-Video output, which you can now plug into your video monitor. In your VCR, the Y/C signals have been mixed and are output in composite form. This was quite popular

**DMOS  
&  
JFETS  
&  
MOSFETS  
&  
TRANSISTORS  
@  
LINEAR SYSTEMS**

Second Source Replacements  
for Interfet, Motorola  
National, Siliconix

- Custom Screening
- Die, SMT, Thru-Hole

**LINEAR SYSTEMS**

Full Service S. Manufacturer  
of Specialty Linear Products  
4042 Clipper Court  
Fremont, CA 94538  
(TEL) 510-490-9160  
(FAX) 510-353-0261  
JFETS@LINEARSYSTEMS.COM  
WWW.LINEARSYSTEMS.COM

Circle #38 on the Reader Service Card

## electronic components

**MOUSER  
ELECTRONICS**

(800) 346-6873

ONLINE FEATURES

- Product Search
- Product Catalog
- Product Data Sheets
- Product Pricing
- Product Availability
- Product Specifications
- Product Descriptions
- Product Images
- Product Videos
- Product Audio
- Product Documents
- Product Manuals
- Product Datasheets
- Product Schematics
- Product CAD Files
- Product 3D Models
- Product 2D Drawings
- Product 1D Drawings
- Product 0D Drawings
- Product 9D Drawings
- Product 8D Drawings
- Product 7D Drawings
- Product 6D Drawings
- Product 5D Drawings
- Product 4D Drawings
- Product 3D Drawings
- Product 2D Drawings
- Product 1D Drawings
- Product 0D Drawings

[www.mouser.com](http://www.mouser.com)

**MOUSER  
ELECTRONICS**

A COMPANY


**1-800-346-6873**

Circle #37 on the Reader Service Card 19



on older and/or cheaper VCRs before the S-Video standard became widespread. Of course, you can go under the hood of your VCR and break out the chroma and brightness signals where they go into the RF modulator, but I wouldn't recommend it unless you really know what you're doing. Which leaves us with an S-Video converter option.

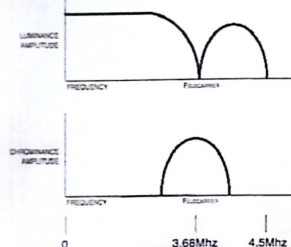The chroma signal is located at 3.68MHz on the video bandwidth, as shown below.




To separate the chroma out, the video must pass through some kind of filtration. This is generally performed by one of two methods. In the first, the chroma is separated from the composite signal using a bandpass filter, and the brightness is separated using a bandstop filter. This can be done using passive components. These converters are inexpensive (about \$40.00 to \$60.00), easily installed, and require no power. (RadioShack sells

them.) The disadvantage of this method is that the filter doesn't have sharp cut-off points, so brightness information that's close to that of the chroma notch is lost.



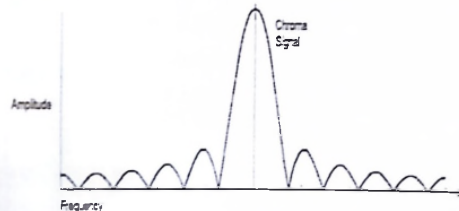sacrificing brightness detail. The technology is based on switched-capacitor technology that provides very steep cut-off points. Unfortunately, comb filter converters are active devices, which are more costly (beginning at about \$130.00) and require a power source. However, the difference in improved image quality is very noticeable and well worth the extra bucks.



So, in answer to your question, it would be hard to build either type. The passive converter would be the easier, but it takes a good design with high tolerance parts. And even after that you need expensive frequency sweep instru-

ments to tune the filters for best picture. The active converter requires a comb filter, generally an IC using switched capacitor technology, that requires several external parts. Again, it needs alignment for best picture, but this time a frequency counter will suffice. And there you have it.


## Newbie Needs Power

I have been an electronics hobbyist for only three months, and I am looking for a dual-polarity, dual-output power supply that can be adjustable from close to one volt to 60 volts, and have a current output anywhere from one amp to 10 amps. I am tired of building a separate power supply and spending more money for every construction project.

I tried everywhere on the web and can't find anything even remotely close to this. If you could help me with a schematic and parts list, I would really appreciate it!

Ryan Weiss  
Wildwood Crest, NJ

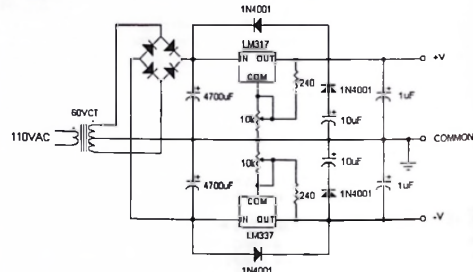Well, 60 volts at 10 amps is quite a stretch, and I doubt many of your experiments will call for that kind of power. Try this circuit.



If you buy the TX-602 (60VCT @ 2A) transformer from All Electronics (800-826-5432; [www.allelectronics.com](http://www.allelectronics.com)), this power supply will deliver a bipolar output of up to 30 volts at 1.5 amps; 60 volts at 1.5 amps if you stack them. I'm sure this will meet most of your needs. Notice that the 10k pots are dual pots; that is, they share a common shaft so that as one voltage changes, the other follows in step.

## Clear The Runway

I'm trying to build a circuit that will flash LEDs in a pattern similar to airplane landing lights. In fact, this circuit is for an R/C airplane powered with a nine-volt battery. What I'm looking for is a timer or oscillator to flash one LED and then a second LED immediately afterwards, pause for 0.5 seconds, and then repeat. I tried using a monostable multivibrator, but didn't have any luck. Any suggestions?

Neil Kaufman  
Silverton, OR

Your problem was trying to match a monostable multivibrator to a task that's beyond its ability. You were right about the circuit needing a

## Build Your Own Intelligent Robot... We Make It Easy!



At Lymotion we cater to the beginner. All of our kits are easy to assemble, requiring only common hand tools in the construction process. The detailed assembly manual includes 2D and 3D exploded view diagrams. The kits can be controlled or programmed in an easy to follow BASIC programming language. The technology is here... the costs are affordable... the support is available... join in and become a robot builder!

Lymotion, Inc.  
300-282-1818  
Fax: 300-282-1294  
sales@lymotion.com  
techsupport@lymotion.com  
Visit our website or ask for our free catalog!

motion

Tel: 300-282-1818

Fax: 300-282-1294

sales@lymotion.com

techsupport@lymotion.com

## 68HC11 & 68HC12 Microcontroller Modules!

Unique design-- just plug them right into your solderless breadboard!

**MicroStamp11™**  
• tiny 1-inch x 1.4-inch 68HC11 module from \$49

**MicroGone-11™**  
• compact 2-inch x 2-inch 68HC11 module from \$68

**Adapt-11™ Family**  
• 68HC11 modules with lots of I/O lines from \$63

**Adapt1812™ Family**  
• based on 68HC12A4 from \$75

**Adapt1912™ Family**  
• choice of B32, D60, D612B from \$99

**MicroBOM12™**  
• lowest-cost BDM pod! only \$79!

Toll-free: 1-877-963-8996

Technological Arts

Via-MasterCard Discover/Amex


Phone: (416) 963-8996

Fax: (416) 963-9179

[www.technologicalarts.com](http://www.technologicalarts.com)



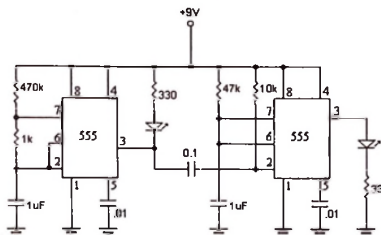multivibrator — but in a slave capacity. This design requires a master timing device to sync the LED flasher sequence you request. Here is your circuit.




The master oscillator is a 555 astable multivibrator, which generates the 0.5-second timing needed to sequence the LEDs. First the left LED flashed which, in turn, triggers the monostable after it flashes pulses to the right LED. The two multivibrators are now reset and wait for the next bang-bang trigger. You can use a 556 — a dual 555 chip — to reduce part count and reduce air-craft weight.

### LM3909 Gone, But Not Forgotten

I am lookin' for an LED flasher that would substitute for the obsolete, hard-to-find LM3909. It would be great if you could design a low-voltage CMOS substitute LED flasher that I could use in hard-to-reach marine markers that would be maintenance free for months.

P.M.  
via Internet

Yes, unfortunately, the next time you'll see one of these versatile oscillator chips will be next to a T. Rex exhibit. Fortunately, I keep an archive of strange circuits that I may need to call on someday, and it looks like that day for the LM3909 substitute is here. I found the circuit below in June 1998 issue of Electronics World (a UK publication). This circuit isn't my design, the creator is Michael Kin, but I've tested it and it works.

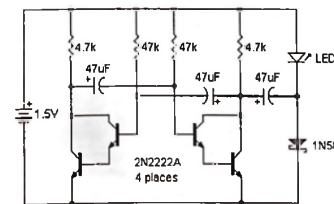

With the values shown, the LED flashes about 15 times a minute; the timing can be changed by altering the value of the feedback capacitors. While this makes a good low-voltage LED flasher, it doesn't have the full span of applications of the LM3909.

### From RS-232 To Fiber And Back

I need to have an RS-232 link between two buildings located approximately 6,000 feet apart (about a mile). The only medium I'm allowed to use is fiber. I need information on building or buying an optical link that can span this distance.

WA4YOG  
via Internet

Here's a short list of suppliers who can fill your needs.

#### B & B Electronics

815-433-5100; [www.bb-elec.com/convert\\_port/fiber\\_optic.asp](http://www.bb-elec.com/convert_port/fiber_optic.asp)

#### JZW Control Systems

+61 2 9975 4011; [www.jzw.com.au/pages1.html](http://www.jzw.com.au/pages1.html)

#### OmniTron Systems Technology

800-675-8410; [www.omnitron-systems.com/catalog/specs/4480view.htm](http://www.omnitron-systems.com/catalog/specs/4480view.htm)

#### Telebyte Fiber Optic Products

800-835-3298; [www.telebyteusa.com/catalog/specs/278.htm](http://www.telebyteusa.com/catalog/specs/278.htm)

#### Versa Technology

909-591-8891; [www.versatek.com/products/vlm-500.html](http://www.versatek.com/products/vlm-500.html)

#### Versitron

800-537-2296; [www.versitron.com/RS232.HTML](http://www.versitron.com/RS232.HTML)

### Reader's Hint

I came across a possibly unknown fact that may be of use to your readers. I was trying to hack together an infrared motion detector with a wireless module to make a battery-powered (portable) motion switch to trigger a camera for wildlife photography. By accident, I discovered that an X10 MS13A wireless motion detector transmits on the same frequency — and with the same code — as a RadioShack wireless door chime, Model #63-874A. (This is the model with the single remote button, not the dual buttons.) Having discovered that, it was a simple matter of wiring the chime actuator to the camera trigger. The code on the RadioShack receiver should be set to A, as it does not appear to work on codes B or C. The MS13A can be purchased separately or in the FireCracker interface kit.

Warren Shedrick  
via Internet

### MAILBAG

Dear TJ:

I was waiting for the errors to be corrected in later issues, but they were not. In the April 2001 issue, you told Jim Zink to tie all unused inputs to ground. This is poor advice. For TTL inputs, each input will draw between 400 uA and 1.6 mA of wasted current when tied low (TTL inputs will stay at a marginal one if left open). Most designers advise tying them high through a 2.2k or 3.3k resistor. Some designers have said to tie extra inputs together, like the fourth input of a four input gate to the third input, but this is bad practice, as well (power and speed). CMOS can be tied either way. For analog devices, it pays to read the data sheet.

In summary, the best advice is to read the data sheet. In most cases it pays to tie inputs someplace for noise reasons. But you can cause functional and power problems if you are not careful.

Steve McChrystal  
Santa Clara, CA

## New Retail Store

980 S First Street San Jose, CA 95110

PHONE: 408 275-8711 FAX: 408 275 0688

<p><b>9 VDC 500 mA WALLWART</b> Center negative coaxial connector. 96E008 \$4.95 each</p>	<p><b>"FLUKE" TYPE METER PROBE KIT</b> Shrouded type banana plugs fit Fluke and other popular DMMs. 97Z017 \$4.95 set</p>	<p><b>DONUT MAGNET</b> 750 Gauss, 2 1/4" OD, 1 1/4" ID, 1/2" thick. 99N005 \$4.95</p>
<p><b>OPEN FRAME POWER SUPPLY</b> 15VDC or ±12VDC @ 5A. Power One HDD15-5-A, unused in factory box with full documentation. 20E009 \$24.95 each</p>	<p><b>115VAC MUFFIN FAN</b> Input 50Hz @ 0.20A or 60Hz @ 0.18A. Size 4.675" square x 1.5". 21F001 \$7.95 each</p>	<p><b>RECYCLED DISKETTES!</b> 1.44MB, 3.5", bulk erased. From unsold software. 95C017 100 for \$9.95</p>
<p><b>24V DIAPHRAGM AIR PUMP</b> 24VDC @ 400mA (max.). Free air 0.3 CFM. Max. pressure approx. 11 lbs. Max. vacuum approx. 20" Hg. Dimensions 4"W x 4 1/2"L x 3 1/2". 99U002 \$19.95 each</p>	<p><b>53W 12V SOLAR PANEL MODULE</b> Peaks: 53 Watts; 17.2 Volts; 3.08 Amps. 36.8"L x 19.8"W x 0.9"D. 20E002 \$359.00 each</p>	

**alltronics.com**



Mail Orders: PO BOX 730 - Morgan Hill, CA 95038-0730

Phone: (408) 847-0033 Fax: (408) 847-0133

Download our Catalog: <http://www.alltronics.com>

Dealers welcome by appointment. Visa, M/C, AmEx Accepted. All Sales Final. California Residents Add Sales Tax. Shipping Additional on All Orders. Prices Good 60 Days from Date of Publication and Subject to Change Without Notice.







# MIDI-MAN

MANUAL PULSE PROCESSOR



FIGURE 1: MIDI-MAN Rack Cabinet Design Layout

# MIDI-MAN

by Terence Thomas

The advent of MIDI (Musical Instrument Digital Interface) has brought about a revolution in the music industry. The market is constantly being bombarded with new MIDI units all the time and these devices are incredibly sophisticated and have put a measure of control in the hands of the musician that is unprecedented. Even home studios can produce remarkably sophisticated recordings.

Despite this, manufacturers have ignored some aspects of the studio recording experience that are extremely important to the musician. If it is important to you to expand the capabilities of your home studio, then this project is for you.

## MIDI-MAN

The purpose for MIDI-MAN is to provide an interface to enable the use of analog sources. So many musical instruments are not digital that some kind of interface is required, if you are to enlist the services of very important non-digital instruments. Since manufacturers do not provide such interfaces, it becomes necessary to take charge of your own destiny. This project can be the first step in your musical independence. The MIDI-MAN enables the performer to choose the best method for triggering a given sound or effect.

## KEYBOARD

Some voices do not lend themselves to keyboard play; percussion instruments, for example. Drum rolls are both difficult to perform and rough on keyboard mechanisms.

With the MIDI-MAN in multiple mode, you just press a key and it will produce multiple hits. This is accomplished by the use of feedback from MIDI-MAN back to the rhythm generator in your synthesizer. The speed of the hits is determined by the number of keys you press. In fact, it is the reciprocal of the number of keys pressed, which is to say that, two keys divide the speed by two, three keys divide the

speed by three, and four divide it by four, etc., etc. Drum rolls are best simulated by two keys.

## ARPEGGIOS


If pitched voices are used and more than one key is pressed, arpeggios are achieved and no matter how many keys are pressed, they will all sound. An arpeggio chart can be seen in Figure 3. Many special effects can be achieved with this technique, for example, dissonant clusters, octave modulations, and new timbre, and special effects sound generation.

## TOUCH PLATE

A touch plate can be used with the keyboard to expand a player's capabilities. First, a percussion voice is selected and a key is pressed. The note will sound just once. However, if you press the touch plate while holding down keys, a perfect percussion roll will be performed. Weights placed on keys or rods used to hold down keys
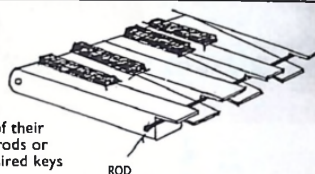
## FIGURE 2: Keyboard — Hold Down Rods

Almost all synthesizers have tabs at the front of their keys, so you can place rods or dowels to keep the desired keys pressed.



will free one hand for other duties while the touch plate controls play. Drummers will be interested in this


method of play to enhance and accompany other percussion voices. Figure 2 shows how the rods are utilized.

- R1 - 270 ohms
- R2 - 100K
- R3 - 68K
- R4 - 15K
- R5 - 1Meg Pot
- R6 - 100K
- R7 - 330K
- R8 - 270 ohms
- R9 - 270 ohms
- R10 - 220 ohms
- R11 - 3K3
- C1 - .1 MFD
- C2 - .01 MFD
- C3 - 3.300 MFD
- Q1 - NPN Transistor 2N2222
- Q2 - NPN Transistor 2N2222
- Q3 - 5-volt regulator LM340T5
- D1 - 1N914
- D2 - 1N914
- D3 - Yellow LED
- IC1 - 4N35 Optoisolator
- IC2 - 555 Timer
- S1 - DPDT Toggle Switch
- J1 - DIN Jack
- J2 - DIN Jack
- J3 - DIN Jack
- J4 - Phone Jack

## Parts List

Aluminum angle pieces for the rack cabinet. Control knob. 12-volt wall transformer. power supply, wire, terminal strips, circuit boards, etchant solution, 12 machine screws and bolts.

## THERMOCOUPLE WELDER

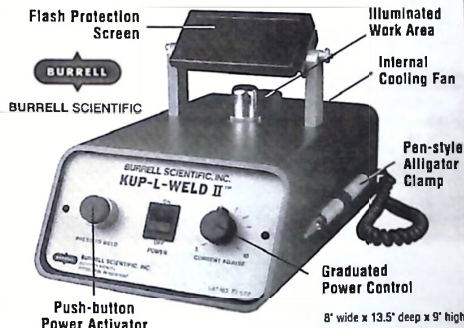









The Burrell KUP-L-WELD<sup>®</sup> II Thermocouple Welder produces superior weld contacts that ensure precise temperature monitoring. Burrell Scientific took advantage of today's advanced technology to improve the entire welding process. It is capable of welding a variety of wires.

The KUP-L-WELD<sup>®</sup> II is easily transported to various work areas. Its metal case is finished with an abrasion- and coating-resistant paint. It is maintenance-free except for the periodic replacement of carbon.

Under \$1,000.00 plus shipping and handling. Delivered ready for operation. VISA/MasterCard and American Express accepted.

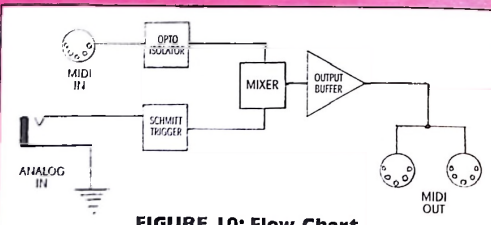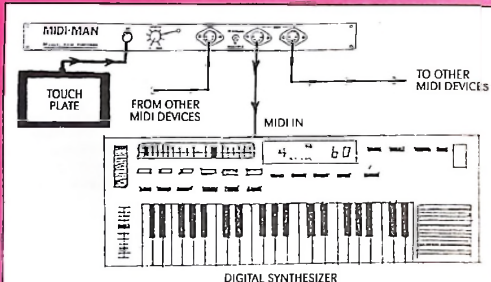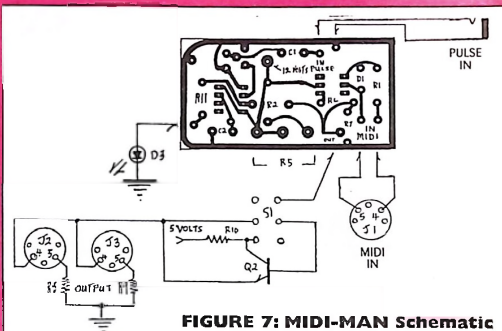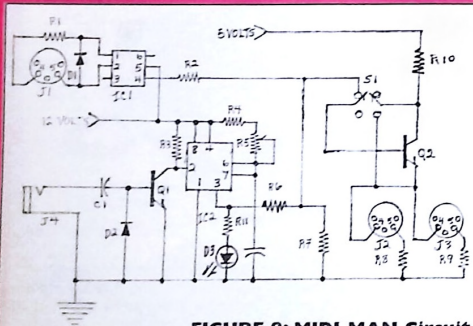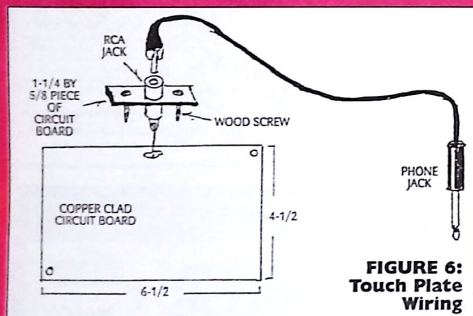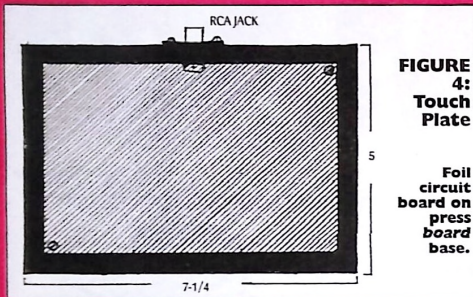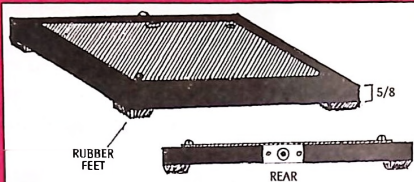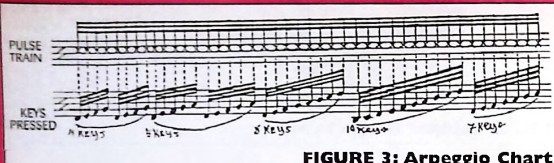For literature: call 1-800-637-6074. For technical information call: 1-412-471-2527 or contact Burrell Scientific at E-mail: [burrellsci2@aol.com](mailto:burrellsci2@aol.com) or visit our web site at: [www.burrellsci.com](http://www.burrellsci.com)





The prototype was built on a 7-1/4 inch by 5-inch piece of press board, as shown in Figures 4 and 5. A 4-1/2 inch by 6-1/2 inch copper clad circuit board is used as the touch plate and is connected to an RCA type jack which is secured to the back of the press board with a small piece of circuit

board that is both glued and fastened with wood screws (Figure 6).


Drum mikes and other electrical devices that are attached to percussion instruments can also trigger the MIDI-

MAN. Pulse generators from analog synthesizers, sequencers, microphones, foot-pedal switches, light-sensitive devices, and samplers are just a few of the devices that can be used as triggering sources.

Other MIDI units can be mixed with analog devices to produce a com-


posite triggering signal for complex rhythm coordination. Nothing is better at coordinating, synchronizing, and mixing analog and digital signals than the MIDI-MAN, and the only limit to the input possibilities is your imagination. Two outputs can feed two MIDI units for even more possibilities. To assure



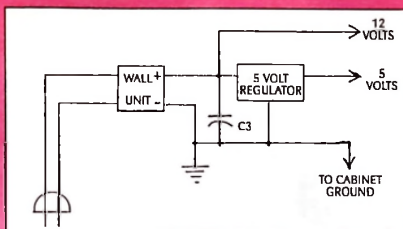

**FIGURE 16: Power Supply**

**FIGURE 17: Rack Cabinet Construction**

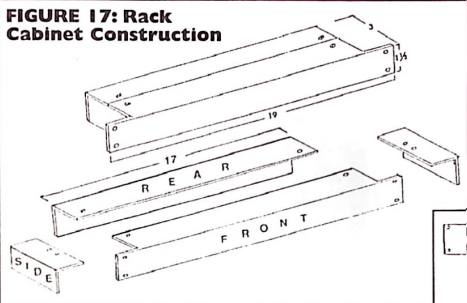

that you get the maximum out of this unit, you should experiment and then experiment more. After three years of using the MIDI-MAN, I have just scratched the surface.

## CONSTRUCTION

The circuit in Figure 8 shows a simple, straightforward design and a foil pattern is shown in Figure 7. Input jack J4 accepts any pulse source from a fraction of a volt to 15 volts. Capacitor C1 decouples the input, while diode D2 prevents negative pulse triggering.

Transistor Q1 provides the negative pulse required for IC2, a 555 timer. Potentiometer R5 is connected directly to the circuit board and provides support and allows you to extend the pulse output to enable a single pulse to produce a number of pre-set pulses.

Output pulses are taken from pin 3 of IC2 and fed to transistor Q2 through resistor R6 and switch S1. This transistor serves as a buffer between the 12-volt operating voltage and the required 5-volt output voltage. Optoisolator IC1 accepts a MIDI signal from DIN jack J1 through resistor R1. The output of IC1 is taken from pin 4 through resistor R2 and mixed with the output of IC2, at switch S2. Resistor R7 serves as a reverse-biasing reference. A 3K3 resistor feeds a yellow analog signal monitoring LED, D3 in the prototype.

Transistor Q2 is mounted on switch S1 and provides the output signal to DIN jacks J2 and J3, through resistors R10, R8, and R9, when the switch is in the manual position. When switch S1 is in the multiple position, transistor Q2 is bypassed and the key-

board alone produces multiple hits when a key is pressed.


Power is supplied by a 12-volt wall unit with a 5-volt regulator and a patching chart, as well as a flow chart which can be seen in Figures 9 and 10, respectively.

## PROFESSIONAL QUALITY


Since most of the professional studio devices come in 19-inch rack cabinets, any unit you are going to build should be in a compatible 19-inch cabinet, as shown in Figure 17.

A practical rack cabinet can be constructed inexpensively from aluminum angle molding, which can be purchased at any hardware store. Although the aluminum is thick enough — 1/8 inch — to provide a sturdy cabinet, it can be easily cut with a hack saw and drill press.


Since the cabinet is only three inches deep, it will not interfere with ventilation holes of other cabinets and does not require much ventilation itself. There is no need to include a bottom to the cabinet so you must make sure

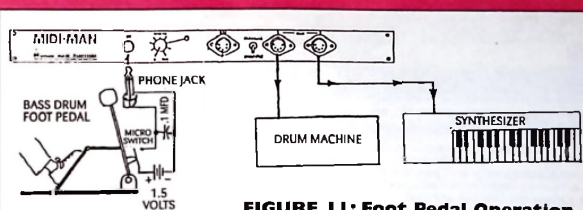


**FIGURE 11: Foot Pedal Operation**

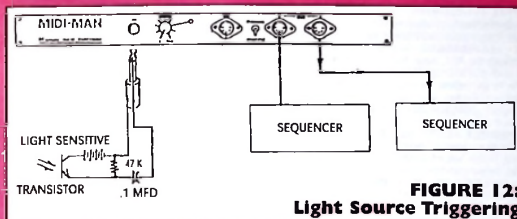


**FIGURE 12: Light Source Triggering**

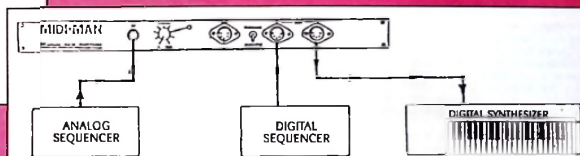

**FIGURE 13: Analog Sequencer Patch**

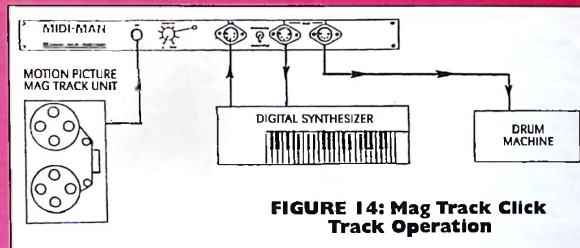

**FIGURE 14: Mag Track Click Track Operation**

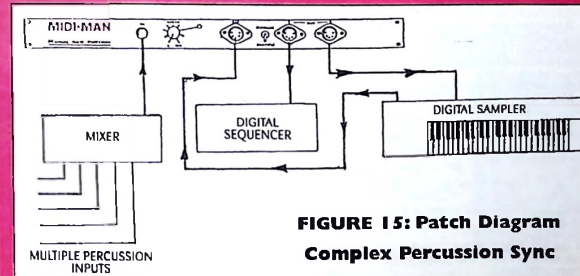

**FIGURE 15: Patch Diagram Complex Percussion Sync**

that circuit boards are insulated from cabinets mounted below ... electrical tape can serve this purpose. With

proper painting and lettering, your project will look great next to the commercial units. **NV**



The Events Calendar is a free service for publicizing electronic events such as amateur radio hamfests, flea markets, etc. If your organization is sponsoring an event and would like a free listing, contact us at least 60 days in advance. Include your flyer, estimated attendance, name of the person to contact, and phone number.

Complimentary issues are available upon request for distribution to your attendees. A street address for UPS is required.

While we strive for accuracy in our calendar, we can not be responsible for errors or omissions. The information contained in this column is for the use of the readers of *Nuts & Volts* and may not be republished in any form without the written permission of T & L Publications, Inc.



# Events CALENDAR

**Delaware Valley RA, Glenn Costello**  
**NZRFM, 609-882-2240.** Email:  
 abbot0903@aol.com Web:  
 http://www.silac.com/W2q  
**OH - BEKA - Hamfest, Cuyahoga County**  
 Fairgrounds, Eastland Road Entrance,  
 8am-2pm. VE exams. Talkin: 146-73-  
 110.9. Hamfest Association of Cleveland,  
 Ed Santavika AARTV, 800-253-3378.  
 Email: info@oharc.org Web:  
 http://www.oharc.org

## September 28-29

**TN - SEVIERVILLE - Hamfest, Ten-Tec,**  
 Stan Brock W0DBGS, 865-453-7172.  
 Email: sales@ten-tec.com  
 Web: http://www.ten-tec.com

## September 29

**AL - DOTHAN - Hamfest, Wiregrass ARC,**  
 Karl Davis K0AEKX, 334-677-7485  
**AZ - KINGMAN - Hamfest, Huialapal ARC,**  
 Bill Beaman K0LVS, 520-753-2293  
**FL - ORMOND BEACH - Hamfest, Daytona**  
 Beach ARC, John Munsey KB9KQ, 907-677-  
 8179. Email: munsey@mindspring.com  
 Web: http://dbara.org  
**MS - STARKVILLE - Hamfest, ARRL MS**  
 Section, Malcolm Keown VY5XK, 601-634-  
 2232. Web: 601-634-0822 home. Email:  
 v5xk@arll.org  
**NY - HORSEHEADS - Hamfest, Chemung**  
 County Fairgrounds, 8am-3pm. FCC exams.  
 Talkin: 146-79-444.20. ARA of the  
 Southern Tier, Randy Vele N2JST, 607-  
 625-8593 (days) or 607-738-6857 (even).  
 Email: n2jst@ararst.org  
 Web: http://www.ararst.org

## September 30

**IA - WEST LIBERTY - Hamfest, Muscatine**  
 & Iowa City ARCS, Mike Hayden KB0TTF,  
 319-262-8790. Email: kb0ttf@arll.net Web:  
 http://www.qsl.net/kb0ttf/hamfest.html  
**MD - WYOMIE - Hamfest, Prince Georges**  
 Stadium, VE exams. Talkin: 147-105-  
 146.520 simplex. FAR, Dan Blasberg  
 KA8VPP, 301-345-7381. Email:  
 dblasberg@earthlink.net  
**NY - YONKERS - Flea Market, Lincoln High**  
 School, Kneeland Ave. 9am-3pm. VE  
 Exams. Talkin: 440-425 PL 156.7, 227.60  
 PL 146.910. 9am-12pm. Metro  
 70cm Network, Otto Supliksi W2SLQJ,  
 914-969-1053. Email: w2slqj@juno.com  
 Web: http://www.metro70cm  
 network.com  
**WA - CHEHALIS - Hamfest, Chehalis Valley**  
 ARS, Bill Hartwell KQ7QH, 360-748-8066.  
 Email: kq7qh@cwars.net Web:  
 http://www.cwars.net

## OCTOBER 2001

### October 5-6

**NH - HOPKINTON - Hamfest, HOSSTRADERS,**  
 Joe Demaso K1RQG, 207-  
 469-3492. Email: k1rQG@aol.com Web:  
 http://www.qsl.net/k1rQG

### October 6

**FL - JACKSONVILLE - Hamfest, FL**  
 Community College, North Campus, 4501  
 Community Rd. 6:30-3pm. Crown Amateur  
 Radio Convention Committee, Billy  
 Williams NU4F, 904-765-3230. Email:  
 n4uf@nflars.org or Willis Layfield KD4UJX,  
 904-765-1104. Email: willis@kd4ujx.com  
 Web: http://www.nflars.org/hamfest.htm  
**KS - HOLTON - Hamfest, Archdison County**  
 ARC, Joel Breakstone K1CQ, 785-945-3763.  
 Email: joel@kd4ord.org  
**MI - HAKENSALE COUNTY - Hamfest, Bergen**  
 Area, James Joyce K2CZ, 201-664-6275.  
 Email: joyce@cybernet.net Web:  
 http://www.bara.org  
**NY - POMPEY HILLS - Hamfest, Radio**  
 Amateurs of Great Syracuse, 315-698-  
 4558. Email: rags@nol.com  
**Web: http://www.pages2net/rngs**  
**CA - LANCASTER COUNTY - Tallgate Fest,**  
 Red Rose Repeater Assn., Dave Phillips  
 W3CWE, 717-872-6578.  
 Email: jdd@prodigy.net  
**Web: http://www.73.org/73rrrrr/**  
**SC - ROCK HILL - Hamfest, York County**  
 ARS, Sheila Parlin K4GCF, 803-328-5980.  
 Email: cyparlin@earthlink.net  
**VA - ROCKY HILL - Hamfest, Bell County Expo**  
 Center, VE testing. Talkin: 146-820- PL 23.  
 Temple ARC, Mike Lefan W4SEQJ, 254-  
 773-3590. Email: hamexp@tarc.org Web:  
 http://www.tarc.org

### October 7

**CT - WALLINGFORD - Hamfest,**  
 Mountaintops Special Event Facility, High  
 Hill Rd., Exit 15, Rt. 91, 9am-3pm. Talkin:  
 147-36. Meriden ARC, Inc.  
 Email: nutmeghamfest@qsl.net  
**Web: www.qsl.net/nutmeghamfest**  
**IL - BEARDSTOWN - Swapmeet, UFWU**  
 Union Hall, Arenzville Rd. 8am-5pm.  
 Talkin: 146-715. The Valley ARC, Tim  
 Childers, 217-245-2661. Email:  
 kb9lq@earthlink.net  
**IL - DECATUR - Decatur Old Fashioned**  
 Hamfest, Jerry Sebok N9RQ, 217-423-  
 2025. Email: jsebok@earthlink.net  
**IN - BEDFORD - Hamfest, Lawrence**  
 County 4th Fairgrounds. FCC testing. Talkin:  
 145-310. Hoosier Hills Ham Club, Jerome  
 Kuchta K4HJ, 812-427-9535. Email:  
 n9lyab@bluewin.net Web:  
 http://www.hoosierhillsamfest.org  
**OH - MEDINA - Hamfest, National Guard**  
 Armory, 920 W. Lafayette Rd. 8am-3pm.  
 VE testing. Talkin: 147-030. Medina Two  
 Meter Group, Mike Rubaszewski N8TZY,  
 330-273-1519. Email: n8tzy@3net.net  
 Web: http://www.qsl.net/m2m

### October 10

**FL - ORLANDO - Hamfest, The Bahia**  
 Shrine, 2300 Pembroke Rd. 8am-2pm.  
 Talkin: 147-390. Larry K4GACN 407-648-  
 8489. Email: king4con@netzone.net. Alan  
 Kuchta K4HJ, 812-427-9535. Email:  
 kb9lq@earthlink.net  
**FL - K4HJ 812-427-9535. Email:**  
 kb9lq@earthlink.net

### October 12-13

**FL - WALDO - Hamfest, The Trading Post**  
 Restaurant. Fri: 2-6pm, Sat: 8am-2pm.  
 Talkin: 145-150. Tony 904-664-9328.  
 Email: hamfest@arll.net. John, email:  
 hamfest@k4uay.net Web:  
 www.angelfire.com/fl/rarba/hamfest.html  
 tlyr

### October 13

**FL - PLANTATION - Cy Harris W4MAQ**  
 Memorial Free Flea Market, 8000 W.  
 Sunset Blvd., Northeast parking lot.  
 Talkin: 146-79-444.20. Robin Terrell N4HHP,  
 954-583-3625. Email:  
 kg4chcw@arll.net Web:  
 www.geocities.com/bceen/freeflea.html  
**IL - STARK - Hamfest, ARC Bradford**  
 Area, John Bradley KU4AY, 904-782-1185.  
 Email: hamfest@ku4ay.net Web:  
 http://ku4ay.net/starkhamfest.html  
**FL - TAMPA - Hamfest, Egypt Shrine**  
 Temple, Keith Dean KA4JLV, 813-879-  
 2449. Email: kwdaen@cs.net  
**CA - AUGUSTA - Hamfest, Evans Middle**  
 School, 9am-3pm. VE testing. Talkin:  
 145-490. ARC of Augusta, Henry  
 Arosteguy KN4W, 706-793-1625. Email:  
 kn4w@earthlink.net or  
 huy K4CZY, 706-634-9504. Email:  
 kg4yle@earthlink.net  
**MI - HONOLULU - State Convention,**  
 Koolau ARC, Walt Niemczura AH6QZ, 808-  
 263-3872. Email: ah6qz@arll.net Web:  
 http://www.chem.hawaii.edu/kar/rl  
**IL - SALEM - Hamfest, Centralia Wireless**  
 Assn., Darryl King AA9EX, 618-532-6666.  
 Email: bking@arll.net  
**NY - LAKE PLACID - Hamfest, Northern**  
 New York ARC, Chuck Orem KD2AJ, 518-  
 563-6851. Email: kd2aj@arll.net Web:  
 http://www.getulies.com/nnyra  
**TN - OAK RIDGE - Hamfest, Fraternal**  
 Order of Eagles Bldg., 1650 Oak Ridge  
 Turnpike, 9am-3pm. VE exams. Talkin:  
 146-88. OAC, Rickson KB9LZP,  
 K4PZT, Email: d.bower@lee.org  
**VA - STAFFORD - Hamfest, Stafford Area,**  
 Rick Diddams KF4UTH, 540-657-8322.  
 Email: riddams@earthlink.net Web:  
 http://www.n4nw.org/Hamfest.htm  
**WA - BREMERTON - Hamfest, North**  
 Kitsap ARC, Susan Johnson AB7MD, 360-  
 697-9379. Email: karc@juno.com Web:  
 www.silverlink.net/nkar/hamfest.html

### October 14

**IL - OAKBROOK TERRACE - Hamfest,**  
 Entrance at Park View Rd., north from  
 Cermack Rd. 8am-1pm. CARC, Melissa  
 Menesky KB9QWZ, 773-384-7514 or Dean  
 NB9Z, 708-331-7764.  
 Email: carc\_inc@hotmail.com  
**Web: http://www.chicagocar.org**  
**IN - GREENFIELD - Swapmeet, Riley Park,**  
 7:30am-2pm. IN National Radio Society,  
 Glenn Fitch, 765-565-6911. Email:  
 glenn.fitch@cnz.com  
**MI - DIMONDIALE - Hamfest, The Summit,**  
 400 Davis Hwy. 8am-2pm. VE testing.  
 Talkin: 145-390. or 146-530 simplex.  
 Central MI ARC & Lansing Field Defense

Repeater Assn. J. Ervin Bates W8ERV, 517-  
 676-2710. Email: w8erv@arll.net Web:  
 http://www.qsl.net/cdr/hamfai.org.html  
**OH - ASHLAND - Hamfest, Ashland**  
 Area ARC, John McMurray KC8AAR,  
 419-283-3117. Email:  
 johnmcmurray@myxcel.com  
**PA - WRIGHTSTOWN - Hamarama 2001.**  
 MC. Arly VHF Radio Club (Packrats), Joe  
 Keer W3KJ, 215-256-1464.  
 Email: packrats\_w3cs@yahoo.com  
 Web: http://www.ij.net/packrats

### October 19-20-21

**CA - CONCORD - Convention, Sheraton**  
 Hotel, Mt. Diablo ARC Web:  
 www.pacificcon.org

### October 20

**CO - GOLDEN - Hamfest, Jefferson County**  
 Fairgrounds, 15200 W. 4th Ave. 8am-2pm.  
 VE testing. Talkin: 144-627145.22. Rocky  
 Mountain Radio League, Inc., Ron Rose  
 N0MOJ, 303-985-8602. Email:  
 rnm@arll.net Web:  
 http://mrml.hamradio.com  
**LA - LAKE CHARLES - Hamfest, Blakenship**  
 W8SND, 337-478-7566. Email:  
 w8snd@yahoo.com  
**OR - RICKERLAKE - Hamfest, Mid-Valley**  
 ARS, Bud Smith W7BUD, 503-838-0266.  
 Email: n7budd@arll.net Web:  
 www.teleport.com/~blinder/swap.html  
**TX - DENTON - Hamfest, Denton County**  
 Arc, Clint Miller KD5BY, 940-390-5338.  
 Email: cmiller@dentonhamfest.org Web:  
 http://dentonhamfest.org  
**TX - HOUSTON - Hamfest, Clear Lake ARC,**  
 John Taylor KD5HO, 713-504-1403. Email:  
 kd5ho@swbell.net Web: www.clarc.org

### October 20-21

**CA - ROME - Hamfest, Northwest GA ARC,**  
 Ed Bore WB5FDM, 760-335-2048. Email:  
 bged5341@aol.com Web:  
 www.wavegate.com/~chall/home.html

### October 21

**MA - CAMBRIDGE - Hamfest, MIT Radio**  
 Society/Harvard Wireless Club/MT UHF  
 Repeater Assn., Steve Finberg W1GSL,  
 email: wslgsl@mit.edu (Nick Altmanberg  
 KA1MOX, 617-253-3776 9am-5pm). Web:  
 http://www.mit.edu/w1mx/www/swapfest  
 .html  
**MI - ALAMAZOZO - Hamfest, Kalamazoo**  
 County Fairgrounds. Talkin: 147-040.  
 Kalamazoo ARC & SW MI Amateur Radio  
 Team, Charlie Burghart KB8BL0, Email:  
 charlie@arll.net Web:  
 http://www.qsl.net/kbbl0/hamfest.htm  
**MI - WARREN - Hamfest, Utica Shelby**  
 Emergency Communication Assn.,  
 Delphine Wrona KC8JSH, 810-791-4669.  
 Email: wrona@uticashelby.net Web:  
 http://www.useca.org  
**NY - QUEENS - Hamfest, Hall of Science**  
 parking lot, Flushing Meadow Corona Park,  
 47-47 11th St. VE exams. Talkin: 444-200  
 repeat, PL 1345, 146.52 simplex. Hal of

## SUMMER SPECIALS!

**PACKS & Chargers for YAESU FT-50R / 40R / 10R:**

FNB-403 (40R)	9.2v	650mAh	\$41.95
FNB-474 (40R)	9.2v	1000mAh	\$49.95
FNB-412 (40R)	9.2v	1000mAh	\$49.95

**For YAESU FT-50R / 40R / 10R:**

FNB-30 (40R)	9.2v	650mAh	\$39.95
For YAESU FT-50R / 40R / 10R / 76:			
FNB-26 (40R)	12.0v	1500mAh	\$42.95
FNB-0275 (40R)	12.0v	1000mAh	\$35.95

**For YAESU FT-411 / 407 / 73 / 33 / 21:**

FNB-11 (40R)	12.0v	650mAh	\$24.95
FNB-01 (40R)	12.0v	1000mAh	\$34.95

**For ALICINO D500 / 582 / 180 radios:**

EDP-2015 pack	7.2v	1500mAh	\$19.95
EBP-221h (50R)	12.0v	1000mAh	\$36.95
EEH-11	8.0v	AA case	\$14.95

**For ICOM IC-21A / 122-42A / 1931-32A / 17A:**

BP-150 (1A)	7.2v	1000mAh	\$49.95
BP-173 (1A)	9.6v	700mAh	\$39.95
BP-1C2 (1A)	12.0v	1600mAh	\$49.95

**THE BEST BATTERIES IN AMERICA!**

**For ICOM IC-25AT / W2A / 35AT / 45AT etc:**

BP-83 pack	7.2v	600mAh	\$23.95
------------	------	--------	---------

**For ICOM 02AT etc & Radio Shack HTV 202 / 404:**

BP-81h pack	8.4v	1400mAh	\$32.95
-------------	------	---------	---------

**BP-202 (40R) etc:**

BP-202 (40R) etc	7.2v	1400mAh	\$29.95
------------------	------	---------	---------

**For IC-N2000 / TH-79A / 42A / 22A:**

BP-31h pack	6.0v	1000mAh	\$29.95
-------------	------	---------	---------

**BP-34h (40R) etc:**

BP-34h (40R) etc	9.6v	1000mAh	\$39.95
------------------	------	---------	---------

**For KENWOOD TH-78 / 48 / 78 / 27:**

BP-13 (40R)	7.2v	700mAh	\$26.95
-------------	------	--------	---------

**For KENWOOD TH-77 / 75 / 55 / 46 / 26 / 25:**

BP-13 (40R)	7.2v	700mAh	\$26.95
-------------	------	--------	---------

Mt. phone & Aircel vellers welcome! Payroll  
 Mastercard / Visa / Discover / American Express  
**Call 608-831-3443 / Fax 608-831-1082**  
 Mr. NiCd - E. J. Yu & Company  
 2211-D Pawnee Road, Middleton, WI 53562  
**CALL OR WRITE FOR OUR FREE CATALOG!**  
 Cellular / Laptop / Vocoder / Commercial & Amateur packs too!  
 E-mail: ehrgst@midplains.net

## SATELLITE TV - HACKERS BIBLE!

### The SECRETS are REVEALED!

Scrambling Systems

- The principles of security
- Descrambler building blocks
- Smart cards, information wars & stupid mistakes
- Cracking codes (includes DirecTV source code)
- Installing and hooking up descramblers
- Video manipulative systems...and much more...

**www.baylink.com**  
**or... call 800-483-2423**

**ORDER BY Internet or Send \$66 plus \$5 s/h to:**  
 Baylink Publications, 1905 Mariposa, Boulder, CO 80302  
 MASTER, VISA & AMEX IC orders accepted

**576 pages, 6 x 8-1/2**  
**NEW! 5th Edition**  
 Telephone: 303-449-4551  
 FAX: 303-438-8720

**FREE CATALOG - Satellite TV books, videos and software**



# Event CALENDAR

**Science ARC, Inc.** Steve Greenbaum  
W2KXZ, 718-898-5559 eves only. Email:  
W2KXZ@earthlink.net  
**PA - KILLBUCKVILLE - Hamfest.** Sellersville  
Fire House, Rt. 152. VE testing. Talkin:  
145.31. RF Hill ARC. Linda Erdman KA3J2,  
215-478-5764. Email: rhlilarc@yahoo.com  
Web: <http://www.rhlilarc.org>

## October 26-27

**OK - KINGSTON - Texoma Hamarama**  
Assn. Len Carlson K4WVL, 972-519-0521.  
Email: k4wvl@earthlink.net  
Web: <http://www.angelfire.com/vx5/T/exomahamarama/>

## October 27

**CANADA - QUEBEC - LONGUEUIL -**  
Hamfest, Montreal South ARC, Micheline  
Simard VE2XW, 514-446-0477. Email:  
ve2xw@amsat.org  
**CT - WATERFORD - Auction.** Senior  
Citizens Center, Waterford Municipal  
Complex, Rt. 85. Talkin: 146.97 PL 153.7.  
Tri-City ARC, Barry DeGross, 860-443-  
7799. Email: DDeGross@aol.com  
**FL - JACKSONVILLE - Hamfest.** Morocco  
Society, 3800 S.W. 30th St. Johnnie Bull  
Rd. Sat. 8am-4pm. VE exams & upgrades.  
Talkin: 146.78, backup 146.88. Greater  
Jacksonville Hamfest Assn., Richard  
Smythe K4PFL, 904-739-9713. Email:  
rmysythe2-bellouth.net Web: [www.jacksonville.net/~richj/AXHAMFEST.html](http://www.jacksonville.net/~richj/AXHAMFEST.html)

**MM - ST. PAUL - Hamfest.** RiverCenter  
8am-4pm. VE exams. Twyn Gies PH Club,  
Amanda Roberts K6DPA, 612-535-0637 or  
651-460-0050. Email: k6dpa@pdlink.com  
Web: <http://www.hamfestmm.org>  
**MO - ST. LOUIS - Hamfest.** Kirkwood  
Community Center, 111 N. Geyer Rd.  
7:30am-1pm. VE exams. Talkin: 146.31-  
V. St. Louis ARC & Gateway to Ham  
Radio Club, Steve Welton W6SWZ, 314-  
631-0159. Email: [stlsw@earthlink.net](mailto:stlsw@earthlink.net)  
Web: <http://www.hallwiltonhamfest.org>  
**NM - ROCHESTER - Hamfest.** Socorro ARC,  
NM Tech ARA, & City of Socorro, Al Braun  
K6JY, 505-835-3370. Email:  
a6braun@juno.com

**NY - WESTMONT - Hamfest.** Carroll  
County Agricultural Center, VE session.  
Talkin: 145.41. Carroll County ARC, Inc.,  
email: k3pzn@earthlink.net. web:  
<http://www.qsl.net/k3pzn>

## October 28

**IA - DES MOINES - Hamfest.** Tikva Tracers  
ARC & Iowa Assn. of AR Club, Rod Ivers  
K6BWW, 515-274-4945 or 515-276-0509.  
Email: k6bww@earthlink.net  
**MD - WESTMINSTER - Hamfest.** Carroll  
County Agricultural Center, VE session.  
Talkin: 145.41. Carroll County ARC, Inc.,  
email: k3pzn@earthlink.net. web:  
<http://www.qsl.net/k3pzn>

**OK - KINGSTON - Texoma Hamarama**  
Assn. Len Carlson K4WVL, 972-519-0521.  
Email: k4wvl@earthlink.net  
Web: <http://www.angelfire.com/vx5/T/exomahamarama/>

**OK - KINGSTON - Texoma Hamarama**  
Assn. Len Carlson K4WVL, 972-519-0521.  
Email: k4wvl@earthlink.net  
Web: <http://www.angelfire.com/vx5/T/exomahamarama/>

**OK - KINGSTON - Texoma Hamarama**  
Assn. Len Carlson K4WVL, 972-519-0521.  
Email: k4wvl@earthlink.net  
Web: <http://www.angelfire.com/vx5/T/exomahamarama/>

**OK - KINGSTON - Texoma Hamarama**  
Assn. Len Carlson K4WVL, 972-519-0521.  
Email: k4wvl@earthlink.net  
Web: <http://www.angelfire.com/vx5/T/exomahamarama/>

**NY - LINDENHURST - Hamfest.** GSBARC &  
SCR, Phil Lewis N2GMB, 631-226-0699.  
Email: info@gsbarc.org  
**OH - CANTON - Hamfest and Auction.**  
Stark County Fairgrounds, 305 Wertz Ave.  
NW, Van Buren, Talkin: 147.18. Massillon  
ARC, Terry Russ WBAT, 330-837-3091.  
Email: marcmandub@juno.com Web:  
<http://www.qsl.net/w8np>

## NOVEMBER 2001

### November 2-3

**TX - ODessa - Hamfest.** West Texas ARC,  
Craig Martindale W5BU, 915-366-4521.  
Email: w5bu@earthlink.net

### November 3

**FL - UMATILLA - Hamfest.** Lake ARA, John  
Gable WBKXC, 352-394-2723. Email:  
wbkxc@aol.com Web:  
<http://www.qsl.net/k4fc>  
**OK - ENID - Hamfest.** Garfield County  
Fairgrounds, Hoover Bldg. 8am-5pm. VE  
testing. Talkin: 145.29-460, 444-400 & S.O.  
Enid Hamfest Group, Tom Worth N5LW,  
580-233-8473 or Fred Selfridge W5UO,  
580-242-3551. Email:  
enidhamfest@yahoo.com

### November 4

**GA - LAWRENCEVILLE - State Convention.**  
Gwinnett County Fairgrounds, Alford  
Memorial RC, Randy Bassett KR4Q, 770-  
663-4244 XT 1989. Email:  
KR4Q@bigfoot.com Web:  
<http://www.totradio.org>

### November 4

**IA - Davenport - Hamfest.** Davenport  
ARC, Dave Mayfield W5WR, 309-762-  
6010. Email: hamfest@wld.com Web:  
<http://www.wld.com/hamfest>  
**MI - ST. JOSEPH/ST. JOSEPH HARBOR -**  
Hamfest. Blossomland ARA, Duane  
Dunfrier KX6D, 616-982-0404. Email:  
comdca@comdca.com Web:  
<http://www.comdca.com/bara>

### November 10

**AL - MONTGOMERY - Hamfest.** AL State  
Fairgrounds, Carreth Coliseum, Federal Rd.  
9am-3pm. CAVEV testing. Talkin: 146.84  
W4AP. Montgomery ARC, Dennis Rumbley  
K4UD, 334-699-9971. Email:  
K4UD@earthlink.net  
**FL - PORT ST. LUCIE - Hamfest.** Port St.  
Lucie ARA, John Cruz KT4VI, 561-465-  
9133. Email: broderick@cs.com  
**OH - CLEVELAND HEIGHTS - Hamfest.** Laura  
Lonczak, 216-663-3258. Email:  
lonczak@vsnl.net

**OH - GEORGETOWN - Hamfest.** Grant ARC,  
Don Siman KB7DO, 937-446-2234. Email:  
Huggins@BrightNet.com  
**SC - MYRTLE BEACH - Hamfest.** Grand

Strand ARC, Gordon Mooneyhan KE4HXL,  
843-449-9379. Email: baehcst2001@hot  
mail.com Web: <http://www.w4gs.org>  
**TX - AZLE - Hamfest.** Tri-County ARC, Jim  
Aielo NSQU, 817-444-9465.  
Email: drjaleio@aol.com Web:  
<http://www.qsl.net/tcarc-nrx>

### November 11

**IL - CHICAGO - Auction.** DeVry Institute of  
Technology, 3300 N. Campbell, Chicago  
ARC, Inc., Melissa Mensey KB9QWZ, 773-  
384-7514 or Dean N892, 708-331-7764.  
Email: carc\_incl@hotmail.com Web:  
<http://www.chicagocar.com>

### November 16-17

**MS - OCEAN SPRINGS - Hamfest.** West  
Hickory County ARC, Emile Girman  
W5DXX, 228-392-2816.  
Email: w5dxx@att.net Web:  
<http://www.datascym.com/~w5dxx>

### November 17-18

**IN - FORT WAYNE - State Convention.**  
Allen County War Memorial Coliseum  
Expo Center, 2000 S. Park Ave. Sat. 9am-  
4pm. Sun. 9am-3pm. Talkin: 146.88.  
ACARCS, James Boyer KB0IH, 219-489-  
6700. Email: jboyer@aol.com  
Web: <http://www.acarcs.com>

### November 24

**FL - OCALA - Hamfest.** Booster Stadium,  
NE 36th Ave. 8am-2pm. Marion County,  
352-236-0744 voice. Email:  
jccom@atlantic.net  
**IN - EVANSVILLE - Hamfest.** EARS, Neil  
Rapp WB9RTP, 812-729-5741.  
Email: ears@w9ear.org Web:  
<http://w9ear.org/hamfest.htm>

### November 25

**IL - WHEATON - Radio Fest & Flea Market.**  
DuPage County Fairgrounds. Fire & Radio  
Traders Society of Northern IL, 630-826-  
7580. Email: al3148@mesnet.net

## DECEMBER 2001

### December 1

**AZ - MESA - Hamfest.** Superstition ARC,  
Ed Cole KB7RM, 520-468-9015. Email:  
colej@cybertrails.com

### December 1-2

**FL - PALMETTO - Hamfest.** Manatee  
County Convention and Civic Center, One  
Haben Blvd. at US41, The Florida Gulf  
Coast ARC, Fred Hendeshot N3BLU, 813-  
671-9556. Email: fgcars@fgcarc.org Web:  
<http://www.fgcarc.org>

### December 2

**MI - HAZELTOWN TOWNSHIP - Hamfest.**  
L'Anse Creuse ARC, Gregg Crump K8CPXJ,

810-463-0729. Email: gcrump@home.com  
Web: <http://www.ameritech.net/users/irc>  
arc/index.html

### December 9

**IN - GREENFIELD - Hamfest.** Greenfield  
Central High School Pavilion, 810 N.  
Broadway St. 8am-2pm. VE testing. Talkin:  
145.330. Hancock ARC, email:  
kb9vz@excite.com Web: <http://www.w9aig.org>

## Why should you subscribe to Nuts & Volts?

I'll tell you why. Because you  
won't want to miss any of the  
great features coming up in  
the next few months.

We have articles in the works  
for launching and tracking  
model rockets, more on giving  
your project a USB interface,  
SCR and Triac principles and  
circuits, controlling lights and  
appliances with your comput-  
er's serial port, furnace fan  
control, computerized heart  
monitor, lots more robotics,  
microcontrollers, kits, projects  
and just about everything else  
an electronics hobbyist could  
ask for.

So don't wait! Just think about  
all you don't want to miss and  
get that order in now! Before  
it's too late!

### On the web

[www.nutsvolts.com](http://www.nutsvolts.com)

### By phone

1-800-783-4624

## EZ-EP DEVICE PROGRAMMER - \$169.95

Check Web! - [www.m2l.com](http://www.m2l.com)

**Fast:** Programs 27C010 in 23 seconds

**Portable:** Connects to PC Parallel Port

**Versatile:** Programs 2716-080 plus IEEE  
and flash (28, 29) to 32 pin

**Inexpensive:** - Best for less than \$200

● Complete implementation of manufacturer  
specified algorithms for fast, reliable  
programming

● Easy to use menu based software has  
binary editor, read, verify, copy, etc.  
File updates via tta or web

● Full over current detection on all  
on-chip sense, success, program, abort  
test chips and reverse insertion

● Broad based for by additional devices  
using adapters listed below

### Available Adapters

EP-10C (10C010) \$24.95

EP-10D (10D010) \$24.95

EP-10E (10E010) \$24.95

EP-10F (10F010) \$24.95

EP-10G (10G010) \$24.95

EP-10H (10H010) \$24.95

EP-10I (10I010) \$24.95

EP-10J (10J010) \$24.95

EP-10K (10K010) \$24.95

EP-10L (10L010) \$24.95

EP-10M (10M010) \$24.95

EP-10N (10N010) \$24.95

EP-10O (10O010) \$24.95

EP-10P (10P010) \$24.95

EP-10Q (10Q010) \$24.95

EP-10R (10R010) \$24.95

EP-10S (10S010) \$24.95

EP-10T (10T010) \$24.95

## EZ-EP M2L ELECTRONICS

San Diego, California 92108-0001

### M2L Electronics

870255-0555

Fax 870255-0777

250 CA 218

Orange, CA 92667

C.O. orders please add 7%

sales tax

<http://www.m2l.com>

## Do You Repair Electronics?

For only \$7.95 a month, you'll receive a wealth of information.

Repair data for TV, VCR, monitor, audio, camcorder, and more.

Over 100,000 constantly updated problem/solutions plus...

- TechsChat live chat room.
- Private user discussion forums.
- Automated email list server.
- UL/FCC number lookup.
- Hot tips bulletin board.
- Manufacturer information.

To access RepairWorld, direct your internet browser to <http://www.repairworld.com>

## RepairWorld.com

Electronix Corp. 1 Herald Sq. Fairborn, OH 45324 (937) 878-9878



CALL TOLL-FREE

(800) 292-7711 Orders Only

Se Habla Español

# C&S SALES

Secure On-line Ordering @ [cs-sales.com](http://cs-sales.com)

CALL OR WRITE FOR OUR

FREE

64 PAGE CATALOG!

(800) 445-3201

## Digital Multimeters

### Elenco Model M-1740



**\$34.95**

- 11 Functions:
- Freq. to 200kHz
- Cap. to 200µF
- AC/DC Voltage
- AC/DC Current
- Diode Test
- Transistor Test
- Meets UL-1244 safety specs

Model M 2780N  
**\$19.95**  
(3 functions)

### Elenco Model LCR-1810



**\$99.95**

- Cap. 0.1pF to 20µF
- Inductance 1µH to 20H
- Resistance 0.01Ω to 2,000MΩ
- Temperature 20°C to 750°C
- DC Voltage 0 - 20V
- Freq. up to 15MHz
- Diode/Auricle Continuity Test
- Signal Output Function
- 3 1/2 Digit Display


### Elenco Model LCM-1950



**\$69.95**

- Large 1" 3 1/2 Digit LCD
- Autorange Freq. to 4MHz
- Cap. to 400µF
- Inductance to 40H
- Res. to 4,000MΩ
- Logic Test
- Diode & Transistor Test
- Auricle Continuity Test

### Fluke 87III

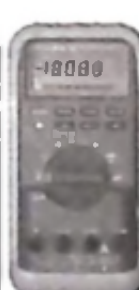

**\$319**

- Features high performance AC/DC voltage and current measurement, frequency, duty cycle, resistance, conductance, and capacitance measurement

**Quantity Discounts Available**

## Deluxe Soldering Stations

### Elenco SL-5 Series

Electronically controlled. Ideal for professionals, students, and hobbyists. Available in kit form or assembled.

As Low As  
**\$29.95**

Works w/ any iron! Turn any soldering iron into a variable iron.



#### Features:

- Cushion Grip Handle
- Soldering Iron (optional) with Grounded Tip for Soldering Static-Sensitive Devices. Easily Replaceable. Uses Long-Life, Plated Conical Tip.
- Heavy Steel, Non-Slip Base.
- Iron Holder Funnel - Reversible, left or right side.
- Steel Tray for Sponge Pad.
- Sponge Pad.

### Ordering Information:

Model SL-5 - No Iron. (Kit SL-5K) **\$29.95**

Model SL-5-40 - Includes 40W UL iron. (Kit SL-5K-40) **\$35.95**

Limited Time Offer: **FREE SP-1A Solder Practice Kit w/ Kit Order!**

Weller WLC-100 - Variable Power Control 5 - 40 watts **\$34.95**

### Elenco Model SL-30



**\$84.95**

- Tip temperature changeable from 300°F (150°C) to 900°F (480°C).
- Temperature is maintained within ±10°F of its preset temperature.
- The tip is isolated from the AC line by a 24V transformer.
- The tip is grounded to eliminate static charges.

SL-10 - Same as SL-30 w/o digital display **\$59.95**

### Weller Model WTCPT

Controlled Output Soldering Station

- Transformer powered soldering station complete w/macro style, low voltage, temperature controlled soldering iron.
- PT Series soldering tips come in a variety of shapes and sizes in three standard temperature ranges: 600°F, 700°F, & 800°F.
- 0-24V output - 60 watts.
- Special "closed loop" method of controlling maximum tip temperature.



**\$125**

## Test Equipment

### 10 Function 1.3GHz Universal Counter Elenco Model F-1300

- Frequency 0.5Hz - 1.3GHz 3 Ranges
- Period - Can read 60Hz to 60,000,000 F=1/T
- Totalize - Counts to 199,999,999
- RPM - 3 to 209,999 RPM
- Duty Cycle
- Max/Min/AVG with Time
- Stop-watch set 2 sec. to 100 hrs.
- Math Functions
- Timer - 2 sec. to 99 days
- Pulse Width - 0.1ms to 66666 Gms

**\$229.95**



### Elenco 3MHz Sweep Function Generator with built-in 60MHz Frequency Counter Model GF-8046

**\$195.95**



This sweep function generator with counter is an instrument capable of generating square, triangle, and sine waveforms, and TTL, CMOS pulse over a frequency range from 0.5Hz to 3MHz. GF-8025 - Without Counter **\$139.95**

### 20MHz Sweep / Function Generator with Frequency Counter Model 4040

- 0.2Hz to 20MHz
- AM & FM Modulation
- Burst Operation
- External Frequency Counter to 30MHz
- Linear and Log Sweep



10MHz Model 4017  
5MHz Model 4011  
3MHz Model 4003

\$325  
\$255  
\$205

**\$425**

### Elenco Handheld Universal Counter 1MHz - 2.8GHz Model F-2800



**\$99**

- Sensitivity:
- <1.5mV @ 100MHz
  - <5mV @ 250MHz
  - <5mV @ 1GHz
  - <100mV @ 2.4GHz

Features 10 digit display, 16 segment and RF signal strength bargraph. Includes antenna, NiCad battery, and AC adapter.

C-2800 Case w/ Belt Clip.....**\$14.95**

### Elenco RF Generator with Counter (100kHz - 150MHz) Model SG-9500



**\$225**

Features internal AM mod. of 1kHz, RF output 100mV - 350mV. Audio output 1kHz @ 1V RMS.

SG-9000 (analog, w/o counter) **\$124**

### Elenco Quad Power Supply Model XP-581

4 Fully Regulated Power Supplies in 1 Unit



**\$85**

4 DC Voltages: 3 fixed, +5V @ 3A, +12V @ 1A, 1 variable, 2.5 - 20V @ 2A - Fully Regulated & Short Protected - Voltage & Current Meters - All Metal Case

### Elenco Power Supply Model XP-603



**\$85**

- 0-30VDC @ 3A Output
- 3A Fused Current Protection
- Current Limiting Short Protection
- 0.025Ω Output Impedance

### Elenco 10Hz - 1MHz Digital Audio Generator Model SG-9300



**\$225**

Features built-in 150MHz frequency counter, low distortion and sine/square waves.

SG-9200 (w/o counter) **\$124**

## Elenco Oscilloscopes

Free Dust Cover and 2 Probes



S-1325 25MHz Dual Trace **\$325** S-1345 40MHz Delayed Sweep **\$569**  
S-1330 25MHz Delayed Sweep **\$439** S-1360 60MHz Delayed Sweep **\$725**  
S-1340 40MHz Dual Trace **\$475** S-1390 100MHz Delayed Sweep **\$895**

### DIGITAL SCOPE SUPER SPECIALS

DS-203 20MHz/10Ms/s Analog/Digital **\$695**  
DS-303 40MHz/20Ms/s Analog/Digital **\$850**  
DS-603 60MHz/20Ms/s Analog/Digital **\$950**

## Elenco Educational Kits

### Model XK-150

Digital / Analog Trainer

**\$89.95**



- 830-pin Breadboard
- 8 Data Switches
- 8 LED Buffered Readouts
- Built-in Function Generator (sine and square wave)
- Built-in Clock Generator
- Variable Power Supply
- 1.25V to 15VDC @ 25A
- 1.25V to 15VDC @ 25A
- 5VDC @ 25A
- 30VAC center-tapped at 15VAC @ 25A

### Model AR-2N6K

2 Meter / 6 Meter Amateur Radio Kit

**\$34.95**



### Model AK-700

Pulse/Tone Telephone Kit

**\$15.95**



### Model AM-780K

Two IC Radio Kit

**\$11.95**



### Model AK-870

Radio Control Car Kit

**\$24.95**



### Model M-1005K

DMM Kit

**\$15.95**



### Model MX-901

Electronic Crystal Radio

**\$6.95**



- Solderless!
- No Batteries Req.

## Electronic Science Lab

### Maxitronix 500-In-1 Electronic Project Lab Model MX-909

Everything you need to build 500 exciting electronic projects:

- Learn the basics of electronics and put your knowledge to work creating 500 different electronic experiments, special lighting effects, radio transmitter and receivers, amazing electronic sound effects, cool games and MORE!
- Includes built-in breadboard for easy wiring and connection of components, and an LCD (Liquid Crystal Display) indicates the information during the experiments in process.
- Build your knowledge by exploring amplifiers, analog and digital circuits plus how to read schematic diagrams.
- Includes transistors, transformers, diodes, resistors, capacitors, phototransistors, LEDs, integrated circuits, speaker, earphone, LEDs, and LED digit display!
- Fact-filled, illustrated, lab-style manual included.
- Requires 6 "AA" batteries (not included).



**\$170**

**Guaranteed Lowest Prices**

UPS SHIPPING 48 STATES 5%  
OTHERS CALL FOR DETAILS  
IL Residents add 8.25% Sales Tax  
**SEE US ON THE WEB**

# C&S SALES, INC.


150 W. CARPENTER AVENUE  
WHEELING, IL 60090

FAX: (847) 541-9904 (847) 541-0710

<http://www.cs-sales.com>


**15 DAY MONEY BACK GUARANTEE**

**2 YEAR FACTORY WARRANTY**

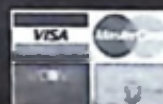

PRICES SUBJECT TO CHANGE WITHOUT NOTICE



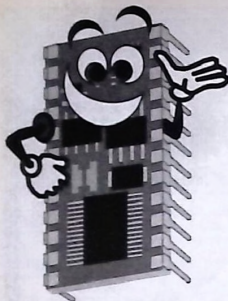

by Jon Williams

# Stamp Applications

## TOOL TIME

**M**y favorite BASIC Stamp peripheral is the character LCD. I love them. I have a truckload on my desk and I use them all the time. I have 2x16, 2x20, 4x20; I have just about every flavor of Scott Edwards serial LCDs. I'll say it again: I love them.

### LCD REDUX

LCDs are good because they're inexpensive (downright cheap in some cases), easy to connect to the Stamp, and allow us to provide a lot of information to the outside world. Naturally, I was thrilled when I learned that the BS2p would have direct support for parallel LCDs and that the commands would work very much like **SEROUT** and **SERIN** — allowing me to use the formatting modifiers. Does it get any better than this?

I'm pretty darned sure that if comedian Tim Allen knew anything about microcontrollers, he'd be a BASIC Stamp user. Of course, he'd rewire it for 220 volts and overclock the PIC/SX to run at 10 GigaHertz so he could point at it proudly and grunt like a pig. (That's how I show off my Stamp projects, don't you?)

Tim and his famous TV alter-ego both love tools — but then, don't we all? Tools are good. They help us build and create things. They're even better when they're free. And that's what we're going to chat about this month: a couple of freebie tools from Parallax. One is new, the other isn't, but has some really neat surprises.

For LCD lovers like me — it just has. About the only thing tedious when using character LCDs is designing custom characters and adding the data to a PBASIC program. Until recently, I would do like you and create my characters on paper. Ugh! Too tedious.

Enter the **LCD Character Creator**. This nifty little program (okay, I wrote it, but I still think it's nifty) lets you design and save custom LCD characters and save the definitions to use later. It supports 5x7 and 5x10 character designs and even includes the standard character set (from the Hitachi HD44780A00 ROM) so you have a starting point. The on-screen preview graphic lets you see what your custom character will look like in a display next to other characters.

Essentially, this is a little paint program for LCD characters. Left-clicking on a pixel will toggle it on or off. There's also clear, fill, invert, mirror, and flip commands. To make it easy to incorporate the new character into a PBASIC program, there's a text line at the bottom of the screen that can be copied right into your PBASIC source (this cool idea comes from Stamp user Steven M).



While the program is very easy to use, it comes with online help (Windows® HTML Help format) that explains all the menu items, includes a connection schematic (Figure 2 is right out of the help file), and demo programs for the BS2, BS2e, BS2sx, and BS2p. It'll even point your browser

to the Parallax web site.

### Cool Digits

While playing one day, I got the idea that I would create a custom set of digits for my LCD projects; you know, something that looked a little more sci-fi or computer-like. Creating the digits was no problem with my new program. But then — oops — I have 10 digits and only eight custom characters in an LCD.

After scratching my head for a few minutes I remembered a trick that Scott Edwards taught me. If you change the definition of a custom character that is being displayed, the LCD will change along with it. So for this project, I changed my thinking from eight custom characters to eight spots on the LCD that I could update at any time.

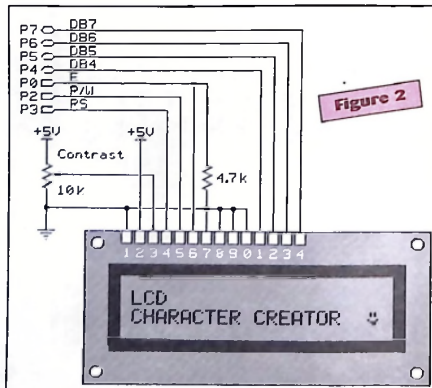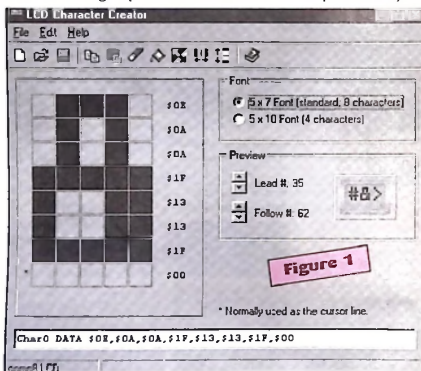



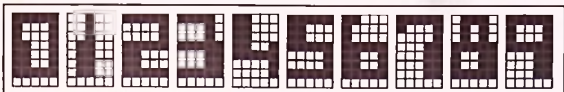


Figure 3

All I have to do is download new information to my assigned position.

Okay, let's do it. Take a look at Listing 1. This is a simple program — short and sweet. Its purpose is to display a running counter with my cool new digits. I'll use a Word variable to count from 0 to 999 and display it as 0.0 to 99.9 by inserting a decimal point between digits.

The EPROM Data section contains the definitions for the new characters that were created with the LCD Character Creator program (you can download the files with the source code for this article). One note: The LCD Character Creator always names the data line "Char0." After pasting each line into the source file, it was renamed. The name is used as a pointer to the start of the character. We need to know the location of each character in the EPROM so we can download it when needed to the LCD.

The LCD is initialized to operate in two-line mode. I used a 2x16 display for my experiment. I mention the width because it affects the placement of the right-justified numbers. Since we want to display three digits, we'll use custom character slots zero, one, and two. Custom character zero will display tenths, digit one will display ones, and digit two will display tens. Initialization is finished by downloading "new" zeros to digits zero and one, and a space to digit two.

Jump down to the **Update\_CC**. This is the code that takes care of downloading an image map to the LCD. When we enter this routine, we pass the custom character to update in **cNum** and the beginning EPROM address of our new character data in **addr**.

Since we've initialized the LCD to use two lines, we're forced to use the (standard) 5x7 character font which means eight bytes per character (the value of the **CLine** constant). The first line of **Update\_CC** uses **LCDCMD** to point into the LCD's CGRAM (Character Generator RAM) based on the character we want to update and the number of bytes required for a definition. A **FOR-NEXT** loop grabs the new character from EPROM with **READ**, then sends it to the LCD with **LCDOUT**. Simple and fast — which is exactly what we need since we're going to change characters on the fly.

Back in the main body of the program, we spit out a label and put our characters onscreen where we want them. Remember that digit zero is tenths, so it will be right-most in the display.

The routine called **Show\_Counter** is the heart of the program. The outer loop counts from zero to 999. The inner loop scans the value of **counter** using the **DIG** operator. This conveniently returns the digit value of the position scanned. It's a simple matter of

using this value to point into our table of definitions for the map of that digit.

The only exception is when the tens digit is zero — we'd rather have a leading space than a leading zero. The code checks to see if the scanned digit is the tens position (character two) and its value is zero. When this is the case we download a custom space (all zeros). It's easier to re-define a custom space than to use the standard ASCII space character (#32). If we did this, we'd actually have more code to write. Eight bytes of EE space for a definition is an easy trade.

So that's it. When the program is run, we'll see a counter with cool, high-

## STAMP APPLICATIONS TOOL TIME

**GET THE CATALOG TODAY!**  
Over 100 NEW products!  
[www.ramseykits.com](http://www.ramseykits.com)

### RAMSEY

#### SYNTHESIZED FM STEREO RADIO STATION



- Synthesized 88 to 108...no drift!
- Built in mono - 2 line inputs and one microphone input!
- High power module available for export use
- Low pass filter for great audio

Our FM100 is used all over the world by serious hobbyists as well as churches, drive in theaters, and schools. The kit includes metal case, whip antenna and built-in 110 volt AC power supply.

FM100 Super-Pro FM Stereo Radio Station Kit \$249.95

FM100WT 1 Watt, Wired Export Version \$399.95

#### SYNTHESIZED FM STEREO TRANSMITTER



- Professional quality rock stable synthesized transmitter. Dip switch settable for any frequency between 88-108 MHz. Strappable for high power output for export applications. Our most popular kit. Start your own radio station today with the FM25!

FM25 Synthesized FM Stereo Transmitter Kit \$219.95

#### FM STEREO TRANSMITTER



- Great entry level FM broadcast kit. Thousands in use. Handy for sending music through house and yard. Ideal for school projects too...you'll be amazed at the exceptional audio quality! Runs on 9V battery or 5 to 15 VDC. Add matching case and whip antenna set for great pro look.

FM100A Tunable FM Stereo Transmitter Kit \$34.95

CFM Matching Case and Antenna Set \$14.95

FMAC 12V DC Wall Plug Adapter \$9.95

#### RF WIRELESS LINK MODULES



- SAW Resonators for high stability — NO Drift!
- Powerful +10 dBm output.
- Range up to 600'
- 433 MHz loose-logic band
- Sensitive superhet receiver with RF LNA
- Stable over full 3-12 VDC range
- Optional on board 12 bit encoder/decoder

Using Hells HT-12 series chips. Quarter not included!

RXD433 433 MHz Receiver/Decoder Mod, Assembled \$26.95

TXE433 433 MHz Transmitter/Encoder Mod, Assembled \$24.95

RX433 433 MHz Data Receiver Mod, Assembled \$21.95

TX433 433 MHz Data Transmitter Mod, Assembled \$19.95

#### THE CUBES! MINIATURE VIDEO TRANSMITTERS



- Wireless crystal clear reception, yet smaller than a quarter! Transmits color or B&W with fantastic quality almost like a hand wire connection to any TV or VCR tuned to color channel 59. Crystal controlled for no frequency drift with performance that equals low enhancement models that cost hundreds more! Basic 20mw unit goes up to 300' while the high power version can virtually double that range! Fully assembled and tested, and ready to go. Powered by a standard V9 battery. Name that Quarter!

C2000 Video Cube, Factory Assembled & Tested \$89.95

C2001 High Power Version, Assembled & Tested \$129.95

#### INFRA-RED VIDEO CAMERA ILLUMINATOR



- Lets video cameras "see in the dark." Invaluable light source to us, but lots of light to CCD B&W cameras! Illuminates the area just like light, yet cannot be seen. Draws 180mA at 12 VDC. 110VAC adapter available.

IR1 Infra-Red Camera Illuminator Kit \$24.95

AC125 12VDC Power Supply \$9.95

#### ELECTRONIC PROTOTYPING SOFTWARE



**Priced for the hobbyist!**  
You can create and test AC and DC circuits minutes after installing this package on your PC. Start from scratch, or from the included library of pre-designed circuits. Drag and drop placement from a complete list of active and passive components. Test using a complete list of virtual instruments: Oscilloscope, voltmeter, ohmmeter, ammeter, and watt meter.

PLAB4 Electronic Prototype Software, Win95/98 \$49.95

#### ANALOG-DIGITAL PORTABLE LAB STATION



The COMPLETE analog-digital lab station in one. Includes function generator, clock output, power supplies, level switches, pulser, probe, LEDs and a LARGE breadboarding area all in one! Includes a custom molded case as shown. Used through the world at universities, technical schools, and R&D labs. Available in "Learn as you Build" kit form or factory assembled and tested. A great buy either way!

ML200 Lab Station, Kit \$155.95

ML200WT Lab Station, Factory Assembled & Tested \$225.95

#### CABLE WIZARD CABLE TRACER



Did you ever have to identify the "other end of that cable?" No more "ohming it out" with the Cable Wizard! Simply connect the Wizard transmitter to one end of the cable and use the receiver to sniff out the other end. It's as simple as that! The transmitter sends a pulsating 2 KHz signal down the cable which is heard when the receiver is close to the cable. Works with any cable including coax, telephone pairs, ethernet and more. Equipped with an RJ45 for all telco connections and dip leads for single wire connections.

WCT20 Wireless Cable Tracer Kit \$39.95

CWCT Matching Case Set for Transmitter & Receiver \$29.95

WCT20WT Factory Assembled & Tested WCT20 \$99.95

#### SPEEDY PERSONAL SPEED RADAR GUN



This low cost microwave radar uses the same principle found in police units costing thousands more. This has been the number one Science Fair project for years. Directed digital readout in miles/hour, kph, meters/hour, or feet/second. An earphone jack allows you to actually hear the Doppler frequency shift of moving objects. Our detailed manual not only guides you through construction, but covers the how's and why's of speed radar theory. Learn while you build. Uses two 110V AC coffee cans for the antenna (not included) and runs on 12 VDC.

S67 Speedy Personal Speed Radar Kit \$99.95

AC125 12VDC Power Supply \$9.95

#### AND...OUR FAMOUS MINI-KITS



- These are easy to build kits that can be used either stand alone or as building blocks for more complex projects.
- T54 Tickle-Back Shockers \$9.95
- B99 Super Snoopy Amplifier Kit \$8.95
- BL1 LED Blinky Kit \$3.95
- TD1 Tone Encoder/Decoder Kit \$6.95
- TT7 Touch Tone Decoder Kit \$29.95
- CP03 Code Practice Oscillator Kit \$9.95
- UT5 Universal Timer Kit \$8.95

**RAMSEY**  
ELECTRONICS, INC.

793 Canning Parkway  
Victor, NY 14564  
716-924-4560  
[sales@ramseykits.com](mailto:sales@ramseykits.com)

**Order Today! 800-446-2295**  
[www.ramseykits.com](http://www.ramseykits.com)







# STAMP APPLICATIONS — TOOL TIME

that allows it to be controlled by other programs. What does this mean? For starters, it means that if your favorite programming editor can launch a program with command line parameters, you can now use it to do Stamp development. You're no longer forced to write your Stamp code in the Stamp editor (but you do need to have the editor installed).


My favorite programming editor is EditPlus 2 ([www.editplus.com](http://www.editplus.com)). It's a \$30.00 shareware program and consistently gets rave reviews. I like it because it has user-definable syntax highlighting and it does a great job with HTML files with its built-in browser. And since it was designed for programmers, EditPlus can launch other executables with command line parameters. It can even do keyword look-ups in your executable's help file.

Take a look at Figure 5. This is a screen shot of EditPlus after compiling and downloading the LCD program we just wrote. On the left edge is a file selection box, the main pane displays our syntax-highlighted source code, and the bottom pane shows the (successful) output from the Stamp compiler.

My purpose here is not to teach you EditPlus, but to show how to connect your favorite programming editor to the Stamp compiler. It's important that the command line switches are correct. For EditPlus, I used this argument string:

```
/download /noprompts "%(FilePath)"
```

The first switch causes the PBASIC source file to be compiled and downloaded. If this process is not successful, you'll be alerted with an appropriate message. The second switch turns off normal message boxes — except **DEBUG**. I like this feature since I can still run programs that use **DEBUG** output from EditPlus. Of course, I can't switch between multiple **DEBUG** windows, but that's never been an issue for me, so I'm not concerned.

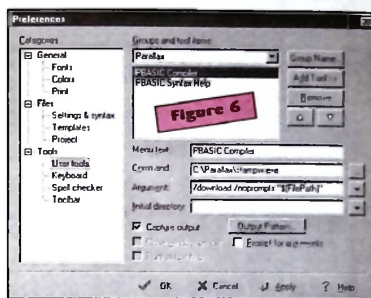

```
Listing 1
Nuts & Volts, September 2001

-----[ Title ]-----
File..... Custom Digits.BSP
Purpose... Advanced LCD Demo - custom numeric font(s)
Author.... Jon Williams
E-mail.... jonwms@aol.com
Started...
Updated...

( $STAMP BS2p 1

-----[ Program Description ]-----
This program demonstrates character definition replacement in order to
create a custom font for numbers. This program uses three of the eight
custom (CGRAM) character slots to display the tens, ones and tenths value
of a counter.

The program analyzes the counter and updates the screen by downloading
the appropriate character map for each digit.

To run this program on the BS2p Demo Board, connect the LCD and
install Jumper X3. Adjust contrast pot for best display.

Refer to the Hitachi HD44780 documentation for details on LCD control.

-----[ Revision History ]-----

-----[ I/O Definitions ]-----
LCDpin      CON    0          ' connect LCD to Out1

-----[ Constants ]-----
NoCmd       CON    500        ' No command in LCDOUT
ClrLCD      CON    501        ' clear the LCD
CsrHm       CON    502        ' move cursor to home position
CsrLf       CON    510        ' move cursor left
CsrRt       CON    514        ' move cursor right
DispLf      CON    518        ' shift displayed chars left
DispRt      CON    51C        ' shift displayed chars right
DdrAm       CON    $80        ' Display Data RAM control
CGRAM       CON    $40        ' Custom character RAM
Line1       CON    $80        ' CGRAM address of line 1
Line2       CON    $C0        ' CGRAM address of line 2

CLines      CON    8          ' lines per character
Space       CON    10        '

-----[ Variables ]-----
char        VAR    Byte      ' character sent to LCD
addr        VAR    Byte      ' address of address of map
idx         VAR    Rib       ' character number
countor     VAR    Word      ' loop counter
```

```
-----[ EEPROM Data ]-----
' character definitions - digits 0 - 9 and space
Dig_0 DATA $1F,$11,$11,$19,$19,$19,$1F,$500
Dig_1 DATA $04,$04,$04,$0C,$0C,$0C,$0C,$500
Dig_2 DATA $1F,$01,$01,$1F,$18,$18,$1F,$500
Dig_3 DATA $1E,$02,$02,$1F,$03,$03,$1F,$500
Dig_4 DATA $18,$18,$18,$19,$1F,$01,$01,$500
Dig_5 DATA $1F,$18,$18,$1F,$01,$01,$1F,$500
Dig_6 DATA $18,$10,$10,$1F,$19,$19,$1F,$500
Dig_7 DATA $1F,$11,$01,$03,$03,$03,$03,$500
Dig_8 DATA $0E,$0A,$0A,$1F,$13,$13,$1F,$500
Dig_9 DATA $1F,$11,$11,$1F,$03,$03,$03,$500
Dig_Spc DATA $00,$00,$00,$00,$00,$00,$00,$500

-----[ Initialization ]-----
Initialize:
PAUSE 500 ' let the LCD settle
LCDCMD LCDpin,100110000 : PAUSE 5 ' 8-bit mode
LCDCMD LCDpin,100110000 : PAUSE 0
LCDCMD LCDpin,100110000 : PAUSE 0
LCDCMD LCDpin,100100000 : PAUSE 0 ' 4-bit mode
LCDCMD LCDpin,100100000 : PAUSE 0 ' 2-line mode
LCDCMD LCDpin,100001100 : PAUSE 0 ' no crsr, no blink
LCDCMD LCDpin,100000110 : PAUSE 0 ' inc crsr, no disp
shift

FOR cNum = 0 TO 2 ' initialize cust chars
LOOKUP cNum,(Dig_0,Dig_1,Dig_Spc),addr
GOSUB Update_CC
NEXT

-----[ Main Code ]-----
Main:
LCDOUT LCDpin,ClrLCD,["CUSTOM DIGITS"] ' setup display
LCDOUT LCDpin,Line2 + 12,1,",".0

ShowCounter:
FOR counter = 0 TO 999 ' count in tenths 0 - 99.9
FOR cNum = 0 TO 2
FOR idx = counter DIG cNum ' get a digit
IF (cNum < 2) OR (addr > 0) THEN DIGITOK ' leading space if < 10
DIGITOK:
addr = addr + CLines ' calculate map for this digit
GOSUB Update_CC ' download to LCD
NEXT
PAUSE 100
NEXT

GOTO Main
END

-----[ Subroutines ]-----
Update_CC:
LCDCMD LCDpin,(CGRAM + (cNum * CLines)) ' update custom character
' point to start of character map
FOR idx = 0 TO (CLines - 1)
READ (addr + idx),char ' get data for character line
LCDOUT LCDpin,NoCmd,[char] ' write to LCD CGRAM
NEXT
RETURN
```



# STAMP APPLICATIONS — TOOL TIME

The "\$FilePath" parameter tells EditPlus to send the filename and complete path to the Stamp compiler. The reason it's quoted is that I use long filenames with spaces. Spaces in the filename will create a problem for the Stamp editor if you don't use the quotes. Better to be safe than sorry.

The Stamp compiler requires command-line controlled output to be directed to a standard output. With EditPlus (and other editors), this output can be captured so no file was specified. If your favorite editor doesn't capture this data, be sure to redirect the output to a text file. You can do that by adding this bit of text to your argument string:

> stampout.txt

If things don't proceed as you expect, you can open this file and find out why.

Well, that's about all we have time for this month. For those of you interested in EditPlus, I've included the PBASIC syntax definition in this month's project files. Be sure to check the Parallax web site for the availability of LCD Character Creator and the new Stamp compiler.

## Couldn't Get Back Issues?

From time-to-time, I'll get a question via email that causes me to reference a past issue of *Nuts & Volts*. Between Scott Edwards, Lon Glazner, and

myself, we've written over 75 Stamp Applications articles. That's a lot of Stamp stuff. Unfortunately, back issues are not always available and occasionally left us scrambling to dig out old files.

Not any more. Ken Gracey of Parallax worked with *Nuts & Volts* to compile Stamp Applications columns 1 through 75 into a two-volume book set. Between the two books, there are nearly 1,000 pages of BASIC Stamp programming tips and projects. All of the source code and related files are included on a CD.

You can order the books from *Nuts & Volts* or Parallax. Better do it quick though — these babies will go fast.

## Resources:

**Jon Williams**

3718 Valley View Lane, #3040  
Irvine, TX 775062  
(972) 659-9090  
jonwms@aol.com

## Parallax

599 Menlo Drive, Suite 100  
Rocklin, CA 95756  
(888) 512-1024  
www.parallaxinc.com

Until next time, Happy  
Stamping. NV

## ALL ELECTRONICS CORPORATION

QUALITY Parts  
FAST Shipping  
DISCOUNT  
Pricing

CALL, WRITE, FAX  
or E-MAIL For A  
Free 96 Page  
CATALOG.  
Outside the U.S.A.  
send \$3.00 postage.

### Solar Panel

Output: approximately  
3 Volts @ 40mA  
2.40" square x 0.13"  
thick epoxy-  
encapsulated  
silicon photovoltaic panel  
removed from solar-  
gating system. Solid,  
smooth, unbreakable module with easy-to-  
connect terminals. Ideal for solar-  
powered battery, chargers and other projects.  
CAT# SPL-60

\$3.50 each

### 30 Watt Stereo Amplifier



"Pump up the volume" with the PowerLite 30  
personal stereo amplifier. Boost the power of  
your computer, personal, CD player, portable  
TV or video game, any audio device with a  
line level output. This ergonomically designed  
desktop amplifier provides 30 (15 x 2) Watts  
of power for a clean, full sound that can be  
played through bookshelf or larger speakers.  
Trackball-like volume control. Tone control.  
LED power indicator. Includes wall-mount  
power supply and stereo mini-to-RCA cable  
to connect to audio source. New units in  
retail display packaging.  
Speakers not included.  
CAT# PBA-30

\$25.00 each

### Rechargeable Battery

Eveready® NH22 Nickel Metal  
Hydride rechargeable battery.  
Replaces 3 Volt batteries in many  
applications. Actual voltage  
7.2 Volts. Can be charged in most  
Nickel-cadmium chargers.  
CAT# NMH-9

\$3.50 each

### Two Speed Worm Gear Motor

Powerful, windable  
worm motor for  
2000-2001 Saturn L  
series automobiles.  
Two speeds: high speed  
is 106 RPM at 12 Vdc,  
4 Amps. Low speed is  
41 RPM at 12 Vdc, 0.91 Amps. 3/8" threaded  
drive shaft with nut. A 2.25" lever with a univer-  
sal joint, attached to the shaft, is easily re-  
moved. 7" overall length x 3.5" x 4".  
CAT# DCM-171

\$19.75 each



### Multimedia Headset w/ Boom Micro

Lattice® LVA-6520  
Designed for PC interactive  
audio applications. Padded  
earpiece headphones with  
electret boom mike.  
Adjustable headset.  
8 foot cord terminated  
with 3.5mm stereo  
phone plugs for mixer  
and headphones.  
CAT# PHN-23


\$7.50 each



### 640 X 480 LCD Panel with CCFT Backlight

Sharp® L145K101. Graphic  
display module with onboard  
drivers. Positive-type  
display. Black dots  
on white  
background.  
Operates on  
5 Vdc (logic)  
and 18 Vdc  
(LCD). Built-in  
CCFT backlight  
(inverter not  
included). Display size: 4.5" x 6".  
Module size: 5.56" x 8" x 0.27" thick.  
Includes hook-up diagram.  
CAT# LCD-61

\$20.00 each

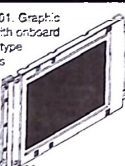

### 16 X 2 Miniature LCD

Vantion®  
M0LS16284-LV-S  
Display size:  
1.91" x 0.48"  
Module size:  
2.61" x 1.45"  
Character size: 0.16" x 0.1"  
5 x 8 dot format. Blue digits on light blue (near  
white) background. Includes hook-up sheet.  
CAT# LCD-64

10 or more for \$4.50 each


\$5.25 each



### 47 Watt Enclosed Supply

Astec® RP54-115/230-C-714A  
Input: 85 - 264 Vac  
Outputs: 5V @ 4Amp,  
12V @ 2A, -5V @  
0.7A. Compact  
enclosed supply  
with on-off switch.  
6.5" x 3.2" x 1.45".  
3.5" leads for output. Requires IEC-type power  
cord (not included). These units removed  
from new equipment in good  
condition. CAT# PS-540

\$8.50 each

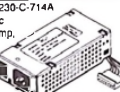

### Special 12 Vdc 1 Amp Wall Transformer

Coax power plug, 2mm i.d.,  
center positive. U.S.A.  
CAT# DCTX-1216

\$5.00 each

100 for \$3.85 each



### 8.4V 250 mA Battery Pack

Seven Sanyo AAA nickel  
cadmium cells in a single  
row. Shrink-wrapped in a  
cable with internal  
thermal cutoff and wire  
leads. This pack comes  
apart easily if you want to  
separate and use the batteries  
individually or reconfigure into new  
packs. Overall size: 2.82" x 1.76" x 0.43".  
CAT# HCB-84

\$3.00

43¢ per cell



ORDER TOLL FREE 1-800-826-5432

Shop ON-LINE www.allelectronics.com

MAIL ORDERS TO:

ALL ELECTRONICS CORP.

P.O. BOX 567 • VAN NUYS, CA 91408-0567

FAX (818) 781-2653 • INFO (818) 904-0524

E-MAIL allcorp@allcorp.com

NO MINIMUM ORDER • All Orders Can Be Charged to: Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail •  
Orders Shipped in the State of California must include California Sales Tax • 10% O.D. • Shipping and Handling \$5.00 for the 48 Continental United  
States • ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to Change without Notice

MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.

## Have You Heard?



\$29.95 each  
or both for  
\$49.95!

All of the first 75 Stamp  
Applications columns have  
been published in a two-volume  
book and are now available  
through Parallax or the  
*Nuts & Volts* Bookstore.

This is a limited printing, so  
don't wait!

Available On the Web  
www.nutsandvolts.com  
www.parallaxinc.com



We accept Visa,  
Mastercard, AmEx,  
and Discover

# Attention: TECHIESTUDS

Fax: 318-424-9771

To Order Call 1-800-227-3971 [www.shrevesystems.com](http://www.shrevesystems.com)

## A MONITOR FOR ANY BUDGET!

14" Voxon VGA NEW


**ONLY....\$59**

15" Voxon VGA NEW

**ONLY....\$89**

16" Rasterops fixed 85%  
X 624

**ONLY....\$79**

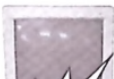

Call Us  
Before it's  
too late!

H.P. 17" fixed res 832 X 724

**ONLY....\$79**

H.P. 17" fixed res 640 X 480

**ONLY....\$79**

14" VGA refurb

**ONLY....\$49**



15" 624x870


Raster Full Page

Display

Refurbished Macs

Only

**ONLY....\$49**

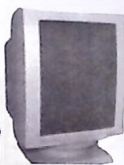

**Call us at 1-800-227-3971!**

Be sure to check us out on the web at <http://www.shrevesystems.com> for the best prices on Vintage Mac gear!

### Peltier Junction BLOWOUT!



**Peltier Junction**  
with heat sink, works on 5V & 12V  
1 3/16x 1 3/16

**\$5 Each or 4 for \$19**

### Paper Shredders On Sale!



12 volt DC  
required

Protect your Privacy!

**ONLY \$5**

### Firewire HD Case Kit

Accepts most  
3.5 IDE Drives  
Includes Cable!



**Only \$59**

### LOGIC BOARD BLOWOUT!



**STARTING AT \$29!**

PM 6100 .....ONLY \$49 7200 .....ONLY \$29  
PM 7100/66 .....ONLY \$99

### FLOPPY DRIVE BLOWOUT!



**NEW STARTING AT \$19!**

NO EXCHANGE  
REQUIRED!  
PART # 661-0474 **1.44 SuperDrives**



**Global Village Gold** Internal Modem  
14.4 Com Slot

**ONLY 50 Cents**



**Apple Color Composite Display**  
Great for Surveillance  
Refurbished

**ONLY \$69**




**ONLY \$19**

**PAS16 Audio Spectrum**  
For Mac LC Family 16  
Bit Sound Editing  
Card

### Global Village Bronze

External Modem  
2400 Bps/9600 Fax

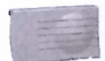

**ONLY 50 Cents**

**ONLY \$5**

**Floppy Media BLOWOUT!**

25 Mac Formatted 3.5  
Diskettes



**PDA Genuine Leather Carry Case**  
Lead your palm pilot  
lead the life of luxury!

**ONLY \$5**

### CMS Tower SCSI Case

Holds 4 5.25 SCSI full ht. drives



**\$79**



**\$3**

**LC Power Supply**  
+5V, -5V, +12V Output

### 20/30 GB Firewire HD

Great for all  
of your  
audio/  
video  
needs!



**As Low As \$169**

### Apple II 256K Memory Expansion Kit

HM51256P-10

**ONLY \$1**

#### Miscellaneous

Apple 8 bit Video Card	\$19
LaserWriter II NT	\$149
Apple ADB Keyboard	\$19
1.44 Super Drive	\$19
Clone ADB Mouse II	\$19
Quicktake 100 Camera	\$99
Bernoulli 90 MB EXT	\$10
44MB SyQuest Ext	\$10
88MB SyQuest Ext	\$19
RAM	
1 MB 30 Pin	\$4 For \$1
4 MB 72 Pin	\$2 For \$5

**\$25 minimum order**

**Shreve Systems**  
1200 Marshall st  
Shreveport, La 71101

Prices reflect a 2% cash discount and are subject to change without notice. Returns are subject to a 15% restocking fee. Not responsible for typographical errors.



# Gravity, Inertia, and the Electromagnetic Spectrum — Part I

by Richard Panosh

**F**ar from the planet, the saucer-shaped earth cruiser approached Altair Four at a velocity close to the speed of light. The two pitted moons of Altair Four were visible as the cruiser spiraled toward the planet. At an altitude of nearly 80 miles above the planet, the navigational computer instructed the craft to decelerate and prepare to plunge into the dense atmosphere of the planet.

In the year 2200, re-entry was not as critical as it had been for earlier rocket-propelled space ships. Early rocket ships had been restricted to a very narrow and precise re-entry cone, otherwise the ship would either dip into the dense atmosphere and burn up, or it would enter at too shallow of an angle and ricochet back out into space.

In a fraction of a second, the spacecraft reduced its velocity for safe entry into the protective atmosphere of the planet. Inside, the occupants were unaware of the change in acceleration. On their forward monitor they saw half of the planet surface below slowly rotating in darkness and the other half was softly illuminated by a green sky that revealed the pink desert surface far below.

The cruiser approached the surface in a long sloping trajectory, crossing over smooth desert plains punctuated with an occasional deep canyon and in some places surrounded by rugged mountains. Aboard the cruiser, sensitive instruments were actively probing the planet with the full array of invasive spread-spectrum electromagnetic waves and also passive detectors were actively recording every minute detail.

Once sentient life forms were detected, the navigational computer immediately made a course correction and the cruiser veered off at a sharp right angle and began to flutter down to the surface of the planet like a leaf in a soft summer breeze.

Is this science fiction or the future magic of technology? In this case, it's the opening scene of the 1956 science fiction movie "Forbidden Planet," but science fiction has a way of becoming reality. Perhaps it is the very nature of these dreams that are indeed projected into reality, because the dream must precede the development.

Today we accept aircraft that travel faster than the speed of sound, vertical take-off aircraft, satellites, space exploration, electronic communications, and the ever-shrinking integrated circuits that make it all possible. Not too long ago, none of these things existed.

The study of physics is an accumulation of man's knowledge dating before Aristotle (384-322 BC). Galileo Galilei (1564-1642) was the first to develop the relationship of mass and acceleration by experimenting with balls that he rolled down inclined planes. Sir Isaac Newton (1642-1727) and many others saw that these ideas could be applied to the moon and planets. In 1666 on a trip to the country, Newton discovered the force of gravity while watching an apple fall from a tree. He realized that this force orchestrated the heavenly bodies in their orbits. He described gravity as a force that acted through a distance, such that the magnitude of the force is proportional to the inverse square of the distance. This is similar to the force developed between charged particles.

Newtonian mechanics was applied to the observation of planetary

motion and able to predict additional planets in our solar system. As late as 1930, the ninth planet of our solar system, Pluto, was discovered from perturbations of Neptune's orbit. In 1969, Neil Armstrong became the first man to walk on the moon. His "...giant leap for mankind" was preceded by a series of unmanned Lunar Orbiters. The job of the unmanned Lunar Orbiters were to plot gravitational anomalies at the moon's surface from orbital perturbations. Computers could then locate these "Mascons" so that the manned orbiters that would eventually follow could be given a rocket boost of power to maintain a correct orbit.

In 1915, Albert Einstein (1879-1955) published his *General Theory of Relativity* concerning space, time, and gravity. Einstein's theory describes gravity not as a force, but as a property of curved space. Matter is visualized as producing a curve in the fabric of space much as a ball on a stretched rubber membrane will form a slight depression in the membrane. The depth of the depression is dependent upon the size or mass of the ball.

You experience the effect of warped space

whenever you push your lawnmower adjacent to a depression in the lawn. The outer set of wheels travel a different distance than the inner wheels and the result is to curve the path of the mower.

While Newtonian mechanics has been quite successful in describing gravitational phenomena, it failed to explain perturbations in the orbit of the planet closest to the Sun, Mercury. It was found that Newtonian mechanics was reasonably accurate in weak fields and at low velocities, but deficiencies became apparent when the gravitational field became larger.

Einstein's theory successfully explained the perturbations in Mercury's orbit and also predicted the bending of light and the shift of light waves to the red/blue wavelength due to the effects of gravity. Newton's theory failed to predict these effects. In addition, Einstein's theory also predicted changes in the unit of length and the unit of time at high velocities and added the phenomenon of gravitational waves. The first two have been verified to a remarkable degree by experiments and the effect of gravitational waves is implied by astronomical observation.

Two experiments are currently underway to improve the sensitivity of gravity wave detectors. The US effort is called LIGO (Laser Interferometer Gravitational-Wave Observatory) and consist of two sites for coincidence experiments.

Each site has already been constructed to house a 4 km long interferometer at Hanford, WA and the second is located 3,000 km away in Livingston, VA. The first sensitive searches of these instruments are due to begin in 2002.

Another experimental set-up is the European

instrument known as VIRGO. Einstein's theory predicts only two modes of polarization for the waves and the propagation velocity should be equal to that of light in the same region of space.

The strong field gravitational interaction was further tested in 1974 with the discovery of the binary pulsar PSR 1913+16 (a pair of very dense neutron stars). Since then, other binary pulsars have furnished tests of the theory just as Newtonian mechanics began to break down at moderate gravitational field strength, so Einstein's theory has been pressed for flaws at ever increasing field intensities.

Astronomers have recognized five stellar configurations that exhibit relativistic effects: white dwarfs, neutron stars, black holes, supermassive stars, and relativistic star clusters. While Einstein's theory has been the most consistent with observation, it does not fully describe the situation. This coupled with the desire to unify gravity with quantum mechanics into a single grand unified theory of all forces requires the theory of Quantum Gravity.

Another theoretical approach that combines quantum mechanical concepts and classical electrodynamics, sometimes referred to as SED (Stochastic Electro-Dynamics), has had a long history of yielding results consistent with QED (Quantum Electro-Dynamics).

The basic theory couples Newtonian mechanics with James Maxwell's (1831-1879) electromagnetic equations. The classical boundary conditions for Maxwell's equations are altered to include a random radiation, referred to as the ZPF (Zero Point Field). This ZPF is basically the texture of space and often described as the boiling, seething quantum foam at the smallest scale of distances of about  $10^{-33}$  cm (smaller than the diameter of an atom by  $10^{21}$ ) and is called Planck's length.

**Far from the planet, the saucer-shaped earth cruiser approached Altair Four at a velocity close to the speed of light.**



SED is a useful tool that is both straightforward and intuitively clear. It has been used to explain the following effects: (1) the Casimir effect in which a force is developed between closely-spaced parallel plates due to the ZPF in a resonant cavity, (2) the Lamb shift in which small perturbations have been detected in the electron orbit of hydrogen caused by the ZPF, (3) the Van der Waals forces between macroscopic objects as a result of the ZPF, (4) the spontaneous emission of photons appears to be stimulated by the ZPF, and (5) quantum noise sets a lower limit to detectability of electromagnetic signals and measurements due to the ZPF.

In 1989, H. Puthoff published a paper "Gravity as a zero-point-fluctuation force" employing SED to expand on an earlier theory proposed by Andrei Sakharov (1921-1989), the father of the Soviet H-Bomb. The theory describes gravity as the force developed between small Planck length dipoles (partons) that make up all matter and interact with the electric field of the ZPF at the shortest wavelengths. The paper develops a Newtonian-style solution with no adjustable parameters.

In this analysis, ordinary matter is defined as a collection of charged point dipoles (partons) that respond as small oscillators that are characterized by a constant radiation damping and a characteristic frequency bathed in ultra short wavelength (Planckian) ZPF radiation from all other matter.

This approach is analogous to the 1900 work of Max Planck (1858-1947) in describing black body radiation in terms of matter that consists of bound oscillators that interact with electromagnetic radiation. Planck's work led to the development of quantum mechanics and further development in this direction was abandoned.

Basically, this theory defines gravity as a force due to the electromagnetic interactions, not as the property of a warped space. In a sense, the warp of space becomes the gradient of the Planck wavelength electromagnetic field.

The interaction of the dipoles and electric field are identical to the forces developed in a dielectric placed between the plates of a capacitor. Part 2 will discuss this aspect in more detail and describe several experiments that were performed.

The SED approach gives a simple picture of gravitational forces and attributes the lack of shielding to the fact that matter is particularly dilute and completely bathed in a sea of very short wavelength random electromagnetic energy (the ZPF). This assumption is valid since Planck's length is on the order of  $10^{-33}$  cm and atoms are on the order of  $10^{-12}$  cm (21 orders of magnitude larger). To be effective, an electromagnetic shield has to be dense enough to attenuate the field distribution and thereby produce shielding.

In 1994, H. Puthoff was co-author with B. Haisch and A. Rueda on the paper "Inertia as a zero-point-field Lorentz force." Using the SED technique, they successfully described inertia as a retarding force produced by the interaction of the electric field of the parton as it is dragged through the magnetic field of the ZPF. Both effects — gravity and inertia — are seen to arise from the very high frequency electromagnetic components of the ZPF, which also explains why it has been so difficult to recognize the connection.

Maxwell developed the equations that describe the propagation of light and all electromagnetic waves in the 1860's. Guglielmo Marconi (1874-1937) and Nikola Tesla (1856-1943) are given credit for the invention of radio around 1895 and Marconi made his famous trans-Atlantic transmission in 1901.

The complete electromagnetic spectrum is illustrated in Figure 1 with the shortest Planck length waves responsible for the effects of gravity and inertia included. The bottom end of the electromagnetic spectrum is, of course, the ultra long wavelengths. The wavelength for a 60 Hz wave is about 3,000 mile long. Currently, much development is being directed in the  $10^3$  cm wavelength band (0.3-10 THz) because it offers high bandwidths, improved spatial resolution, and has applications to molecular spectroscopy.

Imagine the bandwidth available at these short Planck wavelengths. One can only wonder when the FCC will also discover the upper electromagnetic frequencies and try to auction off the gravitational band?

The somewhat oversimplifications of an ideal oscillator interacting with the ZPF, as well as the mathematical complexity of both theories, were obvious sources of skepticism. Recently, an alternate derivation of inertia was developed directly from Maxwell's equation. In addition, a relativistic form of the inertia equation has been derived that circumvents the skepticism and provides deeper insight. While both special relativity and general relativity involve inertia, neither gives any insight into its origins.

Prior to this theory, inertia has only been described as a property of matter. In addition, the introduction of the ZPF is consistent with Ernst Mach's (1838-1916) principle. Mach made the philosophical statement that all motion is relative and any motion is devoid of meaning without the surrounding matter. Other matter is required to establish a frame of reference — "the fixed star" becomes the ZPF.

The gravitational ZPF theory has met with more resistance than the inertia theory. While presenting some insight into a mechanism for the force

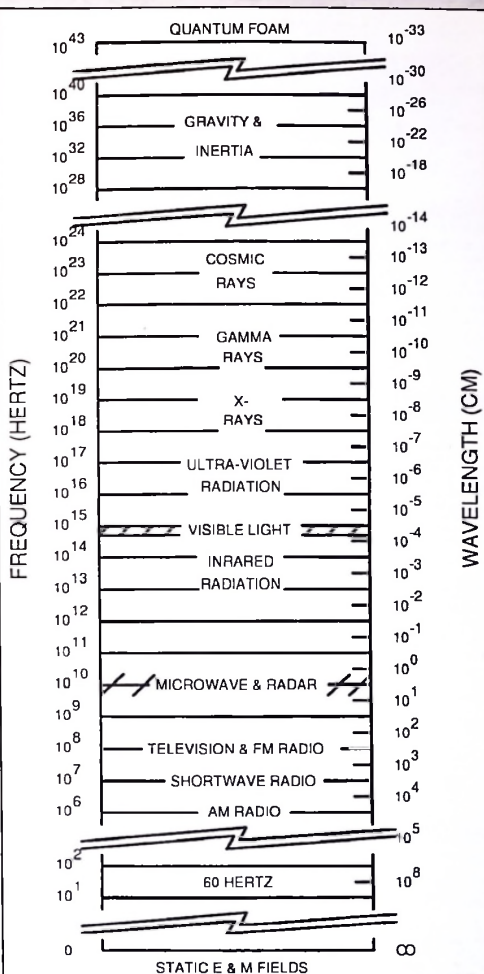


Figure 1. Complete Electromagnetic Spectrum

of gravity and the lack of shielding, it only develops a Newtonian form of equation as opposed to Einstein's space-time curvature that is rich in predictions of lensing, black holes, etc. However, the inertial theory lends much support to the gravitation theory through the intimate definition and interpretation of mass as an interaction with the ZPF.

Obviously, further development is required, but the door stands slightly ajar to the possibility that both gravity and inertia can be manipulated since both properties arise in electrodynamics. This would fulfill Einstein's dream of an "electro-gravity" that would complete the work started by Maxwell. It would also incorporate the concept of controlling inertia inherent with gravitational propulsion that would make possible nearly instantaneous acceleration, right angle turns, and silent hovering to bring us full circle to our science fiction introduction.

Sorry, but there is no warp drive. Guess we will all have to concentrate on that dream, both harder and longer.

Part 2 will deal with some experimental aspects, plus references and web sites for additional information. NV







Nuts &amp; Volts Magazine/SEPTEMBER 2001 39



# TECH FORUM

This is a READER TO READER Column. All questions AND answers will be provided by Nuts & Volts readers and are intended to promote the exchange of ideas and provide assistance for solving problems of a technical nature. All questions submitted are subject to editing and will be published on a space available basis if deemed suitable to the publisher. All answers are submitted by readers and NO GUARANTEES WHATSOEVER are made by the publisher. The implementation of any answer printed in this column may require varying degrees of technical experience and should only be attempted by qualified individuals. Always use common sense and good judgement!

Don't forget to check out the new online electronics forums at the **Nuts & Volts** website. There are currently boards for discussing Robotics, Microcontrollers, Radio, Computers, CNC, and a General forum for discussing any electronic topic at all. We'll even add new dedicated boards for hot topics. Just let us know!

Want to get a jump on things before the magazine arrives? The Tech Forum questions are posted on our website on or before the first of each month. Unanswered questions from recent issues are there also.

## QUESTIONS

I'm looking for schematics on a Foshiba PCX1100 cable modem or any source of information regarding the details of its operation, motherboard layout, etc. Apparently, these modems only work on a 10baseT ethernet. I want to modify the modem so it will work on both 10baseT and 100baseT.

Any help in loading me in the right direction would be fantastic.

9011

Christian  
via Internet

I have an Allen Electric & Equipment Co. (formerly of Kalamazoo, MI), model E313 generator (motor armature tester) that I would first like to rewire, and then learn how to use it!

I need a schematic and operating instructions.

9012

Peter Stratos  
via Internet

I have an old, but still well-used (1977) Heathkit Digital Floor Clock/Chime (GC-1195). It had 24 small incandescent display lamps driven by 24 PNP grounded-emitter transistors that provided a 3.5" high, four-digit display using a 3.5" x 0.25" rectangular lens covers over each segment lamp.

The now very rare/discontinued lamps were replaced with 24 ultra bright (3000 MCD) yellow 1.3/4

Send all material to Nuts & Volts Magazine, 430 Princland Court, Corona, CA 92679, OR fax to (909) 371-3052, OR E-Mail to [forum@nutsvolts.com](mailto:forum@nutsvolts.com)

LEDs with the original dimming function retained. The main clock 40-pin LSI chip was a non-multiplex type of chip that provided 24 actual leads—one to each of the four number segments and colon that has just failed.

There are now only about five or six of these, now very costly, large scale integrated non-mux clock chips left in the world!

I would like to replace the small main clock board with an all new current clock IC chip board (keeping the current display board), but found they are all the multiplex type and while the display (now LED) could be cut up and re-wired to separate/isolate the common ground leads into four groups, there would be additional issues with the seven control segment leads that also multiplex to the clock chime board control inputs and the 1/4 hour chiming outputs.

Is there an easy/practical way to convert a new clock board's seven-segment LED output and multiplexing leads into 24 non-mux leads (i.e., 24 optical isolators with capacitors to block the on/off mux sequencing of the segments or op-amp comparators across the new display segment LEDs, etc.)?

9013

Tom Murtaugh  
via Internet

## ANSWERS

ANSWER TO #8014 - AUG. 2001

I found a web page that told of an American university student who invented a new way of sampling TV images to allow recombining them so as to get 3DTV. He applied for a provisional patent, was written up in some magazines, and has his prototype unit in the basement of his university.

I do not remember anything but these general facts. Can anyone help?

Michael Starks has an extensive background in science with five years of graduate study at UC Berkeley. He began exhaustive research on the patent and technical literature of stenoscopia (true 3D imaging) in 1973.

In 1989, he founded 3DTV Corp. and began producing and selling the world's first commercial home 3DTV system with 3D movies on videotape.

The above has been excerpted from <http://www.3dmagic.com/press.html>.

There is also extensive material on 3D films, TV, and related products on that site.

Barry Cole  
Camas, WA

ANSWER TO #8015 - AUG. 2001

About 10 years ago, I remember there being a short craze on water-powered watches. I'm not sure what principle these worked on, but I would be interested in using it for my own projects.

Any information about this technology would be much appreciated.

I'm not familiar with the craze of water-powered watches, but the technology behind such a thing comes from the fact that even tap water has charged particles known in the industry as ions.

Without getting into physics 101 and keeping it short, each atom in the universe contains either positive or negative values for these ions and thus they can be tapped for this electrical value or potential.

In the chrome factory where I once worked, we had to de-ionize all of the water that ended up in the plating tanks. We had a special de-ionizing plant that would take the charge out of the water through osmosis, chemical action, and filtration because if there was any excess potential leftover in the water, or if the water had the potential to conduct easily because of impurities, it would interfere like a buffer or charge between the metals, the acids, and the generating source. It would either displace some of the metal being deposited or simply deposit those impurities in place of some of the plating materials.

Because most LCD watches consume less than the "static potential" that resides in your body at the present moment, I would assume that a drop of water, especially one that is dirty with some minerals or two, would easily power one of the

## ANSWER INFO

• Include the question number that appears directly below the question you are responding to.

• Payment of \$25.00 will be sent if your answer is printed. Be sure to include your mailing address if responding by E-Mail or we can not send payment.

• Your name, city, and state, will be printed in the magazine, unless you notify us otherwise. If you want your email address printed also, indicate to that effect.

• The question number and a short summary of the original question will be printed above the answer.

• Unanswered questions from a past issue may still be responded to.

• Comments regarding answers printed in this column may be printed in the Reader Feedback section if space allows.

## QUESTION INFO

### TO BE CONSIDERED

All questions should relate to one or more of the following:

- 1) Circuit Design 3) Problem Solving
- 2) Electronic Theory 4) Other Similar Topics

### INFORMATION/RESTRICTIONS

- No questions will be accepted that offer equipment for sale or equipment wanted to buy.
- Selected questions will be printed one time on a space available basis.
- Questions may be subject to editing.

### HELPFUL HINTS

- Be brief but include all pertinent information. If no one knows what you're asking, you won't get any response (and we probably won't print it either).
- Write legibly (or type). If we can't read it, we'll throw it away.
- Include your Name, Address, Phone Number, and email. Only your name, city, and state will be published with the question, but we may need to contact you.

LCD watches for days, if not weeks.

Some of the newer watches will run for three or more years on a single tiny battery making its draw somewhere in the "Pico" amp range, while ionized water can easily hold that amount of charge.

I would say two tiny electrodes placed close together in a tiny vial (or two) should do the trick. I think your physical manufacturing requirements will be your hardest



## ANSWERS TO #8011 - AUG. 2001

My friend bought an older motel. The front desk switchboard for the room's telephones is an aging model with little or no tech support.

Is there a way we can use a desk phone, small laptop computer, and some kind of interface box as a substitute for the old console to control the six phone lines that enter the motel?

The software needs to switch calls between rooms and scan for an open line for outgoing calls.

#1 Having installed and maintained PBXs (Private Branch eXchange) for 20 years, I must tell you it can't be done.

If the PBX console is electronic, its data format for communicating with the PBX is of a proprietary for-

mat. In other words, the engineer that designed the system, made up his own code to transmit between console and system. These codes are not compatible with computers which use ASCII as the transmitted data.

Another thing to consider, if the PBX is capable of communicating with a laptop, it would have already been using one.

**Dennis Hewatt  
Frontenac, KS**

#2 A company called CMP (Call Management Products) sells something like this.

They can be reached at [www.callmgmprod.com](http://www.callmgmprod.com) or 303-465-0651.

**Geoff Probert  
via Internet**

trick if you plan to make it into a watch.

A "stick up clock" or cheap watch would be a good starting point because some of these watches can be run for several seconds or minutes with a dead battery in place just by rubbing the case or glass cover, or even warming it when it's cold with your hands. The only drawback that I can foresee is the fact that you may have to stack multiple water cells similar to multiple batteries in order to gain the potential voltage or current depending on your brand of watch and its requirements.

**Chris  
Bieber, CA**

## ANSWER TO #60110 - JUNE 2001

I'm trying to find a circuit that will replace a voltage regulator assembly from a Homelite EHE 4400 AC generator. From what I see, it's a revolving field type with an exciter coil in the stator.

The rotor and stator are both two pole (3,600 RPM). Their slip ring/brush assembly connecting the rotor to the regulator is, I assume to

deliver DC excitation current to the rotor. When I run the engine and connect DC from my power supply to the rotor, the generator works fine. I rang out all windings and none of the resistance values seem out of the ordinary. Any information on a replacement part or a circuit diagram would be greatly appreciated!

If your AC alternator produces voltage when the field is not energized, then it can be self-starting by rectifying the AC, otherwise you will need a battery to get it started. The regulator should include a transformer and full-wave rectifier, to keep DC out of the alternator stator and minimize the filtering.

I have built a regulator for an automotive DC generator, the same circuit should work here, although the current and voltage requirements may be higher. It may not be necessary to filter the rectified AC, but a ripple in the field current will distort the AC waveform. Contact me at [russk@att.net](mailto:russk@att.net) if you want a copy of my circuit.

**Russell Kincaid  
Milford, NH**

## ANSWERS TO #8016 - AUG. 2001

Is there any way I can power a device already connected to the phone line (providing an audio signal), but also drawing power (6 VDC-60mA) directly from the phone line? A diagram would be greatly appreciated.


#1 You need to give more detail than "device." The more current-consuming "devices" you connect, the more the "busy voltage" drops. Idle telephone lines read around 48 volts, and busy lines will read anywhere from 5 to 12 volts, depending on your distance from the central office. If you connect too many current-consuming "devices" on a line, it may not disconnect after you use it when these devices are first connected.

**Dennis Hewatt  
Frontenac, KS**

#2 The nominal voltage on the telephone line is 48 VDC, so you just need a resistor and zener diode. The current is small enough that the telephone company should not get concerned by the load. The 1uF capacitor is to filter any ring voltage that may otherwise get through.

Parts are available from RadioShack.com: Zener diode = 900-3091, 1uF cap = 900-2170, resistor = 900-0127.

**Russell Kincaid  
Milford, NH**

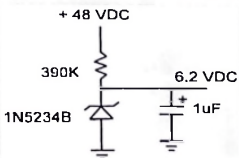

## ANSWER TO #6014 - JUNE 2001

I'm trying to find any information relating to electro magnetic or magnetic power.

I have searched the libraries in California and here in Arizona, and can't seem to find anything that doesn't require a degree in nuclear science.

Can anyone refer me to any publications that can be understood by the average person?

Magnetic properties are nonlinear and therefore complex, but you can sometimes "cookbook" a solution from the manufacturer's data.

I suggest that you check out the websites of Magnetics, Inc. at [www.mag-inc.com](http://www.mag-inc.com) and Micrometals, [www.micrometals.com](http://www.micrometals.com).

**Russell Kincaid  
Milford, NH**

## ANSWER TO #8013 - AUG. 2001

What is the wiring diagram for a ceiling fan with a four-position pull chain switch (off, high, medium, low)? What would happen if the wires for the speed changes were mixed up? Would it only affect the order or would it cause damage?

I just installed a couple of weeks ago, two older ceiling fans that didn't come with any wiring diagrams. The first thing I noticed with both fans was that only two of the four wires are actually for the motor even though one of them was a single-speed fan with external speed control (light dimmer type) and the other was a four position pull chain.

In both cases, the other two wires were for the lighting circuit even though they may or may not have a light fixture installed. One black (power) and one white (neg/ground) wire power the fan motor and the others (two or three wires) are usually for the lighting. Again, in both cases, the lighting wires were smaller in size (16 or 18 gauge) and may be the following colors. Yellow, blue, brown, or red.

If you have a light socket already installed, take it apart to see if there are any exposed wires or shorts, noting the colors. If you have no light fixture installed, then remove the cover plate and again inspect the lighting wires for exposure or shorting and note the colors. There is usually a 1/4" ID hollow tube that runs completely through the center of the fan motor assembly to allow these wires to end up at the other end of the fan to power and hold the light fixture to the fan assembly. This tube is the standard size and thread type used on all American lighting and lamps fixtures found in the home.

**Chris  
Bieber, CA**

PiCmicro MCU development tools from microEngineering Labs, Inc.  
[www.melabs.com](http://www.melabs.com)

## LAB-X Experiment Boards

Assembled development platforms. Each has RS-232 serial port, on-board programming connector, power supply, plus other hardware.  
LAB-X1 for 40-pin (shown) - \$199.95  
LAB-X2 for 28 or 40-pin MCUs - \$289.95  
LAB-X3 for 16-pin MCUs - \$119.95

**PicBasic and PicBasic Pro Compiler**  
Write programs for PICmicro MCUs in BASIC. Can be used in Windows or DOS (includes Windows editor/IDE software).  
PicBasic Compiler - \$99.95  
PicBasic Pro Compiler - \$249.95

## EPIC Plus PICmicro Programmer

Programs the following PICmicro MCUs:  
PIC12CXX, PIC16CXX, PIC16C63, PIC16C64, PIC16C65, PIC16C999, PIC17C000, PIC17C001, PIC17C002, PIC17C003, PIC17C004, PIC17C005, PIC17C006, PIC17C007, PIC17C008, PIC17C009, PIC17C010, PIC17C011, PIC17C012, PIC17C099, PIC17C100, PIC17C101, PIC17C102, PIC17C103, PIC17C104, PIC17C105, PIC17C106, PIC17C107, PIC17C108, PIC17C109, PIC17C110, PIC17C111, PIC17C112, PIC17C113, PIC17C114, PIC17C115, PIC17C116, PIC17C117, PIC17C118, PIC17C119, PIC17C120, PIC17C121, PIC17C122, PIC17C123, PIC17C124, PIC17C125, PIC17C126, PIC17C127, PIC17C128, PIC17C129, PIC17C130, PIC17C131, PIC17C132, PIC17C133, PIC17C134, PIC17C135, PIC17C136, PIC17C137, PIC17C138, PIC17C139, PIC17C140, PIC17C141, PIC17C142, PIC17C143, PIC17C144, PIC17C145, PIC17C146, PIC17C147, PIC17C148, PIC17C14



## ANSWERS TO #8017 - AUG. 2001

I do electronic board repair for a textile mill. A young man whose father used to work with me came to me with a problem.

He overloaded the stereo with speakers and as soon as the power button is pressed, it shows protect, and 24 hours later when powered up, it goes through a display. I have used the buttons to clear the memory several times with no results.

I'm no TV or stereo repair man, but this kid believes in me. Sharp says take it to a repair shop. They quote \$50-\$250, but this kid doesn't have that kind of money.

I wish someone would tell me how to correct this problem. I would sure like to help this kid and I would appreciate anyone coming to our rescue. I've been with Nuts & Volts for about 20 years and have seen it come a long way. I'm self-taught in electronics and try hard, but I know my limits.

#1 It's likely that the power output (ICs) are blown due to the overload. This is causing the power supply to go into protect mode so as not to smoke the unit. If you remove the power ICs and the unit then powers up, replace them. If it still doesn't power up, then you have a power supply problem which should be easy to trace, or you should send the unit to a repair shop.

**Russell Kincaid  
Milford, NH**

#2 Having repaired a few stereos in my time, what it sounds like — if I read you correct — by adding too many speakers to the system you have changed the impedance of the output and this

can act like a heavy load or virtual short. Permanent damage may have already been done.

Resetting codes and playing around with the processor won't help if the finals are damaged or compromised.

The areas I would concentrate on are the impedance matching final resistors which your system may or may not incorporate. If you have these resistors, they will usually be a large "sand-type" resistor about one or two inches long. See if they are smoked, cracked, or they have a burnt smell. Also check to see if they have become unsoldered due to overheating.

Next, I would move along to see if you have a "final" transistor set-up such as the TO-220 or the TO-5 style and, if incorporated, test them for getting hot, see if they have become unsoldered due to overheating, check for "no current flow" because they are fried, or the usual array of transistor checks that are used in any standard circuit.

If you have this design, they will be located fairly close to the back section of the circuit board close to where the speaker wires connect to the back plate or jumpers. Check to see if there are "final" fuses installed in the same area because many manufacturers incorporate these into their design as a fail-safe system in case of a dead short. Some manufacturers replace the fuse with a circuit breaker instead of a one-time fuse.

Next, you may have the "Solid-State Module" type of stereo and again check for input VS output voltages and current. The module may be the complete type which is usually around two square inches in size, and it is always attached to a heatsink of the same size.

It also might be broken down into two or more smaller chip type amps (usually four) and so treat them the same and check each amp separately.

A set of head phones can be modified to check for pre-amp and amp damage or operation. The module or chip can be completely fried so check for overheating, running stone cold, smell, and any physical damage such as a cracked plastic housing or burnt plastic.

Other than this, you need to have good knowledge and experience in troubleshooting and audio circuits because it could be anything.

Depending on age, any one of these systems may be incorporated in your stereo and you need to determine which, if any, is your type.

**Chris  
Bieber, CA**

#3 The protect usually indicates that there is a fault on the output. These circuits are used to detect excessive DC from the power amplifier. There is probably a relay that connects the amplifier section to the output terminals. Find the input side and check for DC. If it is above a few millivolts, then the power amplifier is probably shorted.

This type of failure can put quite a load on the power supply and affect other stages, as well. It is likely that this unit uses a hybrid power module of some kind so, it should be relatively easy to repair.

Please use care when poking around as there is a lot of energy available. Also use an isolation transformer if you have one available.

**Al Sekeet  
Grand Rapids, MI**

## TechKnowledge 2001 Continued From Page 7

### Avanti Executives Fined, Sentenced to Prison


If you have been under the impression that theft of intellectual property always goes unpunished, consider the case of Avanti Corp. ([www.avanti-corp.com](http://www.avanti-corp.com)), the IC design software vendor. Late in July, a six-year-old legal case against the company concluded with co-founder Stephen Wu being dragged away in handcuffs to spend two years in San Quentin State Prison. Wu, who is no longer with the company, also was slapped with \$2.7 million in fines. Other Avanti executives who will be spending time in the slammer include Yuh-Zen Liao (\$2.7 in fines, one year in jail), Eric Cho (\$108,000 in fines, one year in jail), Eric Cheng (\$27,000 in fines, 364 days in jail), and Mitch Igusa (one year in jail). In addition, former president and CEO Gerald Hsu was fined \$2.7 million but, as part of a plea bargaining agreement, will avoid prison and stay on as Chairman and Chief Strategist. Avanti was also ordered to pay more than \$195 million to Cadence Design Systems, Inc. ([www.cadence.com](http://www.cadence.com)),

as restitution for Wu's theft of Cadence's Synbad database code back in 1991.

Avanti's new president, Paul Lo, was quoted as saying that the company is "facing great challenges but also tremendous opportunities." With customers and employees running for the exits, and Avanti stock prices having dropped from a high of \$27.00 in February to \$5.80 as of this writing, it appears that the challenges will take up most of Mr. Lo's time.

### A Dim Ray of Hope for Internet Companies

In an industry in which "dot-com" businesses have been becoming "dot-gone" in droves, there seems to be at least an upturn in the downturn. According to Challenger, Gray & Christmas, Inc., July layoffs in the Internet service industry were only 8,697, which was the lowest since last October, when only 5,677 workers lost their jobs. It was also an improvement over the 9,216 layoffs in June. Challenger ([www.challengergray.com](http://www.challengergray.com)) is a consulting firm that works with employers to find new employment for executive and middle management employees who are being terminated. **NV**



## EPROM+

A device programming system  
complete info at [www.arlabs.com](http://www.arlabs.com)  
♦ EXCEPTIONAL POWER FOR THE PRO  
♦ EASY-TO-USE FOR THE NOVICE

**Here's what you get:** A rugged, portable programming unit including the power pack and program port cable (both of which are made in the USA). A real ground cover and technical manual which includes a schematic diagram for the pin programming unit plus diagrams for all technology family adapters. Comprehensive, easy-to-use software which is specifically designed for all technology families of 16, 18, 24, 28, 32, 36, 48, 64, 72, 96, 128, 144, 192, 256, 288, 360, 432, 512, 576, 640, 768, 8192, 16384, 32768, 65536, 131072, 262144, 524288, 1048576, 2097152, 4194304, 8388608, 16777216, 33554432, 67108864, 134217728, 268435456, 536870912, 1073741824, 2147483648, 4294967296, 8589934592, 17179869184, 34359738368, 68719476736, 137438953472, 274877906944, 549755813888, 1099511627776, 2199023255552, 4398046511104, 8796093022208, 17592186044416, 35184372088832, 70368744177664, 140737488355328, 281474976710656, 562949953421312, 1125899906842624, 2251799813685248, 4503599627370496, 9007199254740992, 18014398509481984, 36028797018963968, 72057594037927936, 144115188075855872, 288230376151711744, 576460752303423488, 1152921504606846976, 2305843009213693952, 4611686018427387904, 9223372036854775808, 18446744073709551616, 36893488147419103232, 73786976294838206464, 147573952589676412416, 295147905179352824832, 590295810358705649664, 1180591620717411299328, 2361183241434822598656, 4722366482869645197312, 9444732965739290394624, 18889465931478580789248, 37778931862957161578496, 75557863725914323156992, 151115727451828646313984, 302231454903657292627968, 604462909807314585255936, 1208925819614629170511168, 2417851639229258341022336, 4835703278458516682044672, 9671406556917033364089344, 19342813113834066728178688, 38685626227668133456357376, 77371252455336266912714752, 154742504910672533825429504, 309485009821345067650859008, 618970019642690135301718016, 1237940039285380270603436032, 2475880078570760541206872224, 4951760157141521082413644448, 9903520314283042164827288896, 1980704062856608432965457792, 3961408125713216865930915584, 7922816251426433731861831168, 15845632502852867463723662336, 31691265005705734927447324672, 63382530011411469854894649344, 126765060022822939709789298688, 253530120045645879419578597376, 507060240091291758839157194752, 1014120480182583517679314389504, 2028240960365167035358628779008, 4056481920730334070717257558016, 8112963841460668141434515116032, 16225927682921336282869030232064, 32451855365842672565738060464128, 64903710731685345131476120928256, 129807421463370690262952241856, 259614842926741380525904483712, 519229685853482761051808967424, 1038459371706965522103617948848, 2076918743413931044207235897696, 4153837486827862088414471795392, 8307674973655724176828943590784, 16615349947311448353657887181568, 33230699894622896707315774363136, 66461399789245793414631548726272, 13292279957849158682926309745544, 26584559915698317365852619491088, 53169119831396634731705238982176, 10633823966279326946341047795328, 21267647932558653892682095590656, 42535295865117307785364191181312, 85070591730234615570728382362624, 170141183460469231141456764725248, 340282366920938462282913529450496, 680564733841876924565827058900992, 1361129467683753851131654117801984, 2722258935367507702263308235603968, 5444517870735015404526616471207936, 10889035741470030809053232942415872, 21778071482940061618106465884831744, 43556142965880123236212931769663488, 87112285931760246472425863539326976, 174224571863520492944851737078653952, 348449143727040985889703474157307904, 696898287454081971779406948314615808, 1393796574908163943558813896629231616, 2787593149816327887117627793258463232, 5575186299632655774235255586516926464, 111503725992653115484705111730338528, 223007451985306230969410223460677056, 446014903970612461838820446921354112, 892029807941224923677640893842708224, 1784059615882449847355281787685416448, 3568119231764899694710563575370832896, 7136238463529799389421127150741665792, 14272476927059598778842254301483331584, 28544953854119197557684508602966663168, 57089907708238395115369017205933326336, 114179815416476790230738034411866652672, 228359630832953580461476068823733305344, 456719261665907160922952137647466610688, 91343852333181432184590427529493322176, 182687704666362864369180855058986644352, 365375409332725728738361710117973288704, 730750818665451457476723420235946577408, 1461501637330902914953446840471891154816, 2923003274661805829906893680943782309632, 5846006549323611659813787361887564619264, 1169201309864722331962757472377512932512, 2338402619729444663925514944755025865024, 4676805239458889327851029889510051730048, 9353610478917778655702059779020103460096, 18707220957835557311404118158040206920192, 37414441915671114622808236316080413840384, 74828883831342229245616472632160827680768, 149657767662684458491232945264321655361536, 299315535325368916982465890528643310722672, 598631070650737833964931781057286621445344, 119726214130147566792986356211457324288688, 239452428260295133585972712422914648577728, 478904856520590267171945424845829297155456, 957809713041180534343890849691658594310912, 1915619426082361068687781699383317180621824, 3831238852164722137375563398766634361243648, 766247770432944427475112679753326872248736, 1532495540865888854950225359506653744497472, 3064991081731777709900450719013307488994848, 6129982163463555419800901438026614979889792, 1225996432692711083960180287605322995977936, 2451992865385422167920360575210645991955872, 4903985730770844335840721150421291983911648, 9807971461541688671681442300842583967823296, 19615942922883377343362884601685167935646592, 39231885845766754686725769203370335871293184, 7846377169153350937345153840674067174258688, 15692754338306701874690310681348134445177376, 3138550867661340374938062136269626889035456, 627710173532268074987612427253925377807104, 1255420347064536155975224854507850755614208, 2510840694129072311950449709015701511228416, 5021681388258144623900899418031403022456832, 1004336277651628924780179883606280604491664, 2008672555303257849560359767212561208983328, 4017345110606515699120719534425122417966592, 8034690221213031398241439068850244835933184, 16069380442426062796482878137700489671866368, 32138760884852125592965756275400979343732736, 64277521769704251185931512550801958687465728, 128555043539408502371863025101603917374931456, 25711008707881700474372605020320783474986304, 514220174157634009487452100406415689497728, 1028440348315268018974904200812831379995552, 2056880696630536037949808401625662759991104, 4113761393261072075899616803251325519982208, 8227522786522144151799233606502651039964416, 16455045573044288303598467213005302079928832, 32910091146088576607196934426010604159857664, 65820182292177153214393868852021208371712896, 131640364584354306428787737704042416743425728, 26328072916870861285757547540808483348685152, 5265614583374172257151509508161696669737024, 10531229166748344514303019016323393391474048, 2106245833349668902860603803264678678294816, 4212491666699337805721207606529357356589632, 8424983333398675611442415213058714713179264, 1684996666679735122288483042611742942635872, 3369993333359470244576966085223485885271744, 6739986666718940489153932170446971770543488, 13479973333437880978307864340893943541086976, 26959946666875761956615728681787887082173504, 53919893333751523913231457363575774164347008, 107839786667503047826462914727151548328694016, 21567957333500609565292582945430309665738832, 43135914667001219130585165890860619331477664, 86271829334002438261170331781721238662955296, 172543658668004876522340663563442477325910592, 345087317336009753044681327126884954651821184, 690174634672019506089362654253769909303642368, 1380349269344039012178725308507539818607284736, 2760698538688078024357450617015079637214569472, 5521397077376156048714901234030159274429138944, 1104279415475231209742980246806031854857827888, 2208558830950462419485960493612063709715755776, 441711766190092483897192098722412741943151155328, 883423532380184967794384197444824883886302310656, 1766847064760369935588768394889649767772604621312, 3533694129520739871177536789779299535545209242624, 7067388259041479742355073579558599071090418485248, 14134776518082959484710147159117198142180836970496, 28269553036165918969420294318234396284361673940992, 56539106072331837938840588636468792568723347881984, 11307821214466367587768117727293758513744669576384, 22615642428932735175536235454587517027489339152768, 45231284857865470351072470909175034054978678305536, 90462569715730940702144941818350068109957356611072, 180925139431461881404289883636700136219914713222144, 36185027886292376280857976727340027243982942644288, 72370055772584752561715953454680054487965885288576, 144740111545169505123431906909360108975931770577152, 28948022309033901024686381381872021795186354115424, 57896044618067802049372762763744043590372708230848, 115792089236135604098745525527488087180745416461696, 231584178472271208197491051054976163561490832923392, 463168356944542416394982102109952326722981665846784, 926336713889084832789964204219904653445963331693504, 1852673427778169665579928408439809306891926663387008, 3705346855556339331159856816879618613783853326774016, 7410693711112678662319713633759237227567706653548032, 14821387422225357324639427267518474455135413071096064, 29642774844450714649278854535036948910270826142192128, 59285549688901429298557709070073897820541652284384256, 118571099377802858597115418140147795641083304568768512, 237142198755605717194230836280295591282166091337536024, 474284397511211434388461672560591182564332182675072048, 948568795022422868776923345121182365128664365350144096, 1897137590044845737553846690242364730257328730700288192, 3794275180089691475107693380484729460514656461400576, 7588550360179382950215386760969458921029312922801153216, 151771007203587659004307735219389178420586258456023024, 303542014407175318008615470438778356841172516912046048, 607084028814350636017230940877556713682345033824092096



# LITTLE AUTO TUNERS FOR LITTLE RADIOS

by Gordon West

One of the best signals you will put out and receive on high frequency (3 MHz-30 MHz) is with a well-elevated halfwave dipole. Each side of the dipole is one-quarter wavelength long, and the overall length of the dipole is half the wavelength you are transmitting on, based on the formula: length in feet =  $486 \div \text{MHz}$ . This is the overall length, end to end, with an insulator or balun in the center to separate each one-quarter wavelength section.

The halfwave dipole is probably the most economic way to get an excellent signal on the high-frequency bands; and if all you have is just one high point of attachment, you could haul up the center of the dipole and droop each end down at about a 45-degree angle which also improves transmission and reception off the ends of the dipole, too.

You may even "roll your own" feedpoint isolator by taking 10 turns of RG58A/U coax around a toilet paper cardboard center, and as long as you trim the dipole one inch at a time, you should be



**Gordo puts automatic antenna tuners and couplers to the sea water ground test.**

**The front and rear of the LDG antenna coupler AT-11MP.**



able to bring the SWR "dip" just about flat anywhere in the single-band operation.

You can even get 15 meters to play on a 40-meter-cut dipole. You may also get three additional lower bands of resonance on a single dipole feedline by fanning out different band half wavelengths below the lowest frequency band, such as 40 meters.

Another way to get multiple-band capabilities out of a dipole antenna system is to purchase multi-band dipoles, already rigged up with individual elements fanned down from the balun or going for a trap dipole. To see what these dipoles

look like, log onto [www.alphadeltacom.com](http://www.alphadeltacom.com) and [www.radioworks.com](http://www.radioworks.com).

Jim Thompson W4THU (at the Radio Works; 757-484-0140), has a terrific free catalog available on wire antennas, plus his popular book *Frequently Asked Questions About Antenna Systems*.

Well-elevated dipoles (at least one-half wavelength above the ground) are the benchmark for measuring gain improvement from beams, as well as comparative "almost as good as a dipole" measurements from vertically loaded antennas like mobile whips and base station trap verticals.

## Graphic Interface With Touch Screen



Graphic display  
Touch screen (optional) or 12x12 input matrix  
Serial communication (RS-232C)  
Eeprom or Flash for screen storage  
Only +5VDC power required (or 9-26VDC)  
Includes graphic controller board  
Easy to use development software  
Powerful friendly instruction Interpreter  
Create screens by PC paintbrush  
Holds 100's of "canned" graphic screens  
Simple to place touch buttons software  
Easy interface with PC/104, 8051, 68HC11, PIC  
Embedded Computer Controller Also Available

Easy Operator Interface  
through serial connection

**DesignTech Engineering Co.**  
2001 S. Blue Island Ave.  
Chicago, IL 60608  
Phone 312-243-4700  
Fax 312-243-4776  
[WWW.DESIGNTechENGINEERING.COM](http://WWW.DESIGNTechENGINEERING.COM)

## What's Under Your FT-817?

**Z-11 QRP Autotuner**  
Microprocessor Controlled  
LED Status Lights  
1.8 to 30 MHz  
.1 to 60 Watts  
Auto Sleep Mode  
+12 VDC Input  
Rugged Metal Case



LDG Electronics, Inc.  
1445 Parran Rd.  
PO Box 48  
St. Leonard, MD 20685

\$175 Assembled  
\$145 Kit and Enclosure



**Zero Power Draw  
Once Tuned!**

Latching relays hold the tune settings so power can be removed!  
Perfect for remote or backpack operation.  
Weights only 15 oz.

Toll Free Sales: 877-890-3003  
Support: 410-586-2177  
Fax: 410-586-3475  
E-Mail: [ldg@ldgelectronics.com](mailto:ldg@ldgelectronics.com)

See your favorite dealer or visit [www.ldgelectronics.com](http://www.ldgelectronics.com)



**Sea water makes antenna systems sound loud!**



## **AUTOMATIC COUPLERS HAVE THEIR PLACE**

The automatic antenna coupler is a several-hundred-dollar, active, antenna-loading tuner specifically designed to take as much of your transmitter power and impress it as RF current into your antenna wire. The automatic antenna coupler is a distinct separate box than what you may find built into the high-frequency ham radio transceiver as a "builtin auto tuner." The transceiver's builtin auto tuner may be more considered an "auto trimmer," resolving elevated SWR down to a minimum for full transmit power out. Most builtin automatic antenna tuners will handle SWRs of less than 4 to 1, but seldom over 5 to 1.

This is well described in *Your Guide To HF Fun*, just released by Dave Ingram K4TWJ, Birmingham, AL, available at most ham radio stores ([www.aesham.com](http://www.aesham.com)).

The fully automatic antenna coupler is usually a remote-mounted, active electronic "box" that gets hidden away near the antenna feedpoint aboard boats, up in attics, on the roofs of motorhomes, and in the tail of airplanes. The

**Only 6" water contact was needed for the tuners to work well.**



remote-mounted automatic antenna coupler relay-clicks in variable amounts of fixed inductors and fixed capacitors to maximize output current to the desired radiating wire. Aboard boats, this wire may be insulated rigging or plastic-covered wire hoisted to the top of the sailboat or power boat mast or superstructure. In an attic, the remote-mounted auto coupler could feed a wire that runs along the main beam. In airplanes, the remote-mounted coupler feeds a tail wire to the wing tip or a trailing wire, and in motorhomes, a wire that may run around the top of the vehicle.

But for the automatic antenna coupler to perform properly, it needs a low-resistance counterpoise and ground system below the tuner. For boats, copper foil temporarily tossed overboard or permanently connected to an underwater ground plate or metallic through-hull does the job nicely. For the attic antenna, the automatic remote-mounted automatic antenna coupler may use water pipes, aluminum ducting, or chicken wire lining the inside walls as an effective ground system. Airplanes and motorhomes may use the body as a ground.

We recently tested automatic antenna couplers from both SGC, Inc. ([www.sgeworld.com](http://www.sgeworld.com)) and a brand new, non-remote mounted tuner from LDG Electronics ([www.ldgelectronics.com](http://www.ldgelectronics.com)). We

chose to test these two lines of automatic antenna couplers because they will work with any high-frequency transceiver without data start and stop tune commands, and both companies produce several different versions of their automatic antenna couplers that will work with the new, exciting, low-power transceivers like the SGC 2020, Yaesu FT-817 (all the way down to one watt), and other high-frequency QRP transceivers from Elecraft, MFJ, Sierra, and Ten Tec.

I decided to test these tuners in a common sailboat maritime mobile configuration where the mariner had insulated a mast supporting stay giving us over 65 feet of unobstructed, almost-vertical radiation. Our ground system would consist of four options — the embedded copper foil ground in the hull (not touching sea water), a second ground system made up of the boat's internal metal tanks with a very long wire run to the sea water, and our third and fourth temporary grounding systems of 3" wide, 3-mil, copper foil that we would temporarily toss over the stern end of the boat. We would use a modified Alphadelta switch to rapidly change over the different ground systems, re-tune, and then see what type of skywave reports we would obtain from other stations thousands of miles away.

The capacitive ground system made all of the tuners hunt and hunt for a proper tune lock. Neither of the two capacitive ground systems inside the hull would generate enough current in the insulated backstay to show a good, strong meter reading with our MFJ antenna current probe, nor any real brilliance on a florescent tube held next to the antenna output wire.


But when we switched over to our copper foil hanging 30 feet underwater to the muddy bottom, antenna current immediately jumped up, the florescent tube glowed brightly, and the distant skywave stations said that our signal went from almost unreadable on the capacitive ground plane to signal strength seven on the sea water direct ground connection. We could also hear the difference on receive, too. The capacitive ground system gave us plenty of noise, but the sea water ground dropped on the onboard noise, and peaked the signal coming in from stations thousands of miles away on several high-frequency ham bands. The automatic antenna couplers were also much faster in their lock up to the sea water ground.

The final test was to see how much sea water contact we needed to achieve strong signal reports, minimum onboard noise pick-up, strong antenna current on the antenna, and a bright florescent tube. Our test would involve switching to the fourth copper foil hanging only four inches in the sea water. Guess what? There was virtually no change in performance as long as our copper foil ground was making just four inches of contact with the sea water. We have seen this phenomena many times — a single copper foil ground to a conductive surface like sea water, vehicle frame, and apartment chicken wire does the grounding trick completely without 1/4 wavelength radials needed.

We repeated the twin foils test several times — one foil ground over 30 feet into the sea water, and the other foil ground just inches below the sea water surface. Signal reports were identical. The tuner would not change tuning steps between the two as further proof that the tuner could not sense four inches of sea water grounding, or almost 40 feet of sea water grounding with 3" wide copper foil.
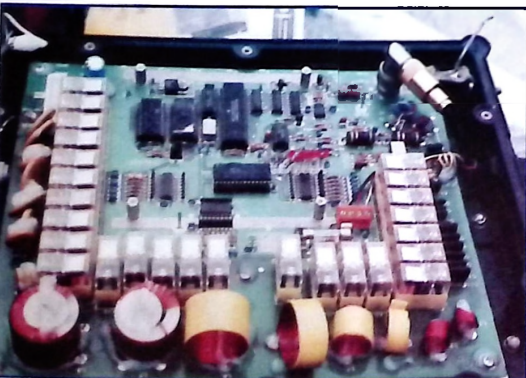
## **ANTENNA COUPLER DIFFERENCES**

We have worked for years with the SGC automatic coupler — SG-230 — in both marine, mobile,




**SGC automatic remote-mounted antenna coupler — inside view.**





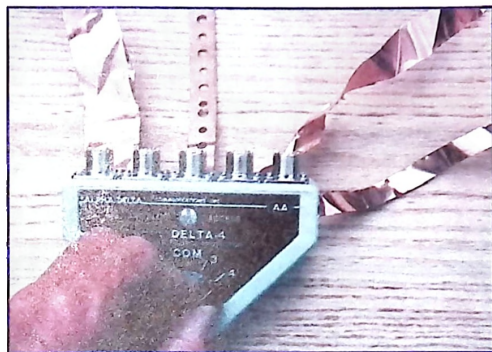**Radio pioneer Art Godson W7AEG verifies tuner output current over sea water ground.**



**Testing how well each tuner worked with different marine ground systems.**

and aeronautical mobile applications. The SGC-230 can handle up to 200 watts of power, and will even let it tune very small three-watt transceivers like the Yaesu FT-817. But this is a big box — and is designed specifically for permanent installation, inside or outside. It is fully waterproof.

SGC now offers the dramatically smaller but fully waterproof Model 237 fully automatic antenna coupler, designed for fixed, portable, and weather protective applications. Like the larger SG-230, the SG-237 series outputs to an active long-wire antenna or the mounting of a portable whip antenna. They also offer the SG-231 slimmer version that might also work up to the amateur radio six-meter band.

Most recently, SGC brought in the SG-239 fully automatic antenna coupler, designed for any application mounting but the need for keeping rain or snow from getting into the exposed circuit board. The exposed section of the circuit board offers little tiny micro switches, push-button style, to manually accomplish the tuning process that is normally done fully automatically. There are literally hundreds of combinations that may be push-button controlled, and the SGC website shows them all.

All of the SGC automatic antenna couplers tuned up our sailor's insulated backstay with just three watts of power, the Yaesu FT-817, plus several other rigs including the SGC-2020, and we really couldn't tell any major difference on both transmit and receive. But I would assume that the

physically larger SGC-237 tuner will run cooler and never are over during prolonged periods of transmit running PSK-31 or FACTOR II. With the physically smaller sized SGC couplers, I would suggest their use with low- or medium-power transceivers that won't necessarily exceed 150 watts output.

We then began testing a new line of automatic antenna couplers/tuners from LDG Electronics. We first tested the LDG Z11, an 1.8 MHz to 30 MHz device that works all the way down to one-tenth of a watt output and up to about 30 watts continuous, 60 watts peak. This tuner would be ideally suited for the new breed of QRP transceivers, not necessarily your big HF marine or ham set that typically puts out in excess of 100 watts plus.

The LDG Z11 was found to be extremely frugal on current consumption, going into a low-current mode of only .0079 amps after tune up. And sure enough, as soon as we gave the unit some forward power, the relays immediately began whirring and the green light-emitting diode blinked on showing tune with low SWR.

The Z11 is not intended for remote mounting as all the SGC automatic couplers. The LDG Z11 mounts by the equipment, and to start the tuning process, you transmit a continuous carrier and press the tune button. If you press the button with your equipment still in receive, you hear a momentary burst of

## Two Step Tuning

### Step One: Pick up microphone.

### Step Two: Transmit.

(Please note: HF Tuning doesn't get much easier than this.)



## SGC Smartuner™

### HF Automatic Antenna Couplers

"For me and my radio dollar, there isn't a better coupler made!"

Jack Hueschen N9XR0

**Power Input: From 1.5W - Up to 500W\***  
**HF Frequency Range: From 1MHz - Up to 60MHz\***  
**Up to 4,000,000 element combinations\***

**Five Sensor Devices**

\*Spec differ per model

"Undoubtedly the best piece of hamgear I have ever owned."

Rennie Kane N9MST

**Marine, Commercial, Amateur Radio,  
Aviation, Special Applications**

# Starting at \$249



[www.sgeworld.com](http://www.sgeworld.com)

Toll Free (800) 259-7131 • Tel (425) 716-6310 • Fax (425) 746-6384 • Email: [sgc@sgeworld.com](mailto:sgc@sgeworld.com)

Mailing: PO Box 3526, Bellevue, WA 98009 • Shipping: 13737 SE 26th St. Bellevue, WA 98005 USA

Circle #28 on the Reader Service Card.


noise in your receiver, and this is a good indicator for you to know you must first transmit the steady carrier and then push the button.

Since the LDG Z11 is at the equipment, not the antenna feedpoint, you are not only tuning the antenna, but also a portion of the coax feeding the antenna. LDG recommends a 4-to-1 or 6-to-1 balun between the antenna and tuner to facilitate


### Little low-cost LDG Z-11 auto tuner.





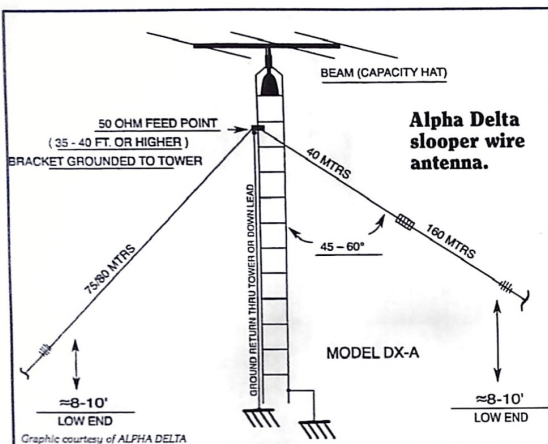

### Alpha Delta slooper wire antenna.

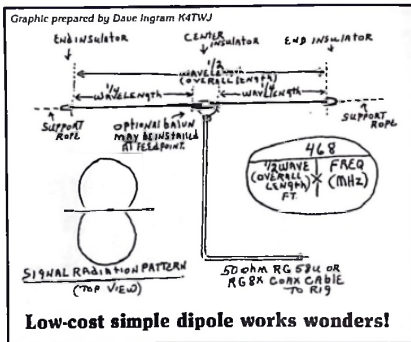

### Low-cost simple dipole works wonders!

the tuning process without putting an over amount of current onto a radiating feedline. We did find that transmit did cause some interesting squeaks and glows in the sailboat instrument panel, but we noticed our feedline was running relatively close to the panel, so we suspect it was a little bit of stray RF getting onto some of the ship's wiring.

The front panel of the Z11 has all sorts of switches so you may manually cycle the tuner into different combinations of inductance and capacitance for the best match.

We also tested the new IDG AT-11 MP automatic tuner with a built-in cross needle SWR bridge. This tuner also features coax output as opposed to a single-wire output featured on SGC automatic couplers. This means the AT-11 MP is placed right next to the equipment, and again it is recommended that a balun be installed at the feedpoint to improve performance. I might also recommend the Radio Works line oscillator to go at the feedpoint in maritime installations for both the Z11, as well as the AT-11.

The LDG AT-11 MP handles more power — up to 150 watts, using relays to configure 256 capacitors and 256 inductors and high-low impedance settings to provide over 130,000 tuning combinations. Most of our reviewers liked the cross needle S-meter and said it really gave them a good idea on how well the automatic antenna tuner was finding matches. We used the cross needle SWR meter

would influence the tuner on different bands without the tuner automatically seeking a different combination of L and C.

An interesting feature we found was capabilities to tie this equipment into an ICOM 706. This would allow the ICOM tune button to switch over to CW, transmit 10 watts, and start the AT-11 MP tuning cycle. There are also capabilities of hooking in a speaker to jack 4 and audio feedback will provide an indication of SWR level. The feedback is a series of one to five beeps where one beep is low SWR, and five beeps indicates SWR above three. For the visually impaired ham, this might be a nice feature although any one of the push-button tuners could allow an operator to simply manually tune and listen to the amount of background noise. That was a nice touch with the audible feedback.

There is even a remote-control head that may be attached to the AT-11 MP. The remote hooks up via a nine-conductor shielded cable with a female dB-conductor at each end. This could let you get the tuner closer to the antenna feedpoint.

Both the SGC, as well as the LDG automatic antenna couplers require 12 volts. For those of you running on batteries with the FT-817 or SGC-2020, power consumption is of primary importance to you, so you may wish to log onto both SGC, as well as LDG websites and see which automatic coupler is going to draw the least amount of power.

We didn't see much difference on our MFJ antenna current meter when we went to an auto coupler that was remote-mounted at the feedpoint to the LDG coupler that mounts by the equipment. We did find that the remote-mounted SGC auto couplers gave us less interference to our onboard ship wiring — but for a home station, chances are you wouldn't see the effects of elevated SWR on the feedline.

No doubt there will be great discussions between SGC and LDG on what type of tuning method is best — 50-ohm output, or a single-wire, high-voltage output right at the feedpoint. Weatherproofing is another consideration, and both SGC, as well as LDG are factory serviced in the United States for USA factory service.

Chances are we're going to see more emphasis on relatively small automatic antenna couplers for the new breed of QRP transceivers. But keep in mind, as trick as automatic antenna couplers are, the homebrew dipole, cut to frequency, takes no additional antenna current and is a fun way to work DX from an antenna system you really feel good about because you designed and built it yourself.

But in special applications like maritime mobile, aeronautical mobile, or when you have a single wire with multiple bands of necessary operation, automatic antenna couplers that tune well beyond the capabilities of built-in automatic antenna tuners are a logical choice. NV

*Next month: HF Antennas Shootout. How much better are bigger coil mobile antennas?*

## Amazing ... \$125

### TICKit 63 Getting Started Package (T63H256K-GSP)

Prototyping laboratory includes: Win 9X IDE software, power supply, download cable, 830 hole solderless breadboard, RS232 interface, PCAT interface, 32K EEPROM (up to 256K), TICKit 63 FBASIC micro-interpreter, Tons of I/O ability. If you like Parallax's Stamp, you'll love this.

www.protean-logic.com

**Protean**  
LOGIC Inc.

(303) 828 9156  
FAX: 828 9316



**FBASIC Controller**

## PROGRAMMABLE SOLENOID

- Low cost motion control
- Wide operating voltage (12 - 28)
- Onboard programming and parameter storage
- Self-contained electronics

### Rotary (PPS-1)



\$95.00 + \$5 s/h

### Linear (PPS-2)



\$145.00 + \$5 s/h

- Simple connection only 3 wires: Power, Ground, and CMD signal
- Long Life: Brushless ball bearing stepper
- Constant current Torque/Force

The brand Programmable Solenoid (PPS) delivers the motion capability of a sophisticated stepper motor system with the simplicity of a solenoid. This eliminates the run time and erratic latching motion of a traditional solenoid. The electronics of the PPS allows the user to program and store the desired motion profile using the simple user interface. The innovative PPS gives programmability to the motion of a solenoid without the expense of a costly motion control system.

## PICARD INDUSTRIES

Specializing In Miniature Smart Motors and Sensors

4960 Quaker Hill Road  
Albion, New York 14411

Phone/Fax 716-589-0358

Email: jcamdep4@iinc.com  
www.picardindustries.com



# New Books

## Electronic Servicing and Repairs

## Electronic Servicing and Repairs


(3rd Edition) by Trevor Linsley

This is a new edition of the successful *Electronics for Electricians and Service Engineers* and completely updates the previous text by taking into account the recent changes in the C&G 2360 (now 2351) and 2240. The new edition also incorporates hardware topics from the popular course, C&G 7261 Information Technology making this an indispensable reference for all those taking C&G courses.

'Electronic Servicing and Repairs' includes an expanded chapter on testing and fault diagnosis, incorporates PLCs and CAD software and introduces automatic test equipment (ATE). Communication and security systems are completely updated — the section on TV receivers, satellite TV, VCRs, CD players, and cable TV has been expanded and a new chapter has been devoted to alarm systems.
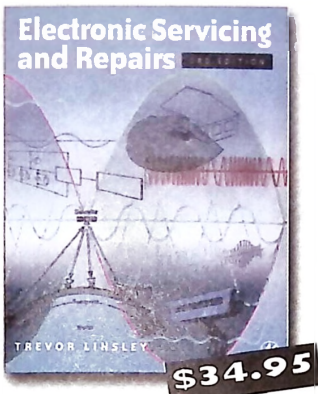
### Contents

Health and safety • Electronic component recognition • Electronic circuit assembly techniques • Electronic semi-conductor devices • Electronic circuits in action • Testing electronic circuits • Digital electronics • Electrical circuit theory • Electronic systems • Communication systems • Security systems • Sensors and transducers • Appendices • Glossary.



## Beginning Digital Electronics Through Projects


by Andrew Singmin

Beginning Digital Electronics Through Projects provides practical exercises, building techniques, and ideas for over 35 useful digital projects. Some digital logic knowledge is necessary, but the theory is limited to "need-to-know" information that will allow you to get started right away without complex math. Many components in this text are common to either analog or digital electronics, and beginners or hobbyists making their start here will find an overview of commonly-used components and their functions described in everyday terms.

Each of the projects builds on the theory and component knowledge developed in earlier chapters, establishing progressively more ambitious goals. Step-by-step learning instructions help you determine the best ways of working with such projects as Schmitt Trigger Circuits, Versatile ICs, Digital Support Circuits, and much more. Two interesting wireless projects (an FM receiver and an FM transmitter) bring the final chapters of this book to a close.

ANDREW SINGMIN
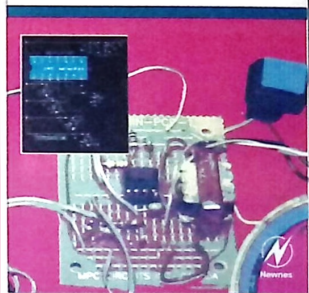
## BEGINNING DIGITAL ELECTRONICS THROUGH PROJECTS



*All of this month's books are published by Newnes Press and are available from the Nuts & Volts bookstore.*

online - [www.nutsvolts.com](http://www.nutsvolts.com)  
phone - 1-800-783-4624

## Microcontroller Cookbook

(2nd Edition) by Mike James

Microcontroller Cookbook guides you through programming, interfacing, development work, and circuit design using two of the most popular microcontroller families. The cookbook approach makes this an ideal book for anyone who has to get up and running quickly, so it is ideal for hard-pressed professionals and advanced electronics hobbyists. Enough theory is included to make this a suitable text for introductory microelectronics courses up to first-year degree level. New sections of reviews make this an ideal text for courses or independent study.

### Contents

Preface; Number systems; Programmable logic design; Memory systems; Input/output systems; Problem analysis and design; Text editor/assembler/linker operation; MCS51 hardware; MCS51 software; PIC hardware; PIC software; Development systems; Microcontrollers Vs SBC; Compilers; Problem solving in C; Index.





# Electronics Showcase

Special products and services for the electronics enthusiast.

Books, Controllers, USB, Stamp, CNC, PC Boards, Security, Kits, Robotics, CAD, and More!

Special  
Advertising  
Section!

**TSC International**  
In business 25+ years - established professionals  
**www.tsc-global.com**  
Exciting Hi-Tech Survival Books, Manuals, Tapes  
Polygraph Secrets \$29 Stopping Power Meters \$29  
PCW-HRM Meters \$29 Bey and Van Eck Tennaet \$29  
Car & Water Security \$199 Tapes (SPM, Van Eck) \$199  
Voice Mail Security \$29 Identity Theft Manual \$29  
Pager (Beeper) Manual \$29 Internet Frauds DataBook \$29  
PBX Security \$29 Internet Tracking/Tracing \$29  
Fax Machine Security \$29 Internet Security: Cookie Term \$29  
Credit Card Security \$29 Bey and Phone Color Boxes \$29  
ATM Manual \$39 Caller ID & ANI Security \$29  
Internet Security \$29 CallPhone/Cellular Guide \$39  
EM Brainblaster \$29 Virus Control: Under Attack! \$29  
High Voltage Devices \$29 Radios Manual: Real Threat! \$29  
Health Technology \$29 Social Engineering \$29  
Check, MO, VISA, MC, S-H, S6 USPS, \$9 UPS or Canada  
Printed Catalog: \$1 w/ order, \$3 w/o (descriptions, policies)  
Order Today!  
P.O. Box 23097, ABQ, NM 87192  
(505) 321-1034, 292-4078 Fax: 275-5637

**Vesta Technology, Inc.**  
Control in Power  
**SBC2000**  
**Low Cost Controllers**  
8bit, 16 bit, 32 bit controllers  
Multiple Interrupts, 6551 Time Clock  
Watchdog, Timer, Sleep Mode  
Digital I/O, and A/D  
Program in C/C++ or Assembler,  
or with Vesta's fast and easy  
embedded Basic language with  
full-featured development environment  
Fast, Flat-Rate Electronic Prototyping  
available for qualified OEM customers  
Pricing and data sheets  
available on the web  
11468 W. 46th St., Albuquerque, NM 87133  
**www.vestatech.com**  
Phone (303) 422-6088 - Fax (303) 422-8800

**ELECTRONIC & PRODUCT DESIGN  
PROTOTYPING & CONTRACT ASSEMBLY  
PROGRAMMING**  
We're small to serve your small business better  
Hardware Services from concept through production:  
Design, Schematic capture, PCB Board layout  
Programmable logic definition Prototyping; Debug  
Contract Manufacturing: Consigned (you provide  
the parts, we assemble); Turnkey (we do everything);  
Surface mount and/or through-hole  
Programming: Microprocessor; PLC Controllers;  
Custom software including Stand-alone programs,  
Database  
**Metrix Technology Corporation**  
845 897 4960 or 877-METRIX  
**www.metrix.com**

**QUALITY KITS**  
SOLAR PANELS, Multimeters, Calipers,  
Oscilloscopes, Camera Modules, PIC & ATME  
Programmer Kits, Relay Cards, Electronic Lab  
Ess, RF CodeLock Kits, Computer Interface Kits,  
Strobe Lights, and much more ...  
Toll Free Order Line:  
**1-888-GO 4 KITS**  
Secure On-Line Ordering  
**www.qkits.com**  
Call 613-544-6333  
for free catalog  
49 McMichael St., Kingston, ON  
K7M 1M8, CANADA

**PC Robotics!**  
Programming and controlling your robot is as easy  
as programming and using your PC. Make your  
robot a PC on wheels (or legs). Use Basic, Java, C,  
C++, or any programming language you choose.  
Inception Systems makes it easy with:  
Embedded PC's  
Servo & Motor Controllers  
Power Supplies and Converters  
High Powered Batteries  
Robots & Chassis  
Sensors and more!  
http://www.inceptionsystems.com  
Inception  
Systems  
Incorporated  
Embedded  
PC's  
Linux  
Shop  
Online!

**Electronics Manufacturing  
Technology** a div. of Ledvision  
**EMT** ISO-9001  
Compliant  
**www.pcbboardinc.com**  
**Bare Printed Circuit Boards**  
• Design & Layout  
• Single, Double & Multi-Layer  
**Automated Assembly**  
• SMT & Thru-Hole  
• Prototypes Thru Production  
• Product Engineering  
• Final Assembly & Test  
303 Sherman Ave., Ackley, Iowa 50601  
(641) 847-3902 Fax: (641) 847-3889  
sales@pcbboardinc.com

**PCBexpress**  
**www.pcbexpress.com**  
• No tooling charge!  
• Lot charges start at \$80  
• Simple order process  
• Quickturn, low quantities  
**TWO SERVICES FOR  
CIRCUIT BOARDS**  
**ECD**  
**www.pcbpro.com**  
• Quick price comparisons  
• More options & added features  
• Prototype & production quantities  
**INSTANT  
ON-LINE QUOTES!**  
(NO SIGN-UP REQUIRED)  
For a  
discount  
on your next  
order enter the  
code: IV3672

**CABLE TV REMOTES  
BLOW-OUT SALE**  
We carry all models  

10pc.	50pc.	100pc.
\$3.75	\$3.50	\$3.25
300pc.	500pc.	1kpc.
\$3.00	\$2.75	\$2.50

  
**Rebellion-3 125ch. Converter**  

12pc.	50pc.	100pc.
\$50.00	\$48.00	\$46.00

  
**Globaltech 1-(800)-582-5116**  
View our On-Line Display Catalog at:  
**www.globaltechdistributors.com**



**\$39.95**

**PROGRAMMING AND CUSTOMIZING THE BASIC STAMP COMPUTER**  
2nd Edition

200 illus., 334p.  
by Scott Edwards

**Order from the Nuts & Volts Bookstore**

**1 800 783-6624**  
[www.nutsvolts.com](http://www.nutsvolts.com)

See our ad on page 92.

**Press-n-Peel Transfer Film**  
**PC Boards in Minutes**

8.5" x 11" Shts.  
\*Or Photocopy  
\*\*Use standard household iron

1. LaserPrint\*
2. Press On\*\*
3. Peel Off
4. Etch

Use Standard Copper Clad Board  
20 Shts. \$30/ 40 Shts. \$50 / 100 Shts. \$100  
Visa/MC/PO/CK/MO \$4 S&H/Foreign Add \$7

**Techniks Inc.**  
P.O. Box 463, Ringoes NJ 08551  
ph. 908.788.8249 fax 908.788.8837  
[www.techniks.com](http://www.techniks.com) Visit Our E-Store On-Line!

**componentkits.com**  
your source for component engineering kits

**We STOCK kits on ALL of the following components:**

- Resistors
- Capacitors
- Attenuators
- Microcontrollers
- Crystals
- Voltage Reg's.

**Over 27 different kits available, ready for immediate shipment!**

**Order online at our secure checkout:**  
[www.componentkits.com](http://www.componentkits.com)

**What do you want to build, today?**

**5 Axis Control 34.95**



Serial and Ethernet Stepper & Servo Controllers  
Keyboard Wedges Animatronics Controllers  
Ethernet to Serial Interfaces and Robots  
The Mercury Group - Loveland Colorado  
978-278-1007

**www.CHAPP.com**

**MATCO, INC**  
**EverSecure™**  
[www.matco.com](http://www.matco.com)

- Manufacturer of OEM Security Products
- Monitors, Camera-Mounts, Cables
- Law Enforcement Equipment
- Discreet Wireless Systems (589-5269)

**End of Summer Specials!**

Canada: (877) 720-9222  
Fax: (847) 303-0660

Sales: (847) 303-9700  
Toll Free: (800) 719-9605

**HVV TECHNOLOGIES**  
HIGH-TECH SOLUTIONS TO HIGH-TECH PROBLEMS

**BASIC Stamp™ Prototyping Made Easy...**



Stamp Stacks™ mount directly on any breadboard to make prototyping easy. Complete - just assemble, connect power and a serial cable - 100% BASIC Stamp™ compatible. Robust, Repairable, Inexpensive. Starter kits available.

PC Computers/Programmers/Protoboard Serial LCDs IR Ranging Sensors...

**HVV Technologies Inc.**  
Tel. (403) 330-8803  
Fax. (403) 330-8803

**VISA/MC Accepted**  
[www.HVVtech.com](http://www.HVVtech.com)

**CONTROL • MEASURE • INPUT**

**MODEL 40-\$109**

- RS-232 Interface
- 28 lines digital I/O
- Eight analog inputs
- PWM output
- Three stepper ports

**MODEL 100-\$279**

- 12-bit 100KHz A/D
- Four analog outputs
- Three timer counters
- 24 digital I/O

**PRAIRIE DIGITAL, INC.**  
920 SEVENTEENTH ST., INDUSTRIAL PARK  
PRAIRIE DU SAC, WI 53578  
TEL: (608) 643-8599 • FAX: (608) 643-6754

**ASSEMBLY & ENGINEERING**

**Producible designs since 1970**

**Contract Assembly**

Embedded Microprocessors  
PCB Layout & Packaging Design  
Analog Including RF to 1 GHz  
Instrumentation  
A/D and D/A

**Contract Assembly**

High-Speed Full Surface Mount  
Through Hole  
Turn-Key or Kit  
Run Sizes one through thousands  
Test and burn-in available

**Bilcor Corp.**  
800-715-5727  
413-351-2276  
[www.bilcorp.com](http://www.bilcorp.com)

**PRINTED CIRCUIT BOARDS**

**QUALITY PRODUCT  
FAST DELIVERY  
COMPETITIVE PRICING**

10 pcs (3 days)  
1 or 2 layers **\$249**  
10 pcs (5 days)  
4 layers **\$695**  
(up to 30 sq in ea.) includes tooling, artwork, LPI mask & legend

**PULSAR, INC.**  
9901 W. Pacific Ave.  
Franklin Park, IL 60131  
Phone 847.233.0012  
Fax 847.233.0013  
Modem 847.233.0014

**PROTOTYPE THROUGH PRODUCTION**

**We will beat any competitor's prices!!!**  
yogil@flash.net • flash.net/yogil

**For Sale**

**3052 Spectrum Analyzer**

Plus microwave, vacuum pumps, lab, robots, and many other items!!!

**Always Buying & Selling, Send list!!**

[www.westshoretech.com](http://www.westshoretech.com)

**ActiveWire® USB Simple USB Interface!**



- Works with MacOS 9.0, Win98/NT/ME
- Free HSD and Linux!
- 24MHz CPU core with USB
- Firmware downloadable via USB
- 16 bit parallel Input/Output
- See web site for add-on boards
- All drivers, manuals, demos are on our web-site for immediate download!

**\$59**  
plus shipping

**ActiveWire, Inc.**  
[www.activewireinc.com](http://www.activewireinc.com)  
ph +1.650.493.8700 x203 fax +1.650.493.2200



# Electronics Showcase

Special products and services  
for the electronics enthusiast.

Special  
Advertising  
Section!

## PCB EXPRESS, INC.

### "PROTOTYPE TO PRODUCTION"

S/SIDED: 5-days, 10 Pcs.	\$275.00
D/SIDED: 5-days, 10 Pcs.	\$300.00
D/SIDED: 5-days, 10 Pcs.	\$350.00
4-LAYERS: 7-days, 10 Pcs.	\$750.00
4-LAYERS: 5-days, 10 Pcs.	\$850.00
6-LAYERS: 7-days, 10 Pcs.	\$950.00
6-LAYERS: 5-days, 10 Pcs.	\$1,175.00

### "SERVICES" — UL Approved

SMOBC, LPI mask & Legend • Photoplotting,  
Electrical Testing • Thru hole/SMT, Gold/Nickel  
Plating • Routing and Scored Panel, Instant Quotes

PH: (888) 427-2920, Fax (847) 427-1949

E-Mail: [cir1920@aol.com](mailto:cir1920@aol.com)

**LOWEST COST & FAST DELIVERY**

## IC PROGRAMMERS

ADVANTECH EETOOLS NEEDRAMS DATA TO 8P MICRO  
XELTEK SYSTEM GENERAL ICE TECHNOLOGY CHROMA

1295 Advantech Labtool-48  
895 Needham EMP-30  
869 EETOOL Togmas  
450 Xeltek SuperPro III  
629 ICE Tech Micromaster IV  
469 Xeltek SuperPro F  
419 Needham EMP-20  
419 EETOOL MegaMax  
379 Xeltek SuperPro LX  
299 EETOOL ChipMax  
279 Xeltek Rommaster II  
209 Needham EMP-10  
Gang Programmers 4 TO 8 Sockets  
CALL Advantech Labtool-848 8XGang  
1055 EETOOL TopMax W/8XGang  
689 Needham SA-20 8XGang  
529 EETOOL MegaMax 4XGang



LABTOOL 48



LABTOOL 848

### General Device Instruments

Sales 916-393-1655 Fax 916-392-4949  
Order Only Toll Free 800-760-3820

[WWW.GENERALDEVICE.COM](http://WWW.GENERALDEVICE.COM) • [WWW.LABTOOL.COM](http://WWW.LABTOOL.COM)

## LedVision Holdings, Inc.



### Scrolling L.E.D. Signs

- Wireless Keyboard
- Includes Windows Software
- Text & Graphics
- Super Bright Multi-Color
- Clock Functions & Scheduler
- Real Time (ASCII) Mode
- 16K Flash Memory
- RS-232 & RS-485 Serial Ports

303 Sherman Ave., Ackley, Iowa 50601

(641) 847-3902 Fax: (641) 847-3889

[sales@ledvision.com](mailto:sales@ledvision.com)

[www.ledvision.com](http://www.ledvision.com)

## CABLE CONVERTS

TV86/3	86/CH	TV86/3V/A
TRIVISION	550/3	\$37.95
VIEW MASTER	2600	
125 CHANNEL UNITS		
TRI 860/3	10 LOT	\$49.95
TRI 860/3V/A	10 LOT	\$59.95
V/MASTER	3800/3V/A	

### FOSS WAREHOUSE DIS.

289 SCIENCE ST. N. TONAWANDA, NY 14120

800-473-0506 • 800-488-0525 FAX

716-694-6400 716-693-4322 FAX

E/M FOSS@BUFFNET.NET

WEB PAGE: [WWW.FOSSW.COM](http://WWW.FOSSW.COM)

NO DESEMBLERS ONLY CABLE CONVERTS

# Computer Desktop Encyclopedia


Experience it today at the Nuts & Volts Web Site.

**For Experts and Novices** — The Encyclopedia contains more than 15,000 definitions, illustrations, photos, charts and diagrams, and covers the field from micro to mainframe.

**Everyone Needs This** — You can't escape computer and telecom lingo in this day and age. The Encyclopedia covers only the high-tech world, but makes it interesting for everyone.

**Twenty Years in the Making** — Starting as The Computer Glossary in 1980, the Encyclopedia is the longest-running computer dictionary. Edited by Alan Freedman, noted computer lexicographer with 40 years of experience in the industry, the Encyclopedia is the most comprehensive reference of its kind.

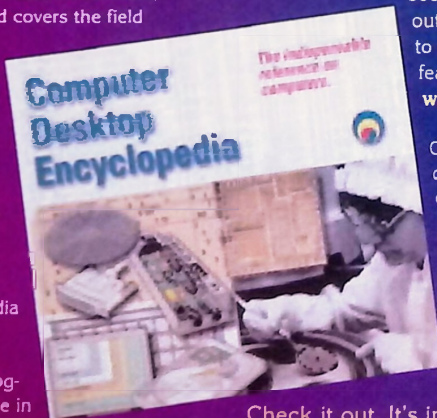If computer terminology or high tech mumbo jumbo seems to leave you on the outside looking in, you need to check out the latest new feature available now at [www.nutsvolts.com](http://www.nutsvolts.com)



Our new computer encyclopedia will have you up-to-speed on everything to do with computers, in nothing flat. As our lives become more integrated with and dependent on technology, this great resource will help you understand the concepts that drive this technological explosion.

Check it out. It's informative, it's here now, and it's brought to you free by Nuts & Volts.



# Build Your Own Universal LCD Interface

Those of us who are a little older will remember the seemingly magical dawn of digital display devices several decades ago. The first digital voltmeter I remember seeing actually had rows of incandescent lamps numbered 0-9 for each decade of the digits! Then, it began with the seven-segment LED readouts and has progressed to the multiple-sized LCD displays of today. And it really gives a professional appearance to any project you might come up with.

A quick look at almost anybody's surplus or electronics catalog will reveal some real bargains out there in LCD displays. The only problem is that an interface is required. The modules typically require set-up and configuration commands to be sent to the device to ready it for operation. And the interface is normally eight-bit parallel with several control lines to boot. So that could stifle the average user a bit ... until now.

What I've come up with is a simple serial interface that includes the most often desired features, as well as simplicity of use. Designed for use with one line by eight character LCDs all the way up to two lines by 40 character LCDs, the interface pretty well covers all the displays out there. Along with two different versions to operate at either 2400 baud or 9600 baud in a standard 8N1 format ... depending on what your speed requirements are.

And only two software commands to simplify control ... a carriage return (Control-L which is ASCII code 12) to clear the display and a line feed (Control-M which is ASCII code 13) to reposition the cursor to the beginning of the second line. So, if you've been looking for a way to really jazz up your next project ... here it is! I think you'll find it's just what you've been looking for ...

## What makes it universal?



Good question. Most LCD displays available to the general public (and hobbyists, in particular) are based on the Hitachi HD44780 LCD interface chip. Since these displays use the same protocol based on this IC, it's possible to make a universal interface that works well with many different displays. And there's some other commonalities, as well.

LCDs are alpha-numeric and display a full range of characters known as ASCII, which stands for American Standard Code for Information Interchange. Based on an eight-bit code (that's why they have eight data lines), the displays

*Visual display devices are an integral part of electronics in this age.*

will show numbers, letters in both upper and lower case, and graphics characters. Since the codes for the numbers and letters (as well as the control codes) are universal, we know that sending the proper code will always generate the proper character.

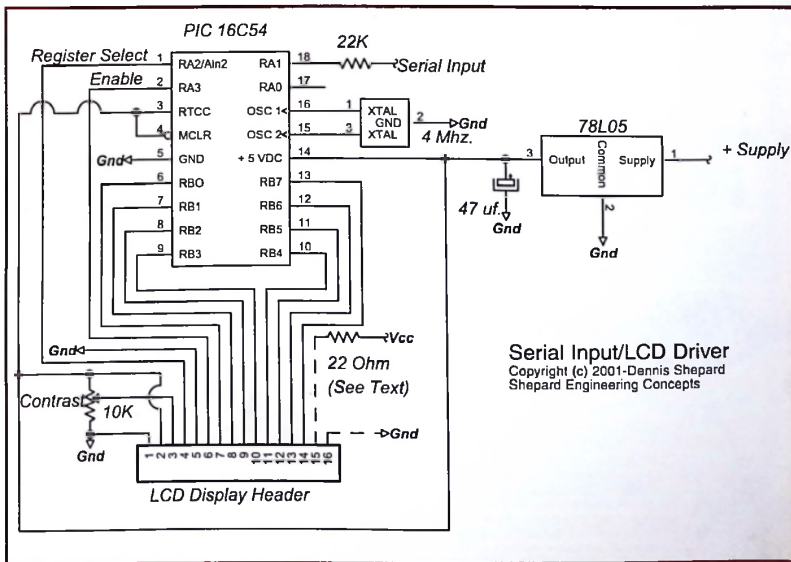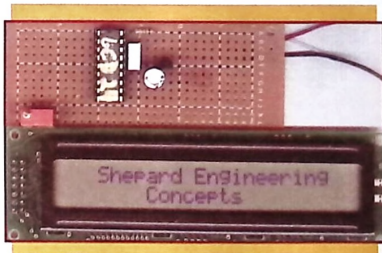LCDs are always set-up with 80 memory locations. Since we have configured the set-up procedure for two-line displays, the first line goes from memory locations 1-40 and the second line starts at memory locations 41-80. So, if you've got a 2x40 LCD display, you can see all 80 locations at once. We'll go into this





*What I've come up with is a simple serial interface that includes the most often desired features, as well as simplicity of use.*


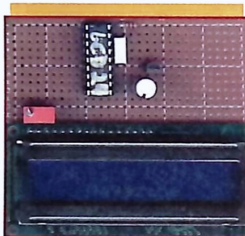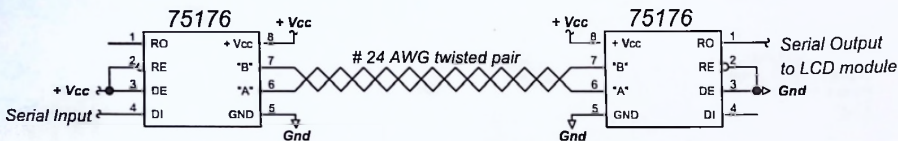
# Universal RS-485 Serial Link Interface

Copyright (c) 2001-Dennis Shepard/Shepard Engineering Concepts



Then we change the I/O lines to outputs and set the Register Select and Enable lines low.

This puts the display in command mode. The display is then programmed for eight-bits, x 7 format, second line on and enabled by toggling the enable line high and low again. Next, the display is turned on and the enable line is toggled. Finally, the display is cleared and the enable line is toggled again. Now, we set the Register Select line high, and we're in the data mode of operation and we're ready to do something.

## The dreaded numbers game

Well ... it's not really that bad! If you'll recall, we discussed earlier about how all LCD modules have 80 memory locations. But unless you've got a 2 line by 40 character display, you're going to reach a point where you send characters to the display and nothing shows up. We're about to solve that mystery right now!

For example, a two line by 16 character LCD display will use memory locations 1-16 for the first line. If you keep sending characters,

more later, but I wanted to touch on it here as part of the standard which LCD manufacturers follow.

LCD displays have great advantages over LED displays in several ways. When was the last time you saw an LED watch or calculator? LCDs use less power, generate less heat, and are easily viewed in many different lighting conditions. Some LCDs have backlighting, which allows them to be viewed in darkened environments! And most LEDs are limited to a seven-segment readout, which limits you to numbers only.

## Initializing the display

This is where it gets interesting. Besides the

eight data lines, LCD modules will also have three other control lines. There's an R/W line, a Register Select line, and an Enable line. The Read/Write line is grounded in this project since we're not interested in reading any information from the LCD. The register Select line allows us to switch from command mode to data mode. And the Enable line determines when the LCD display receives the commands or data.

On start-up, the LCD display goes through its own initialization routine. This takes approximately 15 msec., during which time the display is said to be 'busy.' The first thing we do in the PICs program is to change all I/O lines connected to the module to inputs. This prevents any interference with the display's start-up routine.

*LCD displays have great advantages over LED displays in several ways.*

<b>ECL-1200MN</b>  <b>\$67</b> 1.2 GHz MINIATURE VIDEO TRANS. 500 FT. L.O.S.	<b>ECL-1200MC</b>  <b>\$98</b> HIGH POWER 1.2 GHz VIDEO TRANSMITTER 1000 FT. L.O.S.	<b>ECL-372</b>  <b>\$39</b> 3.5 INCH B/W MINI DOME CAMERA 420 TVL 0.1 LUX	<b>ECL-1200MN</b>  <b>\$67</b> B/W MINI CAM WITH INFRA-RED ILLUMINATORS 0 LUX @ 10 FT	<b>ECL-377</b>  <b>\$67</b> WEATHERPROOF B/W BULLET CAM. 420 TVL 0.1 LUX	<b>ECL-380</b>  <b>\$89</b> WEATHERPROOF B/W CAM WITH INFRA-RED ILLUM. 420 TVL 0 LUX @ 10 FT
<b>ECL-2400MINI</b>  <b>\$47</b> 2.4 GHz M/Ni VIDEO TRANSMITTER 1 1/2 INCH LONG 500 FT. L.O.S.	<b>ECL-2400VR</b>  <b>\$68</b> 2.4 GHz WIRELESS 9 4 CHANNEL RECEIVER AUTO SWITCHING 1.2 GHz ECL-1200VR	<b>ECL-1203</b>  <b>\$96</b> 12 INCH B/W MONITOR 1000 TVL LINES	<b>ECL-SW4</b>  <b>\$47</b> 4 CH. VIDEO SWITCHER ADJ. DWELL TIME	<b>ECL-400Q</b>  <b>\$87</b> 4 CHANNEL B/W REAL TIME QUAD WITH SWITCHER	
<b>4 CAMERA DIGITAL RECORDING AND MONITORING SYSTEM VIEW CAMERAS FROM ANY LOCATION - IP ADDRESSABLE GREAT PLAYBACK RESOLUTION \$350</b>					
<b>SPECIAL: B/W CAMERA WITH 4MM AUTO IRIS LENS PLUS OUTDOOR HOUSING AND BRACKET: \$98</b>					
<b>CALL NOW FOR YOUR FREE COLOR CATALOG!</b>					
<b>1-800-323-8746 WWW.CCTVOUTLET.COM</b>					



# Universal LCD Serial Interface — Parts List

C1 — 47 uF 35 WVDC electrolytic capacitor, **RadioShack #272-1027** or equal  
 \*CR1 — 4.00 MHz Ceramic Resonator, **Digi-Key #PX400-ND** or equal  
 \*IC1 — Microchip Technology PIC 16C54-XT/P microcontroller  
**Digi-Key PIC 16C54-XT/P-ND** (requires programming)  
 POT1 — 10K ohm 15-turn potentiometer, **RadioShack #271-343**

they'll occupy memory locations 17-40, but they won't be displayed because the second line of the display doesn't start at memory location 17, it starts at memory location 41! That's why I've included the line feed command to send the cursor to memory location 41. This puts you in the first position of the second line.

The carriage return command erases all 80 memory locations, clears the entire display, and moves the cursor to memory location 1. All LCD displays automatically increment and display characters from left to right. The only catch — as we discussed earlier — is this memory location thing. So now, you can use this format with any LCD display and manipulate the cursor and characters to suit your needs.

Since you already know how many characters and lines your display will be using, you can send one of two commands to position your characters where you want them. And even overwrite the second line without touching the first! I think it's a rather simple solution to what others have presented as complex in the past. In other words, it doesn't have to be complicated to be useful.

## Long distance for under a buck

No... we're not selling phone cards! A lot of times it's required to send information to be displayed to a remote location. Serial standard EIA/TIA RS-232 is designed for about 50 feet.

However, there is an inexpensive solution. National Semiconductor — among others — makes a 75176 that is an RS-485 transceiver chip and it sells for less than a buck apiece! RS-485 is a balanced transmission medium that's good for over 4,000 feet (over 3/4 of a mile) using a single twisted pair of #24 AWG wires.

Basically, we wanted to include this information in case you needed it. But, you certainly don't have to use it. The circuitry

or equal  
 R1 — 2K ohm 1/4W 5% carbon resistor, **RadioShack #271-1339** or equal  
 \*VR1 — 28L05 5 VDC 100 mA voltage regulator, **Digi-Key #78L05ACZ-ND** or equal  
 Misc. — 0.1" male headers, hook-up wire, etc.

\*The following items are available directly from Shepard Engineering Concepts. A kit of programmed IC1, CR1, and VR1 are available for \$15.00 ppp. These prices are for the continental US only. Please make payment to: **Dennis Shepard, 8315-D Laborough Drive, Bakersfield, CA 93311**. Payment methods preferred are money orders, certified checks, or Western Union.

## ELECTRONIC GOLDMINE

www.goldmine-elec.com  
 1-800-445-0697

## WHITE LEDs are Here!

### 3000 MCD Ultrabright White LED

Crystal clear lens 5mm T1 3/4 LED lights up with such a brilliant beam that you can't look directly at it. These are factory prime LEDs with full length leads. Current 20ma, forward voltage 3.2V to 4.3V, min MCD 2000 - maximum 3500 (typical 3000). Viewing angle 15°. Infrared white. As with almost all white LEDs, there is a slight bluish output.

**Q12703 \$2.48 ea. • 10/\$22.95 • 100/\$200.00 • 1000/\$1850.00**

### Blue Blue Blue Blue Blue Blue

### 3000 MCD Ultrabright Blue LED

Crystal clear lens 5mm T1 3/4 LED lights up with such a brilliant beam that you can't look directly at it. These are factory prime LEDs with full length leads. Current 20ma, forward voltage 3.2V to 4.3V, min MCD 2000 - maximum 3500 (typical 3000). Viewing angle 25°. Wavelength ~470nm.

**Q12702 \$2.39 ea. • 10/\$21.95 • 100/\$190.00 • 1000/\$1750.00**

### 2600 MCD Ultrabright Red LED

Crystal clear lens 5mm T1 3/4 LED light up a brilliant red beam. Factory prime LEDs with full length leads. Forward voltage 2.1V. Current 20ma. Min MCD 2000 - Maximum 3000 MCD (typical 2500). Viewing angle 26°. Peak wavelength = 660nm.

**Q12704 89c ea. • 10/\$7.50 • 100/\$55.00 • 1000/\$450.00**

### Grandcell Rechargeable Alkaline AA Batteries and Charger

Not only does the Grandcell Rechargeable Alkaline Batteries have the highest capacity and long shelf life of primary alkaline batteries, but also they have the cost saving benefits of rechargeable batteries. Each Grandcell battery has a shelf life of up to 5 years. Unlike Ni-Cad batteries, the Grandcell features a full 1.5V initial voltage as compared to 1.2V for Ni-Cads. The initial current rating is 1500mah. Can be recharged in the special Grandcell charger which holds 4 batteries, up to 300 times. We prefer these over Ni-Cads and the performance results have been amazing. The alkaline manganese technology that the Grandcell batteries use represents a more environmentally responsible alternative to the large volume of single-use cells that require disposal over the life of the electronic device. The Grandcell batteries perform best and have the greatest life if they are recharged before they are fully discharged. The cumulative capacity is much greater when shallowly discharged up to 300-400 times. The Grandcell battery system that we are selling is brand new factory fresh stock. It consists of a 4 slot charger (either 2 or 4 batteries can be charged at a time) and B brand new (Date code DEC 2003) Alkaline AA Grandcell batteries. The charger has indicator LEDs to show when charging is complete and "hold in" 120VAC prongs. The charging time for partially discharged batteries is 6 to 8 hours and fully discharged batteries take 8 to 14 hours. Remember these batteries are ready to be used as soon as you receive them, not like Ni-Cads. Brand new in sealed blister pack.

**NV7000 \$14.95 SALE! \$10.95**

### Prime Bright Red LED

These are prime T1 (3mm) diffused red lens LEDs which light up bright red. They are brand new and on tape and reel with full length leads. Since they were designed for auto insertion they don't have the usual fat side or one shorter lead that denotes the cathode. Even though this fact doesn't impact the use or performance of the LED, it did enable us to buy over a million of these beauties for a blowout price, and we're passing the savings on to you. So in full length only you'll be impressed by the quality of this LED. Utmost part # TLHCHE-012

**Q12700 1 full reel 1500 pcs. \$19.95**

**Q12701 Factory box of 2 reels (3000 pcs.) \$29.95**

\*less than a penny per LED

**Call today for your free catalog!!! 1-800-445-0697**

(USA only)

Phone Orders Call: 1-800-445-0697 or Fax Your Orders to: (805) 981-9259 for a Free Catalog Call: 1-800-445-0697

**PO Box 5408 Scottsdale, AZ 85261 www.goldmine-elec.com**

Minimum Order: \$10 (plus min. \$6 Shipping and Handling). We accept MasterCard, Visa and personal checks, however, we cannot accept personal checks on orders outside the US. Minimum Foreign Order Amount: \$50 (plus an airway \$10 S&H). NOTE: All items subject to prior sale. All prices subject to change without notice. Please call for details.

### Complete Laser CD Drive Assembly

These are the main assemblies out of a CD drive. We think they were used in audio applications, but we aren't sure. Consist of a sophisticated SMD and thru hole PCB board, 2 very efficient low voltage DC motors, plus various gears, linear slide mechanism and IR laser head assembly. We have no data, hookup specs or any other info. These are used and sold "as is" only. The nice motor alone are worth more than our low price. Overall size is about 3" x 4" x 1.8".

**Q12761 \$2.00 ea. • 10 units / \$15.00**

### Powerful Lambda +5VDC and +3.3VDC

#### Regulated Power Supply

Part # PW G0050 by Lambda Corporation. +5VDC at 750mA and +3.3VDC at 100mA output. Input is 100 to 240VAC 50-60Hz. Open frame switching supply with .156" headers for output and input. Size only 6" x 3 1/2" x 1 1/4". Weighs 0.82 lbs. Brand new in manufacturer's box.

**Q12705 \$12.95 ea.**

### High Output 7.2V 1100ma

#### Lithium Ion Battery Pack

Battery pack made for Qualcomm phones features two 3.6V 1100ma Lithium Ion batteries connected in series and attached to a small circuit board with lots of SMD parts. To get to the batteries simply break apart the case and remove the batteries. Size of the overall battery is about 5" x 1 3/8" x 3/4". Size of each internal 3.6V battery is about 2 1/2" long x 70" diameter. Most of the internal Lithium Ion batteries are type CGR18650 by Panasonic, but some were also made by Sony. The batteries are fresh and most are already charged. Outer plastic case may have an IR marked on it but the internal batteries are prime and ready to use.

**NV7005 \$5.00/pack SALE! \$4.00/pack**

### This Fine Copper Mesh Pressure Sensitive Shielding Tape

Made for use in the "Mars Observer" NASA program, this high quality 1" wide copper mesh tape cost the government over \$30 per roll in large quantity lots. Each roll is 1" x 25' long and features a peel off backing that exposes the adhesive on the copper mesh. The unique characteristic of this copper mesh tape is that even though it has a very high quality adhesive on one side, the mesh conducts even through the adhesive. Because of this fact, you can cut small 1/8" wide strips of this mesh to make solder panels out of solar cells without using solder for connections. Of course there are hundreds of other applications including non solder PCB board trace repair, shielding, etc. This is one of the most useful items we have purchased. Hurry before we sell out!

**NV7002 \$10.00/ea. SALE! \$8.00 ea.**

In other words, it doesn't have to be complicated to be useful.



```

100000000F0C0500FF0C06003A09020C0500000C5D
10011000060065060600430945056C0025070EAC9
1002000030C2A00320925060304250703052C03E802D9
100300002A00320925060304250703052C03E802D9
1004000017A007C2A00320925060304250703052C03E802D9
100500000D0C8C0043067B0A0C02260065050000BF
1006000065040C0A330A3043A03A360A370AE0A2EA
1007000032A0008620C2800650C2700F7023E0ADD
10080000E8023E0A0008380C2600650500006504F9
100900006209380C26006505000065046209380C09
100A000026006505000065046209380C2600650544
100B00000000650462094504000001C2600650586
100C00000000650462094504000001C2600650586
100D0000E8023E0A0008380C2600650500006504F9
100E00000000650462094504000001C2600650586
100F0000E8023E0A0008380C2600650500006504F9
10100000E8023E0A0008380C2600650500006504F9
101100000000650462094504000001C2600650586
10120000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10130000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10140000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10150000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10160000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10170000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10180000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10190000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
101A0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
101B0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
101C0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
101D0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
101E0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
101F0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10200000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10210000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10220000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10230000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10240000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10250000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10260000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10270000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10280000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10290000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
102A0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
102B0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
102C0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
102D0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
102E0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
102F0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10300000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10310000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10320000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10330000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10340000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10350000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10360000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10370000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10380000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10390000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
103A0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
103B0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
103C0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
103D0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
103E0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
103F0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10400000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10410000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10420000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10430000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10440000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10450000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10460000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10470000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10480000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10490000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
104A0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
104B0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
104C0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
104D0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
104E0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
104F0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10500000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F

```

```

100000000F0C0500FF0C06003A09020C0500000C5D
10011000060065060600430945056C0025070EAC9
100200000F0C2A00320925060304250703052C03E802D9
100300002A00320925060304250703052C03E802D9
1004000017A007C2A00320925060304250703052C03E802D9
100500000D0C8C0043067B0A0C02260065050000BF
1006000065040C0A330A3043A03A360A370AE0A2EA
1007000032A0008620C2800650C2700F7023E0ADD
10080000E8023E0A0008380C2600650500006504F9
100900006209380C26006505000065046209380C09
100A000026006505000065046209380C2600650544
100B00000000650462094504000001C2600650586
100C00000000650462094504000001C2600650586
100D0000E8023E0A0008380C2600650500006504F9
100E00000000650462094504000001C2600650586
100F0000E8023E0A0008380C2600650500006504F9
10100000E8023E0A0008380C2600650500006504F9
101100000000650462094504000001C2600650586
10120000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10130000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10140000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10150000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10160000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10170000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10180000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10190000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
101A0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
101B0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
101C0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
101D0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
101E0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
101F0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10200000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10210000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10220000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10230000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10240000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10250000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10260000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10270000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10280000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10290000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
102A0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
102B0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
102C0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
102D0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
102E0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
102F0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10300000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10310000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10320000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10330000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10340000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10350000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10360000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10370000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10380000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10390000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
103A0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
103B0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
103C0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
103D0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
103E0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
103F0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10400000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10410000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10420000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10430000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10440000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10450000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10460000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10470000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10480000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10490000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
104A0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
104B0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
104C0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
104D0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
104E0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
104F0000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F
10500000FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0FF0F

```

shown in the schematic uses two 75176s ... one set up as a transmitter and the other as a receiver. The data is simply converted from TTL level to RS-485 ... transmitted ... and converted

back to TTL levels at the other end. And, of course, you could tie a RS-232 chip, such as a MAX 232 from Maxim, to change to and from RS-232 in the process, should you need that as well. Lots of options, but better too many than not enough!

### The circuitry itself

There are two standard configurations for interfacing an LCD module. Manufacturers either use a single row of 14 or 16 connections or sometimes use a double row of eight connections. Because the pinout configuration and the location varies from manufacturer to manufacturer, it didn't seem prudent to design a PCB that may or not work with your display. But we are going to cover the pinouts, which are universally accepted. They are:

Pin#	Function
1	Ground
2	+ Power Supply
3	Contrast Adjust
4	Register Select line
5	Read/Write line
6	Enable line
7	Data Bus 0
8	Data Bus 1
9	Data Bus 2
10	Data Bus 3
11	Data Bus 4
12	Data Bus 5
13	Data Bus 6
14	Data Bus 7
15	Backlight Anode (if applicable)
16	Backlight Cathode (if applicable)



The actual circuitry is pretty straightforward. A PIC 16C54 converts from serial to parallel data format and handles all control line functions and the LCD module's initialization, as well. A potentiometer is used to adjust the LCD contrast. If you've got a backlight LCD, pins 15 and 16 supply the power to that function. Typically, a 22-ohm resistor is used to limit current, but you might want to check with the manufacturer of your particular unit for their recommendation.

The 22-ohm resistor is shown with dashed lines on the schematic. It's an optional component since it isn't needed on non-backlit LCD displays. A 22K resistor is used in series with the input to interface directly to RS-232 circuits.

The internal diodes, which protect the inputs of the PIC, will clamp the input voltage to around 5 VDC and this resistor will limit the current, thus protecting the PIC itself. Since we've already covered the operational sequence on startup in the initialization procedure previously, there's no need to repeat it again.

### Wrapping it up

I hope you're going to have as much fun with this as I did! I evaluated two different modules for this project and I consider both of them a good value for the money. I can't guarantee their availability although both suppliers indicated that they expected an ample supply to be available for a while.

All Electronics in Los Angeles, CA (1-800-826-5432) has a 16 character x two line LCD module (part #LCD-53) with backlight which is available for only \$7.50. This module uses a 16-pin SIP layout and works well with the 22-ohm resistor shown in the schematic. But remember, although a backlight display lets you see at night, it also consumes more power, so it might not be your best application for battery-operated equipment.

MPJA in Lake Park, FL (1-800-652-6733) has a 24 character x two line LCD module (part #12856-OP) which is available for only \$8.95. This display uses an Optrex DMC24227 and uses the double row 2 x 8 pin connector, even though it doesn't use pins 15 and 16 since it's not a backlight display. A ribbon cable is probably a good option for interfacing to this display, while a 16-pin SIP header is probably best for the other unit. I think you'll be happy with either display, depending on what your requirements are.

A programmed PIC is available for \$15.00 and includes a 4 MHz ceramic resonator and a 78L05 voltage regulator. Please remember that the regulator is only rated for 100 mA output current so it's probably not going to supply enough current for both the electronics and the

backlighting, if required. Please keep that in mind when interfacing to your project. A 7805 voltage regulator is rated for 1.5 amperes (with a heatsink) so it might be a better choice for backlight displays.

Once again, I hope I've taken some of the mystery out of LCD displays and how useful they can be to your own projects. I've got several projects in the works that will make use of serially interfaced LCD displays. Because of this, I decided a little introduction would be helpful and whet your appetite for bigger and better things yet to come.

Enjoy... NV

**Stay tuned for more articles from Dennis which use LCD modules, including an Energy Monitoring System and a 20-channel Digital Wire Tracer.**

## Tired of Expensive Inkjet Cartridges? Save 90% on Inkjet Inks!

Refill kits Black (8 oz) Color (4 oz C, Y, M) Printer (Call for Others Not Listed)	# of Refills		Cost/Refill		Kit Price	
	Black	Color	Black	Color	Black	Color
HP500 Series, 400, Officejet 300, 350, Fax	7	14	<b>4.71</b>	<b>2.85</b>	32.95	39.95
HP600 Series, Officejet 500, 570, 600, 610 630, 700	7	14	<b>4.71</b>	<b>2.31</b>	32.95	44.95
HP820C, 855C, 870C, 1000C, 1150C, Copier 120, 210	6	12	<b>6.67</b>	<b>3.23</b>	39.95	39.95
HP720C, 722C, 712C, 880C, 890C, 895C, 1120C, 1170C	6	12	<b>6.67</b>	<b>3.75</b>	39.95	44.95
HP900C Series, P1000 Series, Officejet G55, G85, G95	6	12	<b>6.67</b>	<b>3.75</b>	39.95	44.95
HP2000C Pro Color Printer, 2200, 2500	6	12	<b>6.67</b>	<b>3.75</b>	39.95	44.95
Canon BJ-10, 200, 210, 240, 250 Apple StyleWriter 1200, 1500	14	20	<b>2.15</b>	<b>2.00</b>	29.95	39.95
Canon BJC-4000 Series, 2000, 5000 Series, Multipass Series	60	60	<b>0.50</b>	<b>0.67</b>	29.95	39.95
Canon BJC-6000, 3000, S400, S450, S600, Multipass 755	14	8	<b>2.85</b>	<b>1.67</b>	39.95	39.95
Epson Stylus Color 500, 200	20	17	<b>1.50</b>	<b>2.35</b>	29.95	39.95
Epson Stylus Color 400, 600, 800, 850, 1520, Photo	20	17	<b>1.50</b>	<b>2.65</b>	29.95	44.95
Epson Stylus Color 440, 660, 670, 740, 760, 860	20	17	<b>1.50</b>	<b>2.65</b>	29.95	44.95
Epson Stylus Color 480, 580, 880 <b>NEW</b>	20	17	<b>1.50</b>	<b>2.65</b>	29.95	44.95
Lexmark 3200, 5700, Z11, Z12, Z31, Z32,	15	17	<b>2.67</b>	<b>2.35</b>	39.95	39.95
Compaq IJ300, IJ600, IJ700, IJ750, IJ900 Xerox XJ8C	15	17	<b>2.67</b>	<b>2.65</b>	39.95	44.95
Lexmark Z42, Z51, Z52, Z83, Compaq IJ1200, A1000 <b>NEW</b>	15	17	<b>2.67</b>	<b>2.65</b>	39.95	44.95
Lexmark Photo kit for 3200, 5700, 7000, 7200, Z42, Z51, Z52	9				<b>3.11</b>	27.95
Lexmark 2030, 2050, Execjet II/III, Medley 4C, Compaq IJ200	10	17	<b>3.00</b>	<b>2.35</b>	29.95	39.95
Xerox HC 450, XJ4C, XJ6C	22	12	<b>1.36</b>	<b>3.33</b>	29.95	39.95
<b>New Combination Kits</b> Black dye 4 oz / Color 2 oz each						<b>44.95</b>
<b>New Combination Kits</b> Black pigmented 4 oz / Color 2 oz each						<b>49.95</b>

## Save 30 - 60% on New Compatible Cartridges Quantity Discounts for 3 or 6+ cartridges Mix and match

Printer (Call for Others Not Listed)	BLACK Cartridge				COLOR Cartridge			
	Qty	1	3	6+	Qty	1	3	6+
Canon BJC-4000 Series, 2000, 5000 Series, Multipass Series	4.50	3.83	3.69		10.95	9.31	8.98	
Canon BJC-6000, 3000, S400, S450, S600, Multipass 755	7.95	6.76	6.52		7.50	6.38	6.15	
Canon BJC-70, 80, 85 (3 pack Black / 3 pack color)	9.95	8.46	8.16		14.95	12.71	12.26	
Epson Stylus Color, Pro, Pro XL	9.95	8.46	8.16		13.95	11.86	11.44	
Epson Stylus Color II, IIs, 200	9.95	8.46	8.16		13.95	11.86	11.44	
Epson Stylus Color 400, 500, 600, 800, 850, 1520, Photo	9.95	8.46	8.16		13.95	11.86	11.44	
Epson Stylus Color 440, 660, 670, 740, 760, 860	9.95	8.46	8.16		13.95	11.86	11.44	
Epson Stylus Color 750, 900, 980, 1200	10.95	9.31	8.98		15.95	13.51	13.08	
Epson Stylus Color 480, 580, 880 <b>NEW</b>	10.95	9.31	8.98		14.95	12.71	12.26	
Epson Stylus Color 777, 870, 875, 1270 <b>Requires Empty Return</b>	11.95	11.95	11.95		15.95	15.95	15.95	

### Quality Inks and Toner for:

**HP Epson Lexmark  
Canon Apple Xerox**

**Inkjet**  
Southwest



### New Combination Black / Color Kits

4 oz black dye / 2 oz C,M,Y color - **\$44.95**  
4 oz black pigmented / 2 oz C,M,Y - **\$49.95**

**Mon - Fri 8:30-5:30 PDT 11:30-8:30 EST**

**Call or see us online!**

**www.inkjetsw.com**

**(480) 668-1069 Fax**

**1-800-447-3469**

**(480) 668-0959**



# Laser Insight

by Stanley York

This month, we're going to take a break from all the theory and technical stuff. We're going to start a construction project that I promised you earlier. The project is for a light show that you can use with a HeNe laser or a diode laser pointer. There will be a few optional add-ons for this project that can be built later as your time and budget allow.

First, I'll briefly describe what the light show will let you do, then we'll look at the details of all the bits and pieces that make up the whole.

The laser can be any HeNe that you can pick up at surplus stores, hamfests, etc., or it could be one of those laser pointers that you see quite a lot of these days. Edmund Scientific (Barrington, NJ; (800) 363-1592) has a good selection of laser diodes, as well as the larger HeNe lasers, so you should be able to find something there that won't break your bank. Be prepared to spend more if you want anything other than the standard red color though. Always keep in mind, that even though they are small and battery-operated, the little pointer lasers are just as dangerous to the eyes as their bigger counterparts.

They won't blind you, but it will feel as though someone jabbed a finger in your eye.

## Light show description

The basic light show as described will allow you to connect your stereo to the mirror drivers to create weird, non-repeating patterns on a wall or ceiling that changes in response to the musical content. Alternatively, there are inputs to allow a function generator to drive the mirrors. This will create steady or slowly changing patterns that vary according to the types of inputs to the two channels. Or you could mix the oscillator and music inputs to get really bizarre effects.


Optional equipment will allow circular and epicyclic patterns to be generated in addition to the patterns corresponding to the audio input. Finally, there will be a chopper system described that will modulate the laser beam to form dotted lines instead of the more familiar continuous lines. All of these effects can be operated independ-

ently or in unison, making the unit very versatile and far from boring. If two lasers are used — each a different color — and mixed going into the unit, the results will be even more impressive.

## Before we start

To begin building the light show, we will need to gather some parts that may be hard to find. These are the scanner mirrors used to deflect the laser beam. They are rather special, and quite expensive if you have to buy them new. In my system, I used some scanners that I

Figure 4-1 — Schematic drawing of general-purpose audio amplifier.

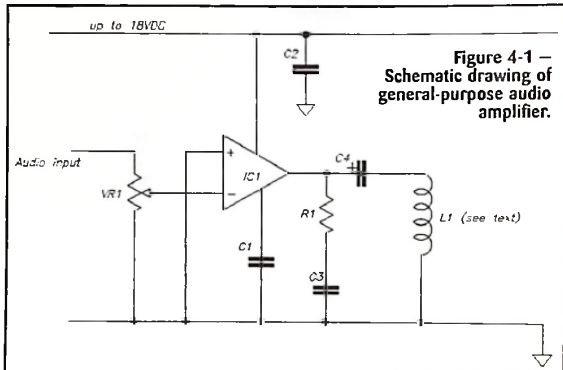

picked up at a surplus store here in Orlando, where I live. You should shop around in your neighborhood to see if there is a surplus store near you. The scanners I used were made by General Scanning (Watertown, MA).

If you have a hard time finding these devices, I will describe a simple method whereby you may try to make your own. Of course, they won't be as good as proper scanners, but the fun and satisfaction with this hobby is making something out of nothing, and making it work! If you are anything like me, you'll take the challenge, and make some scanners. So get that pioneering spirit going.

The driver amplifier for these scanners is shown in Figure 4-1. As you can see, it is a very simple circuit based on a readily available IC. Nothing is critical about the circuit, and you are free to experiment with other ICs.

I chose an LM384 because that's what I had in my parts box, but again, nothing is chiseled in stone here, so go ahead and experiment. You may find that the scanners you end up with may need more power (or less), so don't dwell on the schematic.

You will need two of these amplifiers to drive the scanners though, so try at least to make the two circuits the same, so that you


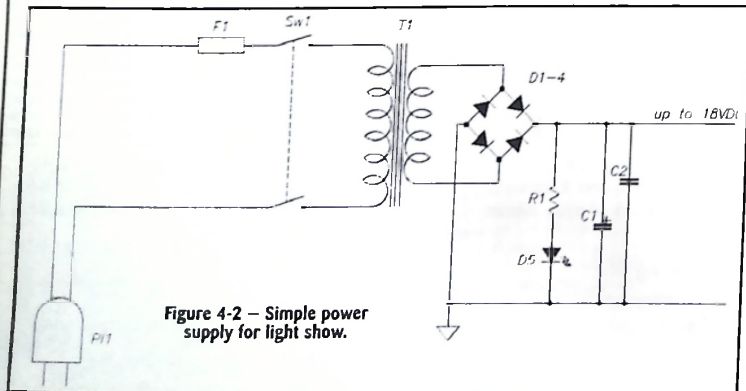


Figure 4-2 — Simple power supply for light show.

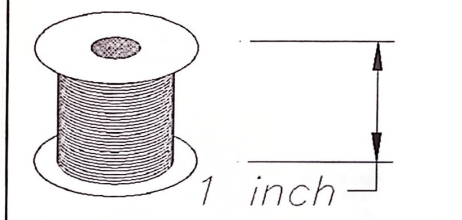

Figure 4-3 — Details of coil.



get equal laser beam deflection characteristics.

In this drawing, L1 is the scanner coil, and should be made such that the coil impedance is similar to a loudspeaker. VR1 acts as a volume control, and is used to scale the size of the projected light patterns. The input signal may be derived from an audio source, a signal generator, or both, using suitable mixing means on the input control circuit (not shown). Nothing is critical in this set-up, and you are free to experiment.

A suitable power supply for driving the amplifiers is shown in Figure 4-2. Again, there is nothing critical about this circuit, but keep in mind the limitations imposed by the amplifiers and scanners you intend to use in your set-up.

Don't use a power supply that is too close to the limits of either, or you'll be inviting trouble. Make sure the transformer can deliver the required power, and that the diode bridge can handle the current. Maximum draw on this unit, with all the options added, should not be more than about 2A. Loud passages of music may cause a peak current of about 3A; depending on how the volume control (VR1) is set. D5 is a red LED used to indi-

cate that the power supply is on. The resistor R1 should limit the LED current to about 15-20mA.

When using main powered equipment, you should always use a double-pole switch to break both lines coming into the equipment. Then, if the connections at the wall socket are miswired, there is no shock hazard when the power is turned off using the switch. Note also, that the fuse is first in line. If the fuse blows for some reason, power is removed from the switch. If the situation were reversed, and the fuse blows, then the switch will still be live. This presents a serious shock hazard when the fuse is located internally to the equipment rather than through a chassis fuse holder. So play it safe.

#### Scanner basics

If you haven't had an opportunity to use scanners before, I'll give you a bit of information about them before we set about making some.

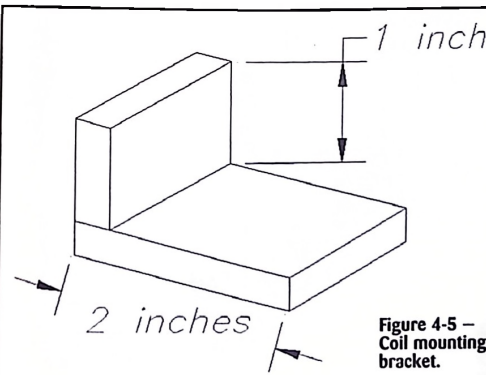


Figure 4-5 — Coil mounting bracket.

## LASERS & ACCESSORIES

### HELIUM NEON LASERS

- ☑ Complete Systems
- ☑ Plasma Tubes
- ☑ Power Supplies

### ACCESSORIES

- ☑ Optics
- ☑ Electro-Optics
- ☑ IR Viewers
- ☑ Books & More



### DIODE LASERS

- ☑ Visible / IR
- ☑ Complete Modules
- ☑ Collimating Optics
- ☑ Drive Circuits

WEBSITE:

WWW.

mi-lasers.com

Phone: 623-934-9387 • Fax: 623-934-9482

Circle #87 on the Reader Service Card.

Edmund Scientific  
PN L31-419  
(long side)

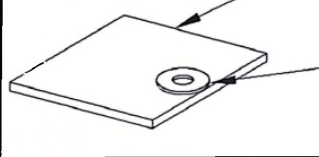


Figure 4-4 — Scanning mirror detail.

#6-32  
steel  
washer

Imagine if you will a simple battery-operated electric motor. Imagine a mirror glued to the shaft of the motor, such that the mirror surface is parallel to the shaft.

Now imagine the motor rotating, and a laser beam directed at the shaft. Each time the mirror presents the silvered side in the general direction of the laser beam, the reflected beam will describe an arc around the room that is at some angle to the rotating shaft.

Now imagine what would happen if the shaft were fixed at one end. The motor would try to turn the shaft against the torsion of the fixed end. The amount of rotation on the shaft would thus be dependent on the torsional strength of the shaft and the strength of the magnetic field trying to turn it. This is exactly the way scanners of the type I use in my system operate.

Commercial scanners are designed with a very thin shaft, fixed at one end, and with rotor coils similar to a normal motor at the other end. When power is applied, there is more or less turning of the shaft at the end where the rotor coils are, depending on the torsional rigidity of the shaft and the strength of the magnetic field trying to turn it. The amount of turning is

thus proportional to the current strength in the rotor coils.

Commercial scanners can only move through a very limited angular motion, but they can be made to move very fast, and in an upcoming article, I will describe how they are used in high-speed laser engraving applications.

Okay, that's how commercially-bought scanners work, but we can't possibly make anything to compare with those. Not on our limited resources, anyway. Our scanners will be simpler, though not as effective. But they will illustrate the principles of scanners and light show systems in particular.


#### Making the scanners

As I said before, I happened to find some surplus scanners in a local store here in Orlando, but for those less fortunate, I will describe now how we can make a poor man's version of the scanner. You will need two of these scanners for the project. There are a number of ways of doing this, and I will describe one simple way. After trying this, you may find other (perhaps better) ways of achieving the same thing.

Figure 4-3 shows a wire spool wound with magnet wire that is used as the deflecting means for



**Figure 4-6—Scanner assembly showing mirror mounting scheme.**

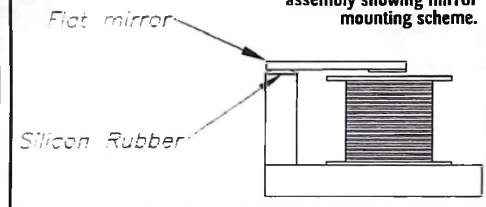

our scanner. I wound this with #26 gauge magnet wire until the spool was full. When I measured the resistance of the coil, it was about four ohms. The coil was about 3/4 inch in diameter and about an inch high.

The strength of the magnet is not much at this point, since the coil has no core. To improve the strength, I found a number of small iron nails and cut off the heads and jammed them into the opening in the core until I could get no more in. Then I secured them with a dab of silicon sealer left over from a plumbing project. I pushed down on the nails so that there was a little (about 1/16") of the nails sticking out on one side.

Turning next to the mirror, I had a mirror left over from another project that I had obtained some years ago from Edmund Scientific. This was a thin mirror that I had to cut in half to reduce weight, and stuck a flat washer to the underside of the mirror on one of the short sides (see Figure 4-4). The washer is used to pull the mirror

Find a scrap of 1/4-inch thick Plexiglas and make two of the small angle brackets shown in Figure 4-5. These will be the scanner mounting brackets when we're done. Use plastic cement or epoxy to assemble this part. The dimensions are not too critical, but you need to get the finished height of the bracket the same as the height of the coil in Figure 4-3. Place a couple of dabs of silicon rubber sealer on the top edge of the Plexiglas block and place the mirror on the sealer as shown in Figure 4-6. Alternatively, you may find that rubber cement works okay too, if you build up a few layers. I haven't tried it yet.

Either way, you will need to hold the mirror off the surface of the Plexiglas, otherwise it won't be able to flex when the coil pulls on it. When the sealer dries, it acts as a spring against the pull of the magnet, so that the stronger the magnetizing force, the greater is the deflection on the mirror.

Put a dab of sealer on the base of the mounting block and position

side of the mirror. You should try to get about 1/16-inch space between the flat washer and the top of the magnetic core when the assembly is finished. Figure 4-7 shows a completed scanner assembly.

Take a look now at Figure 4-8. This shows the general layout of the various scanners, and the path that the laser beam takes on its passage through the system.

In this installation, the laser beam is coming in from the left of the page. At this point, I have only mentioned the two scanners we have just finished building. But there are two more scanners, consisting of circular (or square) mirrors epoxied to the end of two motor shafts. I'll discuss these more later. If you prefer, you can leave out these two scanners until you have the homemade scanners working to your satisfaction.

The laser beam comes in from the left and strikes the first scanner mirror approximately in the center of the glass. The first scanner deflects the laser beam in a vertical direction. The reflected beam then strikes the second scanner mirror approximately in the center. This scanner deflects the beam in a horizontal direction. Note that the two scanners here are mounted so that the deflection angles are perpendicular.


With the simple arrangement described, it is possible to put the laser spot in any position in a square area corresponding to the four maximum deflection positions of the mirrors. If quadrature sinewaves (that is sinewaves that are 90° out of phase) were delivered to the scanner coils, the resulting pattern displayed on a wall or ceiling would be a circle. If sinewaves of different frequencies were delivered instead, the resulting display would be the familiar Lissajous patterns.

On their own, these two scanners would give quite an interesting display that would not repeat or become static if used with speech and music inputs to the amplifiers. But the addition of two more scanners, as depicted in Figure 4-8, make the display even more interesting.

In Figure 4-8 are simply small electric motors with mirrors epoxied to the end of the shaft. The mirrors are purposely not epoxied perpendicular to the shaft, though, otherwise the displayed beam will not move when the motor is running.


Get some pieces of mirror about an inch across, and put a dab of epoxy in the center of the back side. Place the mirror on the end of the shaft and support it while the epoxy sets. Try to get the mirror almost perpendicular (a couple of degrees off is okay). When the epoxy sets, turn the assembly over and reinforce the glued joint with more epoxy. (You don't want the mirror to go flying across the room do you?)

With two circular scanners as

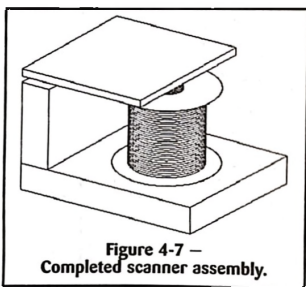

**Figure 4-7 — Completed scanner assembly.**

**Figure 4-8 — Schematic of the laser beam optical path with the optional motors.**

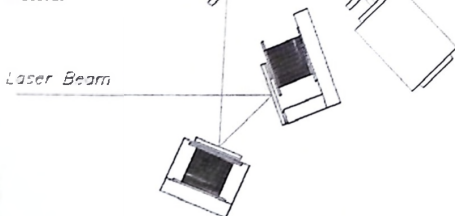

toward the magnet in the final assembly of the scanner. Use epoxy to stick the washer on. Use a small dab, and don't get any on the top of the washer. Place the washer close to the edge on the short side.

the coil so that the core of the coil is directly underneath the washer glued on the back of the mirror. While the silicon sealer is still tacky, slide a piece of thin card between the core of the coil and the back

shown, you will be able to create circular patterns, and circular patterns within the main circle. If you had a Spirograph™ as a kid, you've probably heard of cycloids and epicycloids. By running the motors at different speeds, the two circular scanners will allow you to create similar patterns to those first encountered playing with this toy.

Figure 4-9 shows a suggested layout and method of mounting everything onto a simple fixture. Use 18 AWG aluminum sheet for mounting the two scanners, and use plastic or rubber "P" clips for holding the motors. Rubber works good because it has a little "give" to it, and will help absorb some of the vibration from an out-of-balance motor. As shown, the device will display images onto the ceiling, but can easily be turned around to display on a wall, if desired.

If you want to add one more special effect not shown or discussed thus far, you may want to consider adding another small motor with a chopper wheel attached to its shaft. This will be a simple disk of stiff card or plastic, with a series of holes drilled or punched equally spaced around the

## Rotating scanners

The two other scanners shown



edge of the disk. The disk is attached to the motor shaft in a similar way to the rotary scanners discussed before, but this time try to get the disk perpendicular to the shaft.

Mount the motor similarly to the previous motors, but position it such that the laser beam goes through one of the holes in the disk before striking the first mirror. When this motor is stationary, you will get a continuous line pattern. But when the motor is turning, you will get a dotted line pattern.

As an alternative method of making scanners on the cheap, consider using an old set of bass speakers. Bass speakers work best because they are capable of greater linear displacement than the scanners described above. The usual method is to glue a mirror to the side or bottom of the paper cone, but there are better ways of attaching the mirror without changing the frequency response of the speaker.

All of these scanners and the chopper wheel may be run together or independently through pulse generators, sine wave generators, and audio sources of any kind to create an almost inexhaustible variety of patterns and effects.

ety of patterns and effects.

## Caution

Finally, I can't let this article go without a word of caution.

Whether you use a laser diode or a more powerful HeNe laser, the fact remains that the light coming from the laser is very intense and concentrated, and thereby constitutes a real danger to the unwary eye. The light will damage the retina of the eye. When using this device, or any other device using a laser, **please, please, please be very careful.** Especially if your audience is unaware, or perhaps too young to understand the dangers of laser light.

Make sure that the beam falls safely away from anyone in your audience, and strikes a flat (not glossy or shiny) surface, then the beam cannot reflect back into their faces (or yours). It is easy to be complacent when dealing with these devices, thinking that they are safe because of the low power output, but don't be lulled into a false sense of security. You only have one set of eyes, and they have to last you a lifetime, so don't take any chances. NV

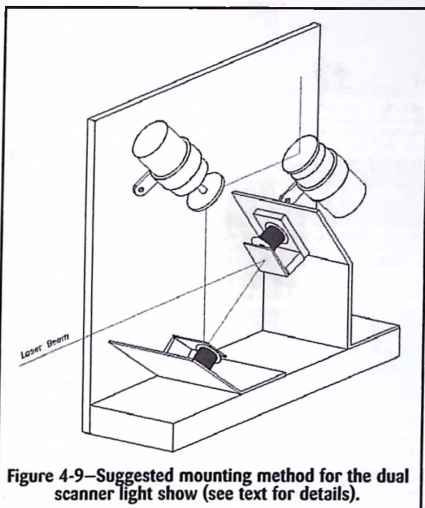


Figure 4-9—Suggested mounting method for the dual scanner light show (see text for details).

This column welcomes your participation. If you have questions, comments, or perhaps an idea for a future project, please let me know through this column. Any ideas or suggestions are welcome. You can email me at stanley.york@att.net.

## LOSS OF DATA CAN PUT YOUR BUSINESS OUT OF BUSINESS DON'T RESTORE LOST DATA, SWAP IT!

#1 For Anyone Serious About NOT Losing Their Data  
The Ultimate Super Computer at an Off The Shelf Price



With 10,000 Viruses Hitting the Web Each Month a **DUAL DRIVE SYSTEM** is a Must. Removable Hard Drives Allow Instant Data Recovery and Multi Operating Systems For The Power User.

**CompuZilla™** Never lose data again due to a crash, virus, power outage, or human error.

Be back up and running within **MINUTES** - not hours, days or weeks

- The ease and convenience of the Dual DVD/CD and CD Recorder makes copying CD's easier than ever before.
- If security is an issue, just unlock and remove the drive. Easy Offsite Data Storage.
- No one has all the features found on this machine regardless of price!

1,300MHz 80Gig 512MgRam

32MgVideo

Server Size Tower  
2 Removable Hard Drives  
DVD Player & CD Recorder  
2 Floppies

Now with **DVD**

FREE SHIPPING Computers

1 Year Warranty - Satisfaction Guaranteed - BEST Customer Service  
FAX 931-851-4120 • Credit Cards CALL 800-407-1020

Find out more: [compu-zilla.com](http://compu-zilla.com) • Email: [sales@compu-zilla.com](mailto:sales@compu-zilla.com)

Circle 908 on the Reader Service Card.

## RF Data Modules



### AM TRANSMITTER

- Small size: 17.78 x 11.43mm
- CMOS/TTL input
- No adjustable components
- Low Current, 4mA typical
- 418MHz or 433.92MHz OOK
- Simple to integrate - simply add antenna, data and power
- Range up to 250ft.
- Wide supply range, 2-14Vdc
- SAW controlled - stability
- SAW available in DIL package

AM-RTS ..... \$12.10

### AM RECEIVER

- Compact size: 38.1 x 13.7mm
- On-board data recovery, CMOS
- Low current, 2-4mA typical
- 2MHz data rate, CMOS/TTL output
- 5Vdc operation
- On 418MHz or 433.92MHz (4xx)
- No adjustable components
- Patented Laser Trimmed component
- High stability
- Sensitivity: -105dBm
- Available also in 0.8mA version


AM-HRR3-4xx ..... \$10.95

### FM TRANSCEIVER

- Only 23 x 33 x 11mm
- Up to 40k bps data rate
- 19200 baud with ASCII
- Up to 500ft. range
- 5V operation
- 0.25mW into 50
- 418 or 433MHz FM
- Fast 1ms enable
- Direct interface to 5V CMOS
- Auto TX/RX changeover

BIM-4xx-F ..... \$87.36

### RS232 TRANSCEIVER MODULES

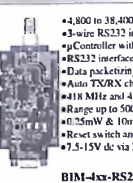

- 4,800 to 38,400 bps half duplex
- 3-wire RS232 interface
- Controller with user EEPROM
- RS232 interface protected to ±15V
- Data packetizing performed by user
- Auto TX/RX changer
- ±18 MHz and 433MHz versions
- Range up to 500ft. (0.25mW var.)
- 0.25mW & 10mW versions
- Reset switch and status LED's
- 7.5-15V dc via DB9 connector, 20mA

BIM-4xx-RS232 .... \$139.30



- Up to 19,200 bps half duplex
- 3 wire RS232 interface
- Range up to 500ft
- Transparent data pk, letzting
- Supports 8 or 9 bit protocols
- Self test function
- Reset Switch & Status LED's
- 1/4 wave wire antenna on board
- Available in a Simplex TX/RX pair (RTComTX & RTComRX)
- 7.5V-15Vdc operation
- RTCom-4xx ..... \$247.90
- RTComTX-4xx ..... \$7.15
- RTComRX-4xx ..... \$185.52

**ABACOM**  
TECHNOLOGIES

Free Catalog

Tel: (416)236-3858  
Fax: (416)236-4856  
[www.abacom-tech.com](http://www.abacom-tech.com)  
[abacomtech@compuserve.com](mailto:abacomtech@compuserve.com)



# Classifieds

## HAM GEAR

**WANTED: ROCKWELL** Collins HF-80 equipment, 8515-1, 2378-3 log periodic. Collins literature. Jim Steiner 805-259-2011, 805-259-3830 (fax), btf@smartlink.net



**2.4GHz ATV** — 8 channel TRANS-MITTERS AND RECEIVERS. 35mW output power, 1 video channel, 2 audio, SMA connectors, NTSC/PAL compatible. Includes 1/4 wave rubber duck antenna. Standard frequencies are 2398, 2405, 2412, 2416, 2420, 2428, 2435, 2442 MHz. Custom frequencies are available. See ad in this section for power and price. **\$79/each for transmitter, \$79/each for receiver** EATV. Visit our website for dealers or order on-line at [www.4stv.com](http://www.4stv.com)



**1.2GHz ATV** — 8 channel TRANS-MITTERS AND RECEIVERS. 75mW output power, 1 video channel, 2 audio, SMA connectors, NTSC/PAL compatible. Includes 1/4 wave rubber duck antenna. Standard frequencies are 1250, 1255, 1260, 1265, 1270, 1275, 1280, 1290 MHz. Custom frequencies are available. **\$79/each for transmitter, \$79/each for receiver** EATV. Visit our website for dealers or order on-line at [www.4stv.com](http://www.4stv.com)



**2.4GHz POWER amplifier** with power supply 10-40 mW input, 1 (one) watt output with in-line SMA connectors and built-in heat sink. Approx. 2" x 2" x 5/8" size. Frequency range 2.3GHz-2.5GHz. **\$18/each**. Compatible with all ATV products. See our website for more info on accessories and transmitter and receiver modules. EATV Visit our website for dealers or order on-line at [www.4stv.com](http://www.4stv.com)



**SUPER HIGH GAIN** 14 dbi flat antenna with N or SMA connector tuned for 2.3-2.5 GHz. Use with 2.4GHz ATVs. 8 channel transmitter or receiver. **\$179/ea**. SPECIAL PRICE EATV Visit our website for dealers or order on-line at [www.4stv.com](http://www.4stv.com)

**SATELLITE TV**. Complete selection of C & Ku band equipment. [WWW.DAVESWEBSTORE.COM](http://WWW.DAVESWEBSTORE.COM)

**YAESU FT-990** S/N 4M400010, purchased new used for one year, includes internal DSP, 2 VFOs, Accessories: 1) MD-1 desk mike and regular mobile mike; 2) SP-6 external speaker with phone patch built in; DVS-2 digital memory recorder; \$1400 plus shipping and packaging. Price is firm. SEND CERTIFIED CHECK INCLUDING ESTIMATED \$100 SHIPPING & PACKAGING COSTS (EXCESS WILL BE RETURNED PROMPTLY: IF NOT ENOUGH, I WILL NOTIFY YOU BEFORE SENDING RADIO). Carroll Marlowe, 1 CEDAR RIDGE, EUREKA, CA 94025. 636-938-3940 WORKU.

**DRAKE TR7 & R7** extender cards. See <http://www.amsatnet-usa.org> \$63.50. Bob W7AVK, w7avk@amsatnet.org 509-765-4721.

## BATTERIES/CHARGERS

**THE SMART BATTERY CHARGER** for lead acid or gel cell batteries. Can be left connected to the battery INDEFINITELY, will not overcharge! Standard kit is 12V @ 1 amp. This kit is 100% complete. For the kit order #150-KIT at \$59.95. For an assembled and tested unit, order #150-ASY at \$79.95. CA residents add 7.75% sales tax. Add \$6.50 per unit shipping. MCM/ISA accepted. A&A Engineering, 2521 W La Palma St, Anaheim, CA 92801. 714-952-2114, FAX 714-952-3280. [www.a-s-engineering.com](http://www.a-s-engineering.com)

## CB — SCANNERS

**SCANNER ANTENNAS**. VHF/UHF. Diskone base antennas \$29.95 + S&H. HF/VHF/UHF super Diskone \$45.95 + S&H. mobile antennas \$24.95 + S&H. super scan duck handheld antennas \$19.95 + S&H. Also antennas for amateur, CB, cell, GMRS, HURS, SWL, TV. Antenna Warehouse, 611 9th Ave., Camanche, IA 52230. MCM/ISA toll free order line: 877-680-7818. [www.antennawarehouse.com](http://www.antennawarehouse.com)

**CB MODIFICATIONS!** Frequencies, books, kits, high-performance accessories, plans, repairs, amplifiers, 10-meter conversions. The best since 1976! Catalog \$3. CB,CI, CB 30655NV, Tucson, AZ 85751. [www.cbcentral.com](http://www.cbcentral.com)

**240+ CHANNEL CB/HAMFIRS/COMMERCIAL RADIOS**. AM/FM/SSB/CW export domestic: RCI, TEK, Motorola, Uniden, Cobra, Alcan, Kenwood, Mics, antennas, linear, meters, mod books, manuals, schematics, night scopes, and tons more stuff! Catalog \$3. MAXTECH, Box 8086, New York, NY 10150. 718-547-8244. [www.penny-circuits.net](http://www.penny-circuits.net)

**CB RADIO REPAIR** \$25 + parts. [www.rileysalelectronics.com](http://www.rileysalelectronics.com) 1-888-834-1495.

## COMPUTER HARDWARE

**HP NETSERVER LX8500** Xeon 750MHz rack mount. Unused cost only \$36K. Make offer. Photo and details on [www.industrialwap.com](http://www.industrialwap.com)



**19" RACKMOUNT ATX PC** chassis, \$149 (with ad). [www.stores.yahoo.com/cti-texas](http://www.stores.yahoo.com/cti-texas), 972-242-8087.

**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro systems (SMS), CHD, Datability, Dialog, DSD, EPL/EX, other DEC compatibles. Please contact us for a quote or fax/email your equipment list. We buy, sell, and trade. **KEYWAYS, INC.** 937-847-2300 or fax 937-847-2350 or email buyer@keyways.com

**BRAND NAME** Perium computers starting at \$50. Call Jerry W2GIA, Disks N Data, 1-800-833-6893 or E-Mail: [dnkcm2@home.com](mailto:dnkcm2@home.com)



**VGA TO COMPOSITE (NTSC) VIDEO CONVERTER** — LUT-2000. Handheld. Powered from keyboard with S-video and RGB outputs, too. 3:1 zoom control with many extras. **\$99/ea**. Matco, Inc., Schaumburg, IL. 1-800-719-9605, sales@matco.com or visit/order on-line at [www.matco.com](http://www.matco.com)

**DATA ACQUISITION**. This very compact and low-cost kit will allow virtually any PC to be used for quick and easy data acquisition and control. It connects to any standard parallel printer port, and despite its tiny size provides eight analog inputs, four digital inputs, and four digital outputs. [www.electronickits.com](http://www.electronickits.com)

**EVERYTHING NEW** w/warranty! Best prices. Motherboards with CPU 900MHz \$195, custom configured systems, modems \$19, DSL modems \$35, multimedia kits, scanners, monitors, cases, \$20. Hard drives sizes to 80 gigabytes. \$40 megabyte \$15. Sound adapter \$10. Call 714-778-0450. Email: [cc@surfside.net](mailto:cc@surfside.net)

**700MHz SYSTEMS** \$199. Computers from \$49, motherboards \$20, color printers \$45, 1.44/1.2 floppies, speakers \$10. 714-778-0450.

**500MHz AMD Duron computer system**. 20 gigabyte hard drive, CD-ROM drive, 128MB memory, 64MB video, 4 USB ports, LAN, 56K modem/voicefax, sound, speakers, keyboard, mouse, ATX case, many FREE applications, 2 year warranty! \$359. 900MHz system same as above but with DVD player. \$449! Upgrade to your old computer. 750MHz CPU and ATX motherboard with video/sound/modem/LAN, all ports \$159! Visa/MasterCard/Amex, order/details toll free 1-877-882-0431, [www.sawere.com](http://www.sawere.com)

**SONY PLAYSTATION plug-in GAME ENHANCER 520 or solder-in mod-chip \$19!** Plays back original or play back up! Visa/MasterCard/Amex, order, details toll free 1-877-882-0431, [www.sawere.com](http://www.sawere.com)

**NewComputer.com COMPARES** prices and detailed product specifications from top online sellers. Visit NewComputer.com to save time when shopping for new computer equipment.

**MAGNETO OPTICAL DRIVES** & media. 230M/128M \$299/\$199 with one piece of media, used 60 day warranty, SCSI interface extra media available. Faster and more durable than zip drives. Bootable PCI or ISA or VLB or EISA SCSI card \$20. SCSI cables, terminators and external enclosures all at great prices! Tape drives and other PC parts and network stuff also in stock! Call UTWEE @ 626-930-1121 or fax 626-930-1123 or email sales@utwewe.com

## COMPUTER SOFTWARE

**HI-TECH SECRETS** — **CDs** Computer/satellite/cable/phone, free e-mail, machines, laser listener, anti-gravity, electromagnetic/electrostatic detectors, pain/virus/AIDs killers, etc. <http://www.hi-techstuff.com>

**KEYSTONE LOGGER**. This new software hides in the background on your computer allowing you to view what other people have been doing on the computer. Great for monitoring the children or the wife. [www.spousewatcher.com](http://www.spousewatcher.com)

## NEW Easy-PC for Windows

**Schematic & PCB Layout CAD**



- True Windows interface
- Integrated Autolace
- Multi-level Undo & Redo
- True Windows 32 bit applications
- Schematic and PCB design as standard
- Intelligent Cut, Copy and Paste, internal & external
- Forward design changes. Schematic to PCB
- Integrated Shape-based AutoRouter (Optional Extra)
- Shape-based copper pour and split power planes
- And now version 4.0 with many new features!!

Call Ohio Automation (740) 596 1023 [www.numberone.com](http://www.numberone.com)


**LIQUIDATION WINDOWS** 95/98, Office suites \$10-69. Windows companion \$5. Windows tutorials \$5, Norton Antivirus, Ghost, Virtual drive \$15. 714-778-0450.

**FREE!!! CD-ROM** and software disk catalog. **MOM 'N' POPPIE'S SOFTWARE**. PO Box 15003-N, Springfield, FL 34609-0111. 352-688-9108. [momnpop@znet.net](mailto:momnpop@znet.net)

**CAM & MOTION**. 2-track PCB (NC) toolpath. Plotcam motion control. [www.ddr-us.com](http://www.ddr-us.com) 321-459-2729. [ddr-us@cllr.com](mailto:ddr-us@cllr.com)

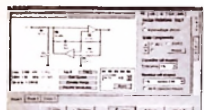**WINDOWS 98 SE \$19! Windows 95B \$79!** Visa/MasterCard/Amex, order/details toll free 1-877-882-0431, [www.sawere.com](http://www.sawere.com)





**WWW.SCHEMATIC.COM** For professional firewire and shareware. Active and passive filter design. 555 designer, linear simulators.

## COMPUTER EQUIPMENT WANTED

**WANTED: FOR** historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-382-2935)

**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), CMD, Datability, Dialog, DSD, EMULEX, other DEC compatibles. Please contact us for a quote or fax/email your equipment list. We buy, sell, and trade. **KEYWAYS, INC.** 937-847-2300 or fax 937-847-2350 or email buyer@keyways.com

**6809 GIMIX CPU** card wanted. Doctor Gordon 305-653-8000. Office 301 16800 NW 2nd Ave., Miami, FL 33169

## TEST EQUIPMENT

**FEITEK PROVIDES** repair, calibration and traceable certifications of test equipment. Free estimates. We buy, sell and trade all makes of test equipment. Visa and MasterCard accepted. Check out our inventory and specials at **WWW.FEITEK.COM** 2752 Walton Road, St. Louis, MO 63114, 314-423-1770.

**KENTRONIX TEST EQUIPMENT SPECIALS.** Check our WEB site at <http://www.kentronix.com> for monthly specials. We are also looking to test equipment, coaxial and waveguide components, manuals, etc. Contact Brian at 732-681-3279 or FAX 732-681-3312. E-Mail: [brian@kentronix.com](mailto:brian@kentronix.com)

**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), CMD, Datability, Dialog, DSD, EMULEX, other DEC compatibles. Please contact us for a quote or fax/email your equipment list. We buy, sell, and trade. **KEYWAYS, INC.** 937-847-2300 or fax 937-847-2350 or email buyer@keyways.com

**TEST EQUIPMENT** technicians needed: calibration and repair techs. Three full-time openings. Our company sells, rents, repairs, and calibrates HP and Tek. We are located in Broomfield, Colorado, between Boulder and Denver. We perform electronic and physical-dimensional calibrations. Please send resume to [irli@calibration.com](mailto:irli@calibration.com)

**WANTED: RADIO** service monitors. IFR, Motorola, HP, Marconi, also late model HP equipment. 716-763-9104 or fax 716-763-0371. <http://www.amtronix.com>

**A-COMM ELECTRONICS.** We buy and sell test equipment. <http://www.a-comm.com> (1891 E. 33rd Avenue, Aurora, CO 80010. Tel: 303-341-2283, fax 303-341-2293)



**PCKET TESTBENCH.** inexpensive RS-232C virtual instrument, with oscilloscope, logic analyzer, counter, and generator models. [www.oricon.com](http://www.oricon.com)

**MODEL 109** pseudo-random noise and arbitrary waveform generator only \$289. TDL Technology, Inc., [www.zianet.com/tld](http://www.zianet.com/tld)

**GIANT DIRECTORY ONLINE.** Over 500 dealers in used test equipment, used semiconductor production equipment, surplus lasers, optics, vacuum equipment, etc. Test equipment auction and rental sites, US and foreign dealers, manual dealers, too! No registration or cookies. [www.big-list.com](http://www.big-list.com)

**POGO PINS** - For automated circuit board testers. Everett/Charles Tech HPA02 & HPA741655 for 10 cents each, now price is over a dollar each. These are reclaimed in excellent condition with no detectable tip wear, heavily gold plated and really nice, your satisfaction guaranteed. \$10 minimum order, 1 pay postage. Send a SASE or email for free sample. Carter Cybernetics, 1655 Sherington Place Z-206, Newport Beach, CA 92663. <http://www.cartercybernetics.com>

**HEWLETT PACKARD** rack mount power supply model 6433B-36VDC and 0-10 amps, with coarse and fine voltage and current adjustments, full documentation, manual, schematics, etc. Gerald Koske, 10204 Thayer Rd., Wonder Lake, IL 60097-9138. Phone 815-648-4046 & 815.

**SENCORE SC-61** oscilloscope. Dual trace 100MHz VHS. Servicing has internal probes, direct probe, demodulator probe, snop loop, manual and LCD digital readout of V-P-P, DCV and frequency. Original cost \$3,200 would sell for \$600. Has less than 20 hours usage. Gerald Koske, 10204 Thayer Rd., Wonder Lake, IL 60097-9138. Phone 815-648-4046.

**CHECK** our growing line of audio test instruments: data sheets, user guides, software. TDL Technology, Inc., [www.zianet.com/tld](http://www.zianet.com/tld)

**KUP-1-WELD® II Thermocouple Welder** produces superior weld contacts that ensure precise temperature monitoring. Features illuminated work area, graduated power control, push-button power activator, internal cooling fan, electronic circuitry, flash protection viewing screen, pen-style alligator-clip holder, 8" wide x 13-1/2" deep x 9" high, weighs 4 lbs. See our ad on page 73. Burrell Scientific, Inc., Pittsburgh, PA, 412-471-2527 or email: [burrellsci2@aol.com](mailto:burrellsci2@aol.com)



**DIGITAL OSCILLOSCOPES.** Our DSO/frequency counters work with your computer, graphic calculator, or Pocket PC. Check out our new 14 MSPS model at [www.electronics.com](http://www.electronics.com) or call us at 704-861-9475.

## SECURITY

**ALARMLAND.COM SECURITY** devices for professionals. Motion detectors, panels, controls, CCTV, and more. Fax your order to 732-840-1390.

**WIRELESS MICROPHONE.** Micro-sized, UHF crystal-controlled, easy-to-assemble kit. Range up to 3,000 feet. Excellent sensitivity \$39. VHS, 1370 Transcon Street, Suite 201, Napa, CA 94558. Email: [Vhs18097@aol.com](mailto:Vhs18097@aol.com)

**SPECIAL PROJECTS** Wild, weird, wacky, wonderful hardware, technical coaching, website designs. Lone Star Consulting Inc. [www.lonestarteknet.com](http://www.lonestarteknet.com)

**KEYSTROKE LOGGER** This tiny piece of hardware installs between your keyboard wire and computer in seconds. Then it logs all keystrokes, which you can view at your convenience. [www.spousewatcher.com](http://www.spousewatcher.com)

**SURVEILLANCE-COUNTERSURVEILLANCE.** I buy and sell used equipment. Steve 410-879-4035.



**WWW.COVERTBUG.COM 8 HR 22 min DIGITAL RECORDER.** Internal microphone & speaker, VOX, external microphone & earphone. Telephone recording code: 4x1-38x9/16in. Visit website for details. Brochure, \$235 + \$6 S&H. Sheffield Electronics, PO Box 377940, Chicago, IL 60637. 773-324-2196. [sheffield@covertbug.com](mailto:sheffield@covertbug.com)



**THE TLP-1** records automatically all telephone conversations up to 12 hrs. on a single tape. 6ers. The **FMX-1** detects and locates bugging devices. 6ers. The **TLP-1** stops others from listening in or recording your telephone conversations. \$499. Send check to Vaki, 2930 Pine Ave., Niagara Falls, NY 14301. Buy wholesale directly from manufacturers.



**9 VOLT IR sensitive B/W high res 430 TVL camera** with optional black low-profile swivel adjustable enclosure. Pin hole or Std. lens type, 6, 8, and 12mm lenses are available. 1/3" CCD. 3.6mm/F2.0 lens included; works from 7.5-13 VDC, highest voltage range in market. 0.08 lux, 1.27" x 1.27" x 0.5"D pinhole or 1" deep standard. \$49 each. Enclosure \$8; optional lens: \$18. Dealers welcome. Matco, Inc., Schaumburg, IL 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)



**PC MONITOR AS SECURITY MONITOR.** The VGA-801 accepts standard NTSC or PAL inputs for display on any existing VGA/SVGA computer monitor. Small compact size. Over 600 lines of resolution, twice that of standard TV monitor! \$69 each. Dealers welcome. Matco, Inc., Schaumburg, IL 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)



**40 DAYS and 40 NIGHTS RECORDER.** Time lapse, can be activated by either contact closure or continuous duty operation with standard T-120 tape. Models from \$349-\$529. Matco, Inc., Schaumburg, IL 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)



**AS-1004 wireless 2.4GHz FCC approved 14GHz transmitter & receiver** with audio! Capable handling total of 4 wireless cameras, range >300'. Built-in camera, 400 TV line. \$199 per system. Additional cameras at \$129/each. Matco, Inc., Schaumburg, IL 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)



**QUAD VIDEO CABLE MODULATOR.** CVS-600 inserts 4 composite video signals on existing cable channels, 1 thru 95. Watch 4 remote security cameras from any TV in your home! Built-in signal amplifier and comb filter eliminates any ghosting and actually IMPROVES existing video! Only one unit needed with existing cable system. \$199/each and \$169/each in qty. of 4. Matco, Inc., Schaumburg, IL 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)



**CCD BULLET CAMERAS B/W & COLOR.** AX-800 series, weather resistant high impact design with swivel bracket. Will work with Matco's scanning motor, 3/4" diameter x 3" long approx. B/WV, 400 line/0.2 lux. \$79/each. Color: 350 lines/2 lux. \$119/each - price reduction. Matco, Inc., Schaumburg, IL 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)

**SECURITY DISTRIBUTORS** needed for our complete line of products. Complete line of products shown above. MATCO, Inc. Visit [www.matco.com](http://www.matco.com) and call 630-350-0299 for more info.



**SCANNING MOTOR - A-330SC** with universal mounting bracket accepts all standard 1/4 x 20 threaded CCTV cameras. No oil, just PAN 75 degree of continuous motion with a scan rate of 5 seconds per cycle. 110 volt indoor operation, but can be adapted for outdoor use. Includes 12 foot power cord. Perfect solution to triple your effective camera viewing area! \$39/each, or \$25/each in qty. of 3. Small size, 3-1/2" x 2-1/2". Matco, Inc., Schaumburg, IL 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)




**WEATHER RESISTANT OUTDOOR CAMERAS.** WR-700 type, high impact tempered glass with stand. Black & white (430 lines), or color (420+ lines) available. Standard 3.6mm lenses with optional lenses of 6, 8, and 12 mm at \$20 extra. B/W \$119/each, color \$179/each. Small compact size with sun shield. Matco, Inc., Schaumburg, IL 1-800-719-9605, [sales@matco.com](mailto:sales@matco.com) or visit/order on-line at [www.matco.com](http://www.matco.com)





**5" AND 5.5" LCD** high definition color monitors wisteria 960 x 240 pixels w/brightness and tint controls. Attractive enclosure with built-in speaker. Great for security or general purpose use. Both models have a small compact foot-print with an ultra-bright display. RCA inputs NTSC or PAL. Special price this month only with regulated power **\$249/each**. Matco, Inc., Schaumburg, IL 1-800-719-9605, sales@matco.com or visit/order on-line at [www.matco.com](http://www.matco.com)

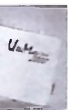

**VGA TO COMPOSITE (NTSC/PAL) VIDEO CONVERTER** — ULT-2000. Small foot-print. Powered from keyboard with 5-video and RGB outputs, too. 3:1 optional zoom control, simultaneous outputs with many extras. **\$99/ea.** Matco, Inc., Schaumburg, IL 1-800-719-9605, sales@matco.com or visit/order on-line at [www.matco.com](http://www.matco.com)



**16 CHANNEL MULTIPLEXER.** Display 4, 8, and 16 video outputs directly on a TV or security monitor. This is the only device which allows full screen display of video on VCR playback (see 40 days and 40 nights recorder). Plenty of options including pliers zoom, individual gain adjustments, etc. Price slashed to **\$649 each** — Winter special! Matco, Inc., Schaumburg, IL 1-800-719-9605, sales@matco.com or visit/order on-line at [www.matco.com](http://www.matco.com)



**14" COLOR** — high resolution SECURITY MONITOR w/4 channel switcher. High impact enclosure with modern front panel 4 channel video and audio switcher. High quality speaker built-in. Components purchased separately would exceed \$560. Winter special! Price slashed to **\$349/each**. Matco, Inc., Schaumburg, IL 1-800-719-9605, sales@matco.com or visit/order on-line at [www.matco.com](http://www.matco.com)



**14" BW** high resolution SECURITY MONITOR. A standard 12" monitor is just too small for most applications. Attractive dark gray enclosure with built-in speaker. 75 ohm termination switch for balancing with all types of CCD board cameras and other video inputs. **\$139/each**. Matco, Inc., Schaumburg, IL 1-800-719-9605, sales@matco.com or visit/order on-line at [www.matco.com](http://www.matco.com)



**INFRARED FILTER ELIMINATES 99.9% OF ALL VISIBLE LIGHT** — IL-9000. All B/W CCD cameras are IR sensitive. Place a 25 watt or less light behind the 3" x 3" filter, and you will see in the DARK. **\$18/each**. Purchase 2 for **\$30**. Matco, Inc., Schaumburg, IL 1-800-719-9605, sales@matco.com or visit/order on-line at [www.matco.com](http://www.matco.com)



**COLOR — LOW LIGHT 2 LUX** 32mm x 32mm, 350 TVL with optional enclosure. Pinhole and standard lens types available. Price reduction, **\$99/ea.** Add \$10 for enclosure with swivel mount. Matco, Inc., Schaumburg, IL 1-800-719-9605, sales@matco.com or visit/order on-line at [www.matco.com](http://www.matco.com)



**ULTRA LOW-LIGHT COLOR — 470 line/0.3 lux camera.** CNL11-C-HR, 1.5" x 1.5" x 1", 1/3" CCD board camera with 3/6mm F2.0 lens. Excellent color rendition using Sony chipset. 12VDC @ 240 mA. Optional 6, 8, 12mm lenses. Special **\$179/each**. Matco, Inc., Schaumburg, IL 1-800-719-9605, sales@matco.com or visit/order on-line at [www.matco.com](http://www.matco.com)

## SATELLITE EQUIPMENT



**FREE BIG DISC catalog.** Low prices! Systems, upgrades, parts, and "ADTV" Skyvision, 1010 Frontier Dr., Fergus Falls, MN 56517, [www.skyvision.com](http://www.skyvision.com). Call 1-800-543-3025.



**BEST PRICING** on 18" satellite TV systems for home and RV. DISH Network DirectTV, multi-room viewing options, accessories, more. [www.skyvision.com](http://www.skyvision.com). Call 1-800-543-3025.

**SATELLITE REPORT:** Find all the latest in satellite descrambling in this 54-page report. Lists all the cheapest and reliable sources for hacked cards and equipment. [www.electronickits.com](http://www.electronickits.com)

**SATELLITE TV.** Complete selection of C & Ku band equipment. [www.daveswebshop.com](http://www.daveswebshop.com)

## MILITARY SURPLUS ELECTRONICS

**DOSIMETERS/RADIATION DETECTING KITS.** New Canadian military surplus, now illegal to import due to recent change in Arms Control laws. Ten dosimeters, two chargers, two radiation meters w/charging case. Single D cell powers chargers and meters. Survival, nuclear war, nuclear power plants, \$125 shipped US. Credit cards, checks. Dealers/quantities welcome. Steve 410-879-4035 or Steve@swsec.com

## AUDIO — VIDEO — LASERS



**ANTIQUE VIDEO TRANSFER SERVICE:** transfer any 2" QUADRIPLEX tape. Affordable fast! Phone/fax 415-821-7500 or 415-821-3359. 5001 Diamond Heights Blvd., San Francisco, CA 94131-1621.

**PC MONITOR AS SECURITY MONITOR.** The VGA-801 accepts standard NTSC or PAL inputs for display on any existing VGA/SGA computer monitor. Small compact size. Over 600 lines of resolution, twice that of standard TV monitor! **\$69 each.** Dealers welcome. Matco, Inc., Schaumburg, IL 1-800-719-9605, sales@matco.com or visit/order on-line at [www.matco.com](http://www.matco.com)

**PRO AUDIO** recording gear & video editing equipment, antique radios, tubes & meters. [www.bibbtek.com](http://www.bibbtek.com) (regular updates) or call Tom 856-222-0636, fax to 856-222-0638 for a fresh list. Credit cards welcome.

**SYNC-A-LINK UNIVERSAL video sync generators.** Phone 918-479-6451. Email: [rlc@stelco.com](mailto:rlc@stelco.com) **Sync-A-Link**, P.O. Box 4, Locust Grove, OK 74352.



**STEREOSCOPIC VR 3D generator.** GenCams. 118-479-6451. Email: [rlc@stelco.com](mailto:rlc@stelco.com) **Sync-A-Link**, P.O. Box 4, Locust Grove, OK 74352.

**SPECIAL PROJECTS:** Wild, weird, wacky, wonderful hardware, technical coaching, website designs. **Lono Star Consulting, Inc.** [www.lonestartek.net](http://www.lonestartek.net)

**XY CUTTING** laser. LaserCam model 4000 24x56" lens top cover, software, & docs. Insurance claim. Smoke damage. Cost \$100K. More info on [www.industrialweld.com](http://www.industrialweld.com) asking \$22 C.O.B.O. [ed@surplus@aol.com](mailto:ed@surplus@aol.com) 541-791-4411.

**PANASONIC S-VHS VCR** model AG-6730 time lapse recorder \$275 & 2 digital CCD color cameras WV-C1320 \$200. 301-8524.

## CABLE TV

**CABLE CONVERTERS.** Brand new Viewmaster, Media Tech. Latest technology. Blowout wholesale prices. Guaranteed, ready to go. Call for flyer 412-833-0773.

**CABLE PARTS for all makes and models.** raw boxes at low prices. Call 1-888-817-8100. No NY sales. [www.chipplace.com](http://www.chipplace.com)



**QUAD VIDEO CABLE MODULATOR.** CVS-600 inserts 4 color or black & white composite video signals on unused cable channels, 81 thru 95. Watch 4 remote security cameras from any TV in your home! Built-in signal amplifier and comb filter eliminates any ghosting and actually **IMPROVES** existing video! Only one unit needed with existing cable system. \$199/each and **\$169/each** in qty. of 4. Matco, Inc., Schaumburg, IL 1-800-719-9605, sales@matco.com or visit/order on-line at [www.matco.com](http://www.matco.com)

**CABLE PARTS & EVERYTHING.** Parts & accessories. Best prices & quantity discounts. WE DON'T SELL BOXES. 1-800-MODULE-0.

**WANTED: TEKNIKA** 6510 cable converter boxes. 707-928-5528. [lorrendaro@webtv.net](mailto:lorrendaro@webtv.net)

**CABLE REPORT:** This 50 page report contains all the latest in how cable systems have been compromised including cheap and reliable sources for test chips and equipment. [www.electronickits.com](http://www.electronickits.com)

**CABLE PARTS:** Computer parts. Call for best prices or visit us on the Web: [www.CB-Electronics.com](http://www.CB-Electronics.com) or call 1-800-436-8630.

**POSITIVE AND** negative cable TV filters. [www.gaffers.com](http://www.gaffers.com) 1-800-235-8080 Mike is back, give us a call. We can help in all situations.

**1-800-380-9530. SPECIALIZING** all your cable needs. Specializing in wholesale pricing on raw unmodified converters. Large quantities in stock ready to ship. Call for monthly specials.

**1-800-322-5286. SPECIALIZING** in raw unmodified converters. We carry all manufacturers. Call for wholesale pricing.

**OV PLUS WHOLESALE** [www.ovplus.com](http://www.ovplus.com) New unmodified 860MHz/125 channel converter. Features channel 3 or 4 switchable output (HRC, ICR, standard); audio & video cables included; parental control; sleep timer; last channel recall; 4 memory + volume remote control. Call for wholesale pricing. See habia español. **DEALERS WANTED. OV PLUS: 1-877-293-6260**

**CABLE TV** converters, brand new 125 eh like VM4000 \$49 (10 lot). Original converters as low as \$29. Warranty. call for best prices. 214-552-0078

**CABLE BROKER'S** is having their final blowout of their warehouse. The following unmodified equipment is available to other brokers and cable companies in 100 lots: Zenith 371600 50MHz/88 5507 \$25 VIP 512 Pioneer 6310 \$40 6111 \$25 V558 \$45 2224SP 2254 \$80 5A 8580 7 button 8570 \$25 8600 \$40 You must prepay shipping on all orders \$175. See habia español. Call 1-800-219-8618

**CABLE PARTS** for all makes and models, computer software, assembly & engineering, parts and accessories. Best prices & quantity discounts. NO CALIFORNIA SALES. <http://www.angellfire.com/movies/testchpt1/index.htm>



## TELEPHONE/FAX

**PHONE MANAGER:** This unit looks exactly like a Caller ID, except it records time, date, and length of all outgoing calls. [www.spousewatcher.com](http://www.spousewatcher.com)

## COMPONENTS

**CASH PAID FOR ICs.** Military or commercial integrated circuits, transistors, diodes, any semiconductor components. **ELECTRONIC SURPLUS, INC.** 5363 Broadway, Cleveland, OH 44127. 216-441-8500 or fax 216-441-8503, since 1946. [www.electronic-surplus.com](http://www.electronic-surplus.com)

**RF TRANSISTORS, TUBES, TEFLON WIRE, SILVER MICA CAPS** 25C2290, 25C2879, 5D1446, MRF455, MRF454, 25C1669, 25C2166, 25B754, 27A222AP, 25C2086, 7A722AP, MRF47, MRF317, 5A7, etc., 4C2508, 4C1000A, 4CX1500B, 3CX400A7/8B74, 3CX3000A7, 4CX400A, 572B, etc. Teflon wire specials, 1,000 ft. 16 gauge .15 cents ft., 1,000 ft. 18 gauge .14 cents ft. silver mica caps, resistors, see our catalog for other products. Westgate 1-800-213-4563.

**MATCO** Will design, engineer, and develop a 2.4GHz wireless 8 channel solution for your remote applications. FCC approved. Matco, Inc., Schaumburg, IL 60196-9605. E-Mail: [msales@matco.com](mailto:msales@matco.com) Web site: [www.matco.com](http://www.matco.com)

**ELECTRONIC COMPONENTS.** kits, test equipment, books, tools, and supplies for hams, hobbiests, and business. Many hard-to-find items like variable capacitors, vernier dials and drives, coil forms, magnet wire, toroids, more. [www.oselectronics.com](http://www.oselectronics.com)

**WANT TO BUY:** ICs, military & aircraft relays, diodes, transistors, connectors, tantalum capacitors, electronic test equipment & most components. Hefly Electronic Inc., E-Mail: [Hefly165@aol.com](mailto:Hefly165@aol.com) 818-718-1165, FAX 818-341-5506.

**PELTIER INFORMATION DIRECTORY ONLINE** Information site on Peltier devices (thermoelectric cooler/heater/generator modules). Tips, manufacturers, supplier sources, etc. Free. No registration. [www.peltier-info.com](http://www.peltier-info.com)

**TUBES GALORE** for sale. Send SASE for list. AE. Also sockets, connectors, Collins plugs, ballast, and time delay tubes. Wanted: tube socket extenders, Cinch-Jones connectors, military connectors, sockets, hi-voltage ceramic capacitors, vernier drives. Ytterronics, PO Box 8873, Ft. Lauderdale, FL 33310-8873. Phone 954-581-1340, fax 954-581-0777. Fred Schmidt N4TT.

## MICROCONTROLLERS

**ATMEL 89CXXXX** programmer, IBM parallel port, C++ source code, schematics. \$250 + S/H. <http://members.aol.com/HawaiianComputer>

**PIC & ATMEL PROGRAMMERS** from \$15.95 and \$29.95! Visit [www.electronic123.com](http://www.electronic123.com) for complete details. Amazon Electronics, Inc. Toll free 1-888-549-3749.

**PIC PROGRAMMERS:** Several different programmer kits that you can build yourself all the most popular PIC and Atmel chips. [www.electronickits.com](http://www.electronickits.com)

## ANTIQUE ELECTRONICS

**WANTED: FOR** historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 2409-1031 (540-763-3311) 540-382-2935.

**WESTERN ELECTRIC** wanted: 1920s-1960s. Amplifiers, mixers, pre-amps, speakers, tubes, etc. FREE OFFER 1-800-251-5454.

**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SIS), CMC, Possibility, Dialog, DSD, EMULEX, other DEC compatibles. Please contact us for a quote or fax/email your equipment list. We buy sell and trade. **KEYWAYS, INC.**, 937-847-2300 or fax 937-847-2350 or email [buyer@keyways.com](mailto:buyer@keyways.com)

## AVIATION ELECTRONICS

**BUY-SELL-TRADE** avionics and avionics test equipment. IFR, Collins, King, Bendix, Lincoln, Sperry, others. Wire markers, Kingley, Eubanks pilot static sets, Setra, tools, Deitch, Daniels, Scorsby, etc. balancers. [www.avionicsplus.net](mailto:www.avionicsplus.net), [sille2k@yahoo.com](mailto:sille2k@yahoo.com) FAX 941-625-0494, PH 941-625-3222.

**KUP-I-WELD® II Thermocouple Welder** produces superior weld contacts that ensure precise temperature monitoring. Features illuminated work area, graduated power control, push-button power activator, internal cooling fan, electronic circuitry, flash protection viewing screen, pen-style alligator-clamp holder, 8" wide x 13-1/2" deep x 9" high, weighs 4 lbs. See our ad on page 23. Burrell Scientific, Inc., Pittsburgh, PA 412-471-2527 or email: [burrellsci2@aol.com](mailto:burrellsci2@aol.com)

## THERMOCOUPLE WELDER

**KUP-I-WELD® II Thermocouple Welder** produces superior weld contacts that ensure precise temperature monitoring. Features illuminated work area, graduated power control, push-button power activator, internal cooling fan, electronic circuitry, flash protection viewing screen, pen-style alligator-clamp holder, 8" wide x 13-1/2" deep x 9" high, weighs 4 lbs. See our ad on page 23. Burrell Scientific, Inc., Pittsburgh, PA 412-471-2527 or email: [burrellsci2@aol.com](mailto:burrellsci2@aol.com)

## PUBLICATIONS

**BASIC STAMP 2** users: "Inside the BASIC Stamp II" tells how the PBASIC interpreter works, how code is stored in EEPROM, how to optimize code for space and speed. 160 pages, 50 illustrations, many examples. See <http://members.aol.com/stamp2book>. Send \$29.95 check or money order (US funds) to Brian Forbes, PMB 326, 19672 Stevens Creek Boulevard, Cupertino, CA 95014-7465.

**WWW.COVERTBUG.COM SURVEILLANCE DESIGN BOOK** 117 production schematics, all types of transmitters, Room, telephone, battery, and mains powered. Countersurveillance chapter with equipment. Visit website for details. Brochure. \$40 + \$6 S&H. Sheffield Electronics, PO Box 377940, Chicago, IL 60637. 773-324-2196. [sheffield@covertbug.com](mailto:sheffield@covertbug.com)

**"The Nuts & Volts of Basic Stamps"** Now Available at [www.nutsvolts.com](http://www.nutsvolts.com) or call toll free 1-800-783-4624

## ROBOTICS

**ROBOT BOOKS.COM** visit our web site for reviews of robotics books, plus robot kits, toys, movies, and magazines! [www.robotbooks.com](http://www.robotbooks.com)

**Arobot KIT** from Arrick Robotics uses the BASIC Stamp II. Quality metal construction. Easy to assemble and very expandable. \$235. <http://www.robotics.com/arobot>

**EASY RC.** Preprogrammed PIC accepts standard RC pulses and sends control signals to motor controller for direction and proportional speed control. Single channel or dual channel with mixing available. Info: 570-735-5053. <http://divelec.tripod.com> email: [carlkj3m@bigfoot.com](mailto:carlkj3m@bigfoot.com)



**MOTOR CONTROLLERS.** PWM, 12V, 24V, 35A, many features from 400 plus \$84. Info: 570-735-5053. Details: <http://divelec.tripod.com> Toll free orders (only) 1-888-314-6998.

**ROBOT KITS.** Over 30 complete robot kits from beginner to advanced at [www.electronickits.com](http://www.electronickits.com)



**THE MBOB** robot base from Tekwid Robotics is compact and powerful. Can carry a 10 pound payload. 8 versions to choose from. Visit our website for more info. \$149.95. [www.tekwid.com](http://www.tekwid.com) 512-447-6476.



**MOBILE ROBOT PLATFORM.** Been wanting to build a powerful robot but don't know where to start? This platform kit is the answer. Includes chassis components, 2 worm-gear, two-speed high-torque motors, large 8" drive wheels, and custom 6" rear idler assembly. Only \$239 plus S&H. Details: <http://www.kadronix.com>. (Mention this ad for 10% discount.)

**NEW - COPROCESSORS** and controller boards for small bots, PIC singleboard computers and other prototyping components. [www.oricomtech.com](http://www.oricomtech.com)



**ROBODYSSEY SYSTEMS, LLC.** Mobile Robotics. Robodyssey™ Systems, LLC. has three new mobile robotics platforms — built to last, laser cut anodized aluminum; drilled and tapped mounting points require minimal hardware; control methods include Stamp™, tether, or analog. Designed to meet requirements of RoboMelee™ (see <http://dpln.home.netcom.com>), IEEE MicroMouse, F-180 Small Size RoboCup, Trinity College Fire Fighting Home Robot, or Beam. Contact: sales@robodyssey.com [www.robodyssey.com](http://www.robodyssey.com)

## CNC

**pBREAK BREAKOUT** board for parallel and game ports. Extensive tutorials. <http://www.pcnkitts.com>

## AFFORDABLE CNC MACHINES



Simple to Use

Run From Any Version of Windows®

[www.flashcutcnc.com](http://www.flashcutcnc.com)

Automated Machine Tools to Produce  
• Panels  
• Chassis/Housings  
• PCB Prototypes • Any 3D Part

**FLASHCUT CNC™**

1263 St Camino Real, Menlo Park, CA 94025  
4949 St. Elmo Avenue, Bethesda, MD 20814  
Tel 888-883-3274 Fax 650-853-1405

## PLANS — KITS — SCHEMATICS

**ELECTRONIC KITS:** Hundreds of electronic kits and projects. Where else except [www.electronickits.com](http://www.electronickits.com)

**FUN KITS,** remote control, motor controllers, PIC experimenter boards. Quality guaranteed. Secure online ordering. [www.dirkits.com](http://www.dirkits.com)

**WWW.COVERTBUG.COM SURVEILLANCE TRANSMITTERS** using all RadioShack's numbered parts are easy to build with our kit type plans. Three room, two telephone transmitters for the FM band and above. \$7. No personal checks. Sheffield Electronics, PO Box 377940, Chicago, IL 60637. 773-324-2196. [sheffield@covertbug.com](mailto:sheffield@covertbug.com)

**ISA DIGITAL/ANALOG BOARD.** Great for experimenters, designers, students. 27 digital I/O lines, eight 8-bit AD inputs, one with mike preamp, two 8-bit DA outputs, one with power amp, buffered data, address and control lines, plus 3 spare selects for expansion. Bare board only \$20, kits and assembled available. More information and FREE control and embedded tutorial at [www.learn-c.com](http://www.learn-c.com)



**MOBILE ROBOT PLANS.** Want to build a powerful radio-controlled mobile robot? These plans explain how includes descriptions and photos. Also includes controller schematic, parts list and BASIC Stamp source code. Only \$29. <http://www.kadronix.com>

## MISCELLANEOUS ELECTRONICS FOR SALE

**HARD-TO-FIND** parts: PTV screens, modules, chassis, flybacks, tuners, tubes, for all brands. Models: 478-271-4561. Scarborough, TN, 1422 Old River Road, East Dublin, GA 31027. [scarborough@pcnow.net](mailto:scarborough@pcnow.net)



**HIGH QUALITY TOOLS AND STAINLESS STEEL HARDWARE.** European and American screwdrivers, nutdrivers, pliers, hexkeys, balldrivers, and more! Wilba, Bondhus, and Knipex. Stainless cap screws, machine screws, nuts, washers, U-bolts, and eyes. Free catalog. Robert Mink Import-Export, Box 64377, Fair Haven, NJ 07704. Telephone or fax 732-758-8388. E-Mail: w2tw@compuserve.com



**SOLAR-POWERED FAN HAT.** Baseball type hat with solar powered fan. Great for sports fans, golfers, etc. Available in red or blue. \$19 plus \$2.00 shipping. CA residents add 7.75% sales tax. Visa/MC/Disc/Amex OK. H.T. Orr Computer Supplies, 249 Juanita Way, Placenta, CA 92676. 714-528-9822. 1-800-377-2023. FAX 714-993-6216.

**RS485/422/232/TTL**

ASC2AT \$45

- Converters
- Repurposers
- Fiber Optics
- Digital I/O
- Multidrop RS232
- Cat-5 Uplink
- Auto TX Enable

**Extensive Interface Product Line**

RS232 "Extension Cords"  
Up to 1152 Kbps, 4000 ft. ++  
Large Multidrop Networks  
Isolated Units, Smart Units  
Remote Relay "Extension Cords"

Call the RS485 Wizards at  
(513) 874-4796

**RES = R.E. Smith**  
www.rs485.com

**FOR SALE:** Transmission Equipment. (2) 24 meter channel master send/receive dish with Prodin non-penetrating mount. (2) 8 watt transmitters. Sierra Com w/cn controller. (2) 18 meter channel master dish w/channel master (Baird) non-penetrating mount. (2) sky dish RF hoods w/ILF boxes 4 watts each. (1) 24 meter Prodin dish w/mount. Contact: Bob Newstead 480-948-0586 or Morris Scott 602-307-0180. Equipment located in Scottsdale, AZ. Buyer responsible for removal.



**ANAHEIM WIRE PRODUCTS. DISTRIBUTOR OF ELECTRICAL WIRE AND CABLE** since 1973. Items available from our stock: Hook up wire, Automotive primary wire, GXL, SXL, Plenum cable, Teflon wire, Multi-conductor cable, Irradiated PVC, SO-CORD, Hi-Spec wire, Building wire, Welding cable, Battery cable, Transformers, Wire, Shrink tubing, Cable ties. Contact: Wire cut & strip to specs. If interested, please call 1-800-626-7540. FAX: 714-563-8309. Visa/MC/Amex USE US ON THE INTERNET: http://www.anahemwire.com OR E-Mail: info@anahemwire.com

**FOR SALE:** Healthkit, other test and audio equipment and miscellaneous. 36 items. LSASE for detailed list. Richard Flaws, 212 Mondovi Drive, Oswego, IL 60543-8408.

## Computer Desktop Encyclopedia

Online Now at  
www.nutsvolts.com

**For Experts and Novices** — The Encyclopedia contains more than 15,000 definitions, illustrations, photos, charts and diagrams, and covers the field from micro to mainframe.

**Twenty Years in the Making** — Starting as The Computer Glossary in 1980, the Encyclopedia is the longest-running computer dictionary. Edited by Alan Freedman, noted computer lexicographer with 40 years of experience in the industry, the Encyclopedia is the most comprehensive reference of its kind.

**NUCLEAR ELECTRONICS** (NIM, CAMAC). PMTs, optics, high vacuum, and high voltage components and equipment. Guaranteed quality at reasonable cost. OE Technologies, Box 703, La Madera, NM 87539. Pk. 505-583-2482. Fax 505-583-9190. E-Mail: oetech@newmexico.com http://www.oetech.com

## MISCELLANEOUS ELECTRONICS WANTED

**DEC EQUIPMENT WANTED!!!** We are buying DEC systems, boards, terminals, devices and peripherals. Also Scientific Micro Systems (SMS), CDC, Datability, Dialog, PDS, EMULEX, other DEC compatibles. Please contact us for a quote or fax/email your equipment list. We buy, sell, and trade. **KEYWAYS, INC.** 937-847-2300 or fax 937-847-2350 or email buyer@keyways.com

**WANTED:** Tubes, radios, transmitters, receivers, gyros, bearings, connectors, relays, lamps, synchros. Hymess Company, 705B Debar Road, Monroe Twp., NJ 08831. Phone: 609-395-1116, Fax: 609-395-1117.

**WANTED: BALANCING** machines & vibration analyzing equipment manufactured by the following: Spectra Dynamics, Hoffmann, Bentley Nevada, Schenck, IRD Mechanalysis, Gishco, Contact Mike Park at E.T. Balancing, 12823 Athens Way, Los Angeles, CA 90061. 310-538-9738, FAX: 310-538-8273.

**CASH PAID FOR ICs.** Military or commercial integrated circuits, transistors, diodes, any semiconductor. **ELECTRONIC SURPLUS, INC.** 5363 Broadway, Cleveland, OH 44127. 216-441-8500 or fax 216-441-6503, since 1946. www.electronic surplus.com

**WANTED: EXCESS ELECTRONIC COMPONENTS, BOARD-LEVEL COMPONENTS; ICs, MEMORY, TRANSISTORS, DIODES, CAPS, RELAYS, ETC. CALL UPS** 562-430-2453 FAX 562-439-0453

**WESTERN ELECTRIC** wanted: 1920s-1960s. Amplifiers, mixers, pre-amplifiers, speakers, tubes, etc. FREE OFFER 1-800-251-5454.

## BBS & ONLINE SERVICES

**WWW.BUSINESS.COM** Your Cherry Master & B's liners website.

## EDUCATION

**MAGICIAN** is available to solve your RF problem. I will teach you in my laboratory how to do it. Young engineers and technicians are welcome. SMT prototyping up to 3GHz for customers. Minaret Radio. John Horvath ph: 909-943-3676.

## BUSINESS OPPORTUNITIES

**AFFILIATES WANTED:** If you have a website you can earn a 10% commission for every person that you refer to our site. See complete details at www.spousewatcher.com

## REPAIRS — SERVICES

**(E)EPROM PROGRAMMING** done quickly and economically. One day turn around. Typical: Simple copy \$3 per device. Also prototyping, design and consulting services available. Call or send SASE to: **Luzer Electronics, 4023 North Bayberry, Wichita, KS 67226.** 316-687-2127. FAX 316-687-3103.

**CIRCUIT BOARDS** for projects, prototypes, short runs. From your artwork. Low cost. Atlas Circuits 704-735-3943. www.pcbatlas.com

**SPECIAL PROJECTS:** Wild, weird, wacky, wonderful hardware, technical coaching, website designs. **Lone Star Consulting, Inc.** www.lonestarok.net

**MECH ENGINEERING CONSULTING:** machine design & packaging from conceptual to manufacturing; detailing, bill of material, part procurement, & proto build. **MECHANICAL ENGINEERING SERVICES** 508-339-7837 or email: SEGSCG@aol.com (Ask for Greg)

**WELD ALUMINUM WITH PROPANE:** EZ, INEXPENSIVE, STRONG. DETAILS: WEEKS. 36 CAROLINA ST. TAYLORS, SC 29687. 1-800-547-WELD(9353) FAX 846-244-6349. http://www.duraloc.com

**Choose a category for your ad from these classifications.**

10. Ham Gear
20. Batteries/Chargers
30. CB/Scanners
40. Music & Accessories
50. Computer Hardware
60. Computer Software
70. Computer Equipment Wanted
80. Test Equipment
85. Security
90. Satellite Equipment
95. Military Surplus Electronics
100. Audio/Video/Lasers
110. Cable TV
115. Telephone/Fax
120. Components
125. Microcontrollers
130. Antique Electronics
135. Aviation Electronics
138. Thermocouple Welder
140. Publications
145. Robotics
148. CNC
150. Plans/Kits/Schematics
155. Manuals/Schematics Wanted
160. Misc. Electronics For Sale
170. Misc. Electronics Wanted
175. BBS & Online Services
180. Education
190. Business Opportunities
200. Repairs/Service

## Classified Ad Instructions

TYPE or PRINT your **ELECTRONICALLY RELATED** ad copy **CLEARLY** (not all caps) on a separate piece of paper. Spell out words when submitting handwritten copy. Calculate the number of words and multiply it by the appropriate rate (see RATE PER WORD section). Include any charges for bold and/or CAPPED words, any artwork costs that would be applicable, and/or costs for boxing your ad (explained below). Choose the appropriate classification for your ad to appear in (see below). If no classification is indicated, it will be placed in Misc. Electronics or wherever we deem most suitable. Enclose your name, address, phone number, and **Nuts & Volts** account number from your mailing label (if available) for identification purposes. Include all payment **CLASSIFIED RUN ON A PRE-PAID BASIS ONLY** — and mail your completed order to:

**NUTS & VOLTS MAGAZINE**  
430 Princeton Ct., Corona, CA 92879.

## RATE PER WORD

The ad rate for current **PAID** subscribers is **60¢** per word. All others pay **\$1.20** per word. There is a **\$9.00** minimum charge per ad per insertion.

## BOLD WORDS AND/OR CAPS

Words to be set in bold or CAPS are each 10¢ extra PER WORD. **BOLD CAPS** are 20¢ extra per word. The first two words of each ad are bold capped at no charge. Indicate bold words by underlining. Words normally written in caps (e.g., IBM) and accepted abbreviations such as VAC or MHz are NOT charged as all cap words. Use a two-letter abbreviation for boxes.

## PHOTOS, DRAWINGS, BOXES

A photo or drawing may be run at the top of your classified ad for an additional **\$10.00** (1" depth max.) for camera-ready art. No words are allowed in this area. To BOX your ad, include an additional **\$50.00** for copy-only ads or **\$75.00** for ads with art or photos. Photos may be emailed to classad@nutsvolts.com.

## EMAILING/FAXING AD COPY

You may email or fax in ad copy or changes before the closing date (5:00pm on the 5th) using MasterCard or Visa. Include credit card expiration date, the name that appears on the card, a daytime phone number, and your Nuts & Volts account number. Email ads to: classad@nutsvolts.com or fax to 909-371-3052. Ads without credit card information will not be listed as received until payment is received in full. **WE DO NOT CALL, EMAIL, OR FAX BACK VERIFICATION OR QUOTES FOR BOLD AND FAXED-IN ADS.** For verification of email or faxed-in ads, please call 909-371-8497.

## DEADLINE

Prepaid ads received by 5:00pm on the closing date (5th of the month) will appear in the following month's issue. Ads submitted through the 5th, but received after the closing date, will be placed in the next available issue. No cancellations or changes after the 5th. Cancellations and changes must be submitted in writing.

## IMPORTANT INFORMATION

All classified ads are running copy only. No special positioning, underlining, dot leaders, extra space, etc. is allowed. All advertising in Nuts & Volts is limited to electronically related items ONLY. All ads are subject to approval by the publisher. We reserve the right to reject or edit any ad submitted. We do not take ad copy or changes over the phone. We do not bill for classified ads. Repeat ads or ads run in multiple classifications within the same issue are allowed. Paid subscribers may run ads at the 60¢ rate only through their subscription expiration date. **NO REFUNDS.** Credit only. No credit for typographical errors will be issued unless you clearly print or type your ad copy.



# Getting Started On A Shoestring

by TJ Byers

*Just getting started in electronics, but don't have access to a lot of equipment or money? If you have \$50.00 and a desire to learn, then you have the beginnings of a new hobby.*

Hey you, over there, the newbie. You say you want to get started in electronics as a hobby, but don't have a lot of money? Yet, you want to work with programmable devices like a PIC or BASIC Stamp?

Fortunately, it doesn't take a lot of cash to get started, just a few basics that you can buy and/or build for about \$50.00. Let me take you along the yellow brick electronics road to a land of fun and fantasy.

## Test Bench Equipment Basics

First, you need a multimeter: a device that measures voltage, current, and resistance. It can be either analog or digital. Personally, I use the 9300G Digital Multimeter that I purchased from Circuit Specialists (800-528-1417; [www.web-tronics.com/9300g.html](http://www.web-tronics.com/9300g.html)) for just \$19.00 any time, any day. Besides the basics, this gem includes a transistor and a diode checker. At the moment, as a special promo offer for *Nuts & Volts* readers, if you purchase \$30.00 or more from Circuit Specialists via the Internet, they'll give you a CSI Techmeter DMM — worth \$29.00 — for free! (To get this promo, you must enter the code "DMM FREE" — if you have a Jun. 01 issue handy, check out their ad on page 92. You can read the fine print about the offer there.)

If you follow the buying suggestions outlined here, you will

easily earn that free DMM and still stay within your \$50.00 budget.


## Getting Juiced

That's because you'll need a power supply for your projects

— which you can build yourself. For most experiments, you'll need three voltage sources. First, is a five-volt source for logic ICs and microcontrollers. Next, is a variable voltage source to power op-amps, A/D converters, and audio



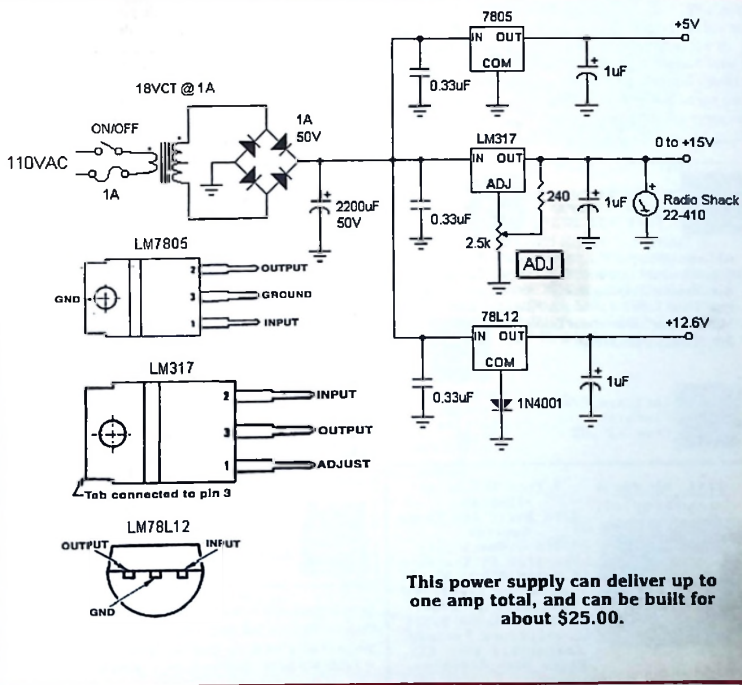For a limited time, Circuit Specialists will give you a CSI Techmeter DMM — worth \$29.00 — for free if you place an order for \$30.00 or more. To qualify for this offer, you must enter the code "DMM FREE" on their web site when placing your order.



**This power supply can deliver up to one amp total, and can be built for about \$25.00.**



# PARTS LISTS

## Power Supply

### Semiconductors

- 7805 – Five-volt regulator
- LM317 – Adjustable voltage regulator
- 78L12 – 12-volt regulator
- 1A, 50V Bridge rectifier
- 1N4001 Diode

### Resistors

- 240 ohms, 1/4W
- 2.5k Potentiometer

### Capacitors

- 1 – 2200uF, 50V electrolytic
- 3 – 0.33uF mylar
- 3 – 1uF tantalum

### Misc.

- 1 – 18VCT, 1A power transformer
- 1 – SPST toggle switch
- 1 – 1A fuse
- 1 – 0-15VDC panel meter (RadioShack 22-410)
- 1 – Cabinet
- 4 – Nylon banana jack binding posts

## Logic Probe

### Semiconductors

- 1 – 4001 NOR gate
- 1 – Green LED (Pulse)
- 1 – Bi-color LED (RadioShack 276-012)
- 1 – 1N34A germanium diode

### Resistors

- 3 – 1k
- 1 – 1Meg
- 1 – 2.2Meg
- 1 – 10 ohms, 1/2 watt (see text)

### Capacitors

- 1 – 1uF tantalum

### Misc.

- Krazy Glue tube
- Perfboard

## NOPPP Programmer

### Semiconductors

- 1 – 2N3904 transistor
- 2 – 1N34A diode
- 1 – 16F84 PIC microcontroller

### Resistors


- 3 – 4.7k
- 3 – 1k
- 1 – 2.2k
- 1 – 330 ohms

### Capacitors

- 2 – 0.1uF mylar
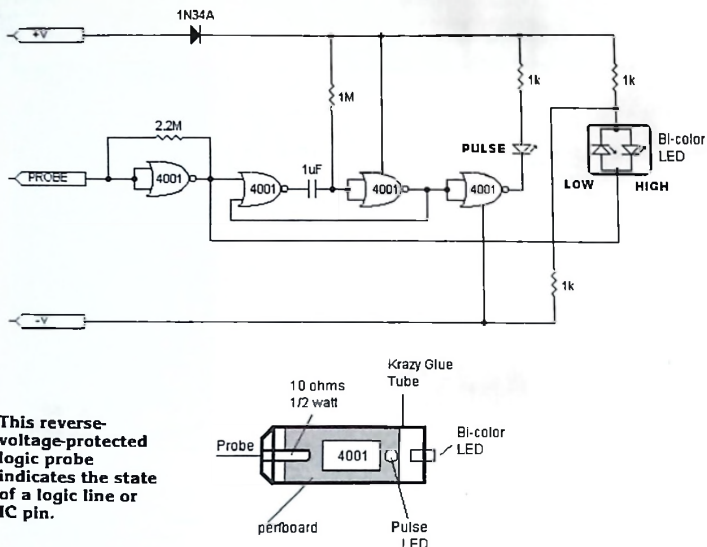
### Misc.

- 1 – 25-pin D-sub connector
- 1 – 18-pin IC socket (non-retention contacts)



This reverse-voltage-protected logic probe indicates the state of a logic line or IC pin.

chips, among other devices. Finally, there's a 12.6-volt voltage source that's needed for programming a PIC chip. The following circuit will fill the bill.

It will provide up to one amp of total current at the five-volt and 0-15-volt outputs; e.g., 500 mA from each. The 12.6-volt output can serve up 100 mA of current.

Notice that each voltage regulator has a 0.33uF capacitor on its input pin.

This cap should not be ignored; it improves the regulator's response time, and has to be placed as close as possible to its associated IC. Cost is about \$25.00 with a decent cabinet and binding posts.

## A Logical Choice

Next, a logic probe would be handy. This device tells you the state of a logic line or IC pin. It indicates whether the line is high or low – or if the signal is a pulse train. That is, the logic is alternating between high and low. The last

**B/W Board**  
Hi-Res Cameras  
From \$32.00



**Hi Power**  
Infrared  
Board  
Cameras From  
\$39.00

[www.INTELLICAMSYSTEMS.com](http://www.INTELLICAMSYSTEMS.com)



**High Res Color**  
Enclosed Pinholes  
From \$99.00

All Cameras Shipped With PlugPlay Cable With RCA Video Out and Standard DC Barrel Plug. Enclosed Camera Case With Miniature Mounting Bracket. All Products On This Page Use 12 Volt DC Standard!! Please Call 1-800-903-3479 For More Information or Email: [Sales@IntelliCamSystems.Com](mailto:Sales@IntelliCamSystems.Com)



**Color Board**  
Pinholes  
Starting At  
\$79.00



**Enclosed B/W**  
Pinholes  
From \$39.00

Your New Headquarters For 24 Ciphers Wireless Solutions. All of our wireless transmitters are FCC compliant. Output vary from 10mw (no license required) to low enforcement grade high power outputs. Some outputs do require certain FCC licenses.



**Camera and**  
Transmitter About  
The Size Of A  
Lightbulb!!



**Our 24-100**  
Wireless  
Transmitter is 4  
channel switchable  
and is the worlds  
smallest PLL  
Crystal Controlled  
TX. Available  
Starting at \$49.00



**Matching 4 Channel**  
Receiver Available  
Starting at \$70.00

From Board Level Pinhole Cameras To Specialty Underwater Color Infrared Cameras, We have what you're looking for at true wholesale prices. Call us now at 1-800-903-3479. Dealers Always Welcome.

**\$136.88 In**  
Quantity



**4 Inch TFT Color**  
Display  
With Audio And Image  
Reverse.  
RCA Connectivity  
Operates On Standard  
12 Volts DC. 49,622  
Pixels For Excellent  
Resolution. Ideal  
For Setting Up Video  
Surveillance Systems.  
Compatible With All  
Video Game Consoles.







feature is especially handy when you can't determine if the signal line is hung up in limbo or changing states faster than the eye can detect. You can buy a logic probe for under \$15.00 in kit form, or build it yourself using the schematic shown in this article.

The electronics can be mounted in a discarded Krazy Glue container (the outer housing for the glue tube), with a probe tip (RadioShack 278-705) glued into

the tapered tip of the cylinder. The LED is a bi-color red/green indicator, like the RadioShack 276-012. It can be mounted in the red end cap of the glue tube holder. If money is tight, the probe tip can be made from the lead of a 10-ohm, 1/2-watt resistor stuck through a hole drilled in the white end of the tube and glued in place with rubber cement. Not as sturdy as a rigid probe, but it will serve you until more funds become

available. The +V and -V leads are made from a pair of mini-alligator jumper cables (RadioShack 278-1156).

## PIC Programmer

For PIC projects, you'll need a programming device that, again, you can build yourself. My favorite is NOPPP, the "No-Parts" PIC programmer at [www.covingtoninnovations.com/](http://www.covingtoninnovations.com/)

noppp. Just be forewarned that it's not really part-less. It does use about \$10.00 of electronic components. The programmer plugs into the parallel port of your PC and programs 16C84, 16F83, and 16F84 PIC chips. For the programmer, you'll want a couple of sturdy IC sockets, because you'll be moving PICs around a lot as you go between programming and testing.

Circuit Specialists sells a similar PIC programmer in kit form (Kit 81; <http://store.yahoo.com/webtronics/intopicprog1.html>), which includes all the hardware and software you need to get you started with PICs, for \$24.95. Be sure to add an extra 16F84 to your order, in case you decide to put one of your inventions to practical use.

You'll also want a datasheet ([www.microchip.com](http://www.microchip.com)) that shows you how to wire and set up your PIC — and a book that teaches you how to program it. A good book for the newbie is *Easy PIC'n: A Beginner's Guide to Using Pic16/17 Microcontrollers from Square 1* by David Benson ([www.sq-1.com](http://www.sq-1.com)). Advanced PIC programming is covered in *Design with PIC Microcontrollers*, by John B. Peatman, published by Prentice-Hall. Intermediate between these is *Programming and Customizing the PIC Microcontroller* by Myke Predko.

If you're into the BASIC Stamp, don't pass up *The Nuts & Volts of BASIC Stamps* — a two-volume collection of 75 articles written by Scott Edwards, Jon Williams, and Lon Glazner ([www.nutsvolts.com/Store\\_Pages/Books/BASIC\\_Stamp.htm](http://www.nutsvolts.com/Store_Pages/Books/BASIC_Stamp.htm)) and check out the [www.geocities.com/SiliconValley/Cable/7772/](http://www.geocities.com/SiliconValley/Cable/7772/) web site.

## The Final Touches

According to my calculator, the total comes to \$36.20 give or take a dollar, DMM and books not included. Oh, don't forget the soldering iron, solder, and hand tools. You'll also need electronic parts, like resistors and capacitors which you can buy from Jameco (800-831-4242; [www.jameco.com](http://www.jameco.com)) for as little as \$4.95 per grab bag. A solderless breadboard is also a good investment; prices start at just \$5.94.

There you have it. Getting into a fun and exciting — and cutting-edge — hobby for less than \$50.00. Now, if I could put the same budget restraints on my girlfriend's shoe collection, I could afford a new car. NV

# Roger's Systems Specialist Inc.

Cables • Computer • Communications • Network • Audio • Video

Mon. - Fri.  
8:30am - 5:30pm

800-366-0579  
661-295-5577  
FAX 661-295-8777

Saturday  
9am - 2pm

24895 Avenue Rockefeller  
Valencia, California 91355

"We Have Great Connections"

www.RogersSystems.com

## CAT. 5 CABLE

Also available  
in many  
colors!!

### Grey

TE-039-L5	3ft. Straight Patch	\$17
TE-078-L5	7 ft. Straight Patch	\$22
TE-128-L5	14ft. Straight Patch	\$32
TE-258-L5	25ft. Straight Patch	\$35
TE-508-L5	50 ft. Straight Patch	\$62
TE-758-L5	75ft. Straight Patch	\$142
TE-108-L5	100 ft. Straight Patch	\$162

## USB

CC-USB-A56	6ft. USB "A"-B" M/M	\$52
CC-USB-A10	10ft. USB "A"-B" M/M	\$62
CC-USB-A15	15ft. USB "A"-B" M/M	\$62
CC-USB-X6	6ft. USB "A"-A" M/F	\$52
CC-USB-X10	10ft. USB "A"-A" M/F	\$62

## E-TV USB CONVERTER

The Easiest-to-Use  
PC to TV Video  
Converter

\$129.00 TM-UT500

### Features

- Up to 32 x 480 to NTSC and PAL
- Plug & play with no software setup, no power adapter needed
- Simultaneous display on TV desktop/VGA monitor
- No interference or any crosstalk
- No heat, Zoom, and Running of the video images
- No need directly from computer to VCR
- For both PC & Mac computers

## Video Converter Cable w/ RCA and S-Video Inputs

\$69.00

TV-USB-V01

### Features:

RCA or S-Video (SVHS) to USB converter/adapter cable. Connect TV, VCR or camcorder to a USB port and capture images or movies! Converts analog to digital video. Supports NTSC and PAL. PC Version

## S-VGA Extensions

male/female  
black

CC-VGA-6MF	6FT.....	\$62
CC-VGA-10MF	10FT.....	\$82
CC-VGA-25MF	25FT.....	\$162
CC-VGA-50MF	50FT.....	\$252
CC-VGA-100MF	100FT.....	\$442

## S-VGA Switch Box Cable

male/male  
black

CC-VGA-6MM	6FT.....	\$62
CC-VGA-10MM	10FT.....	\$82
CC-VGA-25MM	25FT.....	\$162
CC-VGA-50MM	50FT.....	\$252
CC-VGA-100MM	100FT.....	\$442

These premium VGA cables are made with 75 ohm coaxial cables. They are triple shielded to support extremely high bandwidth and unsurpassed protection against interference. Furthermore, our premium cables are Plug-N-Play ready and are compatible with the latest technology.

## VGA Monitor Cables

Have you just upgraded to a larger monitor, and noticed ghosting images and slow data transmission?

These VGA monitor cables are high-resolution multimedia cables with a HDB15 connector to your PC. Recommended for monitors 17" and larger.

CC-VGA-6MM	6ft. Male/Male	\$62
CC-VGA-10MM	10ft. Male/Male	\$82

CC-VGA-6MF	6ft. Male/Female	\$62
CC-VGA-10MF	10ft. Male/Female	\$82

## KVM Cable Sets

1 SVGA 2 PS/2

CC-PS2-VGA6	6ft. Male/Male	\$122
CC-PS2-VGA10	10ft. Male/Male	\$162
CC-PS2-VGA6	6ft. Male/Female	\$142
CC-PS2-VGA10	10ft. Male/Female	\$172

## PATCH PANEL

12 port horizontal CAT 5 Patch panel 110 style T568A/B 350MHz. Comes with panel, bracket, screws and wire covers.

\$39.00

PP-12-BKT

## IEEE-1394 FIREWIRE



\$10.00

FW-6X4-6	6ft 6pin x 4pin.....	\$10.00
FW-6X4-10	10ft 6pin x 4pin.....	\$12.00
FW-4X4-6	6ft 4pin x 4pin.....	\$10.00
FW-4X4-10	10ft 4pin x 4pin.....	\$12.00

## XIRCOM DONGLE

Xircor - Modem Dongle CBEM56  
Model# CABLE-MOD444  
Modem cable for CBEM56G-100BTX.



CA-30D-444

CPU's-Motherboards-HardDrives  
Memory-SCSI Adaptors  
SCSI Cables - CD burners  
CD's & Rewritable CD's  
And Much Much More!!!!





# DEALER DIRECTORY

The dealers listed below carry the latest issue of Nuts & Volts, for your convenience.

## ALABAMA

Little Professor Book Center  
2717 S. Tyndal Ave.  
Birmingham 35209

## ARIZONA

Blatt Electronic Supply  
1261 S. Tyndal Ave.  
Tucson 85713  
**Tower Records**  
3 E. 9th St.  
Tempe 85281

## AUSTRALIA

DonTronics  
P.O. Box 595  
29 Elmira Cres.  
Tullahoma 3843  
www.dontronics.com

## CALIFORNIA

Abletronics  
9155 Archibald Ave., Unit E  
Cucamonga 91730  
**All Electronics**  
905 S. Vermont Ave.  
Los Angeles 90005

14928 Oxnard St.  
Van Nuys 91411  
**Alltronics**  
2300-D Zanker Rd.  
San Jose 95131  
Centerfold International  
716 N. Fairfax Ave.  
Los Angeles 90046

**Del Amo Books & News**  
3758 Sepulveda Blvd.  
Torrance 90505  
**Electro Music**  
2985 E. Harcourt St.  
Rancho Dominguez 90221  
**HSC Electronic Supply**  
4837 Amherst Ln.  
Sacramento 95841

3500 Ryder St.  
Santa Clara 95051

5681 Redwood Dr.  
Rohnert Park 94928  
**JK Electronics**  
6395 Westminster Ave.  
Westminster 92683

**Lion Electronic Labs**  
4048 E. Townsend Ave.  
Fresno 93727

**Max Vac Electronics**  
2001 Harbor Blvd.  
Costa Mesa 92627

12453 Washington Blvd.  
Los Angeles 90046

4747 Hall Blvd.  
Maniclor 91763

2000 Quail Center Dr.  
Ste. 150  
Oxnard 93030

1759 Colnada Blvd.  
Petaluma 94956

2537 Del Paso Blvd.  
Sacramento 95815

5184 Holder Blvd.  
Santa Barbara 93111  
**OPAMP Technical Books**  
1033 N. Sycamore Ave.  
Los Angeles 90038  
**Roger's System Specialists**  
24895 Ave. Rockefeller  
Valencia 91355

**Sav-On Electronics**  
13225 Harbor Blvd.  
Garden Grove 92643  
**The Red Barn**  
Hwy. 209  
Bieber 96009

**Tower Books**  
211 Main St.  
Chico 95928

7840 Macy Plaza Dr.  
Citrus Heights 95610

1280 E. Willow Pass Rd.  
Concord 94520

630 San Antonio Rd.  
Mountain View 94040

1600 Broadway  
Sacramento 95818

2538 Watt Ave.  
Sacramento 95821  
**Tower Records/Video**  
220 N. Beach Blvd.  
Anaheim 92801

6694 Amador Plaza Rd.  
Dublin 94568

5703 Christie Ave.  
Emeryville 94606

4118 Fremont Hub  
Fremont 94537

5611 Blackstone  
Fresno 93710

23541 Calle De La Louisa  
Laguna Hills 92645

6310 E. Pacific Coast Hwy.  
Long Beach 90803

2331 S. Atlantic Blvd.  
Monterey Park 91754

2525 Janes St.  
San Francisco 94133

871 Blossom Hill Rd.  
San Jose 95123

**Video Electronics**  
3829 University Ave.  
San Diego 92105

## CANADA

**Cody Books Ltd.**  
810 Guylafide Dr. #222  
New Westminster, BC  
V3M 6B9

**Com-West Radio Systems Ltd.**  
8171 Main St.  
Vancouver, BC V5X 3L2  
**Emma Marian Ltd.**  
2677 E. Hastings St.  
Vancouver, BC V5K 1Z5  
**Muir Communications Ltd.**  
3214 Douglas St.  
Victoria, BC V8Z 3K6

## COLORADO

**Centennial Electronics, Inc.**  
2324 E. Bijou  
Colorado Springs 80909  
**Tower Records/Video**  
2500 E. 1st Ave.  
Denver 80206

## CONNECTICUT

**Archway News**  
64 Bank St.  
New Milford 06776

**Tower Records**  
1145 High Ridge Rd.  
Stamford 06903

## DELAWARE

**Network Newsstand**  
70 E. Main St.  
Newark 19711

## DISTRICT OF COLUMBIA

**Tower Records**  
2000 Pennsylvania Ave.  
Washington 20006

## FLORIDA

**Alla Electronic Supply**  
6444 Pembroke Rd.  
Miami 33023  
**Astro Too**  
6949 W. Nasa Blvd.  
West Melbourne 32904

**Clarks Out of Town News**  
303 S. Andrews Ave.  
Fort Lauderdale 33301

**Mike's Electronic Distributing Co.**  
1001 N.W. 52nd St.  
Fort Lauderdale 33309

**Sunny's AI Strip, Inc.**  
8260 Sunset Strip  
Sunrise 33322

## HAWAII

**SaluWorks!**  
525 Leleia Blossom Ln.  
Ocean View 96737

**Tower Records**  
4211 Waiolalo Ave.  
Honolulu 96816

611 Keoluolu  
Honolulu 96814

## IDaho

**Current Source**  
451 N. Philippi St.  
Boise 83706

## ILLINOIS

**Tower Records/Video/Books**  
383 W. Army Trail Rd.  
Bloomington 61708

2301 N. Clark St. #200  
Chicago 60614

1209 E. Golf Rd.  
Schaumburg 60173

**INDIANA**  
**Suplus Bargain Center**  
2611 W. Michigan St.  
Indianapolis 46222

## KANSAS

**Hollywood All Home**  
9063 Metcalf Ave.  
Overland Park 66212

## LOUISIANA

**Lakeside News**  
3323 Severn Ave.  
Metairie 70002

## MARYLAND

**Tower Records/Video**  
2566 Solomons Island Rd.  
Annapolis 21401

1601 Rockville Pike #210  
Rockville 20852

## MASSACHUSETTS

**Tower Records/Video**  
1011 Middlesex Turnpike  
Burlington 01803

## MICHIGAN

**Anything Goods**  
5108 Rochester Rd.  
Troy 48069

**Little Professors Book Center**  
22174 Michigan Ave.  
Dearborn 48124

**Purchase Radio Supply, Inc.**  
327 E. Hoover Ave.  
Ann Arbor 48104

**Spectrum Electronics, Inc.**  
1228 Bridge St. NW  
Grand Rapids 49504

## MINNESOTA

**Radio City, Inc.**  
2633 County Road 1  
Mounds View 55112

## MISSOURI

**Electronics Exchange**  
8644 S. Charles Rock Rd.  
St. Louis 63114

## NEVADA

**Amateur Electronic Supply**  
4640 Palatis  
Las Vegas 89103

**House of Drake**  
3129 S. Carson St.  
Carson City 89701

**Radio World**  
1656 Nevada Hwy.  
Boulder City 89005

**Sandy's Electronic Parts**  
961 Malley Ln #100  
Reno 89502

**Tower Records/Video**  
4580 W. Sahara Ave.  
Las Vegas 89102

6450 S. Virginia  
Reno 89511

**NEW JERSEY**  
**H.E.S. Electronics**  
1715 Route 88  
Brick 08724

**Tower Records/Video**  
809 Rt 17 S  
Paramus 07652

## NEW YORK

**Ham Central**  
3 Neplune Rd.  
Poughkeepsie 12601

**Hirsch Sales Corporation**  
219 California Dr.  
Williamsburg 14221

**Tower Records/Video**  
105 Old Country Rd.  
Carle Place 11514

350-370 Route 110  
Huntington 11746

1961 Broadway  
New York 10023

383 Lafayette St.  
New York 10003

## OHIO

**Footsteps**  
4925 Jackson Rd. Store #58  
Toledo 43613

**Hasell Electronics, Inc.**  
2700 Sunset Blvd.  
Steubenville 43952

**Keyways, Inc.**  
204 S. 3rd St.  
Miamisburg 45342

## OKLAHOMA

**Taylor News & Books**  
133 W. Main, Ste. 102  
Oklahoma City 73102

## OREGON

**News & Smokes**  
1060 S.E. M St.  
Grants Pass 97526

**Norvac Electronics**  
7940 S.W. Nimbus Ave. Bldg. 8  
Beaverton 97005

960 Conger  
Eugene 97402

1545 N. Commercial N.E.  
Salem 97303

**Tower Books**  
1307 N.E. 102nd Ave.  
Portland 97220

## PENNSYLVANIA

**Tower Books**  
425 South St.  
Philadelphia 19147

**Tower Records**  
340 W. Dekalb Pike  
King of Prussia 19406

**Tower Records**  
Land Title Bldg.  
100 S. Broad St.  
Philadelphia 19110

**TENNESSEE**  
**Tower Books**  
2404 W. End Ave.  
Nashville 37203

**Tower Records**  
504 Ory Mills Dr.  
Nashville 37214

## TEXAS

**BDL News, Inc.**  
809 Pierce  
Houston 77002

**Electronic Parts Outlet**  
3753-B Fondren Rd.  
Houston 77063

**Mouser Electronics**  
958 N. Main St.  
Mansfield 76063

**Tanner Electronics**  
1301 W. Beltline #105  
Constitution 75006

**Tower Records**  
2403 Guadalupe St.  
Austin 78705

**VIRGINIA**  
**Tower Records/Video**  
6200 Little River Turnpike  
Alexandria 22312

4110 W. Oak Rd. #12124  
Fairfax 22033

1601 Willow Lawn Dr.  
Richmond 23230

8389 E. Leeburg Pike  
Vienna 22182

**WASHINGTON**  
**A-B-C Communications, Inc.**  
17541 15th Ave. N.E.  
Seattle 98155

**Supertronix**  
16550 W. Valley Hwy.  
Seattle 98188

**Tower Books**  
10035 N.E. 8th St.  
Bellevue 98004

20 Mercer St.  
Seattle 98109

**WISCONSIN**  
**Amateur Electronic Supply, Inc.**  
5710 W. Good Hope Rd.  
Milwaukee 53223

**WYOMING**  
**Western Test Systems**  
2701 Westland Ct. #8  
Cheyenne 82001



GRAMP COOKBOOK

by Ray Marston

## Part 3 • Oscillators and Switching Circuits

*Ray Marston looks at practical op-amp oscillators and switching circuits in the third episode of this four-part survey of op-amp principles and applications.*


The opening episode of this 'op-amp' series described the basic operating principles of conventional voltage-differencing op-amps (typified by the 741 type), and showed some basic circuit configurations in which they can be used. The present episode looks at practical ways of using such op-amps in various oscillator and switching applications.

When reading this instalment, note that most practical circuits are shown designed around a standard


741 or 3140-type op-amp and operated from dual 9V supplies, but that these circuits will usually work (without modification) with most voltage-differencing op-amps, and from any DC supply within that op-amp's operating range.

## SINEWAVE OSCILLATORS

An op-amp can be made to act as a sinewave oscillator by connecting it as a linear amplifier in the basic configuration shown in *Figure 1*, in which the amplifier output is

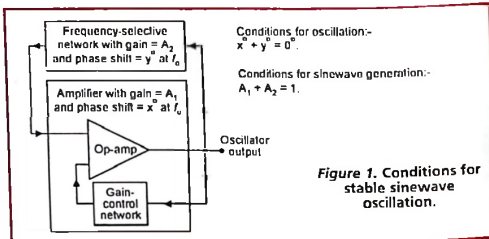

**Figure 1. Conditions for stable sinewave oscillation.**

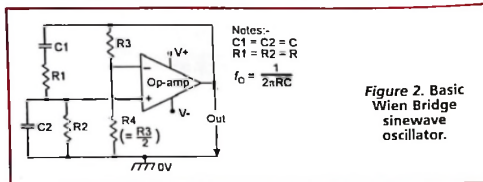

**Figure 2. Basic Wien Bridge sinewave oscillator.**

fed back to the input via a frequency-selective network, and the overall gain of the amplifier is controlled via

a level-sensing system.

For optimum sine-wave generation, the feedback network must provide an overall phase shift of zero degrees and a gain of unity at the desired frequency. If the overall gain is less than unity, the circuit will not oscillate and, if it is greater than unity, the output waveform will be distorted.

One way of implementing the above principle is to connect a Wien Bridge network and an op-amp in the basic configuration shown in Figure 2. Here, the frequency-sensitive Wien Bridge network is constructed from R1-C1 and R2-C2. Normally, the network is symmetrical, so that  $C1 = C2 = C$ , and  $R1 = R2 = R$ . The main feature of the Wien network is that the phase relationship of its output-to-input signals varies from  $-90^\circ$  to  $+90^\circ$ , and is precisely  $0^\circ$  at a center frequency ( $f_0$ ) of  $1/2\pi CR$ . At this center frequency, the symmetrical network has a voltage gain of 0.33.

Thus, in *Figure 2*, the Wien network is connected between the output and the non-inverting input of the op-amp, so that the circuit gives zero overall phase shift at  $f_0$ , and the actual amplifier is given a volt-

[illegible]



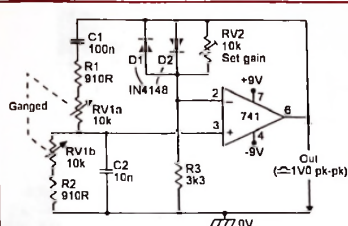


Figure 5. Diode-regulated 150Hz-1.5kHz Wien Bridge oscillator.

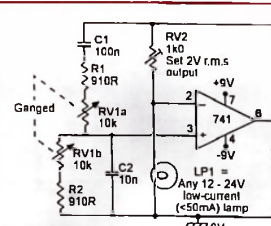


Figure 4. 150Hz-1.5kHz lamp-stabilized Wien Bridge oscillator.

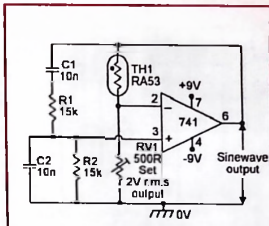


Figure 3. Thermistor-stabilized 1kHz Wien Bridge oscillator.

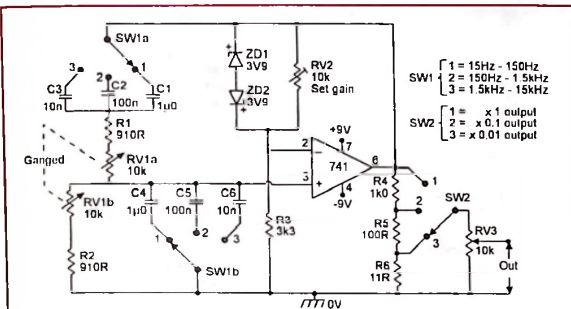


Figure 7. Three-decade (15Hz-15kHz) Wien Bridge oscillator.

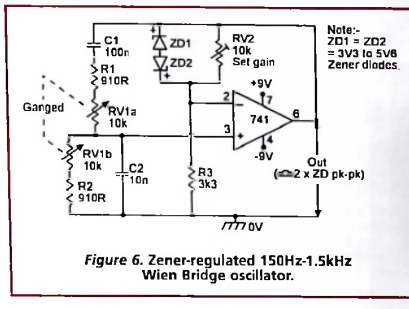


Figure 6. Zener-regulated 150Hz-1.5kHz Wien Bridge oscillator.

age gain of x3 via feedback network R3-R4, to give the total system an overall gain of unity.

The circuit thus provides the basic requirements of sine wave oscillation. In practice, however, the ratios of R3-R4 must be carefully adjusted to give overall voltage gain of precise unity that is necessary for low-distortion sine wave generation.

The basic Figure 2 circuit can easily be modified to give automatic gain adjustment and amplitude stability by replacing the passive R3-R4 gain-determining network with an active gain-control network that is sensitive to the amplitude of the output signal, so that gain decreases as the mean output amplitude increases, and vice versa. Figures 3 to 7 show some practical versions of Wien Bridge oscillators with automatic amplitude stabilization.

## THERMISTOR-STABILIZED CIRCUITS

Figure 3 shows the basic circuit of a 1kHz thermistor-stabilized Wien Bridge oscillator of the type that has been popular in the UK and other European countries for many years. The thermistor used here is a rather expensive and delicate RA53 (or similar) negative-temperature-coeffi-

cient (ntc) type. The thermistor (TH1) and RV1 form a gain-determining network.

The thermistor is heated by the mean output power of the op-amp,

the op-amp a gain of x3 and the overall circuit a gain of unity. If the oscillator output starts to rise, TH1 heats up and reduces its resistance, thereby automatically reducing the

circuit's gain and stabilizing the amplitude of the output signal. An alternative method of thermistor stabilization is shown in Figure 4; this circuit variant is very popular in the USA. In this circuit, a low-current filament lamp is used as a positive-temperature-coefficient (ptc) thermistor, and is placed in the

# AMAZING DEVICES

See in Action video on our web site at [www.amazing1.com](http://www.amazing1.com)

<h3>Ion Ray Guns</h3> <p>Star Wars Technology Directa Energy</p> <p>Star Wars Technology Demonstrates Weapons Potential: Force Fields, Telekinesis, Antigravity etc. Projects electric shocks without contact! Conduct many weird and bizarre experiments! Hand-held battery operated and easy to operate.</p> <p>IGOT9 Plans: \$10.00 IGOT9 Kits/Plans: \$99.50 IGOT9 Assembled/ Tested: \$149.95 Higher Powered Device IGOS9 Kits/Plans: \$129.95 IGOS9 Assembled/ Tested: \$199.95</p>	<h3>Shocker Trigger Ignitor</h3> <p>Variable 20,000 volt pulser used for laser flash tube, spark gap and pyro ignitor, garden pest shocker, electric fence, smoke venturi motor etc.</p> <p>12 volt battery operation.</p> <p>TRIG1K - Kits/Plans: \$29.95 TRIG1K - L20 Assembled: \$49.95</p>	<h3>Body Heat Telescope</h3> <p>Detects living bodies over 300' Haat looks etc. Built in chopper and lens control.</p> <p>BHTK Plans: \$19.00 BHTK Kit: \$29.95 BHTK Ready to use: \$49.95</p>	<h3>Mass Driver</h3> <p>Can be crushed into the shape of an hour glass demonstrating the awesome power of magnetism. Very popular device in science museums as users get to crush and keep their own can. Kids love this!</p>
<h3>Mind &amp; Brain Controllers</h3> <p>Incredible device Turns changes memory. Boost mental powers, Controls stress, Speeds up healing processes and Uncover hidden potentials. High quality unit with many features.</p> <p>DWPLUS APOLLO Ready to use: \$179.95 DWL-EINSTEIN Lower cost unit: \$129.95</p>	<h3>Mini TESLA Coil</h3> <p>Lights up to 4" fluorescent bulb without any contact! Yet only 3" tall!</p> <p>MTCK1 Kits/Plans: \$24.95 MTCK1 Assembled: \$34.95</p>	<h3>Ultra Bright Green Laser</h3> <p>30 to 50x brighter than most red pointers! Full 5mw range in excess of 6000 feet!! Operates for hours from 7 "AAA" batteries.</p> <p>LAUGHS: Review - 5 star for Price!!</p>	<h3>Can Crusher</h3> <p>Generates phenomenal explosive blast for many applications. Create a new artistic concept! Uses our unique high energy pulse shaper explosion chamber.</p>
<h3>Ultrasonic Painfield Generators</h3> <p>For property and personal protection. Four transducer matrix interfaces and concentrates effect on target area.</p> <p>PPFA Plans: \$50.00 PPFA Kit: \$119.95 PPFA Ready to use: \$299.95</p>	<h3>3 MI Voice Transmitter</h3> <p>Crytal clear. Many applications. Easy to build.</p> <p>FMH1 Kits and Plans: \$39.95</p>	<h3>Low Cost 100,000 Volt DC Supply</h3> <p>Amateur experimenters source of HVDC for many applications</p> <ul style="list-style-type: none"> <li>• 100,000 volts @ 2ma</li> <li>• Built in dry filled multigap</li> <li>• Operates on 12vdc or 115vac</li> </ul> <p>HVOLT1 - Plans: \$9.00 HVOLT1K - Kits/Plans: \$149.95 HVOLT1K - Assembled: \$249.95</p>	<h3>Wire Exploding</h3> <p>Generate phenomenal explosive blast for many applications. Create a new artistic concept! Uses our unique high energy pulse shaper explosion chamber.</p>
<h3>Combo Tesla Coil, Jacobs Ladder, Plasma Tornado</h3> <p>Amazing and bizarre effects turn a normal light bulb into a spectacular plasma display! With adjustable frequency control. Safe 12vdc input.</p> <p>TCL3 Plans: \$6.00 TCL4 Kits/Plans: \$59.95 TCL50 Assembled and Tested: \$99.95</p>	<h3>HEPS High Energy Pulsar</h3> <p>Plasma pack includes above RA531 Mass driver, GANCRU1 Can crusher and WIREXPLOD1 Wire exploder/blast set plans. We stock all parts, kits and completed units for the above items.</p>	<h3>Above photo shows burst impact of Mass Driver</h3>	<h3>Above HEPs pulsar is for use for:</h3> <p>BAP / HEPF: Germanium, Build a Flat or Cool Gun, Electrotherm Gun, High Power Pulsed Laser, Mass Wounding etc etc</p>

Information Unlimited PO Box 716 Amherst N.H. U.S.A. 03031

1 800 221 1705 Orders/Catalogs Only! Fax 1 603 672 5406 Information 1 603 673 4730 Free Catalog on Request

Pay by MC, VISA, Cash, Check, MO. Add \$5.00 S&H. Overseas Contact for Proforma



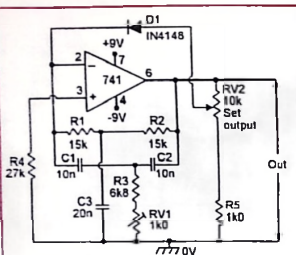


Figure 8. Diode-regulated 1kHz Twin-T oscillator.

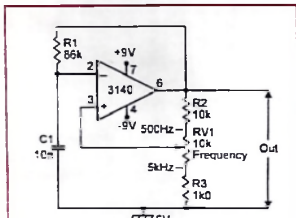


Figure 10. Simple 500Hz-5kHz squarewave generator.

lower part of the gain-determining feedback network.

Thus, if the output amplitude increases, the lamp heats up and increases its resistance, thereby reducing the circuit gain and providing automatic amplitude stabilization.

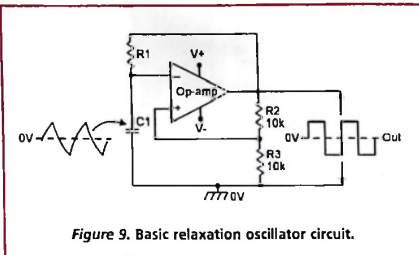


Figure 9. Basic relaxation oscillator circuit.

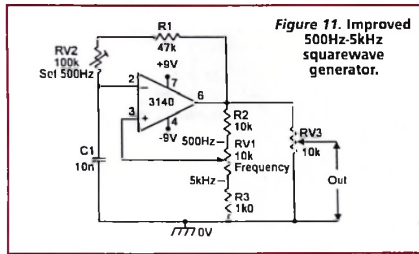


Figure 11. Improved 500Hz-5kHz squarewave generator.

This circuit also shows how the Wien network can be modified by using a twin-gang pot to make the oscillator frequency variable over the range 150Hz to 1.5kHz, and how the sinewave output amplitude can be made variable via RV3.

Note in the Figure 3 and 4 circuits that the pre-set pot should be adjusted to set the maximum mean output signal level to about 2V

RMS, and that under this condition, the sinewave has a typical total harmonic distortion (THD) level of about 0.1%.

If the circuit's thermistor is a low-resistance type, it may be necessary to interpose a bidirectional current-booster stage between the op-amp output and the input of the amplitude control network, to give it adequate drive.

Finally, a slightly annoying feature of thermistor-stabilized circuits

is that, in variable-frequency applications, the sinewave's output amplitude tends to 'judder' or 'bounce' as the frequency control pot is swept up and down its range.

## DIODE STABILIZATION CIRCUITS

The amplitude 'bounce' problem of variable-frequency circuits can be minimized by using the basic circuits in Figures 5 or 6, which rely on the onset of diode or zener conduction for automatic gain control. In essence, RV2 is set so that the circuit gain is slightly greater than unity when the output is close to zero, causing the circuit to oscillate, but as each half-cycle nears the desired peak value, one or other of the diodes starts to conduct and thus reduces the circuit gain, automatically stabilizing the peak amplitude of the output signal.

This 'limiting' technique typically results in the generation of 1% to 2% THD on the sinewave output when RV2 is set so that oscillation is maintained over the whole frequency band. The maximum peak-to-peak output of each circuit is roughly double the breakdown voltage of its diode regulator element. In the Figure 5 circuit, the diodes start to conduct at 500mV, so the circuit gives a peak-to-peak output of about 1V; in the Figure 6 circuit, the zener diodes are connected back-to-back and may have values as high as 5V6, giving a pk-to-pk output of about 12V.

The frequency ranges of the above circuits can be altered by changing the C1 and C2 values; increasing the values by a decade reduces the frequency by a decade. Figure 7 shows the circuit of a variable-frequency Wien oscillator that covers the range 15Hz to 15kHz in three switched decade ranges. The circuit uses zener diode amplitude stabilization; its output amplitude is variable via both switched and fully-variable attenuators. Note that the maximum useful operating frequency of this type of circuit is restricted by the slow-rate limitations of the op-amp. The limit is about 25kHz with a 741 op-amp, or about 70kHz with a CA3140.

## A TWIN-T OSCILLATOR

Another way of making a sinewave oscillator is to wire a Twin-T network between the output and input of an inverting op-amp, as shown in the diode-regulated 1kHz oscillator circuit in Figure 8. The Twin-T network comprises R1-R2-R3, RV1 and C1-C2-C3, and in a 'balanced' circuit, these components

## Miniature Transmitters and Receivers

### 2 Button / 3 Channel Transmitter



RF300T

1...\$22.95

5...\$19.95 ea

10...\$16.95 ea

RF300XT

1...\$25.95

5...\$22.95 ea

10...\$19.95 ea

- 300 (XT) 150 (T) Range
- Frequency 318 MHz
- 55,049 Settable Security Codes
- 12 Volt Battery and Keychain Included
- Current Draw 4.6 ma
- Fully Assembled in Case
- Dimensions: 1.25" x 2.0" x .5"
- Push both buttons for the 3rd Channel
- Side Button Cover Included

### 4 Button / 15 Channel Transmitter



RF304XT

1...\$27.95

5...\$24.95 ea

10...\$21.95 ea

- 250 Range
- Frequency 318 MHz
- 6,561 Settable Security Codes
- 12 Volt Battery and Keychain Included
- Current Draw 4.6 ma
- Fully Assembled in Case
- Dimensions: 1.35" x 2.25" x .5"
- Push combination of buttons to achieve up to 15 channels

### 2-4 Data / 1-3-5 Channel Receivers



RF300RL

RF300RM

1...\$27.95

5...\$24.95 ea

10...\$22.95 ea

RF304RL

RF304RM

1...\$29.95

5...\$26.95 ea

10...\$23.95 ea

- Compatible with 300/4 Transmitters
- 11-24 volts DC Operating Voltage
- 13 ma Current Draw
- Latching (L) or Momentary (M) Output
- Kits Available (subtract \$5.00 ea)
- Dimensions: 1.25" x 3.75" x .5"
- 2 (300) / 4 (304) Output Data Lines
- Binary to Dec / Hex Converter can achieve up to 15 channels

- Alarm Systems
- Garage / Gate Openers
- Lighting Control

- Magic Props
- Medical Alert
- Monitoring Systems

- Industrial Controls
- Surveillance Control
- Motor Control

- Schematics Available
- Receiver Board Layout Available
- Custom Design Consulting Available

Visitect Inc.

(510) 651-1425 Fax: (510) 651-8454  
P.O. Box 14156, Fremont, CA 94539

Email: Support@Visitect.Com  
Visa / Mastercard, COD



are in the ratios  $R1 = R2 = 2 (R3 + RV1)$ , and  $C1 = C2 = C3/2$ .

When the network is perfectly balanced, it acts as a frequency-dependent attenuator that gives zero output at a center frequency ( $f_0$ ) of  $1/2 \pi R1 C1$ , and a finite output at all other frequencies. When the network is imperfectly balanced, it gives a minimal but finite output at  $f_0$ , and the phase of this output depends on the direction of the imbalance: if the imbalance is caused by ( $R3 + RV1$ ) being too low in value, the output phase is inverted relative to the input.

In Figure 8, the 1kHz Twin-T network is wired between the output and the inverting input of the op-amp, and RV1 is critically adjusted so that the Twin-T gives a small inverted output at  $f_0$ ; under this condition zero overall phase inversion occurs around the feedback loop, and the circuit oscillates at the 1kHz center frequency.

In practice, RV1 is adjusted so that oscillation is barely sustained and, under this condition, the sinewave output distortion is less than 1% THD. Automatic amplitude control is provided via D1, which provides a feedback signal via RV2; this diode progressively conducts and reduces the circuit gain when the diode forward voltage exceeds 500mV.

To set up the Figure 8 circuit, first set RV2 slider to the op-amp output and adjust RV1 so that oscillation is just sustained; under this condition, the output signal has an amplitude of about 500mV pk-to-pk. RV2 then enables the output signal to be varied between 170mV and 3V RMS. Note that Twin-T circuits make good fixed-frequency sinewave oscillators, but are not suitable for variable-frequency use, due to the difficulties of varying three or four network components simultaneously.

## SQUAREWAVE GENERATORS

Figure 9 shows a basic op-amp relaxation oscillator or squarewave generator using dual (split) power supplies. Its circuit action is such that C1 alternately charges and discharges (via R1) towards an 'aiming' or reference voltage set by R2-R3, and each time C1 reaches this aiming voltage, a regenerative comparator action occurs and makes the op-amp output switch state (to positive or negative saturation), this action produces a symmetrical squarewave

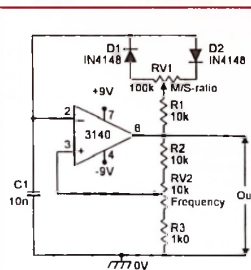


Figure 13. Squarewave generator with variable M/S-ratio and frequency.

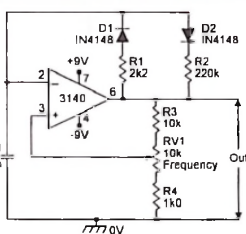


Figure 14. Variable-frequency narrow-pulse generator.

at the op-amp's output and a non-linear trianglewave across C1.

The operating frequency can be varied by altering either the R1 or

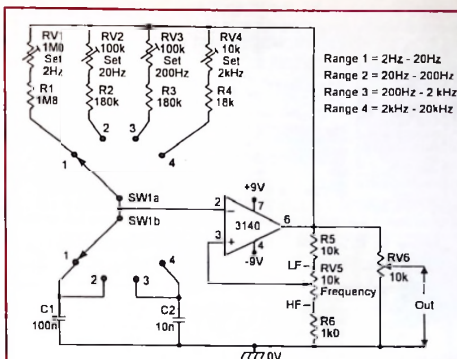


Figure 12. Four-decade, 2Hz-20kHz, squarewave generator.

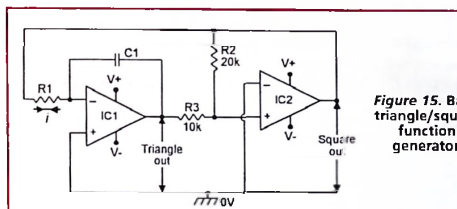


Figure 15. Basic triangle/square function generator.

C1 values or the R2-R3 ratios; this circuit is thus quite versatile. A fast op-amp such as the CA3140 should be used if good output rise and fall times are needed from the squarewave.

Figure 10 shows the basic circuit

adapted to make a practical 500Hz to 5kHz squarewave generator, with frequency variation obtained by altering the R2-RV1-R3 attenuator ratio. Figure 11 shows the circuit improved by using RV2 to pre-set the range of the RV1 frequency con-

## The Pocket Programmer



The portable programmer that uses the printer port instead of an internal card. Now with easy to use Windows software that programs E(E)prom, Flash & Dallas Ram. 25/27/28 & 29 series from 16K to 8 Megabit with a 32 pin socket. Adapters available for MCU's 874X, 875X, Pic, Atmel, 40-Pin X16, Serial Eprom's, PLCC, Bi-Prom's, Eprom Emulator to 32K X Only \$149.95

Same Name, Address & Phone # for 19 Years.... Isn't it Amazing?

**Intronics, Inc.**  
Box 12723 / 612 Newton St.  
Tel. (913) 422-2094  
Fax (913) 441-1623

Add \$7.00 COD  
Add \$6.00 Shipping

WWW.IN-KS.COM

Visa/MC/Amex/Disc

## PIC'n Books

LEARN ABOUT PIC MICROCONTROLLERS



See Table Of Contents: <http://www.sq-1.com>  
Secure Online Ordering is Available


PIC is a trademark of Microchip Technology Inc.

**SQUARE 1 ELECTRONICS**

Voice (707) 279-8881 Fax (707) 279-8883

<http://www.sq-1.com>



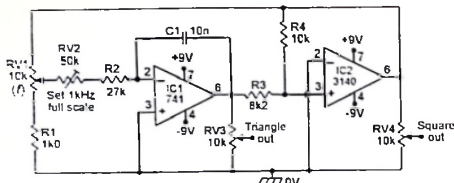

**Figure 16. 100Hz-1kHz triangle/square function generator.**


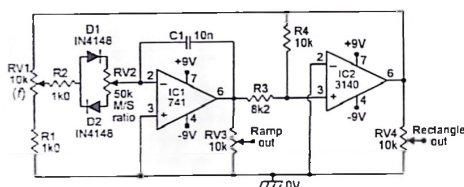



Figure 17. 100Hz-1kHz ramp/rectangle generator with variable slope-M/S ratio.

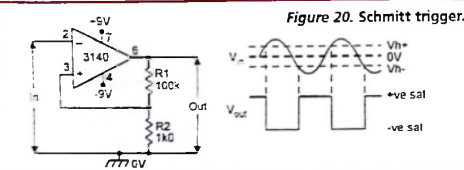


**Figure 20. Schmitt trigger.**

trol, and by using RV3 as an output amplitude control.

Figure 12 shows how the above circuit can be modified to make a

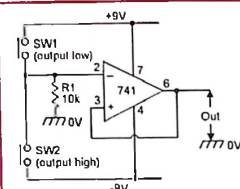

**Figure 18. Simple manually-triggered bistable.**

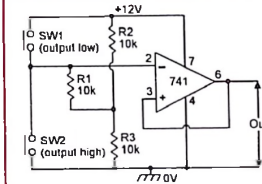

**Figure 19. Single-supply manually-triggered bistable.**

general-purpose squarewave generator that covers the 2Hz to 20kHz range in four switched decade ranges. Pre-set pots RV1 to RV4 are used to precisely set the minimum frequency of the 2Hz to 20Hz, 20Hz to 200Hz, 20Hz to 2kHz, and 2kHz to 20kHz ranges, respectively.

## VARIABLE SYMMETRY

In the basic *Figure 9* circuit, C1 alternately charges and discharges

via R1, and the circuit generates a symmetrical squarewave output. The circuit can easily be modified to give a variable-symmetry output by providing C1 with alternate charge and discharge paths, as shown in *Figures 13 and 14*.

In the *Figure 13* circuit, the mark/space (M/S) ratio of the output waveform is fully variable from 1:1 to 1:11 via RV1, and the frequency is variable from 650Hz to 6.5kHz via RV2. The circuit action is such that C1 alternately charges up via R1-D1 and the left-hand side of RV1, and discharges via R1-D2 and the right-hand side of RV1, to provide a variable-symmetry output. In practice, variation of RV1 has negligible effect on the operating frequency of the circuit.

In the *Figure 14* circuit, the mark period is determined by C1:D1-R1, and the space period by C1:D2-R2; these periods differ by a factor of 100, so the circuit generates a narrow pulse waveform. The

## TRIANGLE-SQUARE GENERATION

Figure 15 shows the basic circuit of a function generator that simultaneously generates a linear triangle and a square waveform, using two op-amps. IC1 is wired as an integrator, driven from the output of IC2, and IC2 is wired as a differential voltage comparator, driven from the output of IC1 via potential divider R2-R3, which is connected between the outputs of IC1 and IC2. The squarewave output of IC2 switches alternately between positive and negative saturation. The circuit functions as follows.

Suppose initially that the output of IC1 is positive and the output of IC2 has just switched to positive saturation. The inverting input of IC1 is a virtual earth point, so a current  $(i)$  of  $+V_{sat}/R1$  flows into R1, causing the output of IC1 to start to swing down linearly at a rate of  $i/C1$  volts per second. This output is fed – via the R2-R3 divider – to the non-inverting input of IC2, which has its inverting terminal referenced directly to ground.

Consequently, the output of IC1 swings linearly to a negative value until the R2-R3 junction voltage falls to zero, at which point IC2 enters a regenerative switching phase, in which its output abruptly switches to negative saturation. This reverses the inputs of IC1 and IC2, so IC1 output starts to rise linearly, until it

[illegible]

**REFILL INKS FOR  
INKJET PRINTERS**



*Refill your old cartridge and save. All refill kits come with instructions and needed materials for refilling inkjet cartridges. Available for Canon, Epson, Hewlett Packard, Apple, Compaq, and Lexmark printers.*

## HAND-TO-GET PRINTER RIBBONS



Gorilla Banana, Commodore, Texas Instruments, Centronics, Riteman, Apple, Printronix, Star

Over 200 different ribbons in stock.  
All ribbons new, not re-linked.

*Check our web page or write for complete price list.*

---

**H.T. ORR Computer Supplies**  
249 Juanita Way, Placentia, CA 92670-2215  
**714-528-9822 • FAX 714-993-8216**

Toll Free 1-800-377-2023  
e-mail: Htorr@aol.com

<http://members.home.net/hotorr/index.htm>









reaches a positive value at which the R2-R3 junction voltage reaches the zero volts reference value, initiating another switching action. The whole process then repeats ad infinitum.

Important points to note about the Figure 15 circuit are that the peak amplitude of the linear triangle waveform is controlled by the R2-R3 ratio, and that the circuit's operating frequency can be altered by changing either the ratios of R2-R3, the values of R1 or C1, or by feeding R1 from a potential divider connected to the output of IC2 (rather than directly from IC2 output). Figure 16 shows the practical circuit of a variable-frequency triangle/square generator that uses the latter technique.

In Figure 16, the input current of C1 (obtained from RV2-R2) can be varied over a 10:1 range via RV1, enabling the frequency to be varied from 100Hz to 1kHz; RV2 enables the full-scale frequency to be set to precisely 1kHz. The amplitude of the linear triangle output waveform is fully variable via RV3, and of the squarewave via RV4.

The Figure 16 circuit generates symmetrical output waveforms, since C1 alternately charges and discharges at equal current values (determined by RV2-R2, etc.). Figure 17 shows how the circuit can be modified to make a variable-symmetry ramp/rectangle generator, in which the slope is variable via RV2. C1 alternately charges via R2-D1 and the upper half of RV2, and discharges via R2-D2 and the lower half of RV2.

## SWITCHING CIRCUITS

To conclude this month's edition of the 'OP-AMP COOKBOOK,' Figures 18 to 20 show three ways of using op-amps as simple regenerative switches. Figure 18 shows the connections for making a simple manually-triggered bistable circuit. Note here that the inverting terminal of the op-amp is tied to ground via R1, and the non-inverting terminal is tied directly to the output. The circuit operates as follows.

Normally, SW1 and SW2 are open. If SW1 is briefly closed, the op-amp inverting terminal is momentarily pulled high and the output is driven to negative saturation; consequently, when SW1 is released again, the inverting terminal returns to zero volts, but the output and the non-inverting terminals remain in negative saturation.

The output remains in this state until SW2 is briefly closed, at which point, the op-amp output switches to positive saturation, and locks into

this state until SW1 is again operated. The circuit thus gives a bistable form of operation. Figure 19 shows how the circuit can be modified for operation from a single-ended power supply. In this case, the op-amp's inverting terminal is biased to half-supply volts via R1 and the R2-R3 potential divider.

Finally, Figure 20 shows how to connect an op-amp as a Schmitt trigger, which can (for example), be used to convert a sinewave input into a squarewave output. The circuit operates as follows.

Suppose initially that the op-amp output is at a positive saturation value of 8V0. Under this condition, the R1-R2 divider feeds a positive reference voltage of 8V x (R1+R2)/R2 (= about 80mV in this case) to the op-amp's non-inverting pin. Consequently, the output remains in this state until the input rises to a value equal to this voltage, at which point the op-amp output switches regeneratively to a negative saturation level of -8V0, feeding a reference voltage of -80mV to the non-inverting input.

The output remains in this state until the input signal falls to -80mV, at which point, the op-amp output switches regeneratively back to the positive saturation level. The process then repeats ad infinitum. The actual switching levels can be altered by changing the R1 value. NV

*Next month, Ray looks at practical op-amp instrumentation and test gear circuits in the final installment of this four-part series.*

**C and H SALES COMPANY**  
2176 E. Colorado Blvd. • Pasadena, CA 91107  
VISIT US ON THE WEB AT:  
<http://www.candhsales.com>  
email: [candhsales@earthlink.net](mailto:candhsales@earthlink.net)  
**TOLL FREE:**  
**1-800-325-9465**

**C & H SALES COMPANY HAS BEEN IN BUSINESS FOR OVER FIFTY YEARS. WE'RE THE BEST SOURCE FOR GREAT BUYS ON ITEMS LIKE THESE - AND MORE!**

### ELECTRONIC COUNTER

HEWLETT PACKARD, Model 5328A. Universal counter. Suitable to 100 MHz, 100 ns single shot resolution. Has frequency, period, period average, ratio, total, scale functions. Two input channels provide individual slope, polarity and level settings. Has 9 digit LED readout. Input power 100-240 VAC, 48-66 Hz, 100 VA max. Dimensions: 17" wide x 17-1/4" deep x 3-1/2" high.

Stock #TE9808 \$250.00



### SOLA CONSTANT VOLTAGE TRANSFORMER

SOLA ELECTRIC, #931-3-150. Harmonically neutralized constant voltage transformer. Rated at 500 watts. Input voltage 95 to 130 VAC 60 Hz. Output voltage 120 VAC. This unit is designed for rack or bench mounting. The meters on the front panel indicate output current and input/output voltage. A toggle switch is provided for selection of input or output voltage. The input voltage is connected at the rear of the unit via a covered electrical panel. Two standard 3-wire grounded electrical outlets are supplied on the front and rear panels. Dimensions: 18" wide x 14-1/4" high x 10-1/4" deep. Weight 59 lbs.

Stock #STR900 \$225.00

### MILLIOMETER

HEWLETT PACKARD, Model 4328A. Designed to measure very low resistances. Measurement range 1m ohm to 100 ohms. Resolution 20 ohms. Analog meter readout. Ideal for measuring contact resistance of switches or relays. This unit is also useful for measuring the resistivity of semiconductor devices. (Requires special A terminal probes which are not supplied, but probably are available from Hewlett-Packard.) Power input: 115-230 VAC 48-66 Hz, 5 VA max. Dimensions: 5-1/8" wide x 11-1/2" deep x 6-1/2" high.

Stock #TE9812 \$200.00

### PRECISION LINEAR WAY BEARING

This assembly consists of a linear ball bearing track rail and two ball bearing slider elements. 280mm long with 14 countersunk holes for rail mounting. Stainless steel.

Stock #RR2002 \$57.50

### DIAPHRAGM

PUMP THOMAS INDUSTRIES Single diaphragm oil-less pump. Motor rated 115 VAC 60 Hz. Pump output is 0.69 cfm free air. Max. continuous operating pressure 20 psi.

Stock #PC9504 \$49.50

☒ Master Charge ☒ Visa ☒ American Express ☒ Discover

Call us first if you have surplus inventories of electronic, optical, or mechanical items for disposal

**WE BUY & SELL!**

Circle #123 on the Reader Service Card.

# Test Equipment Connection Corporation

Test Equipment Connection is looking to purchase your excess or underutilized electronic test and measurement equipment. We buy the largest variety of electronic test equipment in the industry.

**WE BUY TEST EQUIPMENT**



RENT

REPAIR



TRADE

SELL



CALL: 800.615.8378

FAX: 800.819.8378

[WWW.TestEquipmentConnection.COM](http://WWW.TestEquipmentConnection.COM)

Specialist in Hewlett-Packard, Tektronix, and many more manufacturers.

Circle #118 on the Reader Service Card.







megohm resistor, 10 microamperes at the approximately 50 volts on the line. (Ten megohms, five microamperes, is better.) The PhoneTester allows easy measurement of this current. (For preventive maintenance, the phone company measures the current when the line is not in use, to check for leakage.)

## Circuit Description

The PhoneTester allows measurement of the phone line voltage, the leakage current in microamps, and the in-use current in milliamperes. The schematic is shown in Figure 1. The input is through a standard RJ-11 modular telephone plug and cable, PL1. The plug which was removed to allow connection of PL1 is connected to output jack J1, to allow measurement of line current. Measurements are made with a digital multimeter (DMM) connected to J2 and J3, or with an optional digital panel meter built into the PhoneTester case.

J2 is connected to the negative side of the input line. When S1 is in the voltage position, J3 is connected to the positive side of the input. When S1 is in the current position, J2 and J3 are connected across one-ohm resistor R1. One milliamperes through R1 produces a reading of one millivolt, giving a direct reading of the current in the phone line.

If an auto-ranging DMM is used, changing the DMM range is not necessary when switching between voltage and current measurement. To measure leakage current, normally-closed push-button switch S2 is pressed, placing 1,000-ohm resistor R2 in the circuit. Now, a reading of one millivolt indicates a current of one microampere. If ring voltage is sent over the line while S2 is open, D2 and D3 limit the

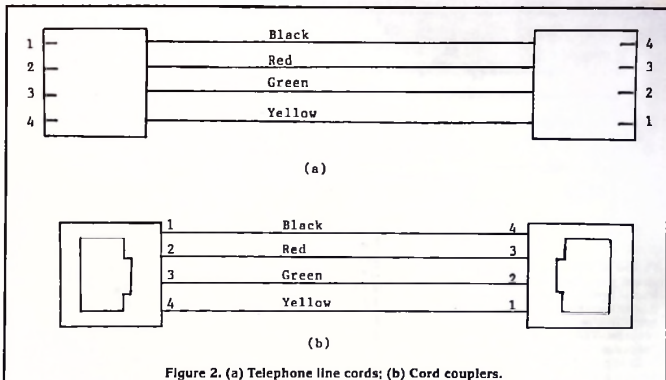


Figure 2. (a) Telephone line cords; (b) Cord couplers.

voltage across R2 and the DMM, and allow the ring voltage to reach J1.

LED1 and DPDT switch S3 provide a check for line polarity, while NE1 indicates the presence of ring voltage on the line. LED1 should be a low-current LED (2 mA), since the 15 to 20 mA current of a standard LED will send an "off-hook" signal to the phone company. Diode D1 prevents the negative cycles of the ring voltage from reaching LED1, while R4 and zener diode D4 limit the maximum voltage of the positive cycles. C1 bypasses any possible high-frequency noise. R4 and R5 provide the voltage-dropping resistance for LED1. The resistance was split into two resistors to allow

use of a higher-voltage zener diode. (Very low-voltage zeners seem to have poorer regulation than those over about five volts.)

## Construction


The prototype PhoneTester was built in a plastic project case that measures about 4 by 2.5 by 2.5 inches. The switches, jacks, LED1, and NE1 were mounted on the case. Remaining parts were mounted on a small prototype PC board, cut from a larger board with a fine-tooth hacksaw. The board and the parts mounted on the case were connected with stranded hook-up wire. J1 is a surface-mount

# \$59 PCBs

And our layout software is **FREE**

Select our MiniBoard service and get 3 top quality 2.5" x 3.8" PCBs for only \$59

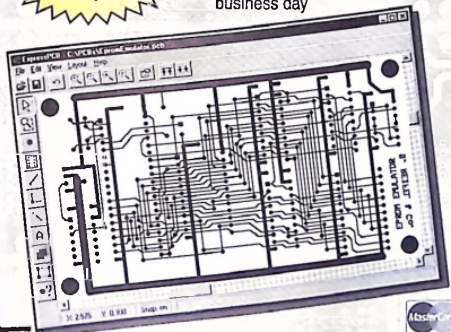- 1 Download our board layout software
- 2 Design your 2-sided plated-through PCB
- 3 Select the type of boards you want
- 4 Send us your layout over the Internet
- 5 Small orders are shipped the next business day



[www.expresspcb.com](http://www.expresspcb.com)



## Turn Your Multimedia PC into a Powerful Real-Time Audio Spectrum Analyzer

### Features


- 20 kHz real-time bandwidth
- Fast 32 bit executable
- Dual channel analysis
- High Resolution FFT
- Octave Analysis
- THD, THD+N, SNR measurements
- Signal Generation
- Triggering, Decimation
- Transfer Functions, Coherence
- Time Series, Spectrum Phase, and 3-D Surface plots
- Real-Time Recording and Post-Processing modes

### Applications

- Distortion Analysis
- Frequency Response Testing
- Vibration Measurements
- Acoustic Research
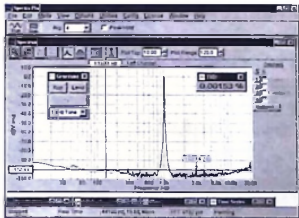
### System Requirements

- 486 CPU or greater
- 8 MB RAM minimum
- Win. 95, NT, or Win. 3.1 + Win. 32s
- Mouse and Math coprocessor
- 16 bit sound card



**Priced from \$299**

(U.S. sales only - not for export/resale)

**DOWNLOAD FREE 30 DAY TRIAL!**

[www.spectraplus.com](http://www.spectraplus.com)

**PHS** Pioneer HiFi Software  
24460 Mason Rd.  
Poulsbo, WA 98370  
a subsidiary of Sound Technology, Inc.

Sales: (360) 697-3472

Fax: (360) 697-7717

e-mail: [pioneer@telebyte.com](mailto:pioneer@telebyte.com)

**Spectra Plus**  
FFT Spectral Analysis System







## PhoneTester Parts List

D1 - 1N4003 or 1N4004 Silicon diode  
 D2, D3 - 1N4001 Silicon diode  
 D4 - 1N4738 Zener diode, 8.2 volts  
 LED1 - Low-current (2 mA) LED (see text)  
 R1 - 1.0 ohm, 1% resistor (see text)  
 R2 - 1,000 ohm, 1% resistor (see text)  
 R3 - 82K 1/4 watt 5% resistor  
 R4 - 22K 1/4 watt 5% resistor  
 R5 - 3.3K 1/4 watt 5% resistor  
 C1 - 0.1 uF 50-volt ceramic capacitor  
 S1 - SPDT toggle switch  
 S2 - SPST push-button switch, normally closed  
 S3 - DPDT toggle switch  
 J1 - RJ-11 telephone jack  
 J2, J3 - tip jack  
 NE1 - NE1 (A1A) neon lamp (see text)  
 PL1 - telephone cord with RJ-11 plug (see text)  
 Misc: Enclosure, wire, etc.

## Parts List — Optional Circuits

LED2 - standard (20 mA) LED, green  
 LED3 - standard (20 mA) LED, red  
 LED4, LED5 - Low-current (2 mA) LED  
 R6 - 270 ohm 1/4 watt 5% resistor  
 R7 - 330 ohm 1/4 watt 5% resistor  
 R8 - 39K 1/4 watt 5% resistor  
 R9 - 2K 1% resistor (see text)  
 R10 - 2 Meg 1% resistor (see text)  
 C2, C3 - 1.0 uF 250 WVDC capacitor  
 (RadioShack 272-1055 or similar)  
 T1 - 600 ohm - 600-ohm transformer  
 (RadioShack 273-1374 or similar)  
 J4 - Mono phone jack (or other connector as desired)  
 S4, S5, S6 - SPST toggle switch  
 DPM1 - Digital Panel Meter module (see text)  
 B1 - Nine-volt battery


The current is listed as three mA and the package is marked "minimum voltage 95 VAC." (Both indicate a high-intensity lamp.) The catalog no. 272-1102 is listed both in the catalogs and on the package as C2A (NE-2H), so it cannot be used. I have not checked the RSU 11338928, but the catalog says it is an A94 (NE-2E), with a current rating of 0.7 mA, which could be used for NE1. Type NE-2 is available from several other suppliers, including RadioShack.com, Jameco Electronics, and Mouser Electronics.

## Telephone Cord Polarity

A problem in building telephone accessories is line cord polarity. The wiring of a telephone line is shown in Figure 2a. This has sometimes been called "straight-through" wiring (*Telephone Repair Illustrated*, Stephen J. Bigelow, TAB Books (1993), pages 93 and 95), but if the plug terminals are numbered, as in Figure 2a, it is actually cross-wired; terminal 1 of one plug is connected to terminal 4 of the other plug, terminal 2 to 3, 3 to 2, and 4 to 1.

Because of the cross-wiring of cords, a coupler used to connect two cords to make a longer cord, must also be cross-wired (Figure 2b). In most cases, the black and yellow wires are not used. They may be used for the second line in a two-line installation, and the black wire has sometimes been used for ground. When you buy a single-line telephone, the line cord with it often has only the red and green wires. Most replacement cords have all four wires, but there is sometimes a low price on two-wire cords.

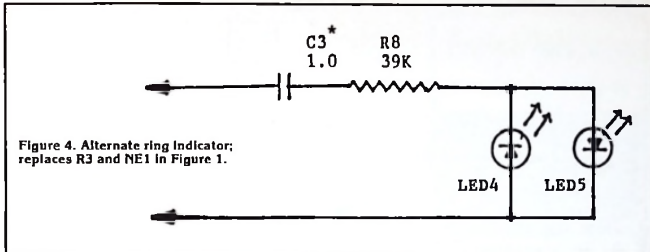As a further complication, there are cords and couplers available, intended for data use



(networking/computer sharing), which look like telephone cords, but are straight-wired (1 to 1, 2 to 2, etc.). Both types of cords are listed in the catalogs of Jameco Electronics, Marlin P. Jones & Associates, Hosfelt Electronics, and All Electronics.

I have not found straight-wired data cords listed by any other supplier, and they have been dropped from All Electronics' recent catalog (no. 500), but there are reports of cords being purchased for telephone use which were found to be straight-wired (*Nuts & Volts*, Fred Blechman, Mar. 2000, page 86, bottom of column 1.)

Some circuits for telephone accessories have been published which use jacks for both input and output. Since such a device is actually a coupler with extra circuitry between the input and output jacks, it must also be cross-wired. It is also necessary to check the input cord used with it to make sure it is cross-wired. I prefer a permanently attached input cord and plug for the PhoneTester. It needs to be checked only once, when it is built.

How do you make sure of the polarity of your PL1 input cord? Check it! Telephone cords can be purchased which have a plug on one end and wires on the other. If you have a phone cord crimping tool, RJ-11 plugs, and flat telephone wire, you can make a cord. I usually buy a cord with plugs on both ends and cut it in half. In this case, on one end, the red wire will be negative, and on the other half, it will be positive. In any case, the PhoneTester input cord should be checked to make sure which wire is negative. (For this reason, I did not indicate wire colors on PL1 of the PhoneTester schematic.)

One method for checking polarity of the cord is to use an RJ-11 telephone jack which has color-coded wires or terminals. Connect a DC voltage source to the jack, negative to red and positive to green. Plug the cord being checked into the jack and use a voltmeter to determine which wire of the cord is negative. Another way is to plug the cord into an in-use telephone jack and use a voltmeter to determine the polarity of the output wires of the cord. In this case, it is necessary to make sure the in-use jack has the correct polarity, since you may find reversed polarity in existing phone wiring. This can be done by using a phone line polarity tester such as the RadioShack 43-104, or by removing the cover of the in-use jack and using a voltmeter to make sure the red wire is negative.

After determining which wire from PL1 is negative, it is connected to the junction of R1 and J2. The positive wire is connected to the junction of the green wire from J1 with S1 and S3. You may want to connect the yellow and black wires between PL1 and J1. If the red wire from PL1 is negative, connect yellow to yellow and black to black. If the red wire from PL1 is

positive, connect yellow to black and black to yellow. (Most telephones and commercially-sold accessories will work even if the input polarity is reversed. This is done by feeding polarity-sensitive parts of the circuit through a full-wave bridge rectifier, which will have the correct output polarity regardless of the input polarity.)

## Testing

First, connect a DMM to measure the resistance between J2 and J3. With S1 in the voltage position, there should be no reading on the highest range. With S1 in the current position, the reading should be one ohm, and with S2 pressed, 1,000 ohms. Next, change the DMM to DC voltage, and plug PL1 into a working telephone jack. (Testing the jack for correct polarity has been described above.) With S1 in the voltage position, the meter should read about 48 to 50 volts. LED1 should light in the normal position of S3, and not light in the reverse position.

With S1 in the current position and S3 in the normal position (LED1 lit), the meter should read about 2 millivolts, indicating a current of about 2 mA through LED1. With S3 in the reverse position, the meter should read zero. Pressing S2 to test for leakage in the PhoneTester should also give a reading of zero. A telephone connected to J1 should work normally.

The easiest way to test ringing indicator NE1 is to have a friend call your number. On some older phone company equipment, if you dial your own number and hang up, your phone will ring. On newer equipment this feature — called ringback — requires a code number which the phone company does not usually want to give out.

## Using the PhoneTester

As mentioned, the PhoneTester can be used to check your wiring and equipment by connecting it at the telephone interface box. PL1 of the PhoneTester is connected to the jack in the interface box. The plug in the box is connected to J1 of the PhoneTester. The voltage should be near 50 volts. The leakage current — when the line is not in use — should be a few microamps. (Note that when measuring either current or voltage, S3 should be in the position where LED1 is not lit. The 2 mA current of LED1 will cause a drop of about three volts in the line voltage.) It is a good idea to measure and record these values when the telephones are working properly. My home phone wiring, most of it about 40 years old, has a total not-in-use current of about 10 microamps, with four telephones connected to the wiring. Line-in-use indicators, which light an LED when the line is in use, have a few



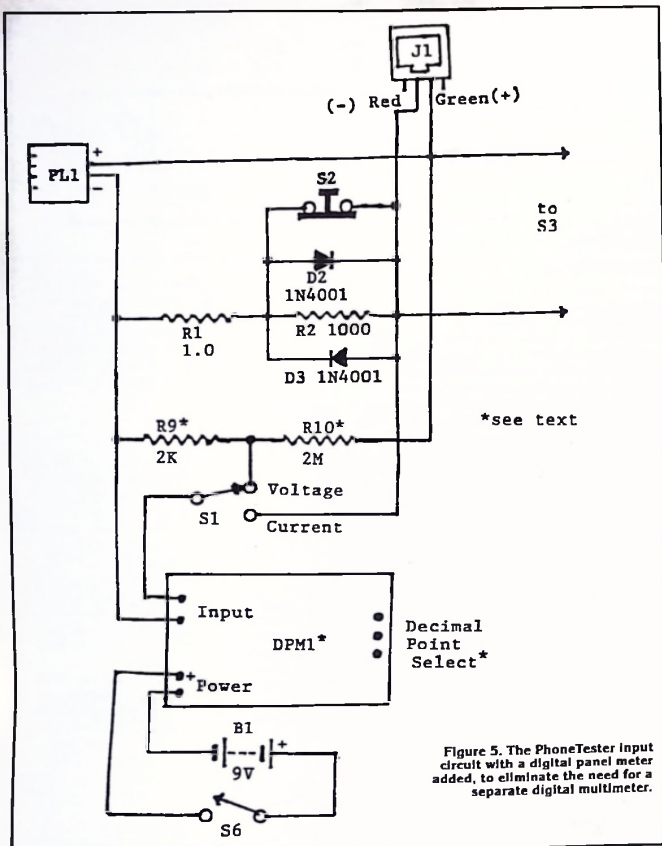


Figure 5. The PhoneTester input circuit with a digital panel meter added, to eliminate the need for a separate digital multimeter.

microamps of not-in-use current. (The not-in-use current of the RadioShack 43-443 is four to five microamps.) If used, these will raise the total leakage current.

The PhoneTester can also be used at individual telephone jacks to test for proper voltage and polarity, and to test the equipment connected to that jack for leakage and for proper in-use current. As mentioned earlier, FCC regulations specify a maximum current — when the line is not in use — of 10 microamps for each telephone or other unit, and the actual current of most units is much lower.

### Optional Circuits

Adding the circuit in Figure 3a to the PhoneTester allows feeding audio from the phone line to a recorder or amplifier.

Transformer T1 is a 600 to 600 ohm unit which can be salvaged from an old modem or purchased from most parts suppliers. C2 must have a working voltage rating of at least 100 VAC or 250 VDC, because of the ring voltage. It cannot be a non-polarized electrolytic, they have too much leakage. J4 can be any desired connector; I used a quarter-inch phone jack. This circuit can also be used to feed audio into

a phone line (such as for music-on-hold), but it requires a source of low-impedance line-level audio. I have used the headphone jack of a small stereo. I made an adapter with a stereo phone plug at one end and a mono phone plug, to connect to J4 of the PhoneTester, at the other end. A 47-ohm load resistor is connected from each output terminal of the stereo plug to the common terminal. A 600-ohm or larger isolation resistor is connected from each output terminal of the stereo plug to the center terminal of the mono plug.

The basic PhoneTester in Figure 1 allows measurement of the on-hook voltage and leakage current, but a telephone must be connected to J1 to allow measuring the off-hook current and voltage, which could be low because of a high-resistance connection in the wiring. I added the circuit in Figure 3b, a "standard" load, to the PhoneTester to allow measurement of off-hook values without connecting a telephone. On my phone line, this load produces an off-hook voltage of 9.45 VDC, with a current of 26 mA. This will vary slightly on different lines, because of variations in the on-hook voltage and the line resistance. LED2 and LED3 are standard-current (20 mA) LEDs, which also give a second check of line polarity.

## Parts Suppliers

**RadioShack.com**  
P.O. Box 1981  
Fort Worth, TX 76101-1981  
1-800-THE SHACK  
www.radioshack.com

**Mouser Electronics**  
958 N. Main St.  
Mansfield, TX 76063-4827  
1-800-346-6873  
www.mouser.com

**MCM Electronics**  
650 Congress Park Dr.  
Centerville, OH 45459-4072  
1-800-543-4330  
www.mcmelectronics.com

In addition to other parts,  
they also carry DPM1:

**Jameco Electronics**  
1355 Shoreway Rd.  
Belmont, CA 94002-4100  
1-800-831-4242  
www.jameco.com

**All Electronics**  
P.O. Box 567  
Van Nuys, CA 91408-0567  
1-800-826-5432  
www.allelectronics.com

**Circuit Specialists, Inc.**  
220 S. Country Club Dr.  
Mesa, AZ 85210  
1-800-528-1417  
www.webtronics.com

**Hosfelt Electronics**  
2700 Sunset Blvd.  
Stebenville, OH 43952-1158  
1-888-264-6464

**Marlin P. Jones & Assoc., Inc.**  
P.O. Box 12685  
Lake Park, FL 33403-0685  
1-800-652-6733  
www.mjpa.com

A ring indicator which can be substituted for R3 and NE1 is shown in Figure 4. LED4 and LED5 are — like LED1 — low-current (2 mA) units. Without C3, one of the LEDs would light from the 48 VDC on the line. Like C2, C3 must have a minimum working voltage rating of 100 VAC or 250 VDC.

If the PhoneTester will be used frequently, it will be easier to use if it has a built-in meter instead of using a separate DMM. Figure 5 is a schematic of the input portion of the PhoneTester with a digital panel meter, DPM1, added to make a self-contained unit. (This will require a larger case. S3 and the circuit to the right of S3 are the same as in Figure 1.) DPM1 can be one of the low-priced units (about \$10.00) available from several parts suppliers. Those with a power supply rating of 7 to 12 volts are usually designed to be used with a nine-volt battery. The DPM basic voltage range should be 200 millivolts. The voltage divider — R9 and R10 — produces a 200-volt range for measuring phone line voltage. The ratio of R9 to R10 should be 1 to 999, but with a ratio of 1 to 1,000 — as in Figure 5 — the error is only 0.1%.

For an important phone line, the circuit in Figure 5 could be used as a permanently



installed line monitor. S3 and the components to the right of S3 in Figure 1 would probably not be needed, except possibly the ring indicator. The values of R9 and R10 would need to be increased to at least 5K ohms and five megohms, with 10K ohms and 10 megohms better, to keep the line-not-in-use current below the FCC requirements. One-percent resistors are not readily available with values above two megohms, so R10 could be made of 1% resistors in series, or by measuring several 5% resistors and using one in the middle of the range.

The nine-volt battery could be replaced by a small nine-volt power supply. However, even with DPMs called "isolated power supply," there is an internal connection between the power terminals and the common input terminal. Since the common input terminal of the DPM is connected to one side of the phone line, the output of the power supply must be well isolated to prevent unbalancing the phone line. Power supplies with a three-prong grounding plug often have the negative output grounded to the plug ground prong. These could not be used, even a fair-sized capacitor from the power supply output to ground or to one side of the AC line (sometimes used for EMI reduction) could unbalance the phone line.

## Problems

Because of the small space between the contact wires in RJ-11 jacks and plugs, spilling any conductive fluid into them may cause leakage between the red and green wires, which are next to each other. When I had this problem in my phone wiring, the only apparent problem was in ringing. The higher ring voltage caused visible sparking between the contact wires, and ringing was weak. This occurred before I built the PhoneTester, but I think the leakage would have shown up in leakage tests with the PhoneTester at the 50 VDC on-hook voltage on the line.

I also have had leakage in S3 of the PhoneTester and in PL1. The leakage in S3 was apparent in the leakage test in the PhoneTester, but to find the leakage in PL1, I built an auxiliary tester. This is an RJ-11 jack with a 1,500-ohm, two-watt resistor connected to the green terminal. I have a bench power

supply with a maximum output voltage of about 48 volts. I connected this to the resistor and to the red terminal of the jack, with a DMM, on its 200-millivolt range, across the resistor, making a leakage tester similar to the leakage test in the PhoneTester. The test jack itself is first checked for leakage, then PL1 of the PhoneTester is connected to the test jack to test for leakage in the PhoneTester.

This test jack can also be used to test a telephone or other item without connecting it to a phone line. Power supplies of other voltages — as low as 15 volts — can be used by changing the value of the resistor. Using a typical off-hook voltage and current of 7 volts and 28 mA, a minor rearrangement of the Ohm's Law formula gives the value of resistor R for any supply voltage V:

$$R = \frac{(V-7)}{0.028}$$

The specifications of the 1N400x series diodes give a maximum reverse leakage current of 10 microamps. This amount of leakage in D1 would affect leakage measurements, although the prototype PhoneTester shows no leakage reading when S3 is in the reverse position. I tested about 25 1N4004 and 1N4007 diodes, using a 50-volt power supply and leakage test circuit of the PhoneTester. None of them gave any reading on the meter, indicating reverse leakage of less than one microamp. It appears that the actual reverse leakage of most 1N400x series diodes is much less than the specified maximum. If you want to be sure of preventing reverse leakage in D1 from affecting leakage measurements, a DPDT switch with a center off position (such as RadioShack 275-664) can be used for S3.

I have mentioned the FCC leakage requirements, but not that the FCC test specifies a test voltage of 100 VDC. Usually, using the PhoneTester with the 50 volts on the phone line or from a power supply will find any leakage, but if you want to test at 100 volts, a suitable power supply can be connected to the auxiliary test jack, with the resistor changed to 3,300 ohms, 5 watts. At 100 volts, the current will be 20 microamps for 5 megohms and 10 microamps for 10 megohms; but be careful, 100 volts can be dangerous, even deadly! NV

Visit us at [www.nutsvolts.com](http://www.nutsvolts.com)

**DesignNotes.com**

Your Design Resource on the Web

Improve Your Design Skills, Find Project Advice and More

## Velleman's HPS5



Hand Held Oscilloscope  
**\$179.00**

Complete with alkaline batteries, clip leads and carry bag

Visit Our Online Forum

## On-Line Circuit Archive

Hundreds of Circuits.  
Over 23 Different Topics

## Designing for Dollars

Submit your favorite circuit or program. Each month the best design entry (Judged by your peers) wins \$100 in cash. Monthly winners are eligible for the yearly \$1200 Grand Prize!

Share What You Know and Learn What You Don't

Visit Us at  
[www.designnotes.com](http://www.designnotes.com)

Circle #59 on the Reader Service Card.

**Electro Mavin**  
Great Buys - Great Products - Great Gadgets  
Check Out Our Great WebSite at

<http://mavin.com>

For Computer Items, Hobbist Projects,  
Microwave Goodies and Some of the  
Greatest Prices on the Web....

800-421-2442 or FAX 310-632-3557

E-Mail

[john@mavin.com](mailto:john@mavin.com) or [sean@mavin.com](mailto:sean@mavin.com)

## PIC 16F84 On Screen Display Project Board



This project board combines a 16F84 with the STV5730A OSD IC. It is designed to overlay text and graphics characters onto any composite video signal. Example programs are available for call sign generation, GPS data display and serial control pre-programmed and as PIC source code. To be used as the basis of your own projects. 16F84 programs can now be easily interfaced to any video equipment.

Visit [www.STV5730A.co.uk](http://www.STV5730A.co.uk) for full product details  
Enquiries: [sales@STV5730A.co.uk](mailto:sales@STV5730A.co.uk)

The BlackBoxCamera™ Company Ltd.

Coastal House, 180 Bridge Road, Southampton, SO31 7EH, England



# Amateur Robotics

**N**ext I have a few words to say about the hearts of robot builders. We don't often think about the most important component of our robotics designs — our own personalities. Personality unavoidably affects everything we do, from tools we use to the metaphors by which we describe ourselves, and maybe there's something to learn there. But first, I'll jump right into the PDM.

## Power to the Steppers

My four-phase step motors are rated for 1.8A per phase at one volt, and since I'd be driving them with the

windings arranged in two sets of two series-connected windings, that meant each motor would require 1.8A at 2V to produce its full rated torque. Since I had three motors to run, I needed a power supply rated for  $3 \times 1.8 = 5.4\text{A}$ , right? Well, maybe not.

I was puzzled about why Dan Mauch's documentation for the Camtronics three-axis 2A Chopper called for a 10A, 12V supply. By my previous analysis, I "knew" that three 2A step motors would require just 6A. Why had Dan apparently over-designed his power supply? Dan is conservative, but 167% seemed overkill, even for him. I dug deeper.

The problem, I soon concluded,


was with my original analysis. Back when I was designing my power supply, I had neglected to remember that two phases of each motor would be drawing current at a time instead of just one. Call it sleep deprivation or battle fatigue — Nadav was just a month old at the time, so I had some excuse. Whatever the case, I discovered the error long after I had ordered all the parts for a supply designed to produce only 8A. A stupid mistake, I know, but it happens. As a calculus professor of mine once told me, "You know engineers aren't perfect, because otherwise there wouldn't be such things in the world as shims."

Shucks and other saltier com-

ments.

Okay, start over. Three motors with two phases on, means, um, (let's see ... carry the one, drop the calculator, scratch my head, try again ...) I need  $3 \times 3.6\text{A} = 10.8\text{amps}$ . Throw in a couple 12V cooling fans and the current draw of the chopper drive board, and the current required of the power supply comes to over 11 amps.

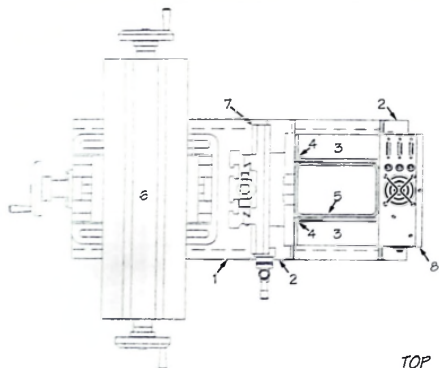That can't be right, can it? The Camtronics board is rated to drive 2A per phase motors. Three such motors would require 12A by this reasoning. Now I was beginning to wonder if Dan had under designed the supply. Knowing Dan, this seemed unlikely. What was really going on?





TOP

- 1 Machine bed, 1 ea, hot-rolled steel channel,  $10'' \times 3'' \times .5'' \times 24''\text{L}$  (26 lb/ft)
- 2 Column bracket, 2 ea, hot-rolled steel angle,  $2'' \times 2'' \times 1/4''\text{T} \times 10''\text{L}$
- 3 Column bracket, 2 ea, hot-rolled steel angle,  $2'' \times 2'' \times 1/4''\text{T} \times 6''\text{L}$
- 4 Z-axis bracket, 2 ea, hot-rolled steel angle,  $2'' \times 2'' \times 1/4''\text{T} \times 10.75''\text{L}$
- 5 Column, 1 ea, hot-rolled rect. steel tube,  $6'' \times 4'' \times 1/4''\text{T} \times 24''\text{L}$
- 6 Enco Heavy-Duty Mill & Drill Table, Model 201-2536
- 7 Enco Compound Slide Milling & Drilling Table, Model 201-2826
- 8 Power Supply and Step Motor Drive Chassis

SIDE

REAR

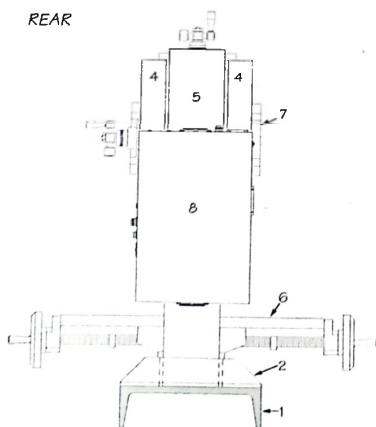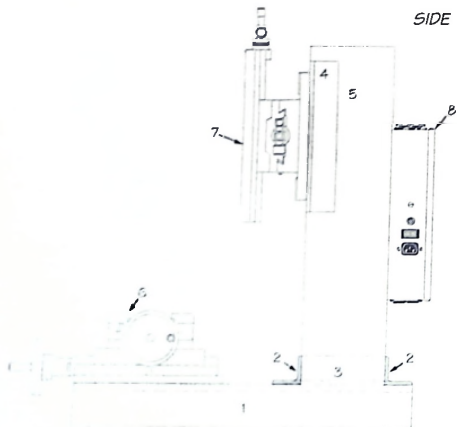




## Nuts &amp; Volts Magazine/SEPTEMBER 2001 83


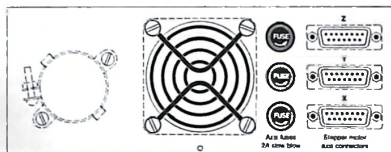
# Robotics


Chassis layout of the major components of the power supply and 3-axis stepper driver. Chassis shown center with cover removed. The stepper drive board is arranged vertically on the open centerline of the chassis to allow passive convection cooling without fans for low-current applications. (under 1A per axis). In addition, intake and exhaust fans are located bottom and top in-line with the L200 driver heat-sinks to assist convection cooling at higher current outputs—up to 2A per axis. Each axis has its own connector, fuse, and status indicator. Each connector provides enough pins to control a 4-wire stepper motor, with pins left over for Home and Limit switches and future expansion, such as an optical limit encoder.




**Top Panel**



Right Panel

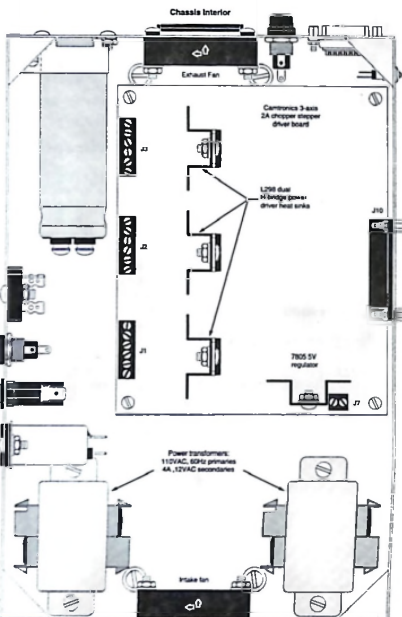


### Chassis Interior

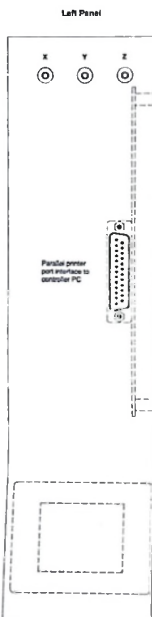

Left Panel

### Bottom Panel

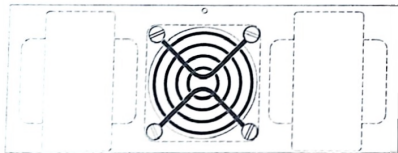

in which the chopper might also fit. I solved the problem by choosing two small transformers. This turned out to be more flexible — and cheaper.

The Chopper board is 5.6'D x 6.8'W x 2.2'H, and I wanted an inch or two space on all sides of the board. Enclosure choice came down to a 17" x 10" x 4" chassis with plain flat plate cover vs. a chassis 12" x 8" x 3" with cap cover. I chose the latter because it was more rigid with triangular reinforcement gussets; the cover was more rigid.

too, and sealed against the environment better. As with the transformers, two small fans were easier to work with than one big one. This allowed me to keep the ventilation axis on the centerline of the enclosure and that, in turn, allowed the main column of Heavy Iron to provide a baffle against flying metal chips entering ventilation openings.

## Connections

1 these DB15 connectors to con-

nect the steppers because they are cheap, rugged, dust resistant, and offer enough pins to add extra functionality to individual axes. I investigated military-style circular connectors, but they come with a military-style price: over \$16.00 per connector set, compared to under \$6.00 for a DB15 set. Plus, they are smaller.

An IEC modular power connector and line filter helps isolate 110 wiring and line noise from the chopper board. Miniature fuse holders save space inside

the chassis, with separate fuses for each axis and LED indicators to show status as mentioned earlier. An illuminated switch completes the design.

## Alchemy and Bonsai

Whew! All that hard work has put me in a beer mood, and as night follows day, beer leads directly to philosophy. An ongoing interest of mine is the sociology of robot building. I know some folks claim us gearheads have no lives



# Robotics

and that's why we build robots, but I disagree.

In my other life, I'm a science fiction writer, which makes me something of an armchair anthropologist, too. I spend time wondering about what makes people tick. It begins by asking simple questions. My favorite questions have lately been: Who builds robots? and Why do they build them? I tend to think of two personality types, which I label the Alchemist and The Bonsai Gardener.

The first is the image of the robot builder laboring alone, secretive, like an Alchemist in a dusty laboratory, programming obsolete microcontrollers, fitting aluminum angle, breathing soldering smoke, all energies focused on extracting that one secret that will make robots practical. Believing no one else shares their compulsion to transmute base metals and semiconductors into cyborged, alchemists must invent (and reinvent) the mechanisms and circuitry of their robots — alone.

## Robotnugen?

Sometimes, when a robot is only partly done, they sense possibilities of fame and wealth. Like a current, it tugs at them, urging them on. It could happen, you know: a small flash of insight cascading through improbable luck and hard work, seeking to run over finally to that deep pool, the reservoir of hard-won electromechanical truths that make machines work. Call it design elegance, or call it Robotnugen (remember the Volkswagen commercials?), but let this robot be the one that has enough of it to fulfill the dream.

Mostly the robot never gets finished. In some cases, that's just as well because the act of constructing a failed robot teaches its own valuable lessons; in molding the machine, the builder is molded. It is the best education possible if you are receptive to it. Being open can turn failure into serendipity — the good luck that comes to those who are prepared for it.

Unfortunately, alchemists cling to their preconceptions of how the process should go and, in doing so, create an adversarial relationship with their robots. They strive to force the machine to match the image of the ideal robot. Images are illusion, so their efforts will fail and they will not learn from that failure. Alchemists are not prepared to fail, nor are they really prepared for luck.

## Robotic Gardens

How can you prepare for luck? One way is to regularly devise yourself of preconceived notions about what a robot should be. This is the robot builder as a technological Bonsai

Gardener, sowing ideas and encouraging growth. Bonsai gardening is as much a discipline as a style. Bonsai gardeners don't seek to wrest secrets from an unwilling universe; rather they persuade potential to emerge. Their relationship to work is that of collaboration between creator and created. Design is a two-way communication process.

Gardeners advance hypotheses, the designs accept or refute, the gardeners reformulate, the robots react, and so on. Like bonsai gardening, building a robot is a process of numerous course corrections, each step small, purposeful. The Bonsai Gardener will change as much as the tree in the end, bending a twig to suit the gardener's will and, in turn, the gardener's will bending to suit the twig. For the bonsai gardener, robotnugen is about the journey, not the destination.

Another aspect of the robot-builder-as-gardener is they share information with other gardeners. Alchemists rarely share secrets because they must work so hard to mine them in the first place. Botanists know that ideas are meant to be shared, that they have more than one relationship to the world. If their ideas shape other gardeners' gardens, so will those gardens shape them. Gardeners work for long-term gains; alchemists work for the big splash.

## Notebooks

The differences in philosophical outlook between alchemist and bonsai approaches manifest in less mystical/poetic ways, too. Gardeners keep notebooks, not polished, but complete — including failures. And they share their notes with others often.

Alchemists rarely keep adequate notes, and when they do, they tend toward the purpose of proving priority in patent disputes. Their notes obscure and deny failure. They won't share their notes for fear of losing advantage.

Another practical difference is the scale of their projects. Alchemists prefer big, risky projects that reek of individual glory; instead of a lowly mail-delivery robot, they prefer battlefield robot tanks, idiosyncratic and incompatible with all that has gone before.

Gardeners work incrementally, building whole systems of carefully crafted modules. Upgrading mail-delivery robots to deliver meals in hospitals is more to their liking than robot tanks. Compatibility and teamwork are their hallmarks.

As with any classification scheme that compartmentalizes people, this alchemist/bonsai dichotomy is a gross oversimplification. We all have both alchemist and bonsai gardener tendencies in us. Both can serve useful functions.

To be a successful robot builder, you must find the proper balance between the lone-wolf alchemist and the bonsai gardener. When you achieve this balance, you will know the bliss of Robotnugen.

## Too Much Philosophy

Or too much beer. In either case, I'm outta here. NV

Part	Description	Vendor	Vendor part #
C1	10,000 MFD. 50WVDC electrolytic capacitor	Mouser	539-CGS50V10000
F1	Miniature fuse (5mm x 20mm), 2A, fast-acting	Mouser	5765-35002
F2-F4	Miniature fuse (5mm x 20mm), 2A, slow-blow	Mouser	5765-39002
Fan1,2	2-3/8" sq. x 9/16" 12VDC box fan	MPJA	1271-FN
J14-J16	DB15 15-pin female connector, solder cup, tin	Digi-Key	1115F-ND
J17-J19	DB15 15-pin male connector, solder cup, tin	Digi-Key	1115M-ND
J20	2-pin right-angle friction lock male header	Digi-Key	WM4300-ND
J21	2-pin center crimp terminal housing	Digi-Key	WM2000-ND
LED1,3	Red, diffused, 1.1 (3mm), panel-mount LED	Mouser	35CA001
R1-R3	1.1K ohm, 1/4W, 5% carbon film resistor	Digi-Key	11KQBK-ND
S1	Illuminated rocker switch, SPST 15A, 125VAC w. amber neon lamp & internal resistor	Mouser	10DS22
T1, T2	Transformer, 110/220VAC input, 12VAC output	MPJA	7840-TR
U1	25A, 400V PVR bridge rectifier	Mouser	625-GBPC2504
Misc:			
1 ea.	3-axis 2A Chopper/Step Motor Driver kit	Camtronics	
1 ea.	Vertical capacitor mounting hardware	Mouser	539-VR3
4 ea.	Panel-mount miniature fuse holder	Mouser	441-R3-12
2 ea.	Fan guard for 2-3/8" fan	MPJA	8660-FN
1 ea.	6-ft 3-wire IEC cord set	Mouser	173-63101
1 ea.	IEC connector/line filter, 6A 250VAC 50-60Hz	Mouser	562-857-06/27
1 ea.	8" W x 12" D x 3" H aluminum enclosure	Mouser	537-8123
1 ea.	8" x 12" aluminum enclosure cover	Mouser	537-8123C
3 ea.	DB-15 conn. backshell, shielded plastic	Digi-Key	915CA-ND
6 ea.	4-40 female hex screw/conn. hardware	Digi-Key	160-10F-ND
4 ea.	Hex threaded standoff, alum. 6/32, .25" x .375"	Digi-Key	2209K-ND
2 ea.	Crimp terminals for J10	Digi-Key	WM2200-ND

## Suppliers:

**Camtronics Inc.**  
1820 130th Place NE  
Boothill, WA 98011-3118  
www.seatron.com/~dmauch  
email: dmauch@seatron.com

**Digi-Key Corporation**  
701 Brooks Ave. South  
Thief River Falls, MN 55701-0677  
www.digikey.com  
Tel: 800-344-4539, 218-881-6674  
Fax: 218-681-3380

**Marlin P. Jones & Associates Inc./MPJA**  
P.O. Box 12685  
Lake Park, FL 33403-0685  
www.mpja.com  
Tel: 800-652-6733, 561-848-8236  
Fax: 800-432-9937, 561-848-8299

**Mouser Electronics**  
955 North Main Street  
Mansfield, TX 76063  
www.mouser.com  
Tel: 800-346-6873, 817-483-6848  
Fax: 817-483-6899, 817-483-6898

## Serial in, graphics out. Almost too easy.

These serial displays take RS-232 at 2400 or 9600 baud and produce stunning text and graphics on a supertwist LCD screen. See our complete line at [www.seatron.com](http://www.seatron.com). All models are in stock for immediate delivery.

### G12032 120x32-pixel LCD

- Same size as 2x16 text LCD
- Editable font(s) in 4 sizes
- Up to 6 screens in EEPROM
- Easy terminal protocol



(3.2 x 1.4 in.)



(3.7 x 2.8 in.)

### G12864 128x64-pixel LCD

- Large, sharp LCD
- Editable font(s)
- Up to 14 screens in flash
- Separate text, graphics layers
- DB9 connector built in
- AC adapter jack built in
- Easy terminal protocol

**www.seatron.com**

Scott Edwards Electronics, Inc. • ph 520-459-4802 • fx 520-459-0623 • [sev@seatron.com](mailto:sev@seatron.com)

If you have suggestions, questions, or comments about amateur robotics topics, you can now reach me at:

Robert Nansel  
Box 228  
Ambridge, PA 15003

Email: [bnansel@nauticom.net](mailto:bnansel@nauticom.net)



# Advertiser INDEX

Abacom Technologies	59	DesignNotes.com	81	Information Unlimited	71	MVS	77	Shreve Systems	35
ActiveWire, Inc.	49	DesignTech Engineering Co.	43	InJet Southwest	55	Network Systems Technology Inc.	77	Square 1 Electronics	73
All Electronics Corp.	34	Earth Computer Technologies	87	Intellcam Systems	66	Ohio Automation	78	Sun Equipment Corp.	70
Allison Technology Corp.	7	ECI	48	Intronics, Inc.	42	Parallax, Inc.	Back Cover	Techniks, Inc.	49
Altronics	21	E.H. Yost & Co.	27	J-Works, Inc.	42	PCB Express, Inc.	50	Technological Arts	20
Andromeda Research	42	Electro Mavin	81	Labmetrix Inc.	14	Picard Industries	46	Test Equipment Connection	75
Baylin Publications	27	Electronic Goldmine	53	LDG Electronics	43	Pioneer Hill Software	77	The BlackBoxCamera Co., Ltd.	81
Bloom Corp.	29	Electronics Corp.	28	LedVision Holdings, Inc.	50	Polans Industries	49	The Mercury Group	49
Brian Thomas Robotics	81	EMAC, Inc.	13	Leoma International Co., Inc.	13	Prolean Logic, Inc.	46	The RF Connection	41
Burns Scientific	23	EMT	48	Linear Systems	19	Pulsar, Inc.	20	Unicom Electronics	78
C & S Sales, Inc.	29	ExpressPCB	77	Lynxmotion, Inc.	28	Quality Kits	32	Vista Technology Inc.	31
C & H Sales Co.	81	Fosa Warehouse Distributors	50	M2L Electronics	48	Ramsay Electronics, Inc.	49	Vision Systems International	12
CCTV Outlet	52	Gateway Electronics, Inc.	17	Malco, Inc.	49	Resources Un-Ltd.	22	VisiTech, Inc.	72
Circuit Specialists, Inc.	94	General Device Instruments	50	Meredith Instruments	57	Rogers Systems Specialists	68	Western Test Systems	38-39
Component Kits, LLC	49	Halted Specialties Co.	3	Mouse Electronics	19	Saegle Company	16	Westshore Technologies	42
Consumetronics	48	H.T. On Computer Supplies	74	Mr. N.Cod	27	Scott Edwards Electronics, Inc.	45	Zagros Robotics	32
Corporate Systems Center	2 95	Inception Systems Inc.	48						
Cumero Associates	74								
Custom Software Creators	59								

## AMATEUR RADIO & TV

Alltronics	21
Gateway Electronics, Inc.	17
LDG Electronics	43
Lemco International Co., Inc.	13
Ramsay Electronics, Inc.	31
SGC	45
The RF Connection	41

## ASSEMBLY SERVICES

Bloom Corp.	29
-------------	----

## BATTERIES/CHARGERS

Brian Thomas Robotics	81
Guard Associates	74
E.H. Yost & Co.	27
GlobalTech Distributors	48
Mr. N.Cod	27
Robot Store	83

## BUSINESS OPPORTUNITIES

C and H Sales Company	75
Earth Computer Technologies	87
Rogers Systems Specialist	68

## BUYING ELECTRONIC SURPLUS

## CABLE TV

Fosa Warehouse Distributors	50
GlobalTech Distributors	48
Worldwide	32

## CB/SCANNERS

## CCD CAMERAS/VIDEO

CCTV Outlet	52
Circuit Specialists, Inc.	94
Intellcam Systems	66
Matco, Inc.	49
Polans Industries	49
Ramsay Electronics, Inc.	31
Resources Un-Ltd.	22
The BlackBoxCamera Co., Ltd.	81

## CIRCUIT BOARDS

Guard Associates	74
ECI	48
EMT	48
ExpressPCB	77
PCB Express, Inc.	50
Pulsar, Inc.	49

## COMPONENTS

Component Kits, LLC	49
ECI	48
Linear Systems	19
Pulsar, Inc.	49

Unicom Electronics	78
VisiTech, Inc.	72

## COMPUTER

### Hardware

ActiveWire, Inc.	49
Allison Technology Corp.	7
Corporate Systems Center	2 95
Custom Software Creators	59
Earth Computer Technologies	87
Electro Mavin	81
General Device Instruments	50
Halted Specialties Co.	3
Rogers Systems Specialist	68
Shreve Systems	35
Techniks, Inc.	49

### Software

Consumetronics	48
Electronics Corp.	28
GlobalTech Distributors	48
Pioneer Hill Software	77

### Microcontrollers / I/O Boards

Abacom Technologies	59
EMAC, Inc.	13
microEngineering Labs	41
Micromint	48
MVS	78
Parallax, Inc.	Back Cover
Prairie Digital, Inc.	49
Prolean Logic, Inc.	46
Scott Edwards Electronics, Inc.	85
Square 1 Electronics	73
Technological Arts	20
Vesta Technology, Inc.	48
Worldwide	32

### Printers/Printer Supplies

H.T. On Computer Supplies	74
InJet Southwest	55

## DESIGN/ENGINEERING SERVICES

Bloom Corp.	29
DesignNotes.com	81
DesignTech Engineering	43
EMT	48
ExpressPCB	77
Metrix Technology Corp.	48
Prairie Digital, Inc.	49
Pulsar, Inc.	49
The Mercury Group	49

## EDUCATION

EMAC, Inc.	13
Prolean Logic, Inc.	46

## EVENTS/SHOWS

## KITS

Alltronics	21
Brian Thomas Robotics	81
C & S Sales, Inc.	29
Component Kits, LLC	49

Earth Computer Technologies	87
Electronic Goldmine	53
EMAC, Inc.	13
Gateway Electronics, Inc.	17
HWV Technologies, Inc.	49
Information Unlimited	71
InJet Southwest	55
Quality Kits	32
Ramsay Electronics, Inc.	49
Robot Store	83
Scott Edwards Electronics, Inc.	45
Worldwide	32
Zagros Robotics	32

## LASERS

Information Unlimited	71
Meredith Instruments	57
Resources Un-Ltd.	22
Unicom Electronics	78

## MISC./SURPLUS

All Electronics Corporation	34
C and H Sales Company	75
DesignTech Engineering Co.	53
Electronic Goldmine	53
Gateway Electronics, Inc.	17
Halted Specialties Co.	3
Levision Holdings, Inc.	50
Linear Systems	19
PCB Express, Inc.	50
Picard Industries	46
Resources Un-Ltd.	22
Shreve Systems	35
Unicom Electronics	78
Viking Systems International	12
VisiTech, Inc.	72

## PROGRAMMERS

Andromeda Research	42
General Device Instruments	50
HWV Technologies, Inc.	49
Intronics, Inc.	73
M2L Electronics	48
microEngineering Labs	41
Sun Equipment Corp.	70
Worldwide	32

## PUBLICATIONS

Baylin Publications	27
Consumetronics	48
Mouse Electronics	19
Square 1 Electronics	73

## RF TRANSMITTERS/RECEIVERS

Abacom Technologies	59
Matco, Inc.	49

## ROBOTICS

Brian Thomas Robotics	81
HWV Technologies, Inc.	49
Inception Systems, Inc.	48
Lemos International Co., Inc.	13
Lynxmotion, Inc.	20
Prolean Logic, Inc.	46

Robot Store	83
The Mercury Group	49
Zagros Robotics	32

## SATELLITE

Baylin Publications	27
Worldwide	32

## SECURITY

CCTV Outlet	52
Consumetronics	48
Information Unlimited	71
Intellcam Systems	66
Lemos International Co., Inc.	13
Matco, Inc.	49
Polans Industries	49
VisiTech, Inc.	72

## STEPPER MOTORS

Alltronics	21
Component Kits, LLC	49
The Mercury Group	49

## TELEPHONE

Bloom Corp.	29
GlobalTech Distributors	48

## TEST EQUIPMENT

Allison Technology Corp.	7
C & S Sales, Inc.	29
C and H Sales Company	75
Circuit Specialists, Inc.	94
DesignNotes.com	81
Intronics, Inc.	73
J-Works, Inc.	42
Labmetrix, Inc.	14
Pioneer Hill Software	77
Prairie Digital, Inc.	49
Saegle Company	16
Sun Equipment Corp.	70
Test Equipment Connection	75
Western Test Systems	38-39
Westshore Technologies	42
Worldwide	32

## THERMOCOUPLE WELDER

Burrell Scientific	23
--------------------	----

## TOOLS

C & S Sales, Inc.	29
Sun Equipment Corp.	70
The RF Connection	41

## WIRE/CABLE & CONNECTORS

Rogers Systems Specialist	68
The RF Connection	41



Build this security module for your X-10 home automation system and never worry again about someone inadvertently controlling your lights and appliances. Best of all, no modifications are necessary to any X-10 modules or the power line — simply plug in the X-Lock and you're protected!

Or picture this. The same coffee pot. You have a friend come over and they bring their toddler with them. While you're talking, you don't notice the child pick up one of your X-10 remotes. Perhaps thinking it's a TV remote — or randomly punching buttons just as children do with the telephone — before you know it that darn coffee pot gets turned on again. Just as you're leaving for the airport!

16

Start Code   H1 H2 H3 H4 H5 H6 D1 D2 D3 D4 D5 D6 D16

1 1 1 0 0 1 1 0 1 0 0 1 1 0 1 0 1 0 1

11110   0110   111100

Start Code   House Code 'A'   Key Number 'Z'

Consider the following scenarios. You control your coffeepot via the X-10 system. One day, a neighbor purchases an X-10 system and starts using it to control his/her home using the same house code (after all, there's only 16 to choose from; I wonder what percentage leave on code A). Or worse yet, the bored teenager next door starts going through all the house codes to see what he (no way

## Nuts &amp; Volts Magazine/SEPTEMBER 2001 87








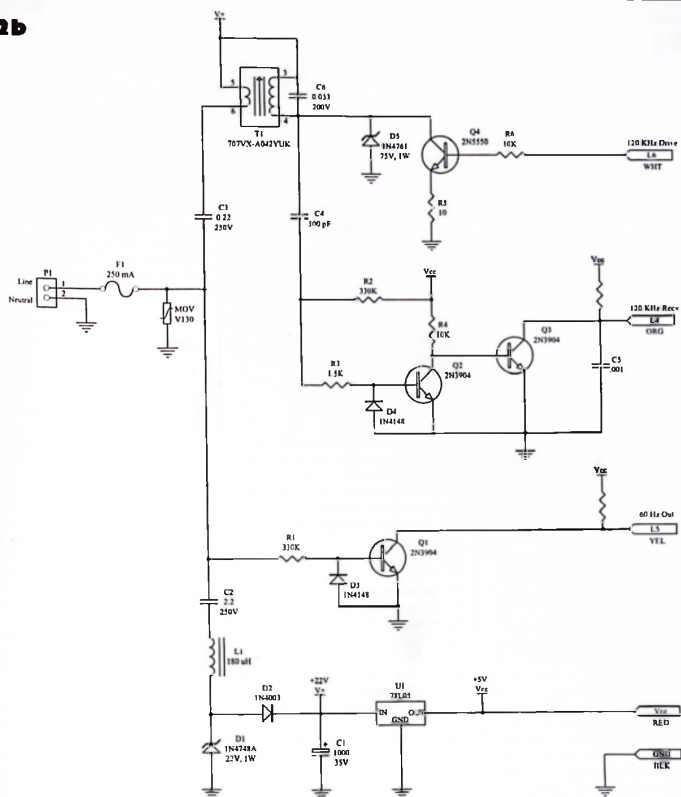


Figure 3. Digital board on left connects via ribbon cable to analog board on right.

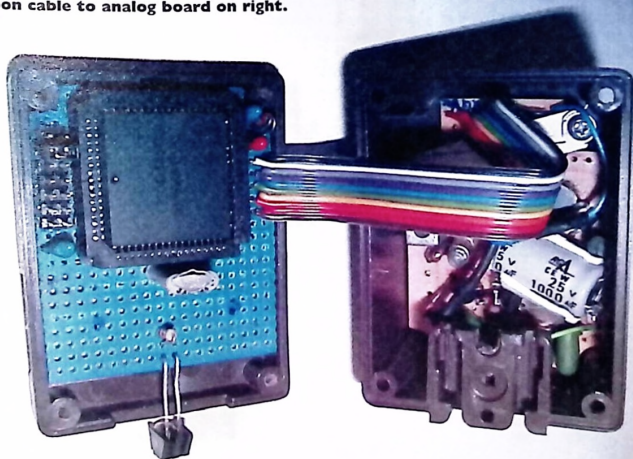

respond. Actually, most modules require both transmissions to be error free before they react; but just to be sure, we jam in the middle of the function bit of the first transmission to make sure no valid streams get through.

When not jamming, the X-Lock also looks for the proper arm and disarm passcode sequences. In Mode 1 (high security, single deactivation operation), when the disarm passcode is correctly received, the X-Lock temporarily goes to sleep allowing the following authorized commands to be sent unjammed. While snoozing, it keeps an ear on the line and waits until no more signals have been transmitted for a preset amount of time.

When this window closes, the X-Lock re-arms itself and begins protecting the line again. In Mode 2 (arm/disarm operation), the disarm passcode permanently disables the X-Lock until the arming code is received.

One minor detail is also accomplished whenever disarming the X-Lock. Since the passcode numeric keys are received by all modules while they are entered, any action keys pressed after entering the passcode would be acted upon by these modules.

In other words, if the passcode was 1-2-3 and then you pressed 4 ON to turn on module 4, modules 1, 2, and 3 would also go on. To prevent this, the X-Lock sends a dummy command (actually the seldom used HAIL ACK command) just before disarming. This resets any previously addressed modules so they do not respond.

## Microcontroller Selection


As for the brains of this device, several microcontrollers were examined. Readers of this magazine may be very familiar with the PIC controllers from MicroChip. Many X-10 designs have been built around these chips. They are inexpensive and easy to program. For this design however, I chose to use a COP8FLASH microcontroller from National Semiconductor.

The COP8FLASH microcontroller family provides a number of features, which make the design of this device much simpler. In several cases, specific features of the microcontroller allowed a function normally designed in hardware to be moved into the software code, adding flexibility and reducing parts count (and, of course, cost).

For example, the design calls for a keyable, 120 KHz oscillator. In almost every other X-10 implementation, this is provided by an analog circuit using tuned components. While having a CPU generate this signal sounds trivial, very few microcontrollers would be up to the task. Creating this signal using a software loop would require very fast instruction times, not to mention the difficulty in creating a symmetrical loop and maintaining a stable frequency and duty cycle for an extended period.



**Figure 4. Duplicating the rotary switches using a portion of the original Printed Circuit Board.**

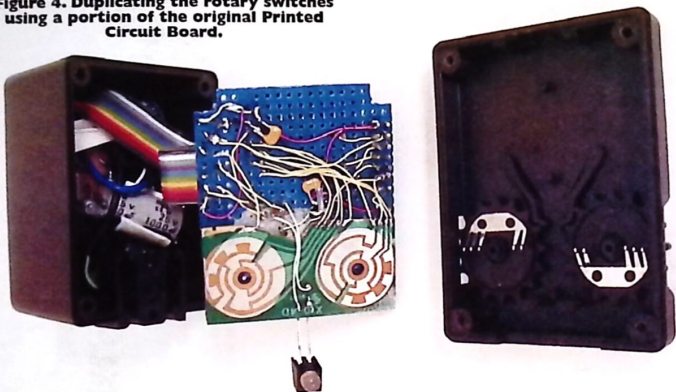

Initially, I planned to rely upon an external oscillator using the microcontroller to simply gate it on and off. However, the PWM mode of the COP8 timers seemed perfect for the job. Using the high-speed mode, I was easily able to create an independent oscillator and control the phase of its off state. I even found a way to calibrate the frequency, further eliminating parts from the hardware side. All in all, quite a savings in parts, board space, and manual construction.

Non-volatile storage was essential to saving user parameters across power outages. Since only a small amount was needed, the ability to create a Virtual EEPROM within the on-chip flash memory made for a very efficient design. Elimination of other components — such as two rotary switches — is also possible with software, although this would complicate the user interface and operation appreciably.

High current drive allowed a bipolar LED to connect directly across two data outputs for user feedback.

Another part-saving design is the 120 Hz interrupt generator. Normally, this requires a full wave bridge supply or a differentiator to create 120 Hz from the 60-Hz power line. The bridge approach adds complexity and prevents using one leg of the power line as a common ground. A differentiator would add an asymmetrical delay to the zero crossing detection.

Instead, this design uses the programmable edge detection on the interrupt inputs available in the COP8. Thus, after triggering on the positive edge of the power cycle, the COP8 is reprogrammed to look for the next negative edge. The next interrupt then reverses this and the cycle repeats.

Low power CMOS technology may not seem vital to this design, however being powered directly off the AC powerline places several

restrictions on the size of components for a given supply current. Thus, the COP8's low power requirements translated into an efficient, low-cost power supply circuit. Other power-saving features of the COP8 may prove useful in future designs that add battery back-up operation.

### Building the X-Lock

After building a prototype to test out the feasibility of this design (see sidebar, "The X-Lock's Interesting Heritage"), I examined the options for building a self-contained interface. Anyone who has tinkered with X-10 and computer control is probably aware of the TW523 interface which X-10 makes available for such projects. However, the TW523 does not output the data stream during the first transmission and unfortunately, this design "feature" makes it unsuitable for our purposes.

Therefore, all of the functions of receiving and transmitting X-10 sig-

nals would have to be included, as well as a control system. To be truly self-contained, a power supply would also have to be built within the module. The complete schematic is shown in Figure 2.

The simplest way to construct this project is to "cannibalize" a lamp or appliance module; if you have a defunct module, all the better. Several key components can be salvaged from the module (unless, of course they were the reason the module failed) and the empty case is a perfect enclosure for the completed project.

Like the donor module, the X-Lock is built on two circuit boards: a digital board and an analog board (see Figure 3). The digital board contains a single active device — the COP8FLASH microcontroller (MCU). Except for a few bypass capacitors and programming header, the only other circuitry on this board is a 3.58-MHz crystal with its load capacitors and a dual color LED.

On the back of the digital board,

circuit traces implement the two 16-position rotary switches. This is easily accomplished using a cut-off portion from the donor module to provide this function (see Figure 4). This board mounts to the top half of the module case, where the wiper portions of the rotary switches reside. The digital board then connects to the analog board inside the bottom half using a five-conductor ribbon cable.

The analog board comprises a power supply and interface circuitry to condition the 60-Hz and 120-KHz detectors and the 120-KHz drive signal. The power supply has rather unusual requirements in that it must connect directly across the 120-VAC power line, drop a considerably high voltage without dissipating too much power, handle the transients and noise commonly found, and allow coupling of the 120-KHz signals. A power transformer could be used, but would unduly add to the cost and size of this device.

Like other devices designed for power line carrier communications, this module uses a capacitor to isolate and drop most of the incoming 120V (340V P-P) AC signal. A rectifier and zener provide a rough 22V supply. An RF choke is also placed in series with the incoming line to keep the power supply from swamping out the signaling RF imposed on the line. The 22-volt supply is used solely by the 120-KHz drive circuit via a tank coil which is part of a tuned circuit to couple as much signal to the line as possible. This supply also feeds a 78L05 regulator IC that provides +5V to the remaining circuit (including the MCU).

The same tuned transformer used by the drive circuit is also used by the 120-KHz RF detector. The RF present on the line is multiplied by the turns ratio of T1 and the Q of this circuit (roughly 7-10) yielding a 2-50V P-P signal, which is fed to a squared/integrator (Q2, Q3, and C5). The output from the integrator is normally high, but remains low as long as the 120-KHz RF is present.

This signal is presented to the D4 bit of Port L of the MCU. More elaborate detector circuits could be used (such as one based on the obsolete LM1893 Carrier-Current Transceiver), but this simple design has proven very effective.

The power line is also squared and buffered by Q1 to provide a reference signal to the MCU. This signal is applied to the D5 bit of Port L. The program detects both positive and negative zero crossings of the power line to synchronize the detection algorithm.

The MCU generates a 120-KHz signal to "talk" on the power line. This squarewave is independently created by the MCU Timer 3 operating in its PWM mode. Thus, the program only needs to set a single control bit to toggle the oscillator on or off. This signal, which comes out the T3A pin of the MCU, is used to drive Q4 which places the drive signal across the sec-

## PARTS LIST

### Analog Board

- C1 - 1000 uF, 35VDC electrolytic capacitor
- C2 - 2.2 uF, 250V NP mylar capacitor
- C3 - 0.22 uF, 250V NP mylar capacitor
- C4 - 300 pF, 100V capacitor
- C5 - 0.001 uF capacitor
- C6 - 0.033 uF, 200V polypropylene capacitor
- D1 - 1N4748A zener diode, 22V, 1W
- D2 - 1N4003 diode, 200V, 1A
- D3, D4 - 1N4148 silicon diode
- D5 - 1N4761A zener diode, 75V, 1W
- F1 - 250 mA fuse
- L1 - 180 uH, 250 mA inductor
- MOV - V130 type transient suppressor
- PI - line cord/plug
- Q1-Q3 - 2N3904 NPN transistor

- Q4 - 2N5550 NPN HV transistor
- R1,2 - 330K ohm 1/4W carbon resistor
- R3 - 1.5K ohm 1/4W carbon resistor
- R4, R6 - 10K ohm 1/4W carbon resistor
- R5 - 10 ohm 1/4W carbon resistor
- T1 - 120 KHz signal transformer (Toko P/N 707YX-A042YUK)
- U1 - 78L05 regulator IC, 5V

### Digital Board

- C1 - 1 uF, 25VDC tantalum capacitor
- C2 - 0.1 uF, 25VDC mono capacitor
- C3, C4 - 20 pF capacitor
- LED1 - bipolar, three color LED
- R1 - 470 ohm 1/4W carbon resistor
- SW1, SW2 - 16 position, 4 pole switch
- U1 - COP8SCR9 microcontroller
- X1 - 3.58 MHz crystal



ondary of T1. The tuned circuit creates a nice sine wave, which is coupled onto the power line.

## The Firmware

Listing 1 (which is available for download at [www.nutsvolts.com](http://www.nutsvolts.com)) shows the software needed to run the X-Lock. It is burned into the CPU's flash memory and controls the entire operation. If anybody adapts this code to work on a PIC, let me know!

## Installation and Passcode Programming

Set the House Code switch on the X-Lock to match your other modules. Set the Mode Switch (Unit Code) to position 16 (Passcode Programming). Plug the X-Lock into any convenient outlet. You may wish to choose a location where you can see the module and its indicator LED.

Setting the X-Lock Mode switch to position 16 allows you to program the disarming and (optional) arming passcodes. Each passcode can consist of 1-7 "digits," where a digit is any numeric or function key except DIM. Programming can be accomplished from any controller. Follow this procedure to enter your passcodes:

1. Set Mode switch to position 16. LED should be off.
2. Press the "DIM" key. LED should blink red.
3. Enter up to seven digits for your disarm passcode. Note that some controllers send two commands for a single keypress (e.g., 2-ON). This would be considered two digits and may require two buttons on other controllers.
4. Press the "DIM" key again. LED should blink green.
5. Optionally, enter up to seven digits for your arm passcode (used by some modes).
6. Press the "DIM" key once more. LED should turn off.
7. After programming, change the Mode Switch to the desired operating mode position (see below).

NOTE: You can skip step 5 if you do not want a separate arm code; in this case, the arm code will be the same as the previously entered disarm code.

## Operation

Simply dial in the desired operating mode. You may choose from:

### Hi-security mode (Mode 1)

In this mode, the X-Lock will continuously monitor the line and prevent any X-10 activity. This is indicated by the red LED showing that the system is armed. To control your devices, you will first need to enter the disarm passcode. After entering the proper code, the X-Lock will disarm (LED turns green). You can now send whatever commands you wish.

The system will remain disarmed for a fixed period of time following the last command issued (i.e., until no keys have been pressed for that amount of time). The default time is 12 seconds but may be changed using the Advanced Programming mode. When the disarm period expires, the X-Lock will return to the armed mode and prevent any further access.

### Arm/disarm mode (Mode 2)

When the mode switch is placed in position 2, the LED will turn red, indicating that the system is armed. When you wish to gain access, enter the disarming passcode (LED turns green). This allows unrestricted control of your X-10 modules. To restrict access again, enter the arm passcode.

### Advanced programming mode (Mode 15)

Used to change the disarm window time.

1. Set Mode switch to position 15. LED should be off.
2. Press the "DIM" key. LED should blink green.
3. Enter desired time key (see table). LED will go off.
4. After programming, change the Mode Switch to the desired operating mode position.

### Window Timing Table

Key	Time (sec)
3	8
7	20
14	32
10	60

### Other LED Indications

When the system is armed, the LED will flash green when it detects any attempt to send a command.

If the X-Lock detects an error condition, it will disable itself and alternately flash red and green. Move either switch to reset the X-Lock.

### Computer Control

If your X-10 system contains any timer or computer interfaces, you will need to re-program them to send the



PAID  
SUBSCRIBERS  
ARE  
AUTOMATICALLY  
ENTERED  
EACH MONTH!

## WIN with Nuts & Volts

### This month's sponsor ...

Check out their ad on page 68!

**Roger's Systems Specialist Inc.**

**A \$50 Value!**

Altec Lansing  
Three-piece  
Subwoofer/  
Speaker System  
High quality, high  
performance  
Three-piece system

- Delivers audiophile power and quality to desktop audio
- Compact speaker satellites are powered and magnetically shielded
- Powered subwoofer extends the low frequency response to add realism and bass

[www.RogersSystems.com](http://www.RogersSystems.com)  
661-295-5577 • Fax: 661-295-8777

### This month's winners ...

**Jonathan Williams of Raleigh, NC**  
**Brian Morrison of Fayetteville, NC**  
**Mark Colton of Salt Lake City, UT**

To Subscribe - just fill in and mail the card supplied in the magazine or call our toll free order line at (800) 783-4624 with a Visa or MasterCard. If you do not wish to order a subscription, but would like to be entered in our drawing, simply send or email your name, address, and telephone number to Nuts & Volts, 430 Princeton Ct., Corona, CA 92709 or drawing@nutsvolts.com. No phone entries accepted. All orders/entries must be received by the last day of the month to be included in that particular month's drawing.

disarm code before each command (or set of commands, if they are sent as a group). Since many controllers must send an "action" key with each program step, you should pick a passcode such as 13-ON, 12-OFF, 13-OFF.

Of course, the same applies to sending the arm code for Mode 2. However, since the system is "active"

**Robotzone.com**

**RobotCity.com**

Circle 850 on the Reader Service Card.

## REFERENCES

David Rye, Technical Note, "The X-10 POWERHOUSE Power Line Interface Model #PLS13 and Two-Way Power Line Interface Model #TW523"  
LM1893/LM2893 Carrier Current Transceiver  
Datasheet, National Semiconductor, 1995.

### Web Sites:


<http://www.x10.com/>  
[http://www.x10.com/pressroom/pressroom\\_coretech\\_news.htm](http://www.x10.com/pressroom/pressroom_coretech_news.htm)  
Main X-10 commercial site and technology theory  
<http://www.x10.org/>

<http://www.smarthomeforum.com/x10.shtml>  
<http://www.execulink.com/~hometechn/x10faq.htm>  
<http://www.automationfaq.com/forumserve/cache/4.html>  
FAQ pages


<http://nav.webring.yahoo.com/hub/ring=homeauto&list>  
<http://www.concentric.net/~Reboston/list.html>  
Home Automation forums
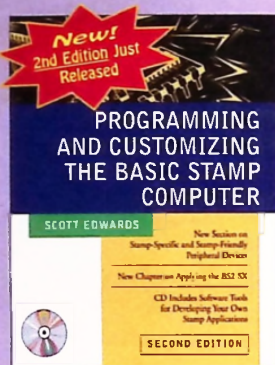
<http://www3.edgnet.net/lingling/x10-mods.html>  
<http://www.nysaes.cornell.edu/ccstaff/pool/homeauto/>  
Schematics of X-10 stuff and other hobbyist info.






\$39.95 List **\$35.95** Subscriber

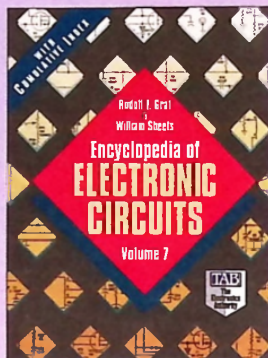

\$39.95 List **\$35.95** Subscriber

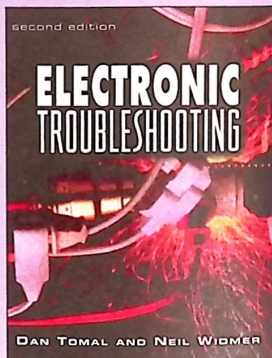


\$34.95 List **\$31.45** Subscriber

# 10% OFF


FOR PAID SUBSCRIBERS
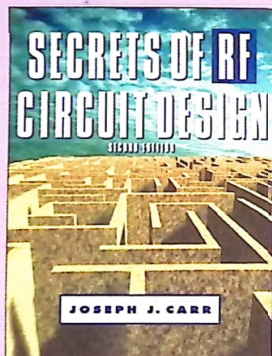
## Nuts & Volts Book Store


Now you can order on-line! Check out our Book Store at [www.nutsvolts.com](http://www.nutsvolts.com) for a complete listing of available titles.




\$39.95 List **\$35.95** Subscriber

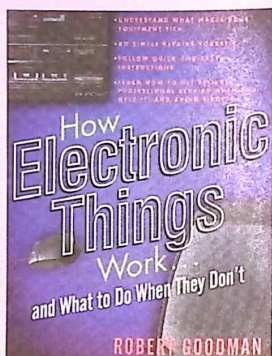

\$24.95 List **\$22.45** Subscriber

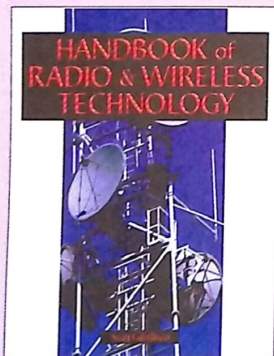

\$44.95 List **\$40.45** Subscriber

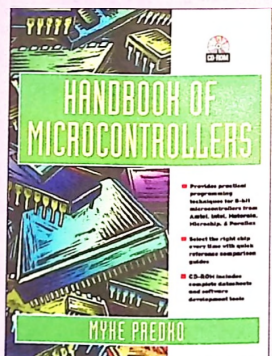

\$54.95 List **\$49.45** Subscriber

**Call 1-800-783-4624 today!**

WE ACCEPT VISA AND MASTERCARD

Send check or money order to Nuts & Volts, 430 Princland Court, Corona, CA 92789. Include a complete shipping address (no P.O. Boxes, please). Shipping & handling \$4.50. CA residents add 7.75% sales tax. Or, call our toll-free order-only line at 1-800-783-4624 and use your MasterCard or Visa. Or order on-line at [www.nutsvolts.com](http://www.nutsvolts.com). ALL ORDERS MUST BE PREPAID.



# New Product News

## Mini-FlashLED™

LEDtronics announces the Mini-FlashLED™ pocket flashlight, the newest addition to its line of high-powered LED flashlights that integrate a 5mm discrete LED lamp, an anodized aluminum casing, and a cabochon lens that optimizes the light intensity.

LED light output — measured in End Foot Candles (EFC) — is impressive: Blue 32 EFC, Green 140 EFC, White 150 EFC, Red 100 EFC, and Yellow 30 EFC.

This pocket-sized light measures just 5" in length and weighs only 2.1 ounces, making it ideal for carrying in briefcases, backpacks, purses, and toolboxes.

The long-lasting LED lamp operates for more than 100,000 hours (10 years) before requiring replacement. Energy-efficient, Mini-FlashLED operates between 9 and 257 hours depending on the LED lamp, on three replaceable E90 N-cell alkaline batteries or equivalents. Also, the Mini-FlashLED can house and run on four AA alkaline batteries further extending its operating time by reducing bright.



Mini-FlashLED is available in six colors: Cool White, Ultra Red, Orange, Yellow, Aqua Green, and Pure Blue. Price is \$26.50 per flashlight. Ask for datasheet #105.

For further information, contact:

**LEDTRONICS, INC.**  
23105 KASHIWA CT., DEPT. NV  
TORRANCE, CA 90505  
310-534-1505 FAX: 310-534-1424  
WEB: [www.ledtronics.com](http://www.ledtronics.com)

## HIGH-END PIC SINGLE BOARD MICROCONTROLLER MODULES FOR THE PIC17C756 OR PIC18C658

Tech Systems is offering pre-assembled, high End PIC single board microcontroller modules for prototyping or end-product use.

These modules incorporate either a 68-pin PLCC PIC17C756 or a 68-pin PLCC PIC18C658 microcontroller on the main board. These microcontrollers represent Microchip's most powerful processors to date. The main board also includes all the necessary components and circuitry needed to power the microcontroller: 5-volt regulator, 32.768 MHz external oscillator, and reset circuitry. In addition, the main board includes RS232 serial interface circuitry, a DB9 serial connector, a 931C66 serial EEPROM non-volatile memory unit wired to the I/O pins, an LED wired to one I/O pin, and a prototyping area.

A daughter board fits onto the main board through a 50-pin connector. The standard "blank" daughter board contains a prototyping area so that different projects can be built onto separate daughter boards and still use the same main board. In addition, a dedicated daughter board can be laid out and fabricated for use in test fixtures or end-user products. The main



boards can be purchased in larger quantities at reduced rates for pilot production runs that use specialized daughter boards. Daughter boards with specialized components such as LCD modules, stepper motor drivers, etc. will be available as well soon.

A programming adapter to adapt the 68-pin UV erasable 18C658 to the Microchip PICSTART-PLUS 40-pin DIP connector is also available. This will allow program development for the 18C658 using the Microchip development programmer.

For more information, contact:

**TECH SYSTEMS**  
125 BETHANY DR., STE. G  
SCOTT'S VALLEY, CA 95066  
831-479-7000  
EMAIL:  
[sales@techsystemsembedded.com](mailto:sales@techsystemsembedded.com)  
WEB:  
[www.techsystemsembedded.com](http://www.techsystemsembedded.com)

## DRIVER16 EXPANSION BOARD

JK microsystems, Inc., now has the new Driver16 expansion board available for shipment.

This new addition to the product line provides many JK microsystems single board computers the ability to convert regular TTL level I/O lines into

as many as 16 high-current outputs. This miniature board (less than 2" square) gives users the capability of driving relays, lamps, and small motors directly.

Starting at \$29.00 for one unit, the Driver16 is aggressively discounted with quantity orders. The development kit, which is only \$39.00, contains a

## WORKMAN MOBILE ROBOT PLATFORM

The Workman Mobile Robot Platform was created to be the basis of a specialized mobile robot. Suitable for applications such as

education, industrial inspection, fire-fighting, etc., Workman provides plenty of surface area for sensors and other devices. Also ideal for the hobbyist, Workman addresses the problem most robot builders face: designing a suitable platform. Measuring 15"L x 19"W x 10"H, Workman solves this problem, enabling you to

focus on the design and implementation of the internals such as controller, power source, batteries, etc.

The Workman platform is user-friendly. Made of four individually molded plastic enclosures, it is easily drilled or modified to accommodate your application. The modular design provides compartments for your internals. Two of the compart-

ments house the motors (included), while the two remaining compartments contain components that you specify. For instance, one compartment could contain a controller board, while the other could house battery and radio receiver.

Boasting 8" drive wheels, 6" rear swivel wheels, and two high-torque worm-gear motors, this machine is a dynamo. Available in kit-form or completely assembled, Workman is powerful, able to scale small obstacles with ease. It can handle light-to-moderate jobs such as pulling, pushing, or carrying small loads.

The Workman Mobile Robot Platform kit sells for \$239.00 (un assembled). Manual with photos included.

For more information, contact:

**KADTRONIX**  
321-757-9280  
EMAIL: [info@kadtronix.com](mailto:info@kadtronix.com)  
WEB: <http://www.kadtronix.com>



## TOTALLY REDESIGNED KUP-L-WELD® II THERMOCOUPLE WELDER

The KUP-L-WELD® II Thermocouple Welder was originally introduced by Burrell Scientific, Inc., over 45 years ago. While the KUP-L-WELD Welder has been modified over the years, Burrell took advantage of today's advanced technology in redesigning it to improve control of the entire welding process. The original focus of the redesign was to have the KUP-L-WELD II Welders produce superior weld contacts that would ensure precise temperature monitoring.

Features of the new, self-contained KUP-L-WELD II Welder include an illuminated work area, graduated power control, push-button power activator, internal cooling fan, electronic circuit board, flash protection viewing screen, and a pen-style alligator-clip holder.

The KUP-L-WELD II unit is 8" wide, 13-1/2" deep, and 9" high, so it takes up less than a square foot of counter space. The KUP-L-WELD weighs just four pounds, so it's easily



moved. The metal case is finished with an abrasion- and corrosion-resistant paint. Access to the case is easy and components are readily accessible for servicing or replacement.

Burrell Scientific recommends the KUP-L-WELD II Thermocouple Welder for welding 30- to 14-gauge constantan; platinum; platinum/rhodium; iron constantan; and chromel-alumel. When the graduated power control is set and activated to make a weld, the 115-volt, 60-cycle unit can pull a minimum of 19 amps to a maximum of 28 amps.

For more information, contact:

**BURRELL SCIENTIFIC, INC.**  
412-471-2527 FAX: 412-391-4231  
1-800-637-6074  
EMAIL: [burrellsci2@aol.com](mailto:burrellsci2@aol.com)



Driver16 and all the items necessary for integration with the industry proven LogicFlex, Flashlite 386Ex, or V25 controllers.

For additional information, contact:

**JK MICROSYSTEMS, INC.**  
1403 5TH ST., STE. D, DEPT. NV  
DAVIS, CA 95616  
530-297-6073 FAX: 530-297-6074  
EMAIL: [sales@jkmicro.com](mailto:sales@jkmicro.com)  
WEB: [www.jkmicro.com](http://www.jkmicro.com)



**Enclosed Switching Power Supplies**

Single, Dual &amp; Triple Output Models

Triple Output Supplies

100W, 5V/12V/-5V As Low as \$44.00

100W, 5V/12V/-12V As Low as \$44.00

**UL Approved****Single Output Supplies (5V, 12V, 15V & 25V)**

25 watt series As Low as \$20.55 ea.!

50 watt series As Low as \$27.95 ea.!

150 watt series As Low as \$42.95 ea.!

200 watt series As Low as \$50.00 ea.!

**Dual Output Supplies**

100 W, 5V/12V As Low as \$38.00 ea

100 W, 5V/24V As Low as \$38.00 ea.

50 W, 5V/24V As Low as \$27.00 ea.

Note: These are NOT SURPLUS!

**See Our Web site for Details!****Protek 2GHz RF Field Strength Analyzer****ONLY \$2069**

• Frequency Range: 100kHz to 2.0GHz  
 • Noise and Spurious Rejection: 100dB  
 • Wide Band RF (VHF/UHF)  
 • AM and Single Side Band (SSB) Mod. Line 15mV  
 • Pre-Set Receiver  
 • PLL Tuning System for Precise Frequency Measurement and Tuning  
 • USB Backdoor (PC/Mac/Win) (K&A/RT) Model

**#3201**

• Hand-Held or Battery Operated  
 • All Functions are Menu Selected  
 • K&A/RT for PC Interface and Power

See the web site for details

**Removable Hard Drive Rack For IDE/ATA DMA Hard Drives**

This product can be used with any 3.5" IDE hard drive up to 17" high. It includes an internal bracket for easy removal and insertion. Made of ABS 70% recycled plastic. Use this product to protect your hard drive data, save your hard drive between work and home or even use up different users with their own hard drive data, save your hard drive every time they use a PC. Other models available from C.S.I. include RH10 and RH20 series and RH20 series interchangeable within the same insert design. Other Models are Available. See www.web-tronics.com under "hard drive and accessories" for more details and pictures.

We Sold Over 14,000 in 1998!

**ONLY \$14.95****RH-10C-IDE****Removable Hard Drive Rack with Auto Door And Cooling Fan**

- Auto door on the outer frame
- ABS material of outer frame, high efficiency cooling fan
- Worldwide patent pending function
- CE Approved
- Cooling using bottom cover
- For IDE Interface
- For 1" high 3.5" HDD
- Not compatible with our RH10 & RH20 model.

**ONLY \$18.95****#MR-27**

Details at www.web-tronics.com

**Auto-Temp. Solder Station with Ceramic Element**

- With Ceramic Heating Element for More Accurate Temp. Adjustment
- 1 Temperature Control Power Cord
- 230°C/450°F (470°F/900°F)
- Fast Heating Feature

**ONLY \$39****SR-976**

• Extra Tip Options Available. See Web!

For More Info See www.web-tronics.com

**CTRL-D to bookmark this site****www.web-tronics.com**

Don't forget the dash

**Circuit Specialists Inc.**

- Easy to Navigate
- Includes a Search Engine That Really Works
- New Items Added Constantly

In Business Since 1971

**CCD B&W Board Cameras**

ASIC CCD Area Image Sensor

Extremely Low Power Consumption

0.5 Lux Min Illumination

Built-In Electronic Auto Iris for Auto Light Compensation

Detailed Specs on the Web

VM103PA-B 10mmx31mmx23mm, Pinhole lens, 12V/139.00 any qty.

VM103SA 10mmx31mmx23mm, Standard lens, 12V/139.00 any qty.

VM103SA 41mmx41mmx23mm, Standard lens, 12V with back light compensation/149.00 any qty.

VMCB21 41mmx41mmx23mm, with 6 infra-red LEDs, 12V/149.00 any qty.

VM1034A 31mmx31mmx23mm, Standard lens, 12V, reverse mirror image feature/149.00 any qty.

Detailed Specs on the Web

**Bullet CCD Cameras B&W and Color**

Smart Ringed Metal Housing

Extremely Low Power Consumption

12 Volt

CCD Area Image Sensor for Long Camera Life

Built-In Electronic Auto Iris for Auto Light Compensation

No Flickering, No Burning

0.5 Lux Min Illumination (B&amp;W), 1 Lux Min Illumination (color)

VMBLT1020 B&amp;W, 21mm(D)x31mm(L)/154.00 any qty.

VMBLT1020W B&amp;W Weatherproof (no audio), 21mm(D)x31mm(L)/179.00 any qty.

VMBLTJ1919W COLOR Weatherproof (no audio), 17mm(D)x88mm(L)/1139.00 any qty.

Detailed Specs on the Web

**COLOR CCD Mini Board Cameras**

Low Power Consumption

1 Lux Illumination

Built-In Electronic Auto Iris for Auto Light Compensation

Internal Synchronization

12Vdc

400 TV Lines

VM3010PA 31mmx31mmx18mm, Pinhole lens with audio/129.00 any qty.

VM3011-A 41mmx41mmx24mm, Standard lens with audio, single board/199.00 any qty.

VM3010-A 31mmx31mmx23mm, Standard lens with audio/129.00 any qty.

Detailed Specs on the Web

**DC to AC Power Inverters! 150 watt up to 3000 watt models!**

150w modified sine wave/\$29.95(G-12-015B) Check Our Low Prices!

300w modified sine wave/\$39.95(G-12-030)

150w pure sine wave/\$69.00(G-12-150S)

300w pure sine wave/\$109.00(G-12-300S)

800w modified sine wave/\$139.00(G-12-800)

1000w modified sine wave/\$179.00(G-12-100)

3000w modified sine wave(phase corrected), (G-12-3000) \$499.00

See Our web site for DETAILED Specs.!

**Our Most Sophisticated DM11 We Sold Over 800 Last Year!**

With RS-232C Interface &amp; Software, 3-3M Digit, 4000 Count, Auto-Ranging with Analog Bargraph

• True RMS Mode

• Offset Frequency Counter

• Time Mode with Alarm, Clock, Continuity/Beep Test

• Logic Test

• Auto Power Off/Temp. C/F Mode

• Dual Display

• 10 Location Memory

• Pin, Plug and Relative Mode

• Back Light

• Data Hold/Run Mode

• Safety Design, UL134 &amp; VDE 0411

• Protective Housing

• Silicon Test Leads

**NOW ONLY \$149**

More Details on our Web Site

**PROTEK 506****new!****BEST DEALS!****NOW Offering****Direct TV**

Great Equipment &amp; Service

See Our Website for our

Incredible Offers!

Also GREAT HDTV Prices!

**O'Scope Offer**

30MHz! ONLY \$299!

**ONLY \$299****#OSC-1030**

• Dual Channel

• Dual Trace

• Vert Trigger

• 1 Year C.S.I. Warranty!

Includes 1 oscilloscope probe

Manufactured for CSI by a leading O.E.M. manufacturer. See our website for detailed specifications!

**Digital Read Out 3Amp Bench Power Supplies**

Available in 0-30 volt &amp; 0-50 volt versions

High stability digital read-out bench power supplies featuring constant voltage and current outputs. Short-circuit protection and current limiting protection is provided. Highly accurate LED accuracy and stable line regulation make the 3000 series the perfect choice for lab and educational use.

Line Regulation:  $\pm 0.1\%$  mVLED Accuracy: Voltage  $\pm 1\%$  2 digitsCurrent  $\pm 1.5\%$  2 digitsWave Line Noise:  $\leq 1\text{mVrms}$ 

Dimensions: 219mm x 158mm x 136mm

CS13003:0-30V/0-3amp 1-4 / \$99.00 5+ / \$89.00

CS15003:0-50V/0-3amp 1-4 / \$129.00 5+ / \$119.00

Bookmark our WEB Site! Many more Power

Supplies are Available. Look Under Test Equipment

**AS LOW AS \$89**



# PROFESSIONAL DISK DUPLICATION

## CLONE, TEST OR REPAIR ANY HARD DRIVE

www.proworkstation.com

**\$995!**



- SUPPORTS IDE, SCSI, SCA & NOTEBOOK DRIVES
- COPIES AND SERVICES HARD DRIVES
- PRINTS TEST REPORTS ON YOUR PRINTER
- DATA RECOVERY MODE BUILT-IN

Copy entire hard drives with this pro service station. Set up any SCSI or IDE drive with your original software. Attach a blank drive and press start. Make copies quickly and easily.

Use the built-in drive service system to make used drives run like new! Eliminate defective sectors, and restore hard drives to error-free condition with the factory re-mapping system. Test hard drives for top reliability using the built-in software. Print analysis reports on any standard parallel printer. Get the technology used by drive repair services. Call today!

## 25 GB MP3 PLAYER

www.csp3forme.com

**\$395!**

after mail-in rebate



- PLAYS OVER 10,000 SONGS FROM HARD DISK!
- PLAYS STANDARD AUDIO AND MP3 CDs AND CD-R
- DOWNLOADS MP3 FROM CD-R TO HARD DRIVE
- POWER AMPLIFIER DRIVES SPEAKERS DIRECTLY

MP3 is here! Get high performance digital sound and store over 15,000 songs on hard disk. Download over 300 songs from a single CD!

Grab new music from the net. Use your PC to create custom MP3 CDs with just the songs you like. Load them to the internal hard drive for realistic, 3-D theater sound. Patented digital signal processing gives you crystal clear sound. No PC connection is required. Connect any stereo system, or directly power external speakers. Get digital sound and room-filling bass.

The hard drive organizes your music in folders. ID-3 tags display the title, album, and artist on a large LCD. Use the jukebox feature for an entire evening of great music. Play songs randomly or in sequence from the internal hard drive. Unlike CD changers, the A/V certified 25 GB hard drive won't wear out, even under continuous use. Call now and try your MP3 player tomorrow!

## CORPORATE SYSTEMS CENTER

3310 WOODWARD AVE. • SANTA CLARA, CA 95054

WWW.CORPSSYS.COM

**408 330-5524**




Over 80% of the Fortune 500 depend on CSC products. Shouldn't you? Call today. Most orders ship within 24 hours! Call now for more information and a free price comparison guide. Quantity discounts are available for dealers and system builders. Copyright laws must be observed when duplicating CDs and hard drives. © 2001 CSC.

## COPY ANY CD NOW NO PC REQUIRED

www.dupeit.com

**from \$795!**

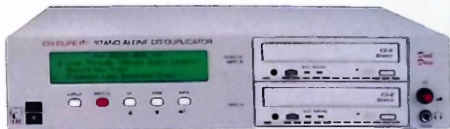

- MULTI-FORMAT DUPLICATION - FAST AND EASY!
- DUAL 8X DRIVES MAKE TWO COPIES AT ONCE
- INTERNAL 25GB HARD DRIVE STORES IMAGES
- PRO AUDIO MODEL HAS S/PDIF AND ANALOG I/O

Instantly copy music and CD-ROM compact discs. Make backup copies of your favorite music and software on rugged, permanent CDs. Produce discs quickly and economically. Make custom audio CDs with just the songs you like.

Use our dual drive units to copy two CDs simultaneously, or choose the Pro Audio model to make crystal clear music CDs from any analog or digital source. Dupe-It copiers are totally self-contained. No additional software or hardware is required. Call today for more information!

## MULTI DRIVE IDE DUPLICATORS

www.driveduplicators.com

**from \$495!**




- COPIES EVERYTHING, PARTITIONS, O.S., THE WORKS!
- BOTH STANDARD AND ULTRA, FOUR AND SEVEN DRIVE MODELS ARE AVAILABLE NOW!
- THE ULTIMATE HIGH SPEED PRODUCTION TOOL FOR SYSTEM BUILDERS AND CORPORATE MISC

Copy entire hard drives with ease. Multi-drive duplicators are an essential tool for dealers and system builders. Why spend hours installing and formatting drives when you can dupe them instantly? Work like the pros. Get your own multi-drive, stand-alone duplicators today. CSC offers a complete line of four and seven drive copiers in both standard and ultra versions. Ultra models transfer data faster than any hard drive! Rates of over 1GB per minute are supported.

Set up any IDE drive with all your original software. Attach blank target drives, and press "start". It's that easy! You can duplicate four drives in less time than it takes to copy one on a fast PC! Your duplicate drives will be identical, bit-for-bit perfect copies, with all the files, partitions, and information on the original drive. Building systems is tough enough. Why spend hours installing software? Save time. Save money. Call today and let us Fed-X your duplicator for a risk-free evaluation!




# NUTS ABOUT STAMPS?

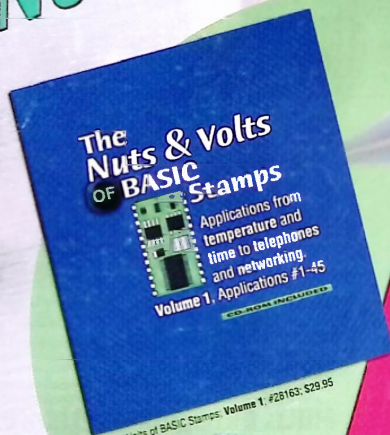

Nuts & Volts of BASIC Stamps: Volume 1, #28163, \$29.95

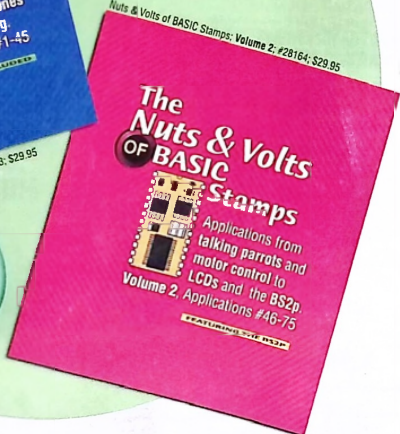**Buy Both  
Volumes  
and save  
over \$10!**



Nuts & Volts of BASIC Stamps: Volume 2, #28164, \$29.95



**Nuts & Volts Magazine** has published over 75 "Stamp Applications Columns" since 1995 for the BASIC Stamp hobbyist and engineer. These applications are now compiled in a 980-page two-volume release entitled *The Nuts & Volts of BASIC Stamps*. Order both volumes for only \$49!

*The Nuts & Volts of BASIC Stamps* is as much of a BASIC Stamp reference book as it is an application idea guide. Reference material includes the popular Beginner's Corner from Scott Edwards and Jon Williams' examples of how to write well-structure PBASIC code. An assortment of math and general command syntax examples to help you squeeze the most from your BASIC Stamp is helpful for all types of applications, whether factory, hobby or educational.

Examples of applications in the *Nuts & Volts of BASIC Stamps* include: measuring water level, measuring temperature and time, controlling DC motors, communication (using modems, RS-485, to the PC, etc.), using keypads, controlling large loads with solid state relays, interfacing Scott Edwards serial LCD modules (text and graphic), controlling Hitachi-compatible LCDs, sound and speech, lighting control and of course examples with 1-Wire and I<sup>2</sup>C with the new BS2p.

## PARALLAX

24-hour online ordering at [www.parallaxinc.com](http://www.parallaxinc.com) or  
call toll-free 888-512-1024 (M-F, 7 a.m. to 5 p.m. PST)

BASIC Stamp and the Parallax logo are registered trademarks of Parallax, Inc.